

ECE 325 – Electric Energy System Components

8- Fundamental Elements of Power Electronics

Instructor:

Kai Sun

Fall 2018


Content

(Selected materials from Chapter 21)

- Power semiconductor switches
 - Diodes, thyristors and controllable switches.
- Principles of AC-to-DC, DC-to-DC and DC-to-AC converters

Introduction

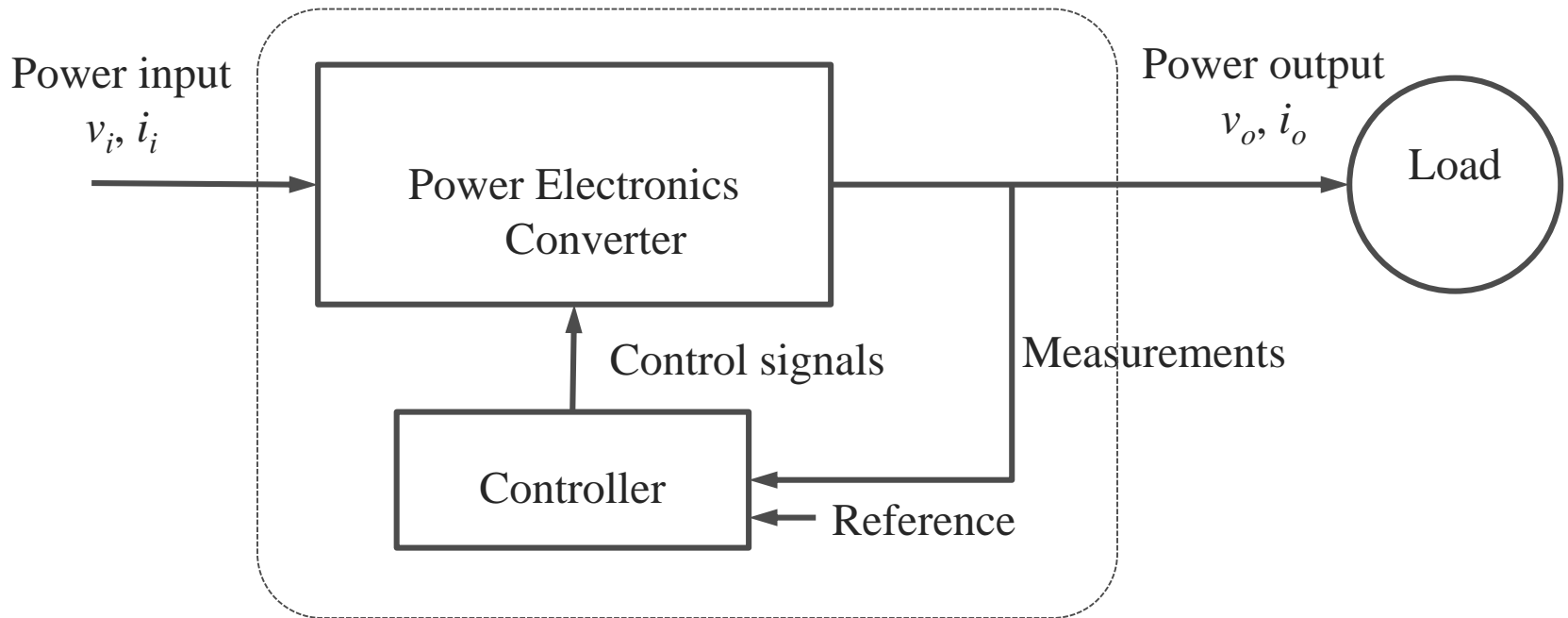- A power electronics system is to process and control the flow of electric energy by supplying voltages and currents in a form that optimally suits the loads
- A typical power electronics (PE) system:



Applications of PE converters

- For **DC voltage/current**, a PE converter can regulate and adjust the **magnitude** to a desired level
- For **AC voltage/current**, a PE converter can adjust the **magnitude and frequency** and change the **number of phases**
- Applications:
 - Switched-mode (DC) power supplies
 - Uninterrupted power supplies (UPS)
 - Adjustable speed motor drives
 - High-voltage DC transmission (HVDC)
 - Battery-based utility energy storage
 - Electric vehicles (EVs) and hybrid electric vehicles (HEVs)
 - Renewable energy integration, e.g. solar PV and wind generation

Classification of PE converters

Four types of PE converters	Examples of application
AC-to-DC (rectifier)	The battery (charging) interface to the power grid and power adapters for electronic devices
DC-to-DC (boost up/step down)	Power supplies for electronic devices
DC-to-AC (inverter, to 1-phase or 3-phase AC)	The battery (discharging) and solar PV interfaces to the power grid
AC-to-AC	Variable-speed motor drive

- Examples of variable-speed motor drives (**AC-to-AC** converters)

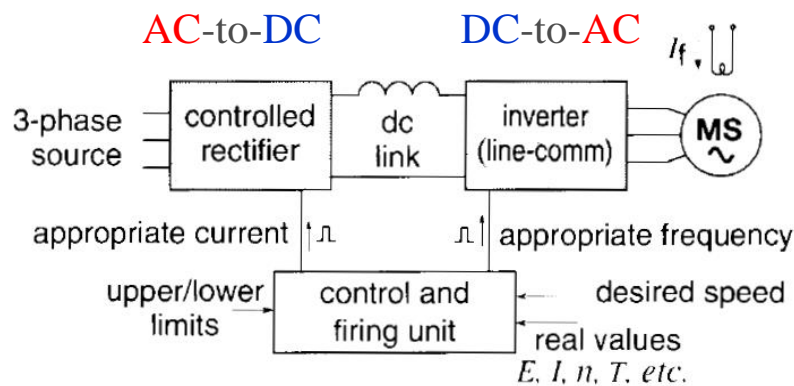


Figure 23.3

Variable-speed synchronous motor drive using a controlled rectifier and a line-commutated inverter fed from a dc link current source (see Section 23.2).

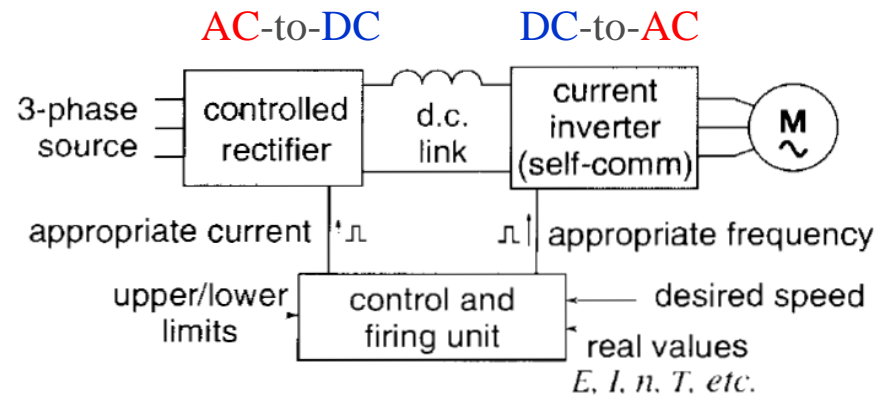


Figure 23.5


Variable-speed drive using a controlled rectifier and a self-commutated inverter fed from a dc link current source (see Section 23.9).

Power semiconductor switches

- They are key functional components in a PE converter besides resistors, inductors and capacitors.
- Two states: ON (conducting) and OFF (open-circuit)
- Three types in terms of the controllability
 - **Not receiving control signal**, e.g.
 - **Diode**: ON and OFF states controlled by the polarity and magnitude of voltage and the magnitude of current.
 - **Partially controlled by a control signal**, e.g.
 - **Thyristor**: turned ON by a control signal and OFF when current goes to zero
 - **Controllable switch**, e.g.
 - **GTO, IGBT, BJT, MOSFET**: both ON and OFF states are controllable by control signals

Ideal and Practical Diodes

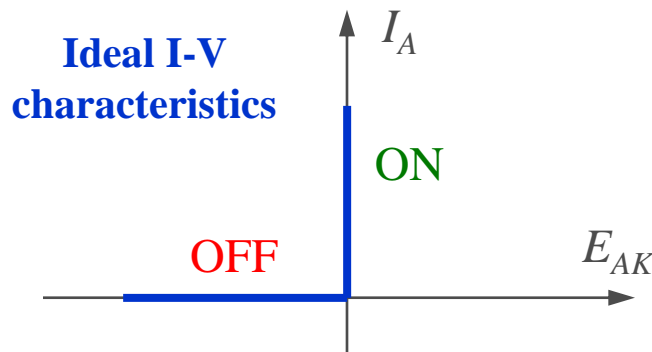- 2 terminals: A (anode) and K (cathode)
- **Rule 1:** OFF when $E_{AK}=0$
- **Rule 2:** OFF when $E_{AK}<0$ (**reverse biased**)
- **Rule 3:** ON (short-circuited) when $E_{AK}>0$ (**forward biased**)
- **Rule 4:** OFF when I becomes 0
- Both ON and OFF switches are instantaneous



Practical Diode:

- Turns ON when forward biased with a voltage V_d about 0.7V or more, and it has a negligible voltage drop $<1.5V$.
- When it is OFF (**reverse biased**), it has a negligible current I_S flowing through.
- At very large reverse bias beyond its peak inverse voltage ($V_{br}=50$ to 4000V), it is usually damaged and begins to conduct in reverse.


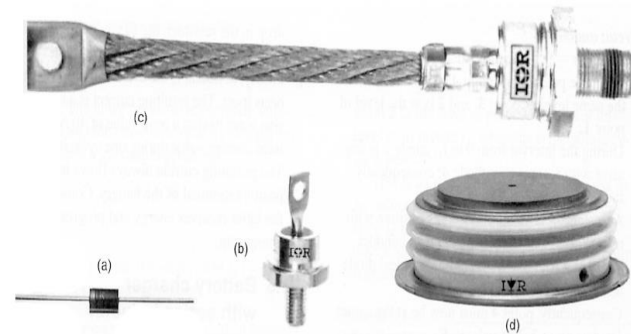
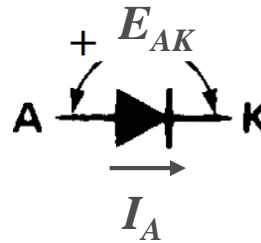





Figure 21.10

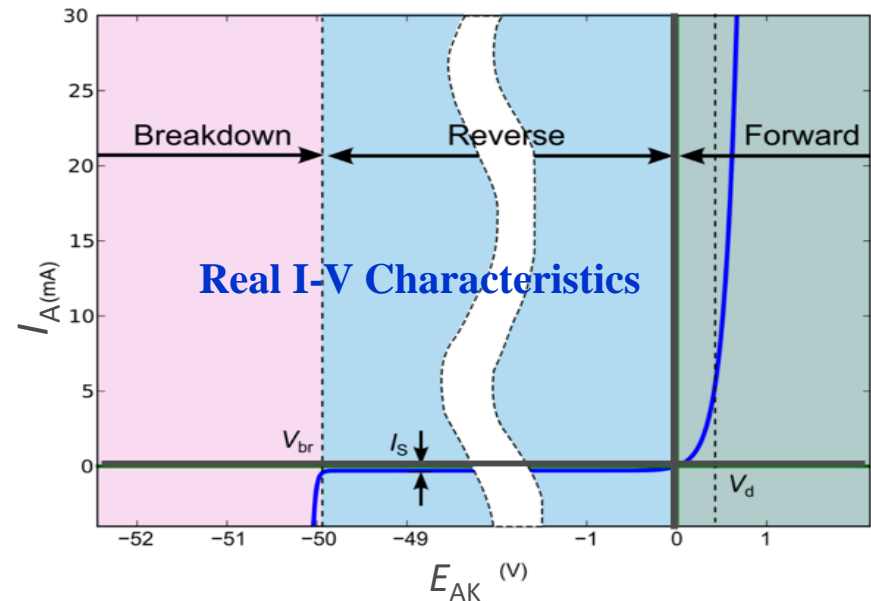a. Average current: 4 A; PIV: 400 V; body length: 10 mm; diameter: 5.6 mm.
 b. Average current: 15 A; PIV: 500 V; stud type; length less thread: 25 mm; diameter: 17 mm.
 c. Average current: 500 A; PIV: 2000 V; length less thread: 244 mm; diameter: 40 mm.
 d. Average current: 2600 A; PIV: 2500 V; Hockey Puk; distance between pole-faces: 35 mm; diameter: 98 mm.
 (Photos courtesy of International Rectifier)




Thyristors


- Usually referred to semiconductor/silicon controlled rectifier (SCR)
- 3 terminals: A (anode), K (cathode) and G (gate)
- A thyristor behaves like a diode except that **the instant of conduction can be controlled by “G”**; that enables converting DC to AC
- Two conditions to conduct
 1. $E_{AK} > 0$
 2. Positive current I_g flows into “G” for at least a few microseconds
- **Once conduction starts, “G” will lose control** and conduction will continue until the current I_A into “A” falls to zero
- If “G” and “K” are short-circuited, the thyristor is blocked
- A thyristor is **partially controllable**

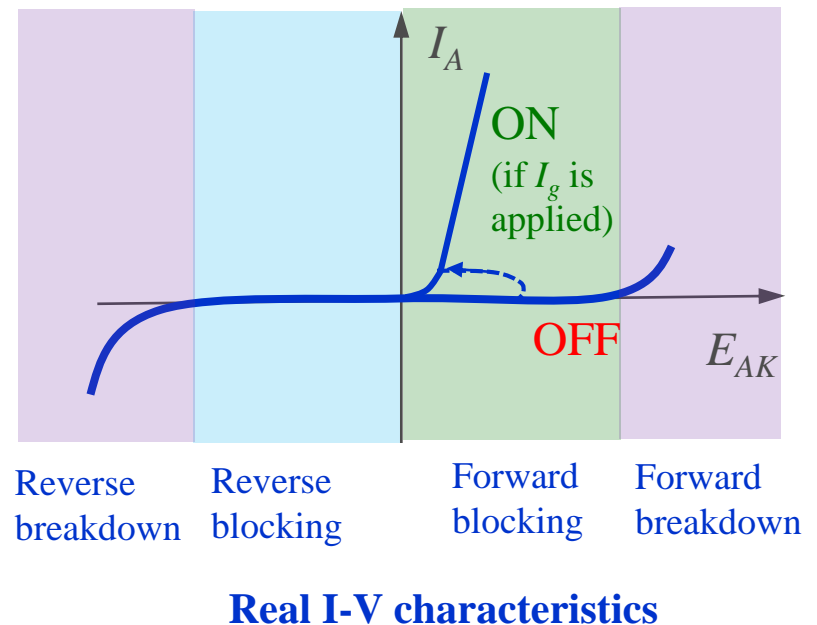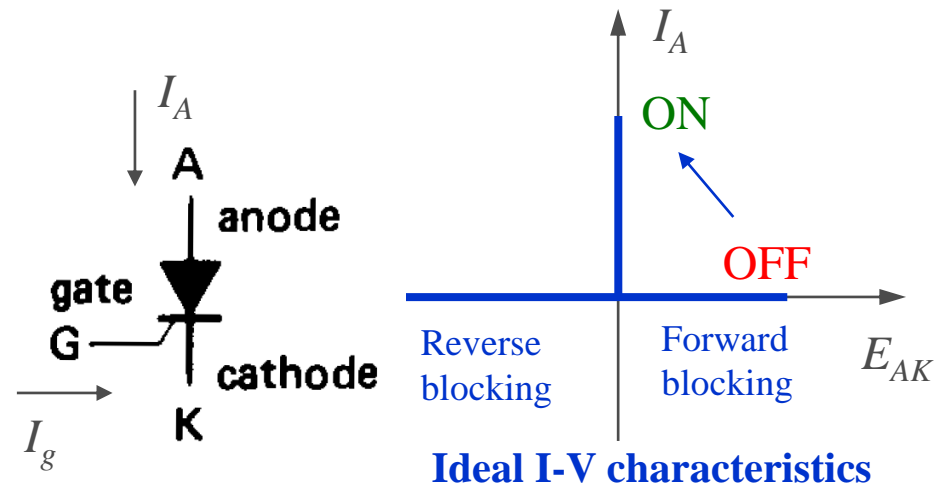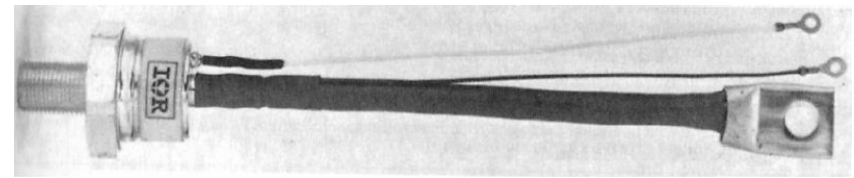

Principles of gate firing

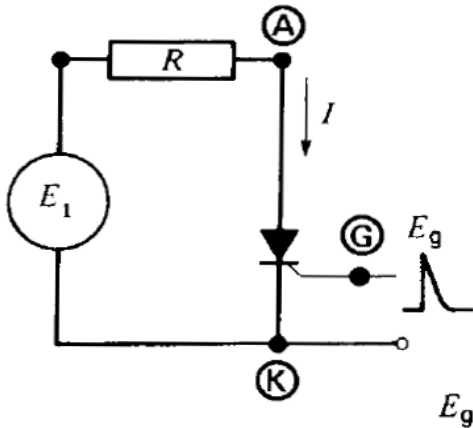

(a)

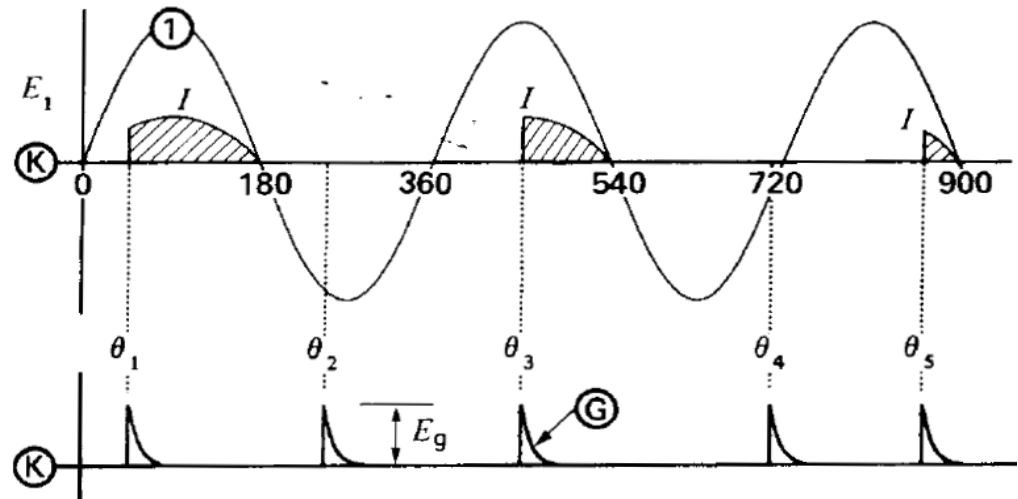

(b)

- We can control the current in an AC circuit by delaying the gate (G) pulses with respect to the start of each positive half-cycle.
 - If the pulses occur at the very beginning of each half-cycle, conduction lasts for 180° like a diode
 - If the pulses are delayed by θ , current only flows during the remaining $180^\circ - \theta$



Controllable power semi-conductor switches

• Examples:

- **GTO** (Gate-turn-off thyristor)
- **IGBT** (Insulated gate bipolar transistor)
- **BJT** (Bipolar junction transistor)
- **MOSFET** (Metal-oxide-semiconductor field effect transistor)

• Ideal switch

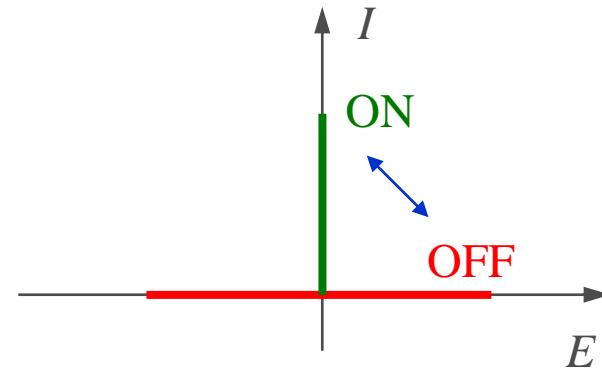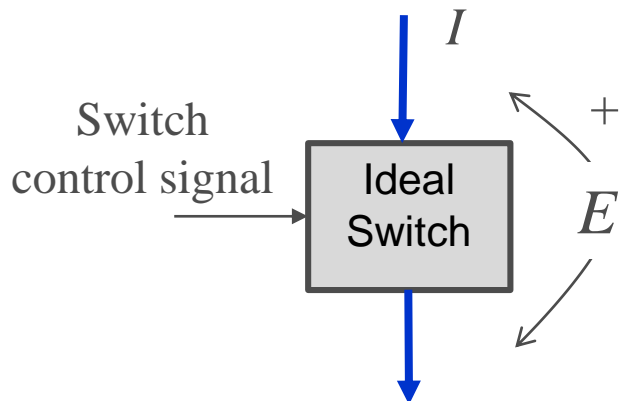
- Vanishingly small power required from the control signal to trigger the switch
- Switch between ON and OFF instantaneously when triggered by the control signal
- When OFF, block arbitrarily large forward and reverse voltages with zero current flow
- When ON, conduct arbitrarily large currents with zero voltage drop



Controllable power semi-conductor switches (cont'd)

• Real switches:

- Requiring control power for switches (the less control power the simpler the control circuit)
- Limited switching frequency
- Having OFF-state leakage current
- Having ON-state voltage (relevant to conducting losses)
- Limited forward- & reverse-voltage blocking capability (the higher voltage blocking capability, the fewer switches in series)
- Limited ON-state current rating (the higher current rating, the fewer switches in parallel)
- Limited dE/dt and dI/dt ratings (requiring additional circuit to limit $|EI|$)

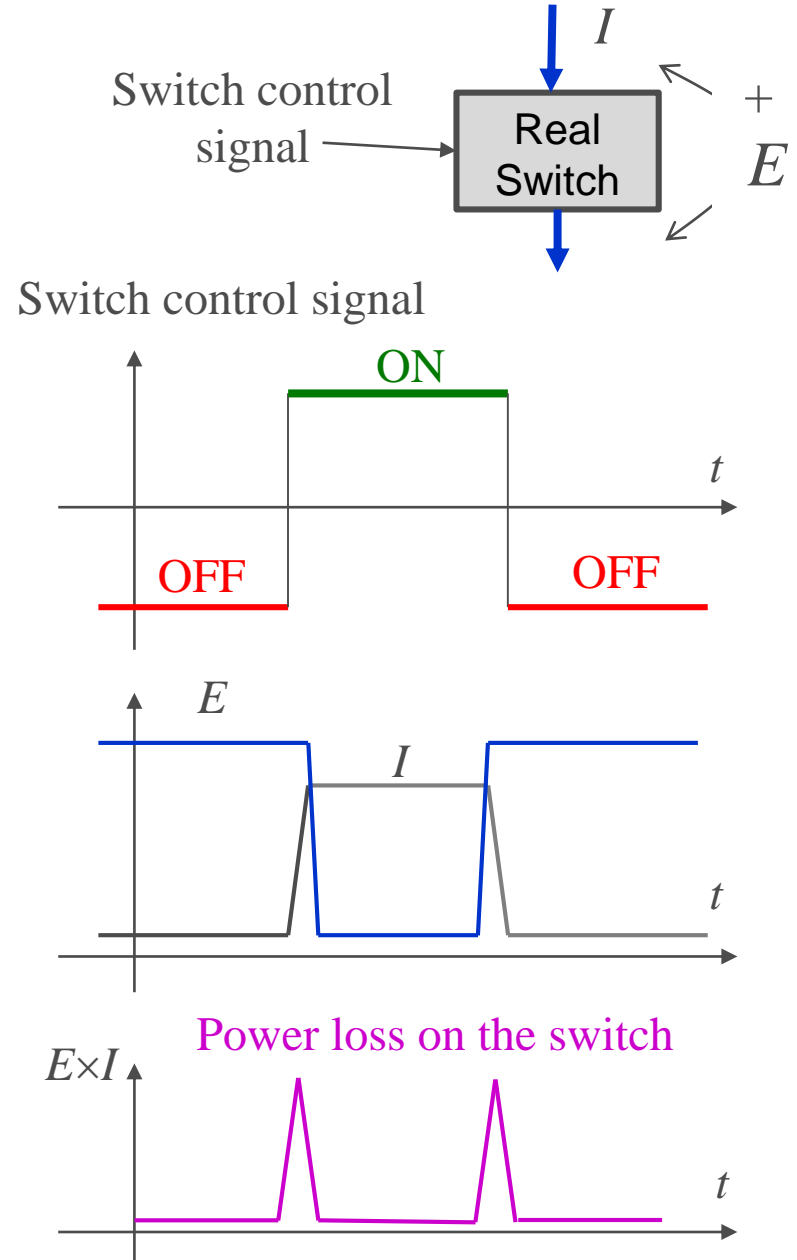

AC-to-DC converter: single-phase, diode bridge rectifier

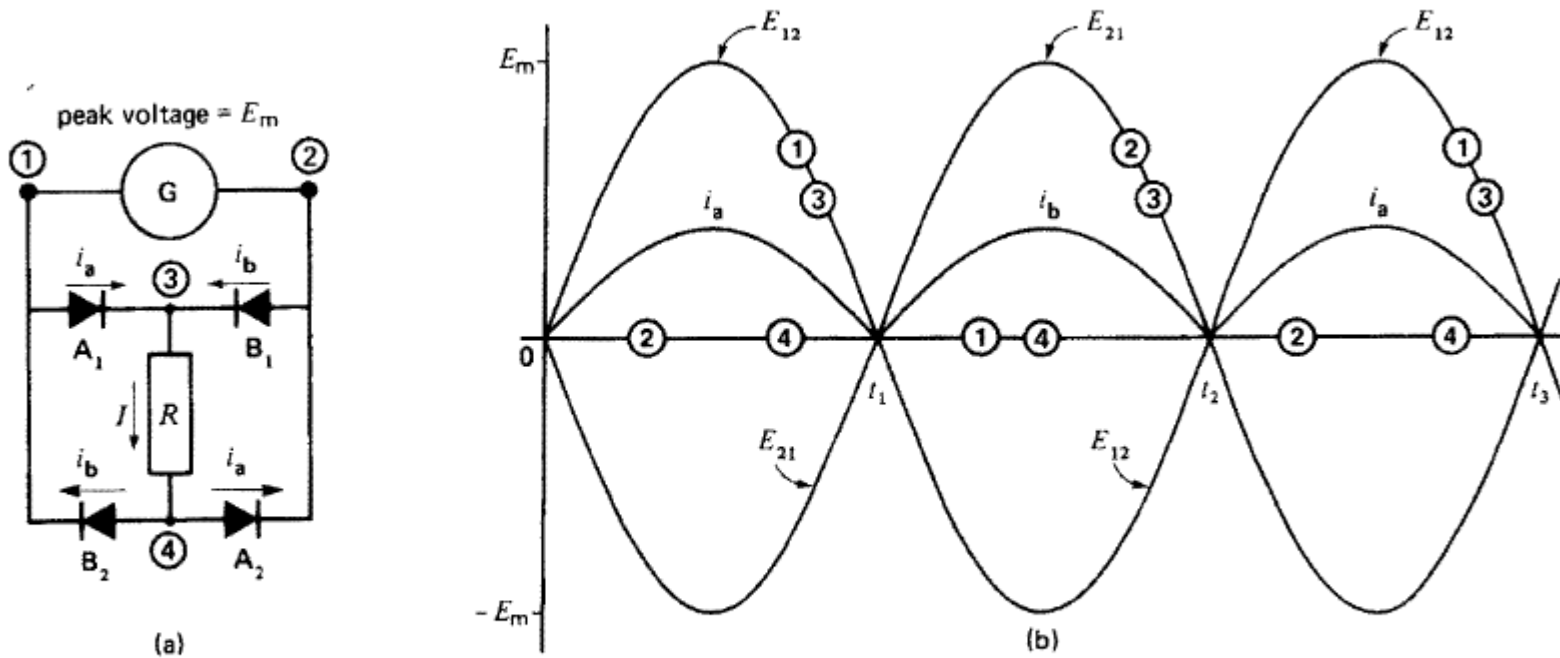


Figure 21.13

- a. Single-phase bridge rectifier.
- b. Voltage levels.

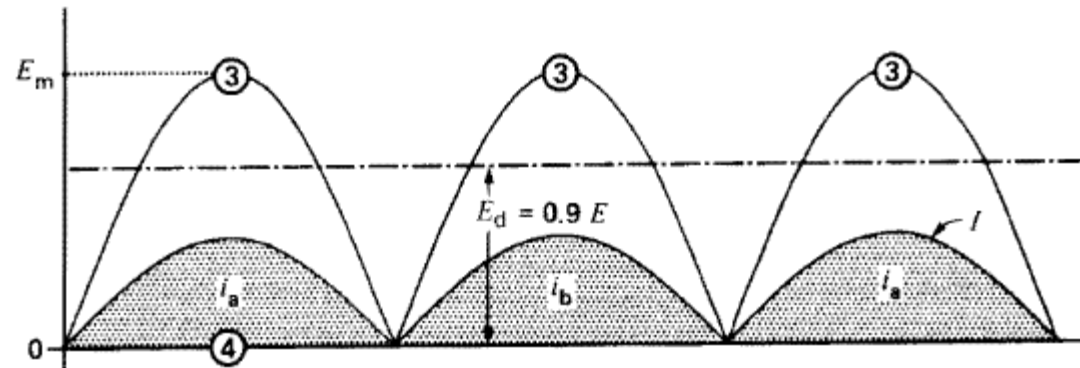




Figure 21.13c



Voltage and current waveforms in load R .

AC-to-DC converter: 3-phase, 6-pulse thyristor rectifier

- Control the DC output voltage E_d by the delay angle α of triggering pulses

$$E_d = 1.35 E \cos \alpha$$

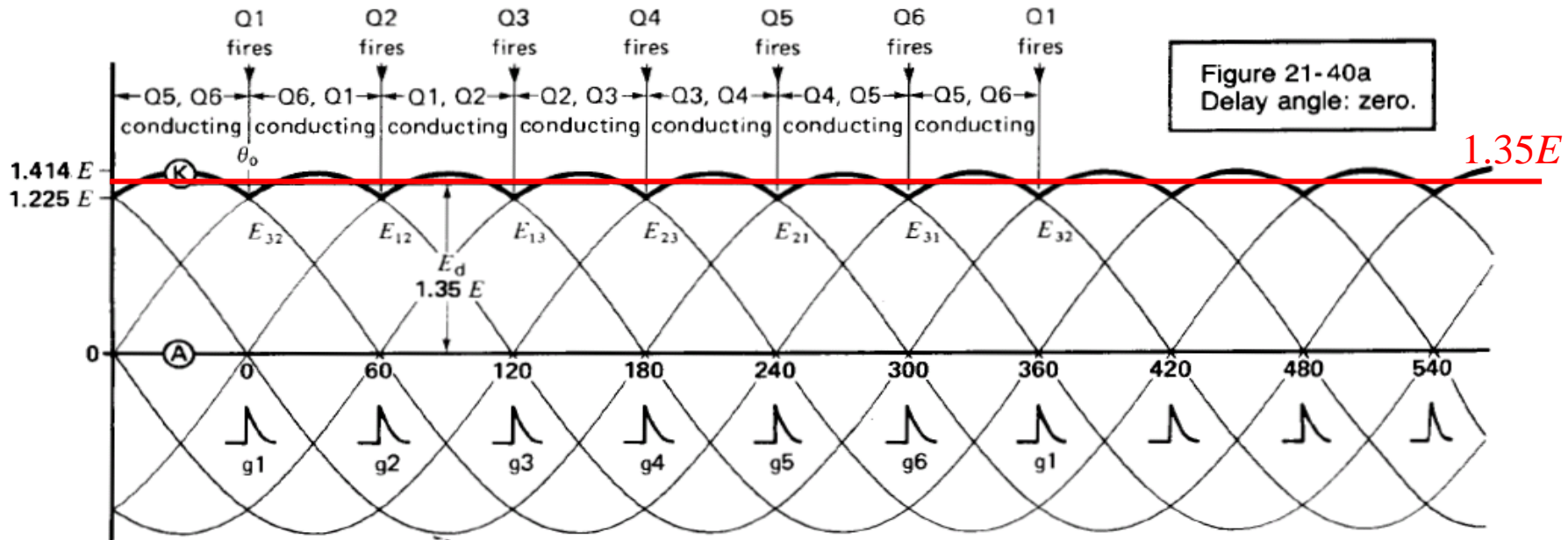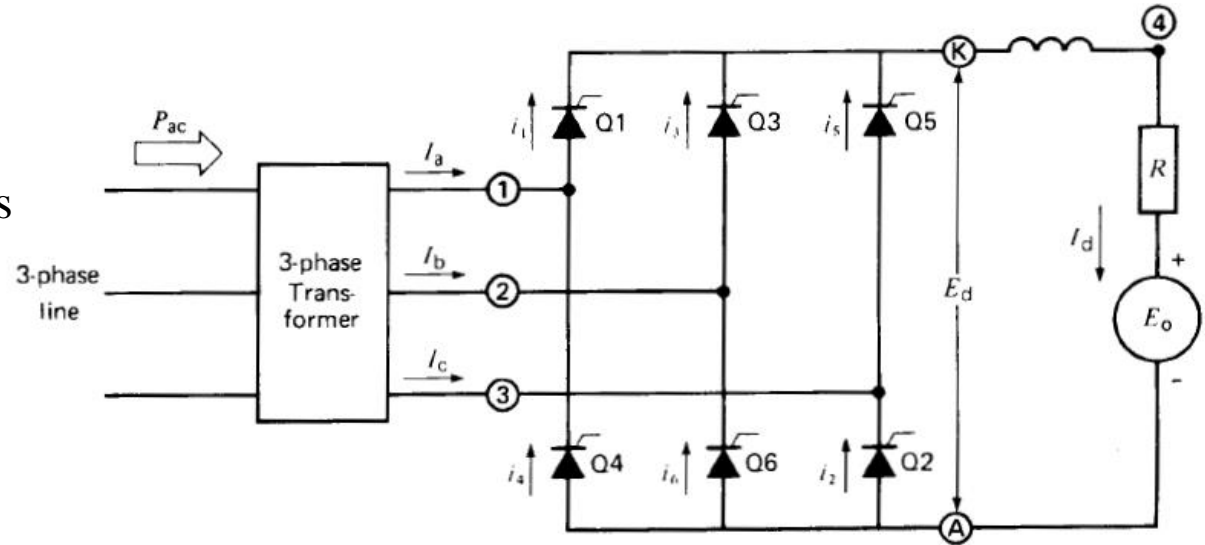

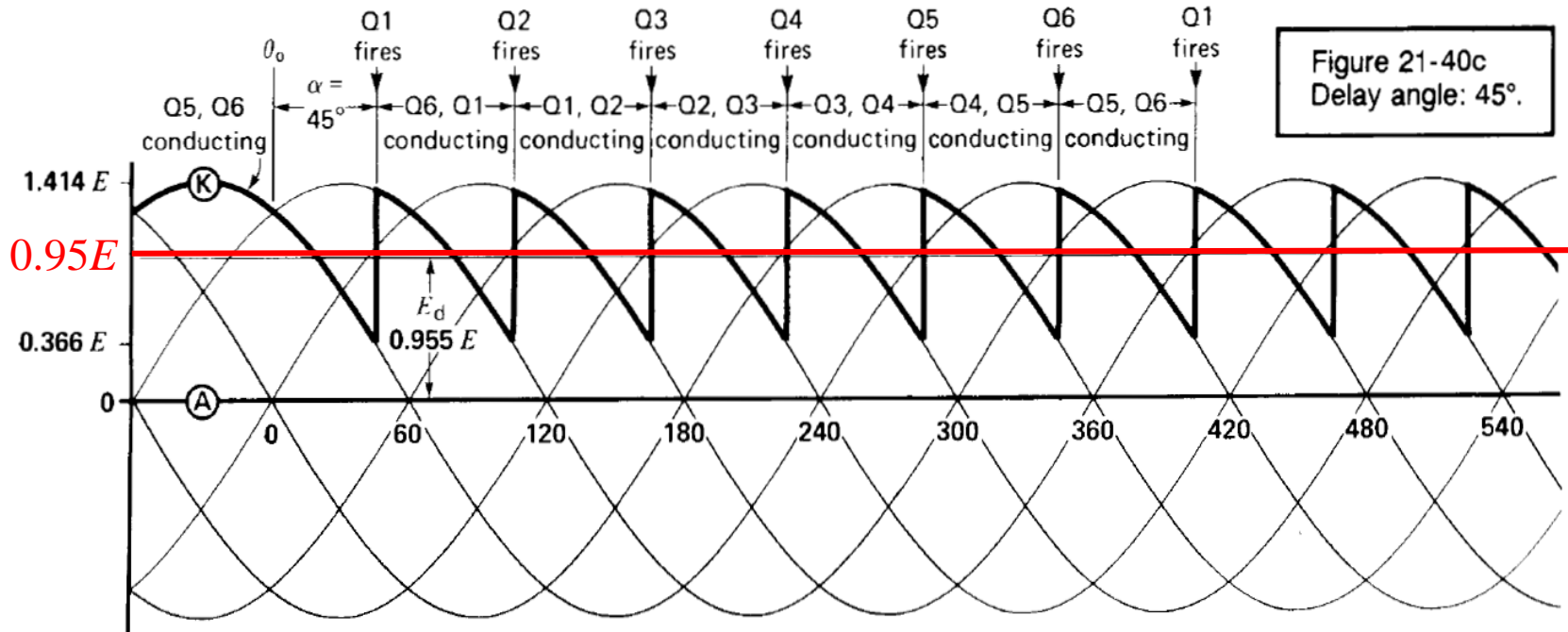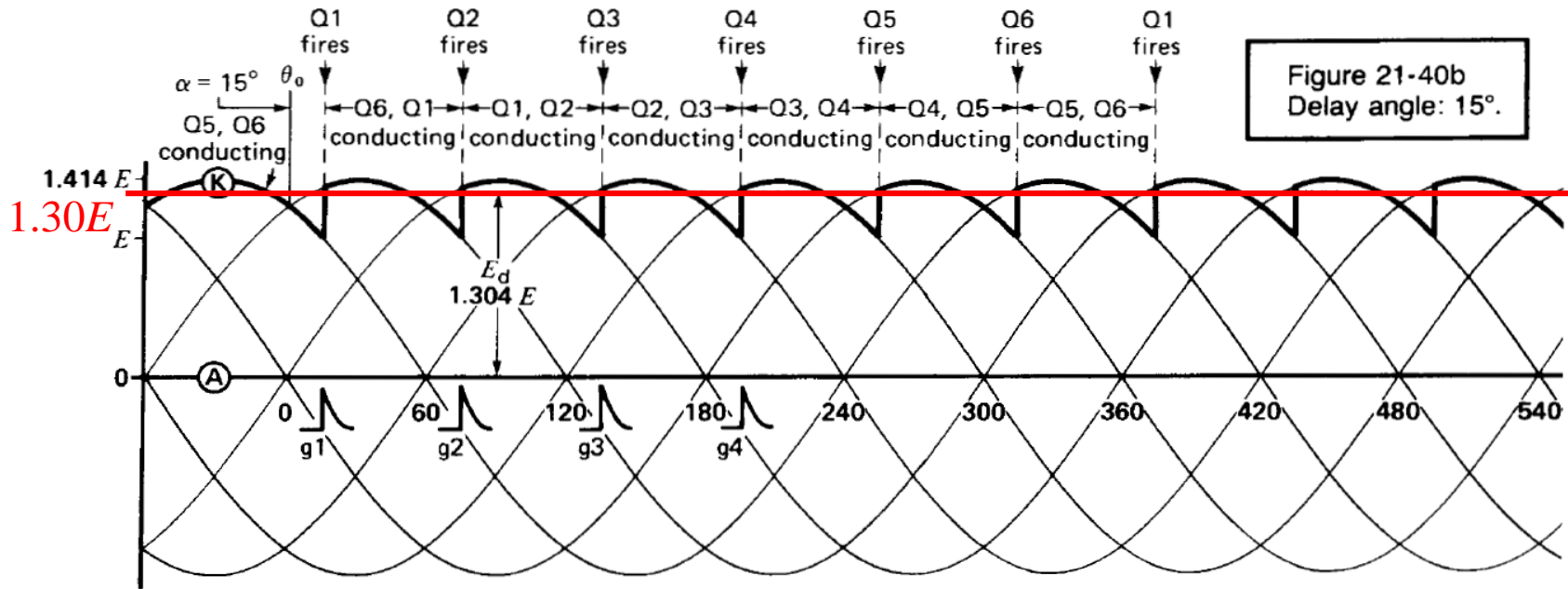

Step-down DC-to-DC converter (buck chopper)




- To transfer power from a high-voltage DC source E_S to a lower-voltage DC load E_O , one solution is to connect them by an inductor and to open and close the circuit periodically

- When switch closes, energy is transferred from E_S to E_O during time of closure T_1

$$E_S - E_O = L \frac{di}{dt} \quad \xrightarrow{\text{Integration}} \quad i = \frac{E_S - E_O}{L} t$$

$$I_a \triangleq i(T_1) = \frac{E_S - E_O}{L} T_1 \quad W = \frac{1}{2} LI_a^2$$

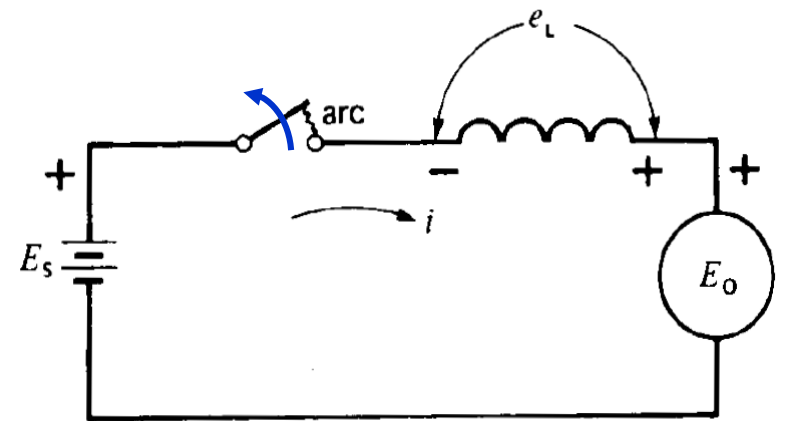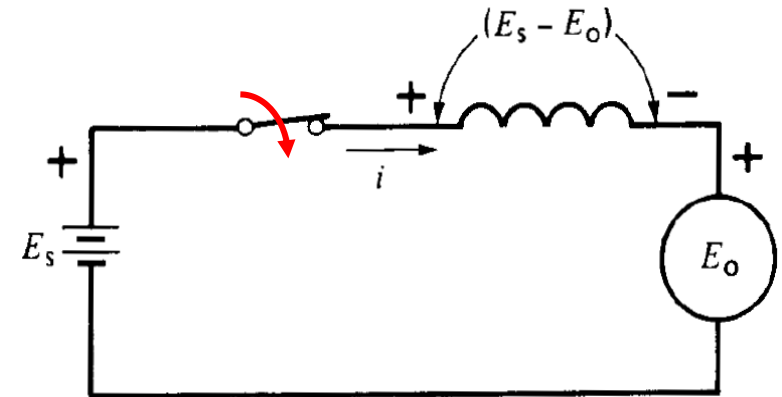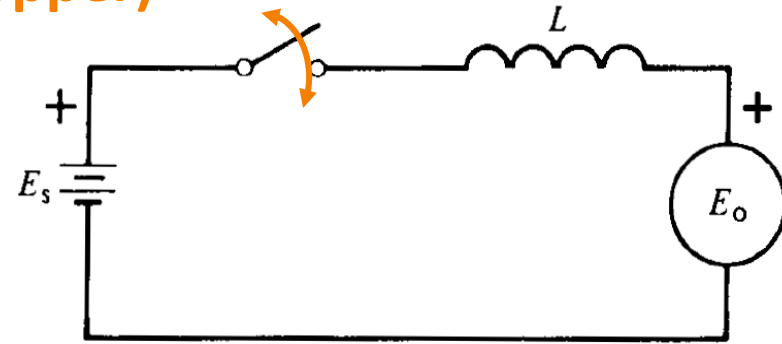- When the switch opens, magnetic energy W stored in the inductor is dissipated in the arc across the switch, so efficiency of power transfer is poor



1-Quadrant DC-to-DC converter

- Add an diode in order to deliver energy W to load E_o also when the switch opens:

$$L \frac{di}{dt} + E_o = 0 \quad \rightarrow \quad i - I_a = -\frac{E_o}{L} t$$

If i takes T_2 to become zero


$$I_a = \frac{E_o}{L} T_2$$

$$I_a = \frac{E_s - E_o}{L} T_1$$

$$E_o T_2 = (E_s - E_o) T_1$$


$$A_- = A_+$$

(from previous the slide)

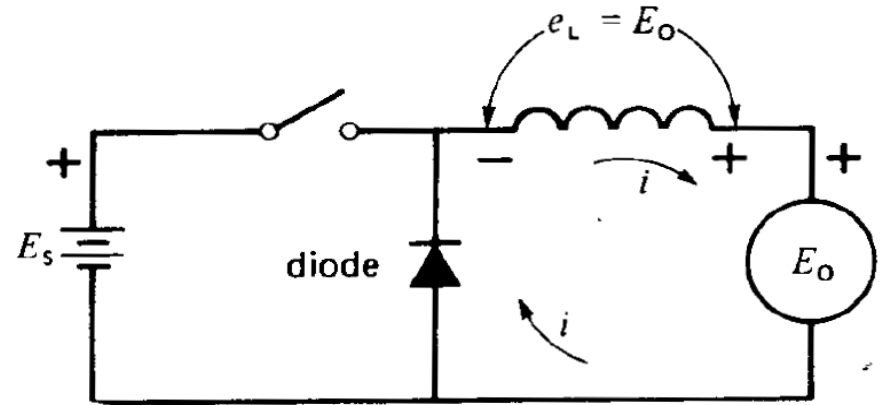

$$\frac{T_2}{T_1} = \frac{E_s - E_o}{E_o}$$

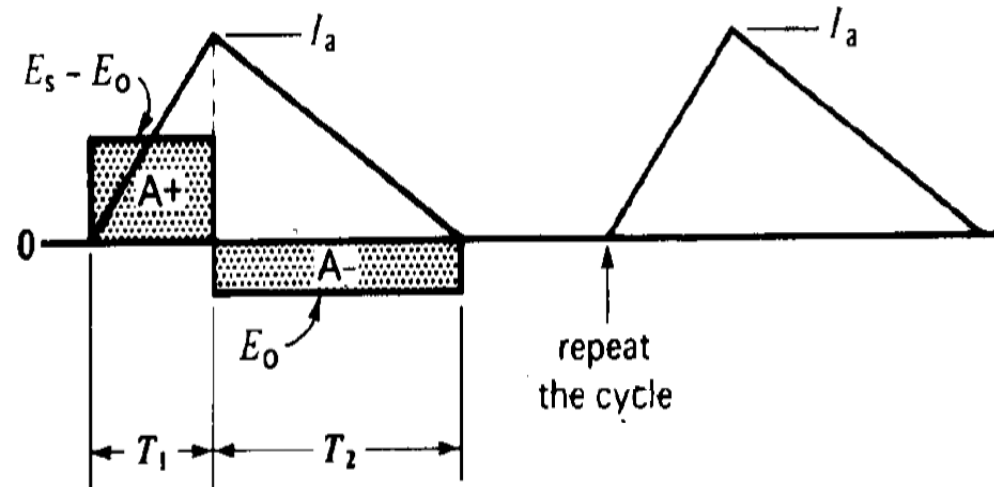- The inductor absorbs energy at a relatively high voltage ($E_s - E_o$) and delivers it at a lower voltage E_o
- This circuit enables us to transfer energy without incurring any losses
- In reality, the mechanical switch is replaced by a controllable semi-conductor switch (GTO, MOSFET or IGBT).



Rapid switching

- Open and close the switch rapidly so that the current increases and decreases in a narrow range between I_a and I_b
 - When the current falls to I_b (after T_b), the switch recloses
 - When the current rises to I_a (after T_a), the switch reopens

- Duty cycle:

$$D = T_a / (T_a + T_b) = T_a / T < 1$$

- Average DC current to the load:

$$I_o = (I_a + I_b) / 2$$

- Average DC current from the source:

$$I_s = I_o (T_a / T) = I_o D \Rightarrow I_o = I_s / D$$

- If there is no power loss

$$E_s I_s = E_o I_o = E_o I_s / D \Rightarrow E_o = D E_s$$

DC output voltage can simply be controlled by varying the duty cycle

- See Example 21-11

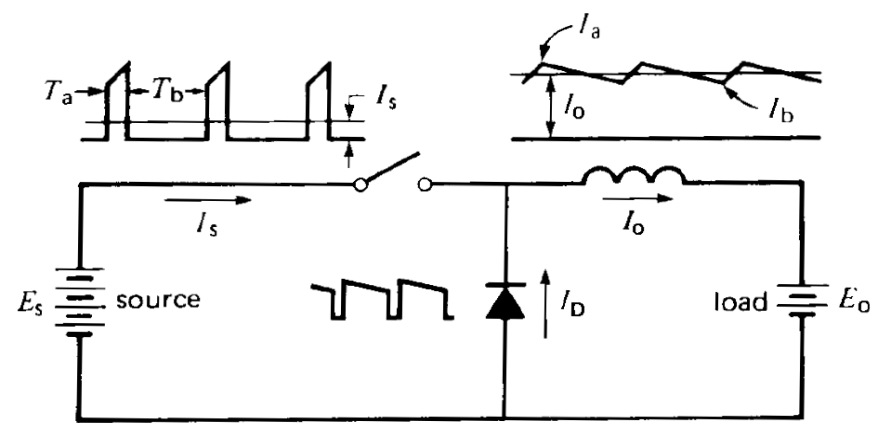


Figure 21.60a

Currents in a chopper circuit.

$$I_a - I_b = \frac{E_s - E_o}{L} T_a = \frac{E_o}{L} T_b$$

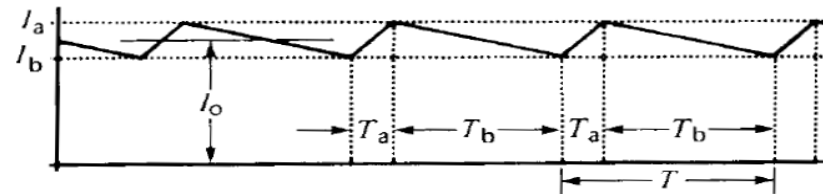


Figure 21.60b

Current in the load.

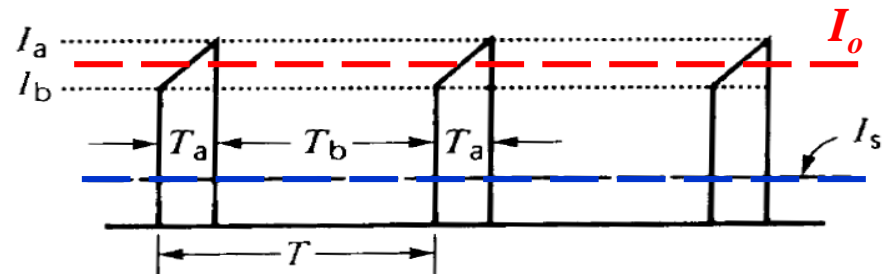


Figure 21.60c

Current pulses provided by the source.

Impedance transformation

Duty cycle $D < 1$

$$I_o = I_s / D \quad E_o = D E_s$$

$$R_o = E_o / I_o$$

$$R_s = E_s / I_s = (E_o / D) / (I_o D) \\ = R_o / D^2$$


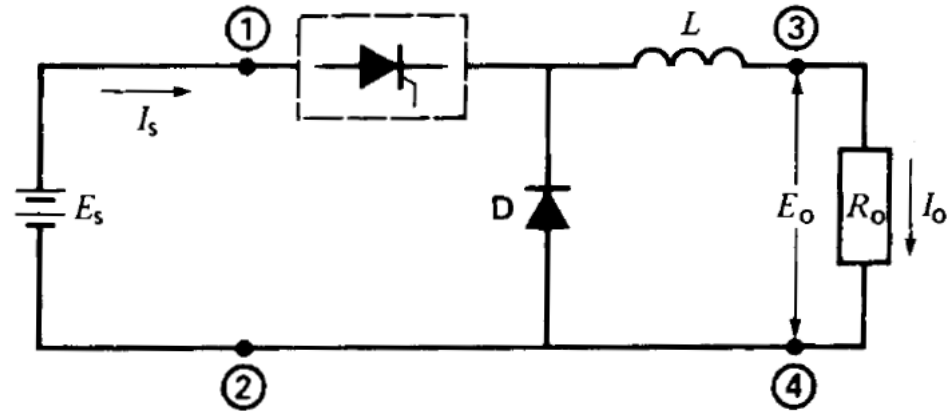
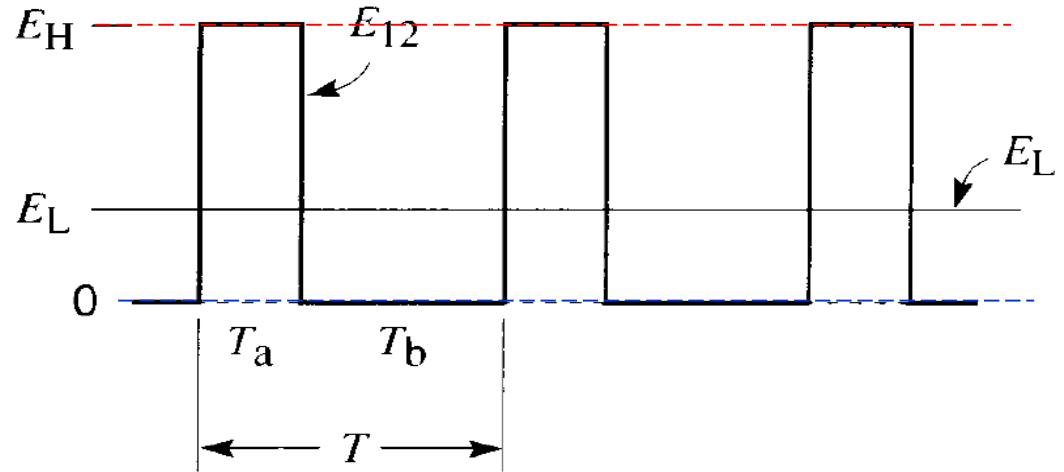


Figure 21.62

A chopper can make a fixed resistor R_o appear as a variable resistance between terminals 1-2.

- The 1-quadrant DC-to-DC converter can transform the resistance of a fixed resistor to a higher value depending on D .
 - It behaves like a DC transformer whose turns ratio is $1/D$
 - Unlike a transformer, which allows power to flow bi-directionally, a step-down chopper can transfer power only from the high-voltage side to the low-voltage side
- See Example 21-12

2-quadrant DC-to-DC converter

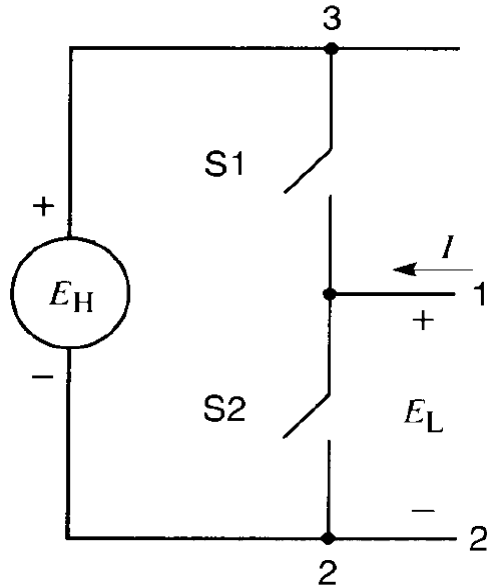

- Consider two mechanical switches S1 and S2 that open and close alternatively
 - Within the time of a cycle $T=T_a+T_b$, S1 is closed for T_a and S2 is closed for T_b
 - S1 has duty cycle $D=T_a/T$ and S2 has duty cycle $T_b/T=(1-D)$
 - Output voltage E_{12} fluctuates between E_H and 0, having the average DC output

$$E_L=DE_H \quad (\text{variable by varying } D)$$

• 2-quadrant converter:

- **Specific voltage polarity:** Terminal 1 is always (+) with respect to terminal 2
- **Bidirectional current:** current and power can flow from E_H to E_L , or vice versa since current always circulate through either S1 or S2

- Assume the load to be a battery E_o with internal resistance R
 - Use inductor L as a buffer between the fluctuating E_{12} and constant E_o
- Average current $I_L = (E_L - E_o) / R$
- If average DC voltage $E_L = E_o$, then $I_L = 0$ and no dc power exchange happens

- **Step-down chopper (buck mode):**

- If $E_L > E_o$, power = $|E_L I_L|$ flows to E_o

- **Step-up chopper (boost mode):**

- If $E_L < E_o$, power = $|E_L I_L|$ flows to E_H

- In reality, mechanical switches S1 and S2 are replaced by semi-conductor switches Q1 and Q2 each with a diode placed in antiparallel for bi-directional currents
- Q1 and Q2 cannot be closed at the same time to avoid a short-circuit across E_H ; in each half cycle, they both open for a very brief **dead time** (zero current from E_H) for a safety margin

- See Example 21-13

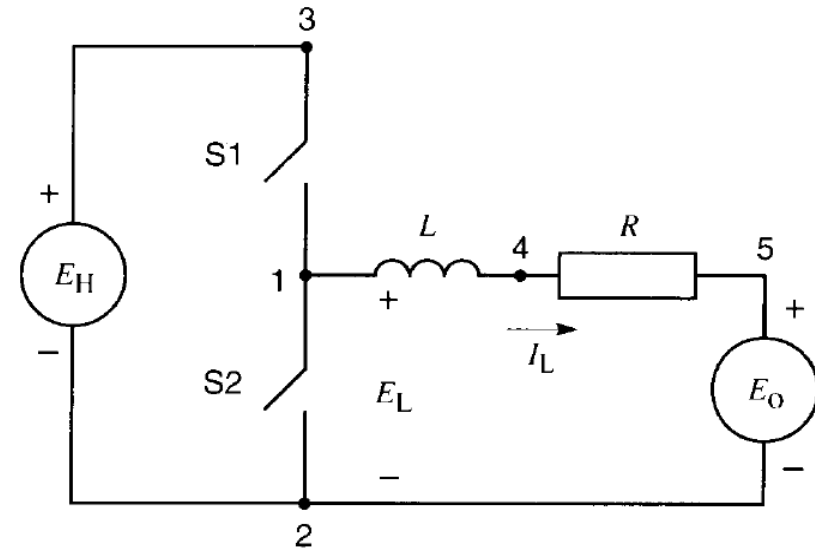


Figure 21.64

Power can flow from E_H to E_o and vice versa.

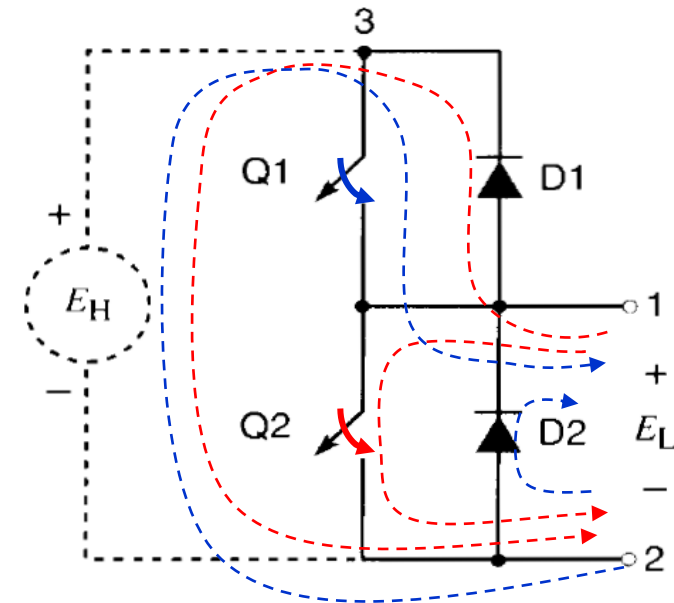


Figure 21.69

Two-quadrant electronic converter.

Output voltage ripple filter

- A LC low-pass filter is applied to create almost flat DC output voltage E_o
- Ripples only appear in I_L , not I_o .

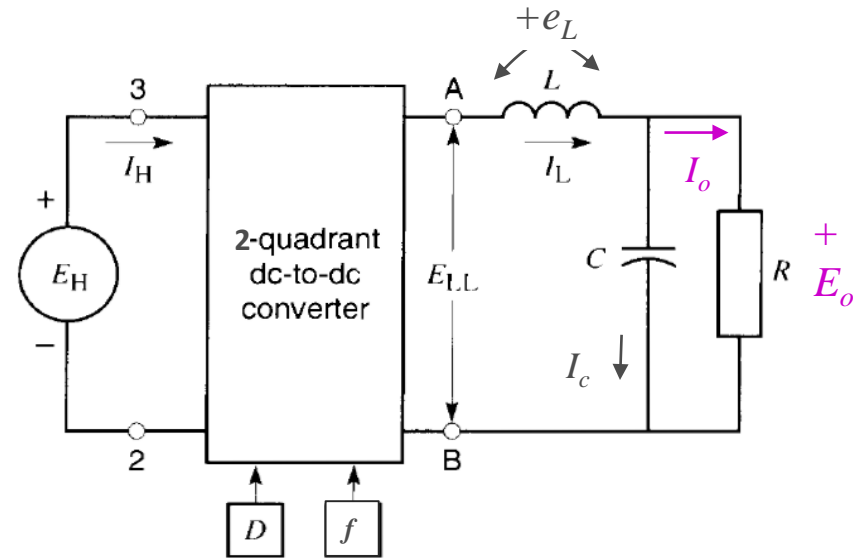
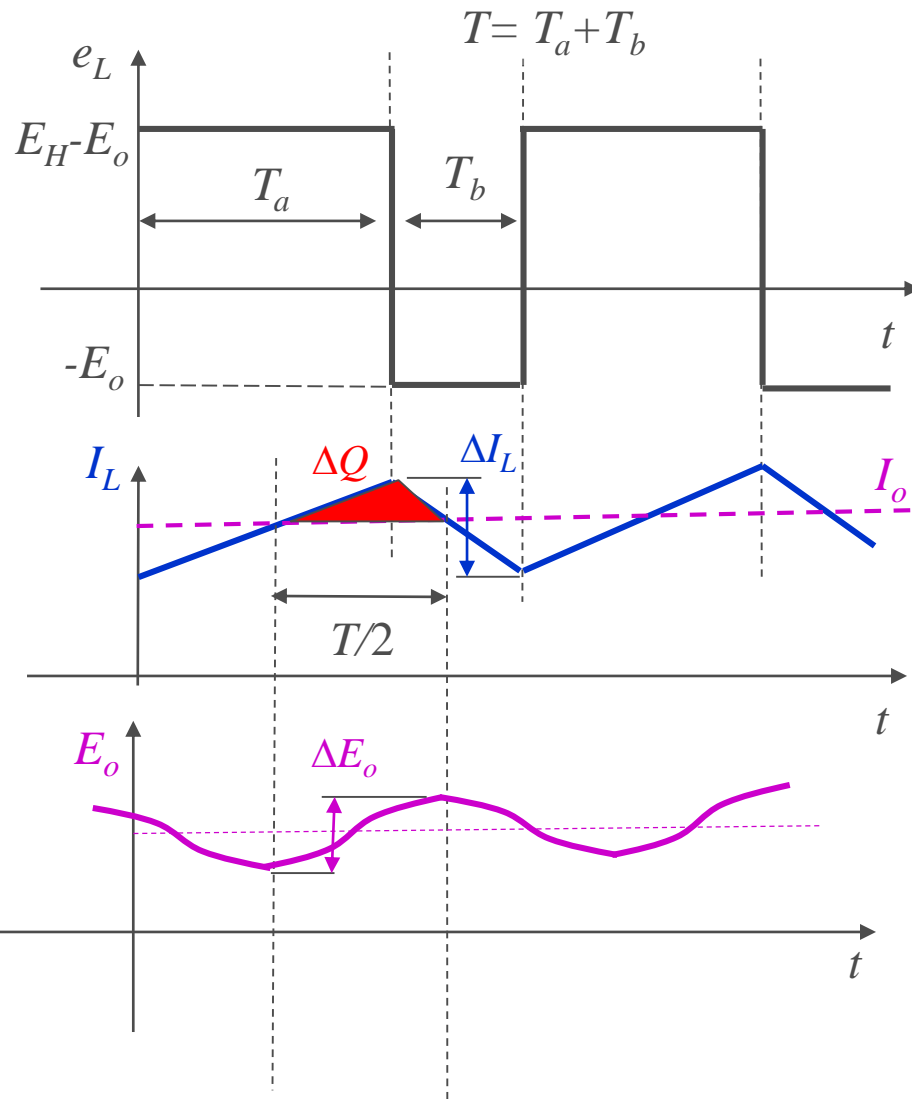


Figure 21.73

Four-quadrant dc-to-dc converter feeding a passive dc load R .

$$f_{LC} = \frac{1}{2\pi\sqrt{LC}} \ll f = \frac{1}{T}$$


$$\Delta I_L = \frac{E_o}{L} T_b = \frac{E_o}{L} (1-D)T$$

$$\Delta Q = \int I_c dt = \frac{1}{2} \frac{\Delta I_L}{2} \frac{T}{2} = \frac{\Delta I_L T}{8} = \frac{E_o}{8L} (1-D)T^2$$

$$\frac{\Delta E_o}{E_o} = \frac{\Delta Q}{CE_o} = \frac{(1-D)T^2}{8LC} = \frac{\pi^2(1-D)}{2} \left(\frac{f_{LC}}{f} \right)^2 \approx 0$$

4-quadrant DC-to-DC converter

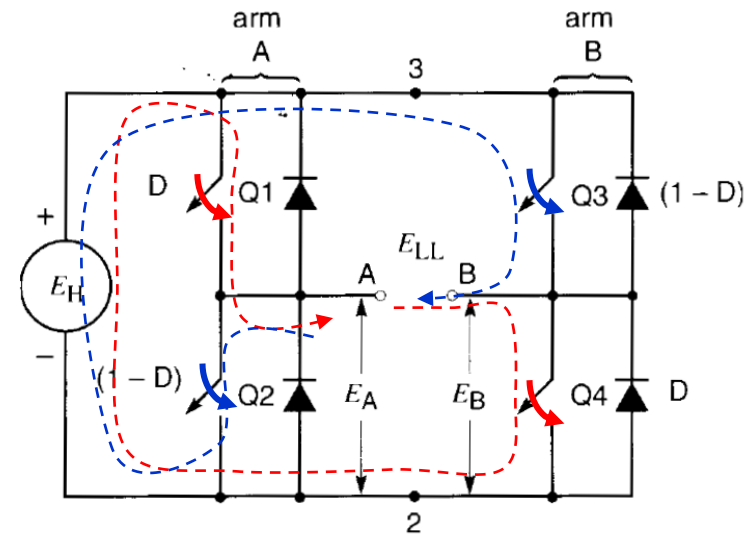- It consists of two identical 2-quadrant converters having the same switching frequency, e.g. 100kHz
- **Switching rules:**
 - Q1 and Q2 on arm A open and close alternately
 - Q3 and Q4 on arm B open and close alternately
 - Q1 and Q4 open and close simultaneously (duty cycle D)
 - Q2 and Q3 open and close simultaneously (duty cycle $1-D$)



$$E_{A2} = DE_H \quad E_{B2} = (1-D)E_H$$

$$E_{LL} = E_{A2} - E_{B2} = (2D-1)E_H$$

- **4-quadrant:**

- E_{LL} changes between $-E_H$ and $+E_H$
- The DC current flow of the load between A and B is bidirectional

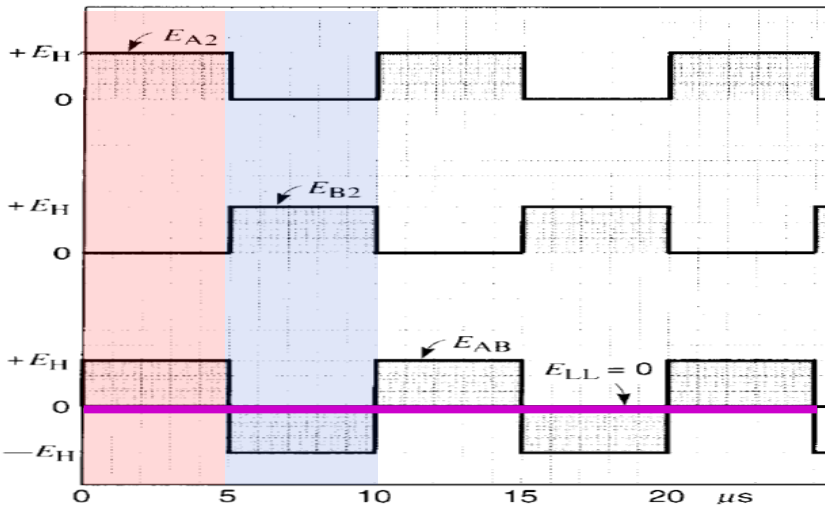


Figure 21.71
Voltage output when $D = 0.5$. The average voltage is zero.



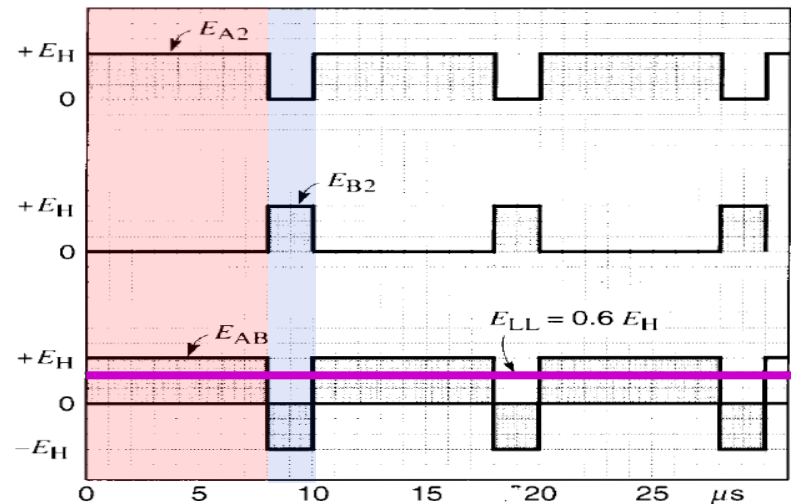


Figure 21.72
Voltage output when $D = 0.8$. The average voltage E_{LL} is $0.6 E_H$.

DC-to-AC rectangular wave converter

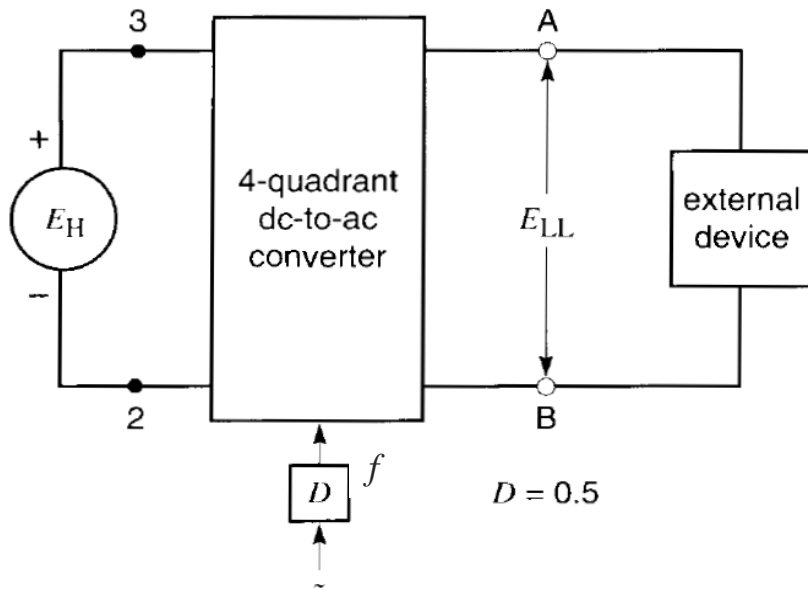




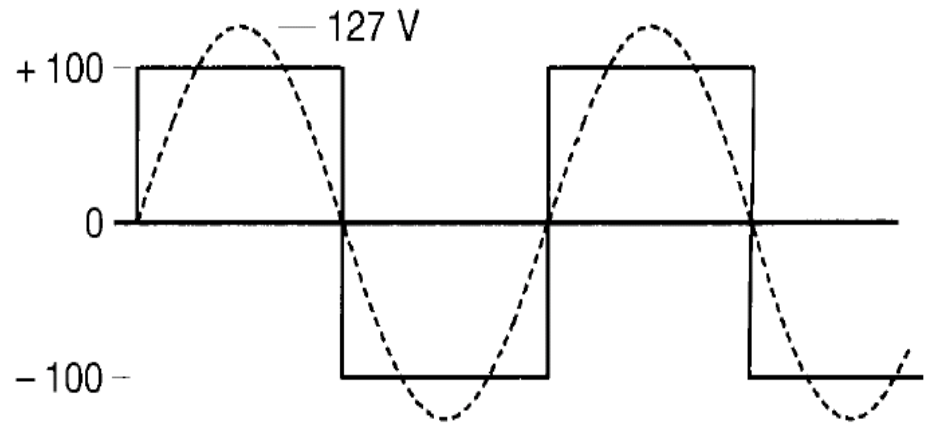
$$E_{LL} = \frac{400}{\pi} \left[\sin(2\pi ft) + \frac{1}{3} \sin(6\pi ft) + \frac{1}{5} \sin(10\pi ft) + \dots \right]$$



- The 4-quadrant converter with $D=0.5$ is able to transform a DC voltage E_H into a rectangular AC voltage $\pm E_H$, which contains a fundamental sinusoidal component having an amplitude of $1.27E_H$ and an effective value of $1.27E_H/\sqrt{2}=0.90E_H$
- It is bidirectional (DC-to-AC and AC-to-DC) and frequency-variable
- The output has a fixed amplitude and large 3rd, 5th and 7th harmonics.

PWM (pulse width modulation)

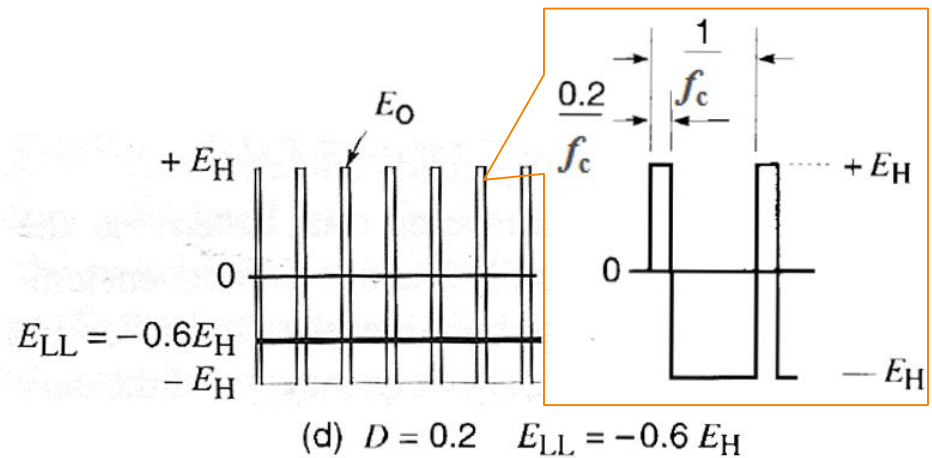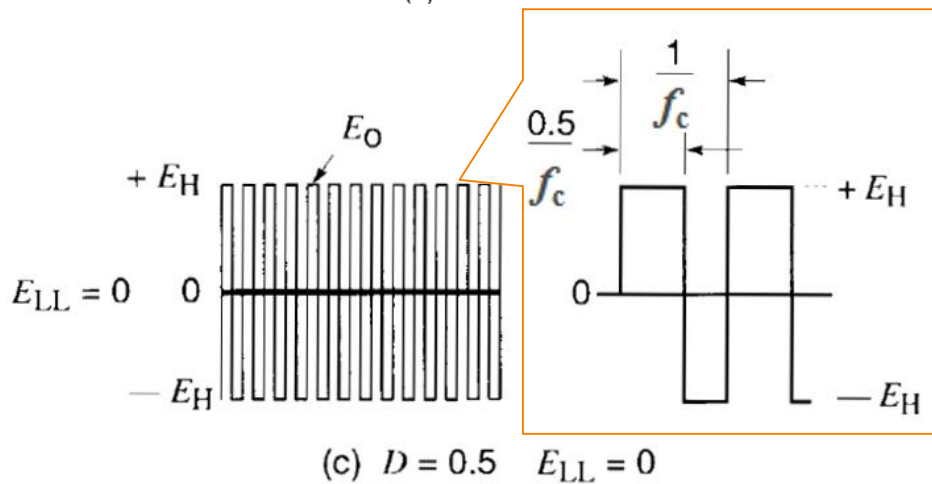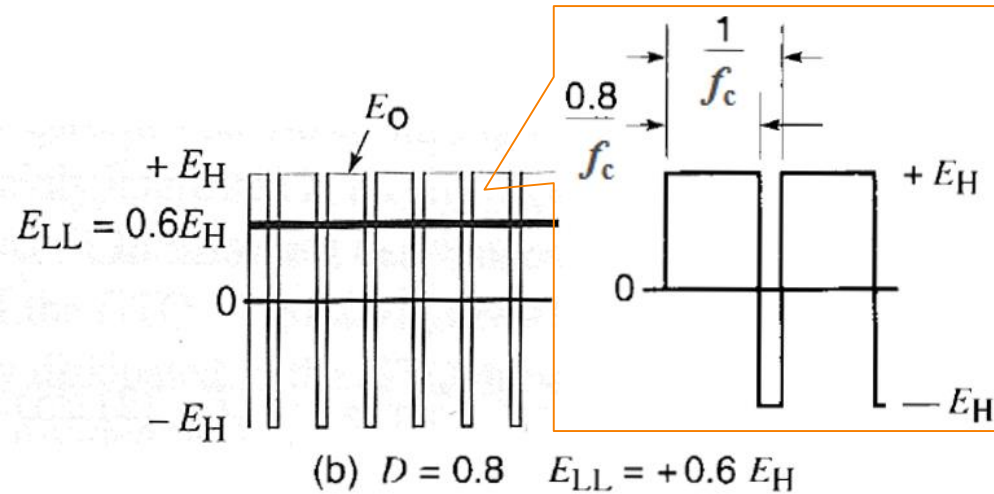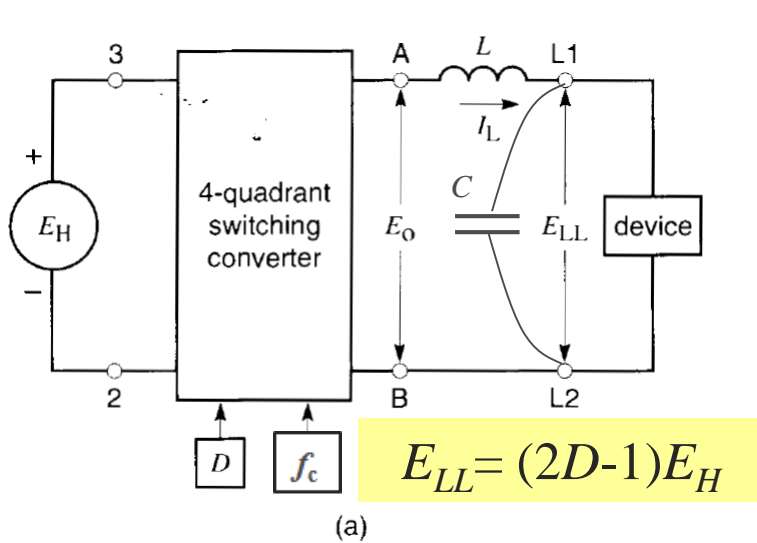- 4-quadrant DC-to-DC converter using a carrier frequency f_c and different values of D







- To obtain $E_{LL}(t) =$ a periodical waveform $g(t)$,

$$D(t) = \frac{g(t)}{2E_H} + \frac{1}{2}$$

DC-to-AC non-sine wave converters with PWM

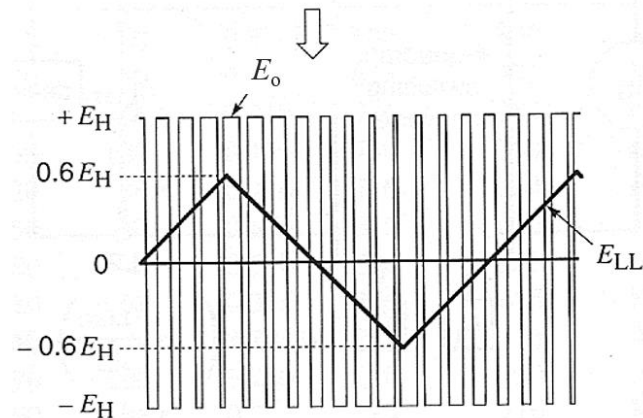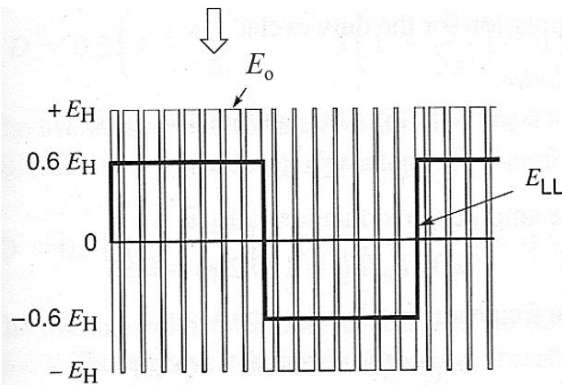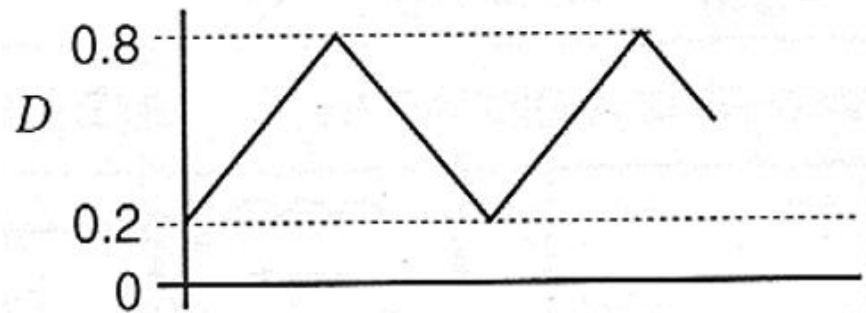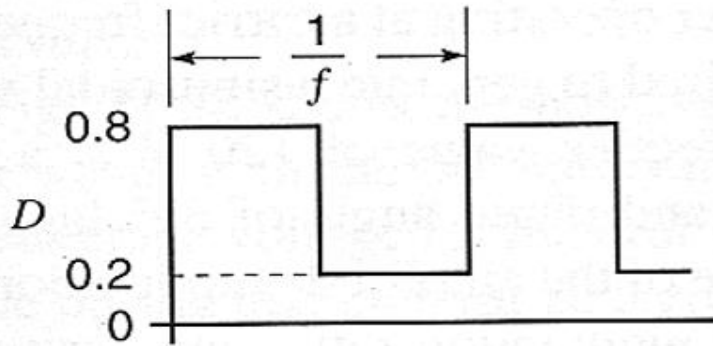- With D varying periodically between 0.8 and 0.2 at a frequency $f < 0.1f_c$
- Although f_c is fixed, the ON/OFF pulse widths change continually with D .
- That is why this type of switching is called **Pulse Width Modulation (PMW)**



DC-to-AC sine wave converter with PMW

- To obtain $E_{LL}(t) = E_m \sin(2\pi ft + \theta)$

$$D(t) = \frac{E_m}{2E_H} \sin(2\pi ft + \theta) + \frac{1}{2}$$

Amplitude modulation ratio $m = E_m / E_H$

Frequency modulation ratio $m_f = f_c / f = T / T_c$

- Create a 83.33Hz sine voltage wave with peak value $E_m = 100V$ using a DC-to-AC converter with $E_H = 200V$ and $f_c = 1000Hz$:

$$T = 1/83.33 = 0.012s = 12000\mu s$$

$$T_c = 1/1000 = 1000\mu s$$

$m_f = T / T_c = 12$, so each T_c covers $360/12 = 30^\circ$

Calculate D for $\phi(t) = 2\pi ft + \theta = 0^\circ, 30^\circ, 60^\circ, \dots$, which correspond to $E_{LL} = 100 \sin \phi$ (V)

In each carrier period T_c , Q1&Q4 are ON for first $DT_c = 1000D$ (μs) and then Q2&Q3 are ON for the remaining $(1-D)T_c = 1000(1-D)$ (μs)

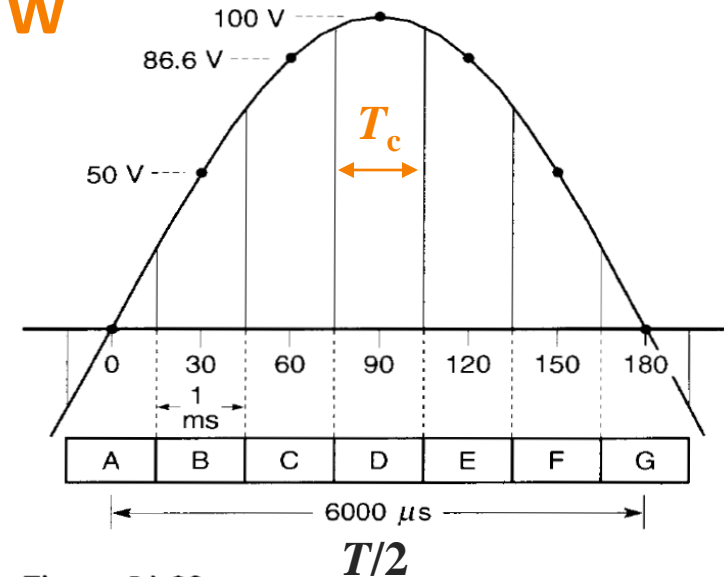


Figure 21.82
Positive half-cycle of the fundamental 83.33 Hz voltage comprises six carrier periods of 1 ms each.

TABLE 21E GENERATING A SINE WAVE

angle [deg]	E_{LL} [V]	D	Q1, Q4 on [μs]	Q2, Q3 on [μs]	interval
0	0	0.5	500	500	A
30	50	0.625	625	375	B
60	86.6	0.716	716	284	C
90	100	0.75	750	250	D
120	86.6	0.716	716	284	E
150	50	0.625	625	375	F
180	0	0.5	500	500	G
210	-50	0.375	375	625	H
240	-86.6	0.284	284	716	I
270	-100	0.250	250	750	J
300	-86.6	0.284	284	716	K
330	-50	0.375	375	625	L
360	0	0.5	500	500	M

DC-to-AC sine wave converter with Bipolar/Unipolar PWM

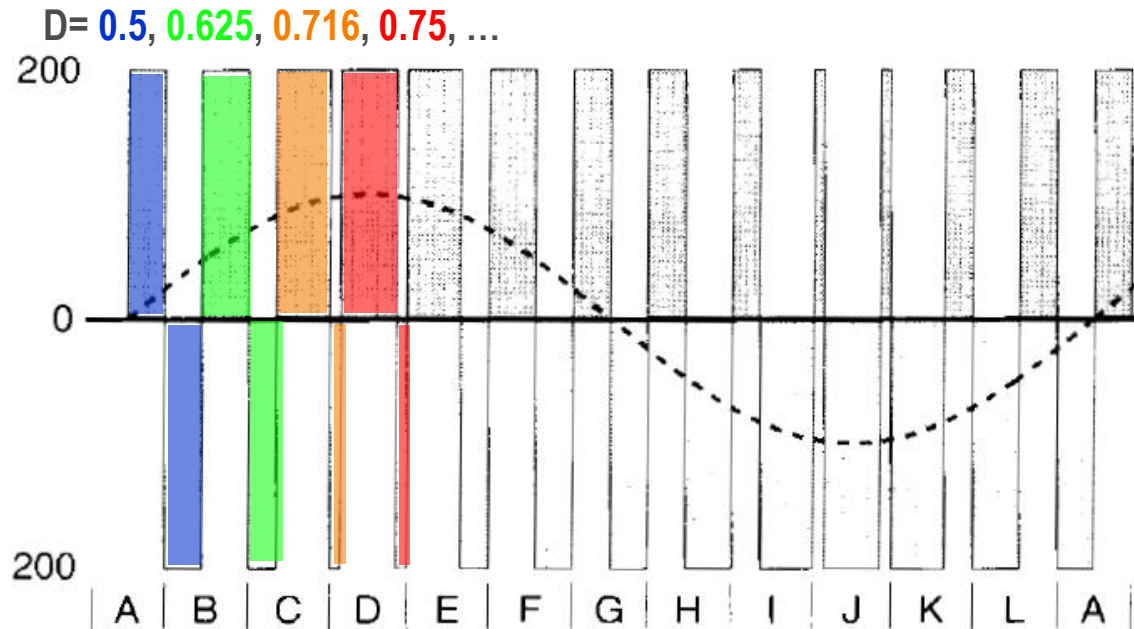


Figure 21.83

Alternative (+) and (-) pulses contain the sinusoidal component.

- Once the carrier frequency is filtered out, the resulting voltage will be sinusoidal
- A higher carrier frequency would yield a better sinusoidal waveform but would increase the power losses of the electronic switches, e.g. IGBTs

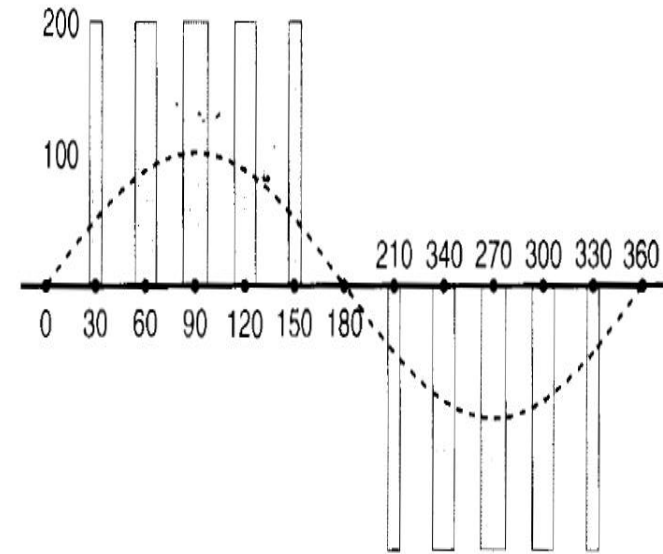


Figure 21.84

Sequential (+) and (-) pulses contain the sinusoidal components.