

45. For the circuit of Fig. 13.65, $v_s = 117 \sin 500t$ V. Calculate v_2 if the terminals marked a and b are (a) left open-circuited; (b) short-circuited; (c) bridged by a 2Ω resistor.


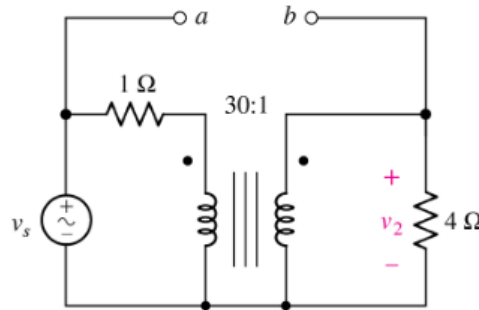


FIGURE 13.65

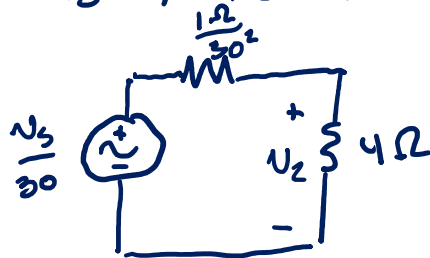a) Reflect v_s & the 1Ω resistor through the transformer



$$V_2 = \frac{v_s}{30} \left(\frac{4}{4 + \frac{1}{30^2}} \right)$$

≈ 1


$$V_2 \approx \frac{v_s}{30} = 3.9 \sin 500t \text{ V}$$

exact amplitude : 3.899


b) when shorted, $v_s = v_2$

$$V_2 = 117 \sin 500t \text{ V}$$


c) split v_s into two:

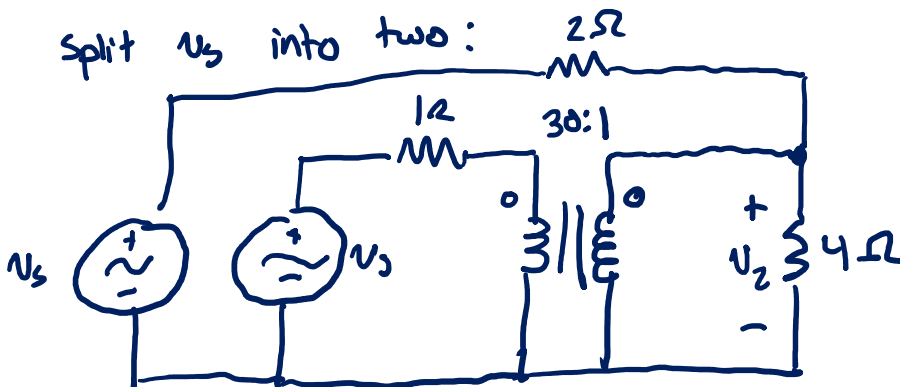

Redraw:

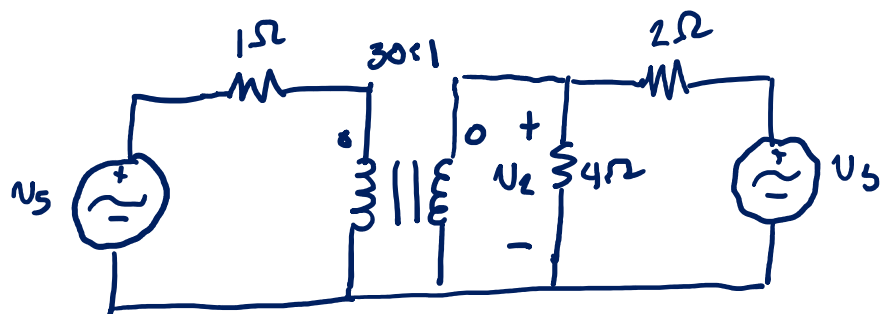

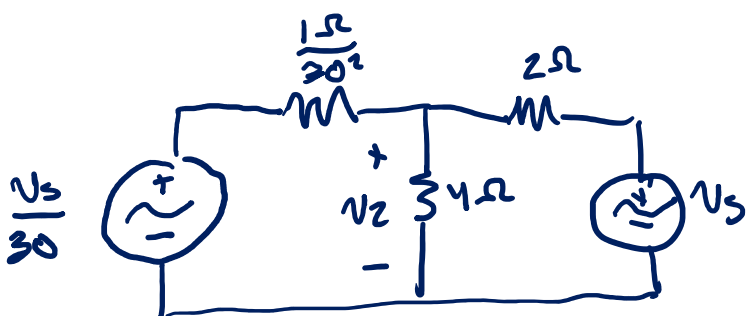Reflect the left side through the transformer



Superposition:

$$v_2 = \frac{v_s}{30} \frac{4 \parallel 2}{\frac{1}{30^2} + 4 \parallel 2} + v_s \frac{4 \parallel \frac{1}{30^2}}{2 + 4 \parallel \frac{1}{30^2}}$$

$\underbrace{\hspace{10em}}_{\approx 1} \qquad \underbrace{\hspace{10em}}_{\approx \phi}$

$$v_2 \approx \frac{v_s}{30} = 3.9 \sin 500t$$

exact: $3.96 \sin 500t$