

60. The circuit in **Fig. 11.51** uses a Pi network to match the impedance between source and load for maximum power transfer. A 60 Hz source has a series impedance of  $50 + j5 \Omega$ . What load impedance would a Pi network with  $C_S = 70.1 \mu\text{F}$ ,  $C_L = 39.8 \mu\text{F}$ , and  $L = 0.225 \text{ H}$  correspond to for maximum power transfer?


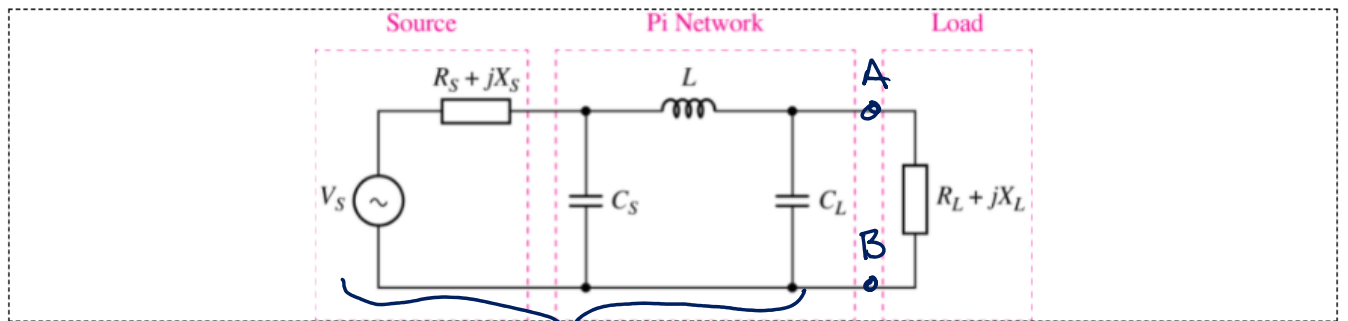


FIGURE 11.51

$$\omega = 2\pi 60$$

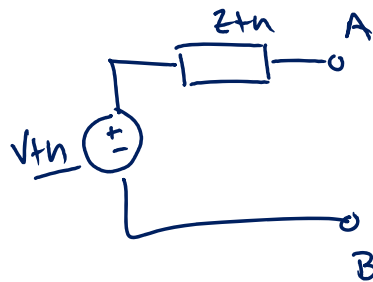

$$Z_{th} = \left( \left[ (R_s + jX_s) \parallel \frac{-j}{\omega C_S} \right] + j\omega L \right) \parallel \frac{-j}{\omega C_L}$$

MATLAB Calculation:

```
w = 2*pi*60
Zs = 50 + 1j*5;
ZCs = -1j/w/70.1e-6;
ZCL = -1j/w/39.8e-6;
ZL = 1j*w*225e-3;

Zeq1 = 1/(1/Zs + 1/ZCs);
Zth = 1/(1/(Zeq1 + ZL) + 1/ZCL)


>> Zth = 2.0068e+02 - 1.2038e+00i
```

$$Z_{th} = 200 - j1.2$$

for maximum power  $Z_L = Z_{th}^*$

$$\text{so } Z_L = Z_{th}^* = R_L + jX_L = 200 + j1.2$$

# Validate with LTSpice

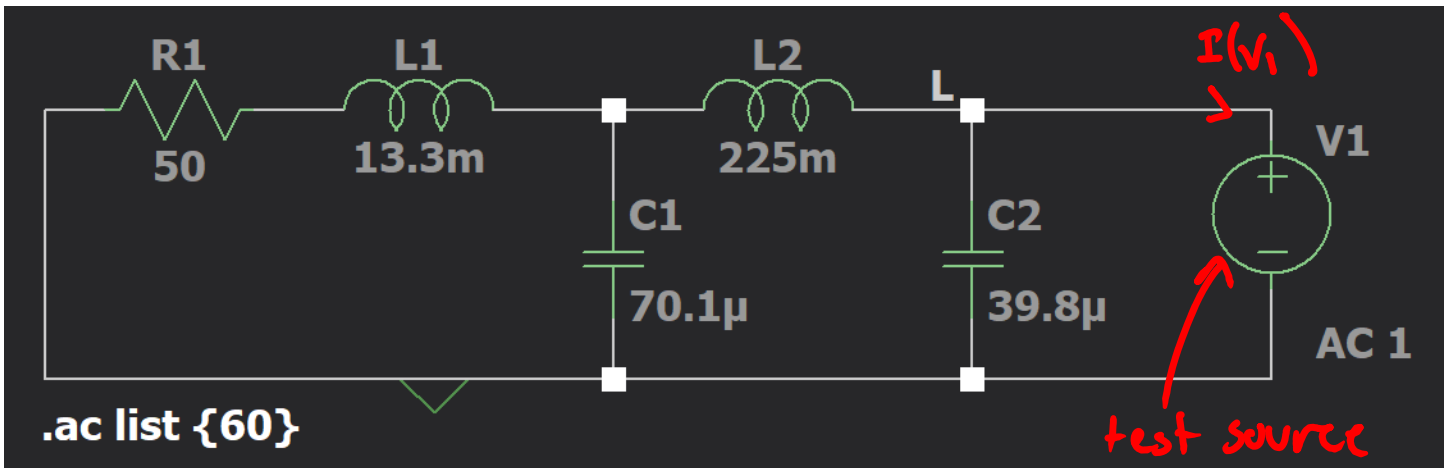

\* H:\Courses\ECE 202\Spring 2022\Solutions\Draft1.asc

--- AC Analysis ---

frequency:	60	Hz		
V(n001):	mag: 0.499204	phase: -128.304°	voltage	
V(n002):	mag: 0.501718	phase: -122.577°	voltage	
V(L):	mag: 1	phase: -2.42657e-020°	voltage	
I(C2):	mag: 0.0150042	phase: 90°	device_current	
I(C1):	mag: 0.0132589	phase: -32.5772°	device_current	
I(L2):	mag: 0.0157818	phase: 108.411°	device_current	
I(L1):	mag: 0.00998409	phase: 51.6964°	device_current	
I(R1):	mag: 0.00998409	phase: -128.304°	device_current	
I(V1):	mag: 0.00498454	phase: -179.652°	device_current	

$$Z_{th} = \frac{v(V_1)}{-I(V_1)} = \frac{140^\circ \text{ V}}{-4.984 \angle -179.6^\circ \text{ mA}}$$

$$= -200 \angle 179.6^\circ \Omega$$

$$= 200 - j1.2 \Omega \quad \checkmark$$