

36. With regard to the circuit depicted in [Fig. 14.44](#), the initial voltage across the capacitor is $v(0^-) = 1.5$ V and the current source is $i_s = 700u(t)$ mA. (a) Write the differential equation which arises from KCL, in terms of the nodal voltage $v(t)$. (b) Take the Laplace transform of the differential equation. (c) Determine the frequency-domain representation of the nodal voltage. (d) Solve for the time-domain voltage $v(t)$.

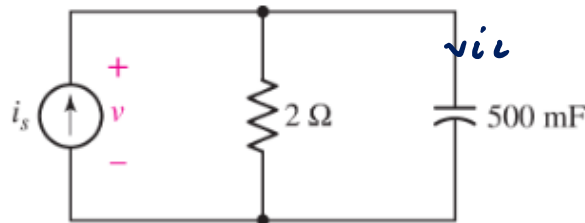


FIGURE 14.44

$$(a) \quad i_s(t) = \frac{v(t)}{2\Omega} + (500 \text{ mF}) \frac{dv(t)}{dt}$$

$$(b) \quad I(s) = \frac{1}{2}V(s) + \frac{1}{2} [sV(s) - v(0^-)]$$

$$I(s) = \mathcal{L}\{0.7u(t)\} = 0.7 \frac{1}{s}$$

$$v(0^-) = 1.5$$

$$\frac{0.7}{s} = \frac{1}{2}V(s) + \frac{s}{2}V(s) - \frac{1.5}{2}$$

$$(c) \quad v(s) = \frac{\left(\frac{0.7}{s} + \frac{1.5}{2}\right)}{\left(\frac{1}{2} + \frac{s}{2}\right)} = \frac{1.4 + 1.5s}{s + s^2}$$

$$(d) \quad \frac{1.4 + 1.5s}{s(s+1)} = \frac{k_1}{s} + \frac{k_2}{s+1}$$

$$\begin{cases} k_1 = \left. \frac{1.4 + 1.5s}{s+1} \right|_{s=0} = 1.4 \\ k_2 = \left. \frac{1.4 + 1.5s}{s} \right|_{s=-1} = 0.1 \end{cases}$$

$$\mathcal{L}^{-1}\left\{\frac{1.4}{s} + \frac{0.1}{s+1}\right\} = \boxed{1.4u(t) + 0.1e^{-t}u(t)} = v(t)$$