



Phasor Superposition

3 frequencies
Phasor analysis doesn't apply?

Find $v_o(t)$ for $v_{in}(t) = 10\cos(\omega t) + 10\cos(2\omega t) + 10\cos(0.5\omega t)$
and $\omega = 2\pi 100 \text{ kHz}$, $R = 10 \Omega$, $L = 10 \mu\text{H}$, and $C = 253 \text{ nF}$

Apply superposition in the time domain

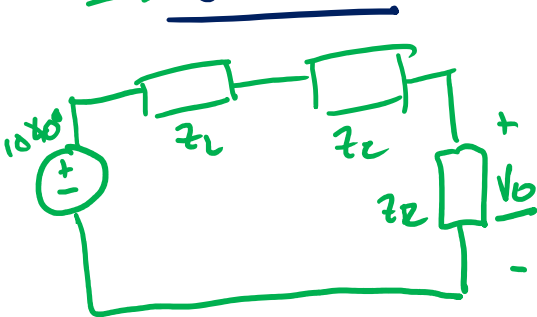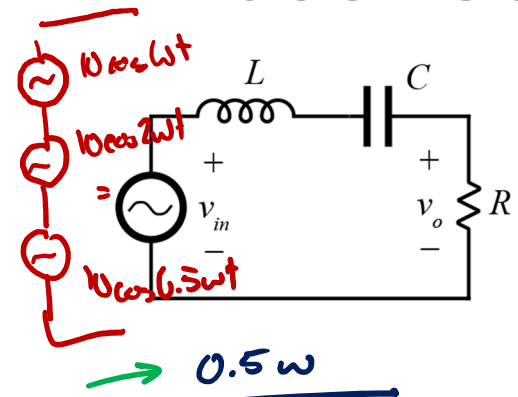$\omega_2 = 2\omega = 2\pi 200 \text{ kHz}$




$$\underline{V}_o = \underline{V}_{in} \frac{z_R}{z_L + z_C + z_R}$$

$$z_L = j(0.5\omega)L \quad z_C = \frac{-j}{(0.5\omega)C}$$

$$\underline{V}_o = 0.73 \angle 43^\circ$$
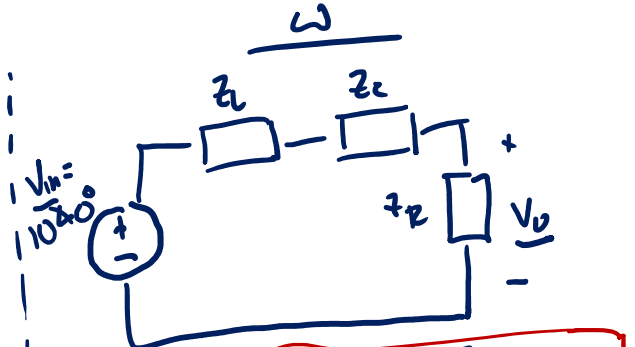
$$v_o(t) = 0.73 \cos(0.5\omega t + 43^\circ)$$



$$\underline{V}_o = \underline{V}_{in} \frac{z_R}{z_L + z_C + z_R}$$

$$\underline{V}_o = 10 \angle 0^\circ$$

$$v_o(t) = 10 \cos(\omega t)$$

$$z_C = \frac{-j}{(2\pi 200 \text{ kHz})(253 \text{ nF})} = -j\pi$$

$$z_L = j(\omega_2 L) = j(2\pi 200 \text{ kHz})(10 \mu\text{H}) = j4\pi$$

$$z_L = j(2\omega)L \quad z_C = \frac{-j}{(2\omega)C}$$

$$\underline{V}_o = 0.73 \angle -43^\circ$$

$$v_o(t) = 0.73 \cos(2\omega t - 43^\circ)$$

$$v_o(t) = 0.73 \cos(0.5\omega t + 43^\circ) + 10 \cos(\omega t) + 0.73 \cos(2\omega t - 43^\circ)$$

Example: WPT Problem

$$v_{tx}(t) = 100 \sin(2\pi 6.78 \text{ MHz } t)$$

