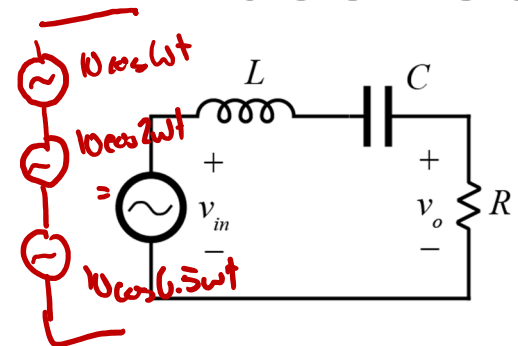


Phasor Superposition

3 frequencies

Phasor analysis doesn't apply



Find $v_o(t)$ for $v_{in}(t) = 10\cos(\omega t) + 10\cos(2\omega t) + 10\cos(0.5\omega t)$
and $\omega = 2\pi 100$ kHz, $R = 10 \Omega$, $L = 10 \mu\text{H}$, and $C = 253$ nF





Example: WPT Problem

