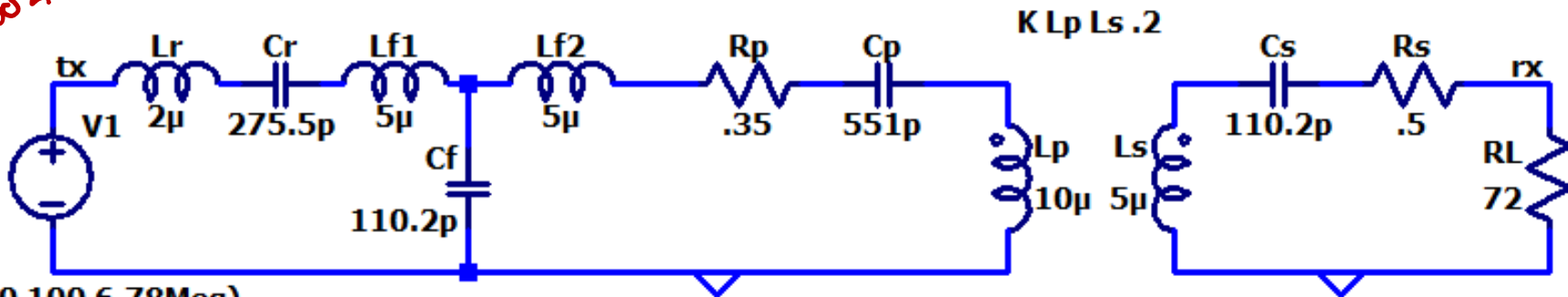


Circuit Solution Tips

- Stay symbolic as long as possible
 - Define new equivalent variables as necessary
- Order of analysis
 - Series/parallel equivalents
 - Source transformations
 - Transformer reflection
 - KVL/KCL equations (if you see a path forward)
 - Element Equations
 - Node Voltage / Mesh Current Analysis (otherwise)

Numerical Example

$V_{TX} = 100 \angle -90^\circ$



SINE(0 100 6.78Meg)

MATLAB Code:

```
Z1 = 1j*(w*Lr + w*Lf1 - 1/w/Cr);
Z2 = 1j/w/Cf;
Z3 = Rp + 1j*(w*Lf2 - 1/w/Cp);
Z4 = 1j*w*Lp;
Z5 = 1j*w*Lk;
Z6 = Rs - 1j/w/Cs;
```

```
Va = N*VTX*(Z1*Z2/(Z1+Z2))/(Z1*(Z3+Z1*Z2/(Z1+Z2)))*1/(1/Z4 ...
    + 1/(Z3 + Z1*Z2/(Z1+Z2)));
Za = N^2*1/(1/(Z3+Z1*Z2/(Z1+Z2)) + 1/Z4);
Zb = Z5*N^2;
```

```
VRX = Va*RL/(Za+Zb+Z6+RL);
```

```
mag = abs(VRX)
phase = angle(VRX)/pi*180
```

imaginary # j in MATLAB
j, i, 1j, 1i




for (i=0:5)

$Z_1 = i \cdot (\omega L_r \dots)$



mag =
28.0892
phase =
-90.0000


$V_{RX} = 28 \angle -90^\circ$
 $V_{RX}(t) = 28 \sin(2\pi 6.78 \text{ MHz } t)$

Circuit Simulation

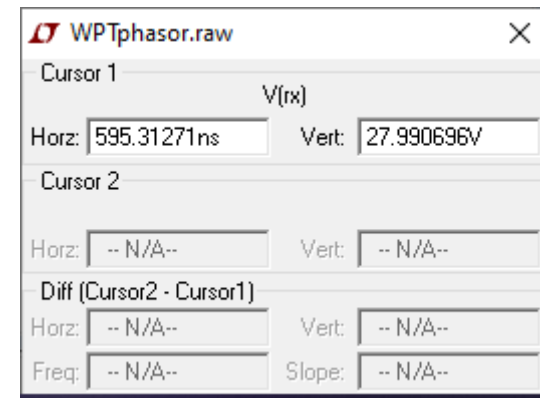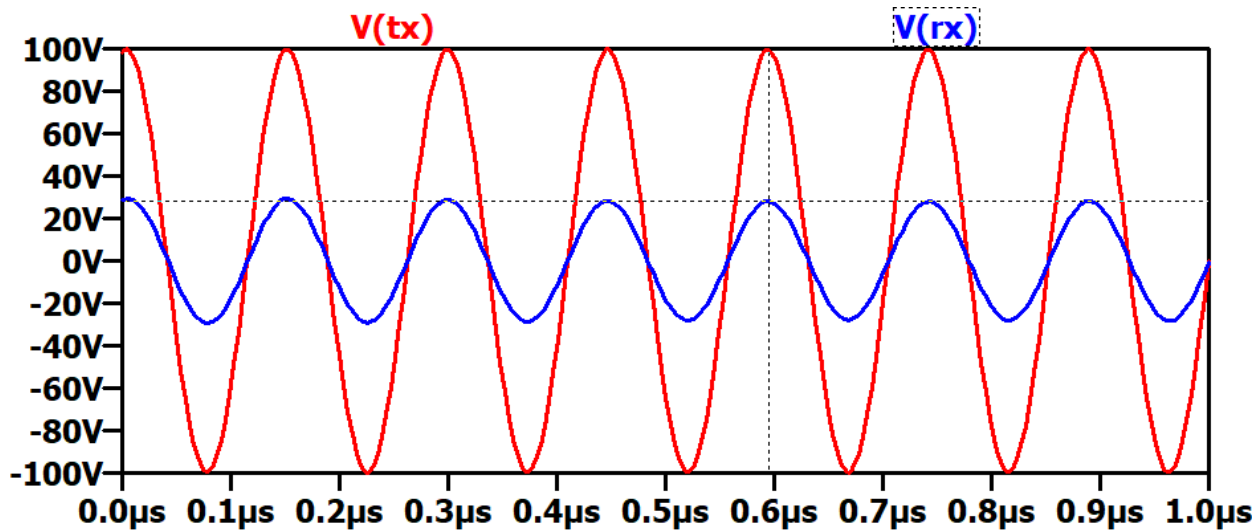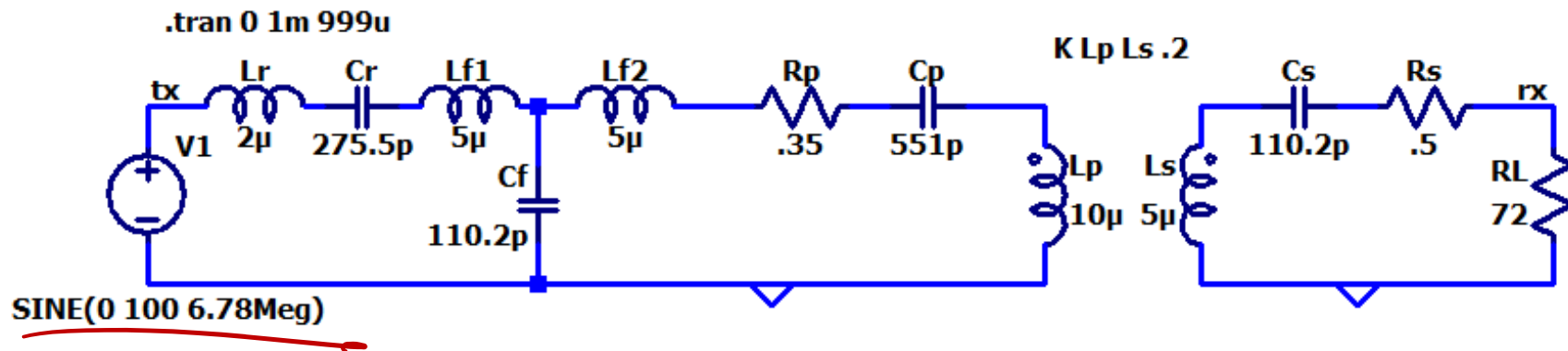

Resonance

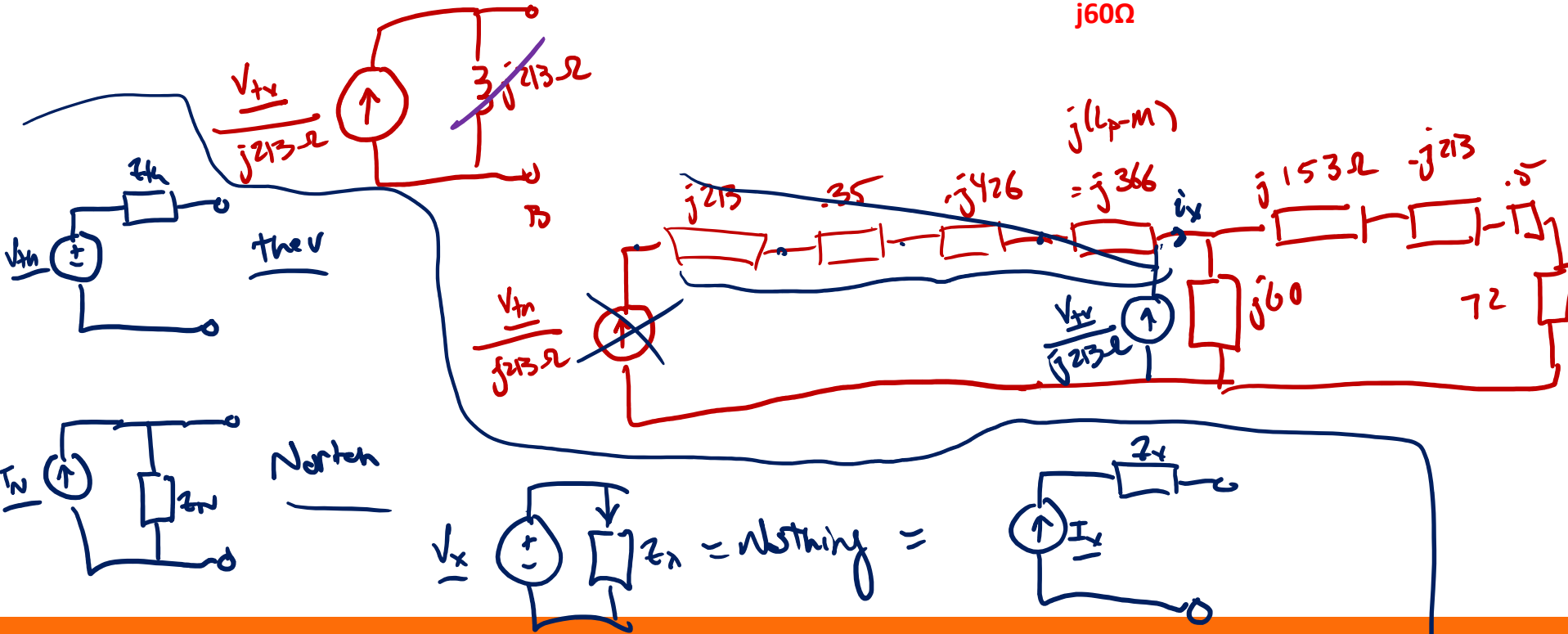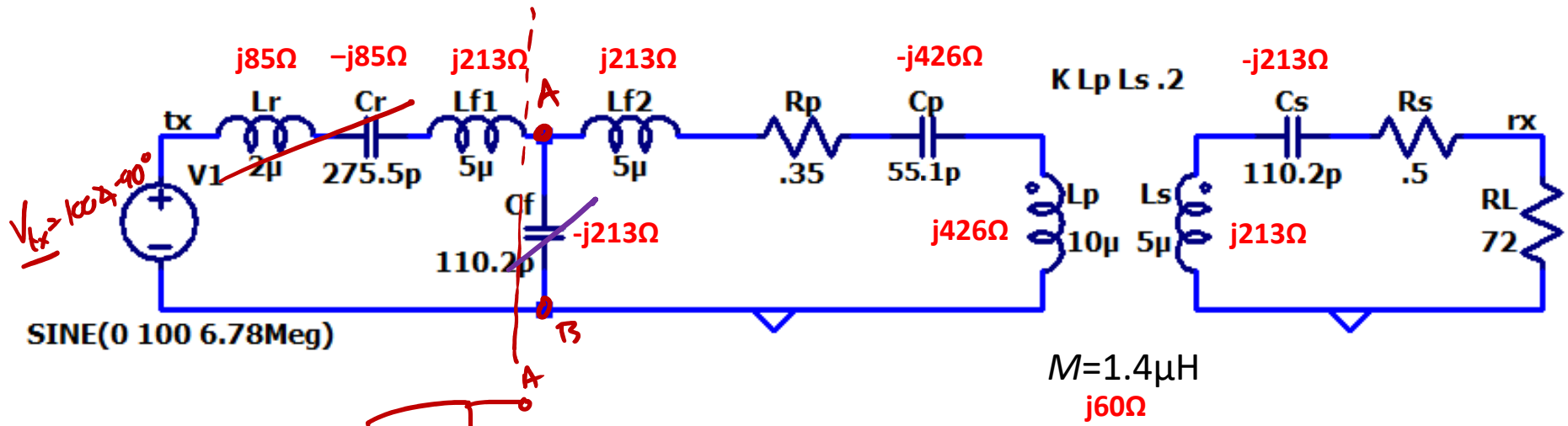

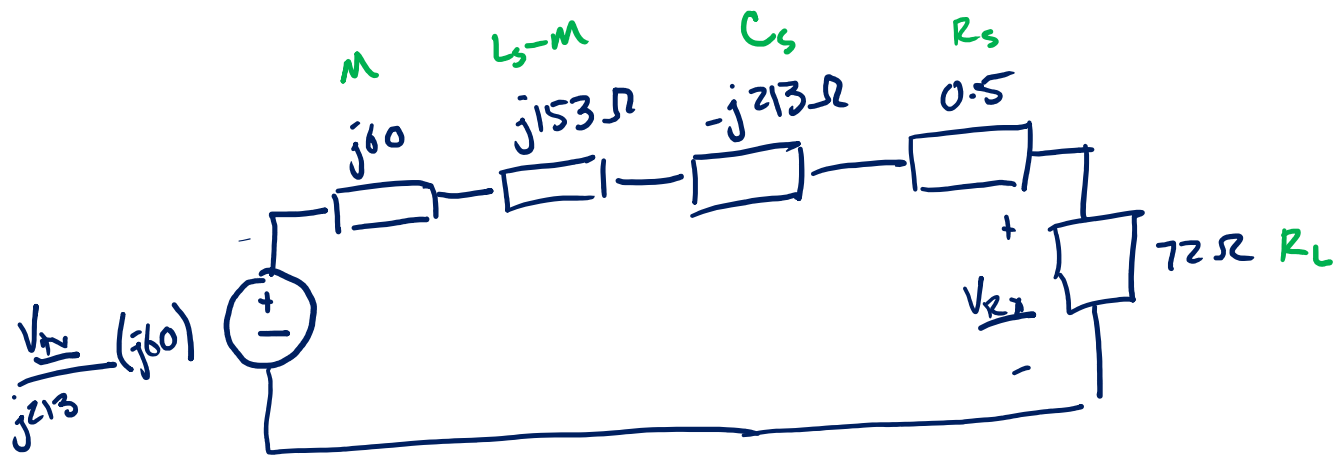

$$\underline{V_{R_L}} =$$