
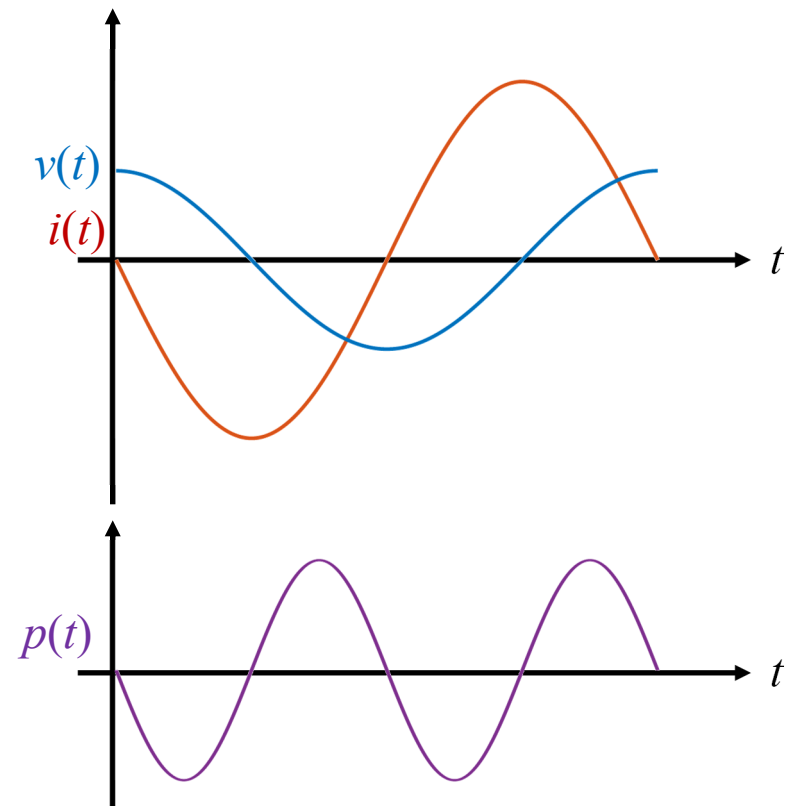


RMS of a sinusoid

Power with Sinusoidal Sources

Power with Sinusoidal Sources

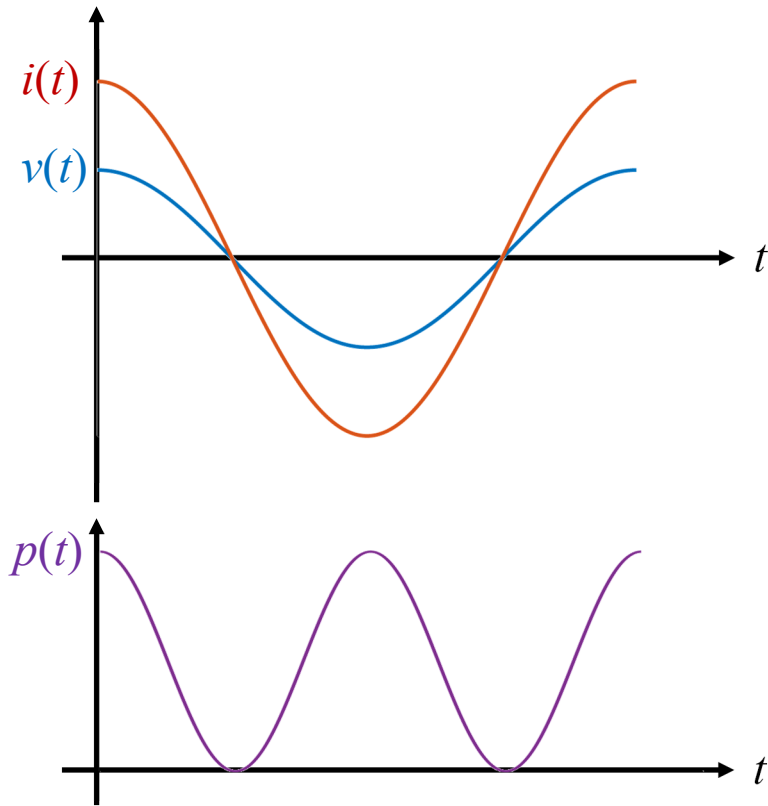

Complex Power

Apparent Power & Power Factor

Maximum Power Transfer