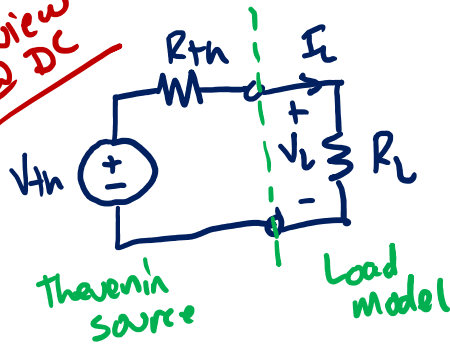


Maximum Power Transfer

Review @ DC



What value of R_L results in maximum power $P_L = V_L \cdot I_L$

Answer: $R_L = R_{th}$

$$P_L = \left(V_{th} \frac{R_L}{R_{th} + R_L} \right) \left(\frac{V_{th}}{R_{th} + R_L} \right) = V_{th}^2 \frac{R_L}{(R_L + R_{th})^2}$$

$$\frac{\partial P_L}{\partial R_L} = 0 = V_{th}^2 \left[\frac{1}{(R_L + R_{th})^2} + \frac{R_L(-2)}{(R_L + R_{th})^3} \right]$$


Numerator only:

$$R_L + R_{th} - 2R_L = 0$$

$$R_L = R_{th}$$

What value of R_{th} gives maximum power to a fixed R_L ?

$$R_{th} = 0$$

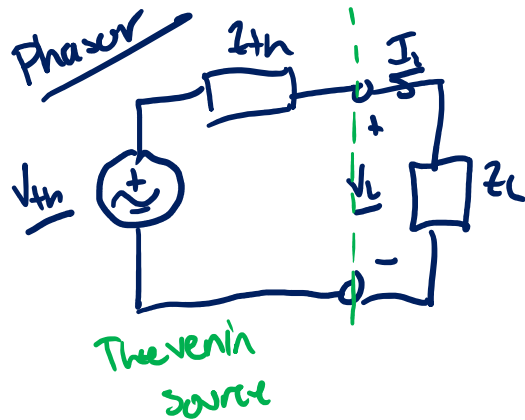




What value of Z_L results in maximum $P_L = \frac{1}{2} R_e \{ \underline{V}_L \underline{I}_L^* \}$

Cancel out imaginary & set real parts equal

$$Z_L = R_e \{ Z_{th} \} - j \text{Im} \{ Z_{th} \}$$

$$Z_L = Z_{th}^*$$


Impedance Matching

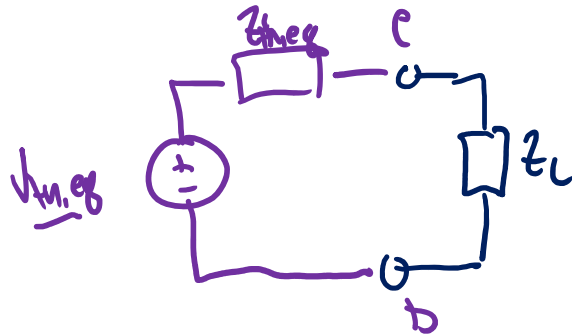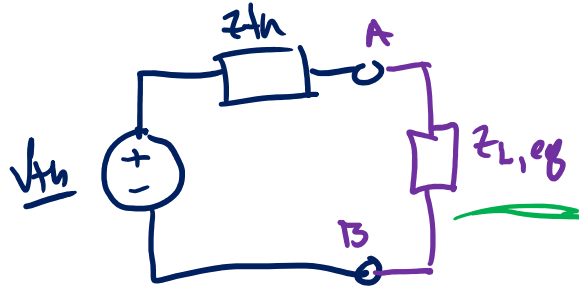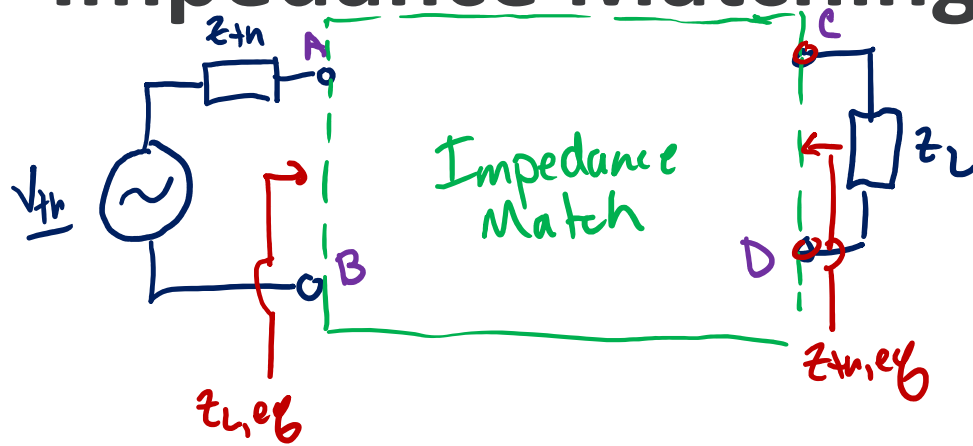

Impedance Matching Goals

- Maximize power to z_L ($z_L = z_{th}^*$)
- Minimize distortion ($z_L = z_{th,eq}$)
- Maximize efficiency ($\text{Re}\{z_L\} \gg \text{Re}\{z_{th,eq}\}$)
- Minimize Q ($\text{Im}\{z_{L,eq}\} = \phi$)

Example Matching Circuits

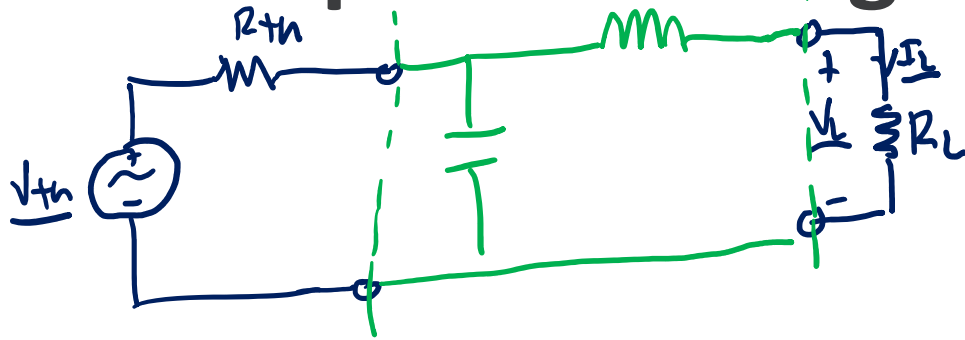

$R_{th} > R_L$
with no matching network
 $P_L < P_{L,max}$