
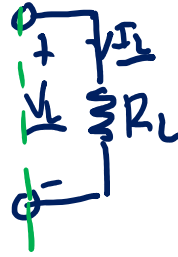


Example Matching Circuits

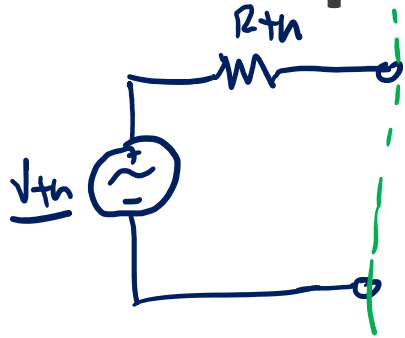

$R_{th} > R_L$
with no matching network
 $P_L < P_{L,max}$

Matching Example



Power Spectrum