
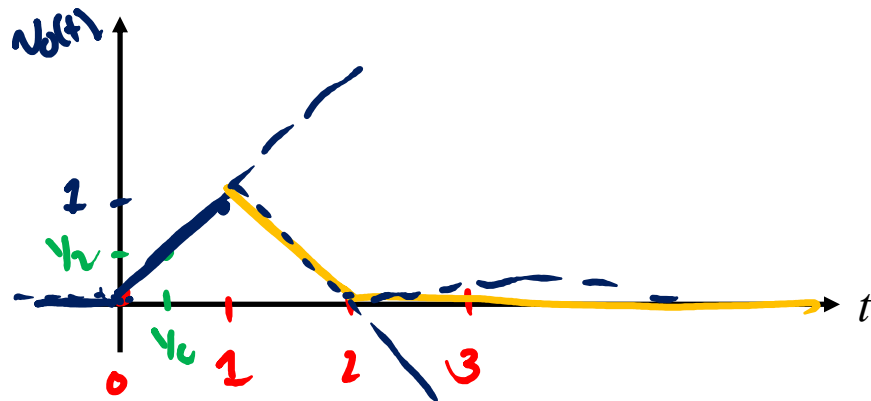
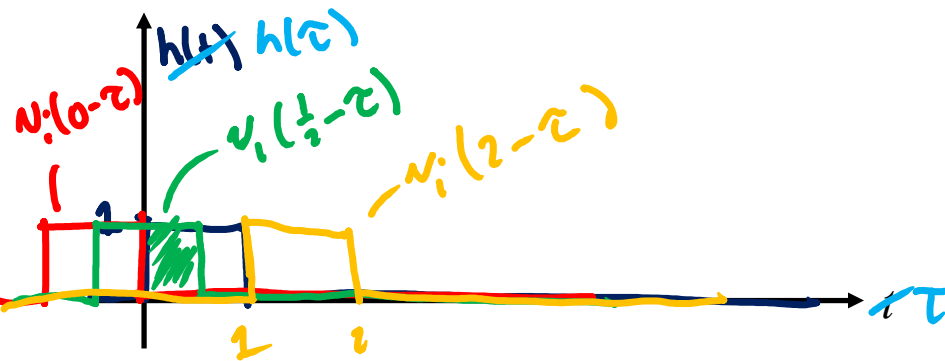


Graphical Convolution

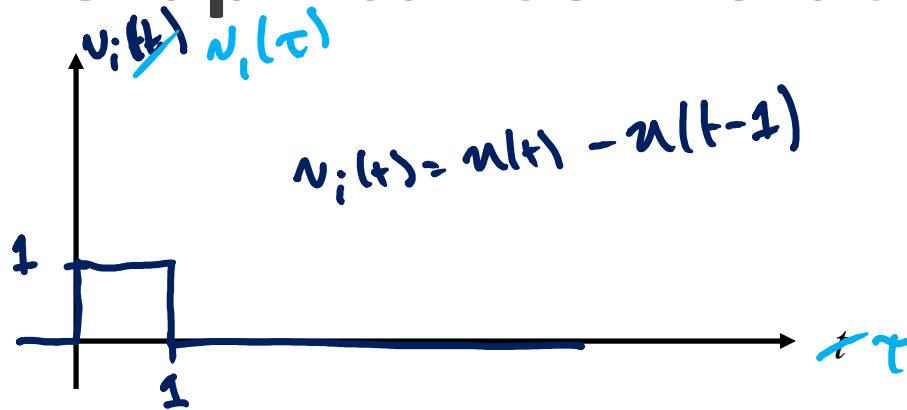

$$v_o(t) = \int_0^{\infty} v_i(t-\tau)h(\tau)d\tau$$

$$v_o(t) = \begin{cases} 0, & t \leq 0 \\ 0, & t \geq 2 \\ \int_0^t 1 dt, & 0 < t < 1 \\ \int_{t-1}^1 1 dt, & 1 < t < 2 \end{cases}$$


$$v_o(t) = r(t) - 2r(t-1) + r(t-2)$$

$$V_I(s) = \frac{1}{s} - \frac{1}{s}e^{-s} = H(s)$$


$$V_o(s) = V_I(s)H(s) = \frac{1}{s^2} + \frac{1}{s^2}e^{-2s} - 2\frac{1}{s^2}e^{-s}$$

$$v_o(t) = r(t) - 2r(t-1) + r(t-2)$$

Example Problem

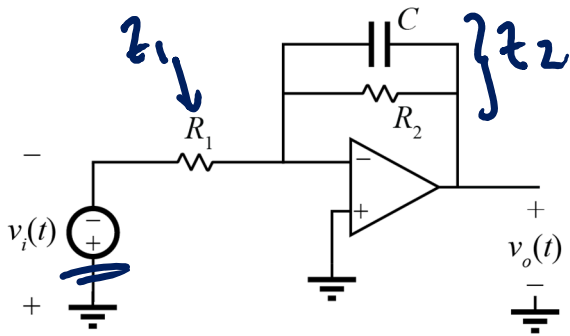

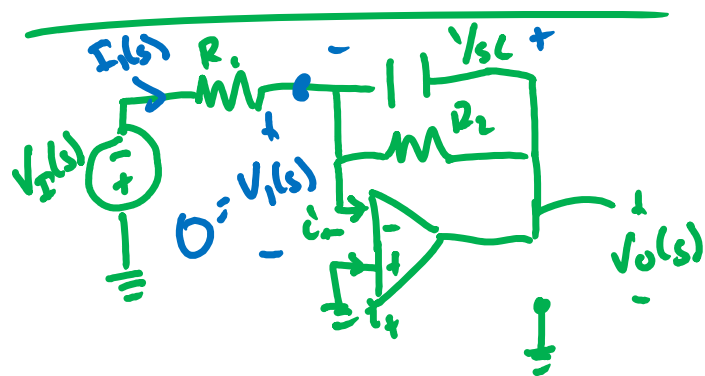from 201: inverting opamp
 $V_o(s) = - \left(-\frac{z_1}{z_2} \right) V_I(s)$



Ideal op-amp assumptions
 (1) virtual short $v_+ = v_-$
 (2) $i_+ = i_- = 0$

$$\begin{aligned}
 I_1(s) &= \frac{-V_I(s)}{R_1} \leftarrow z_1 \\
 V_O(s) &= 0 + (-I_1(s)) \left(\frac{1}{sC} \parallel R_2 \right) \\
 &= \frac{1}{R_1} V_I(s) \frac{R_2 / sC}{R_2 + 1/sC} \\
 &= \frac{1}{R_1} \frac{R_2}{R_2 sC + 1} V_I(s)
 \end{aligned}$$