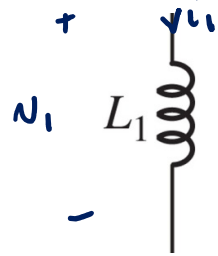


Energy Storage





Review

When \$I_0\$ current flowing through \$L_1\$

$$E_L = \int_0^{t_0} p_L(t) dt = \int_0^{t_0} i_1(t) \cdot v_1(t) dt = \int_0^{t_0} L i_1(t) \frac{di_1}{dt} dt$$
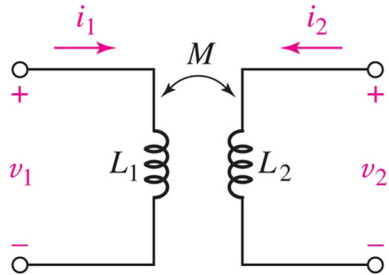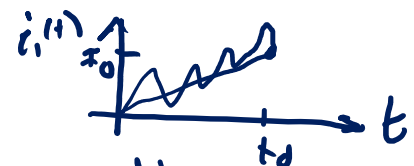
$$= L \int_0^{t_0} \frac{1}{2} \left[\frac{d}{dt} i_1(t)^2 \right] dt = \boxed{\frac{1}{2} L I_0^2} = E_L$$



At \$t_0\$ \$i_1(t) = I_{01}\$ & \$i_2(t) = I_{02}\$

$$E_{12} = \int_0^t (v_1(t) i_1(t) + v_2(t) i_2(t)) dt$$

$$= \int_0^t \left(L_1 i_1(t) \frac{di_1}{dt} \pm M i_2(t) \frac{di_2}{dt} + L_2 i_2(t) \frac{di_2}{dt} \pm M i_1(t) \frac{di_1}{dt} \right) dt$$

$$= \frac{1}{2} L_1 I_{01}^2 + \frac{1}{2} L_2 I_{02}^2 \pm \int_0^t M \left(i_1(t) \frac{di_2}{dt} + i_2(t) \frac{di_1}{dt} \right) dt$$

$= \frac{d}{dt} (i_1 \cdot i_2)$

$$E_{12} = \frac{1}{2} L_1 I_{01}^2 + \frac{1}{2} L_2 I_{02}^2 \pm M I_{01} I_{02}$$

Starting from zero current & bringing up $i_1(t) = I_{01}$ & $i_2(t) = I_{02}$,
 must be true that

$$E_{12} = \frac{1}{2} L_1 I_{01}^2 + \frac{1}{2} L_2 I_{02}^2 + M I_{01} I_{02} \quad \triangleright \phi$$

$$M < \frac{\frac{1}{2} L_1 I_{01}^2 + \frac{1}{2} L_2 I_{02}^2}{I_{01} I_{02}} = \frac{1}{2} L_1 \frac{I_{01}}{I_{02}} + \frac{1}{2} L_2 \frac{I_{02}}{I_{01}}$$

Let $x = \frac{I_{01}}{I_{02}} \rightarrow M < \frac{1}{2} L_1 x + \frac{1}{2} L_2 \frac{1}{x}$

to find minimum:

$$\frac{\partial M}{\partial x} = \frac{1}{2} L_1 + \frac{1}{2} L_2 \frac{-1}{x^2} = 0 \rightarrow x = \sqrt{\frac{L_2}{L_1}}$$

$$\frac{\partial^2 M}{\partial x^2} = \frac{1}{2} L_2 \frac{2}{x^3}$$


$$M < \frac{1}{2} L_1 \sqrt{\frac{L_2}{L_1}} + \frac{1}{2} L_2 \sqrt{\frac{L_1}{L_2}} = \frac{1}{2} \sqrt{\frac{L_1^2 L_2}{L_1}} + \frac{1}{2} \sqrt{\frac{L_2^2 L_1}{L_2}}$$

$$M \leq \sqrt{L_1 L_2}$$

Coupling Coefficient

Define $k = \frac{M}{\sqrt{L_1 L_2}}$ is the "coupling coefficient"

$$0 \leq k \leq 1$$

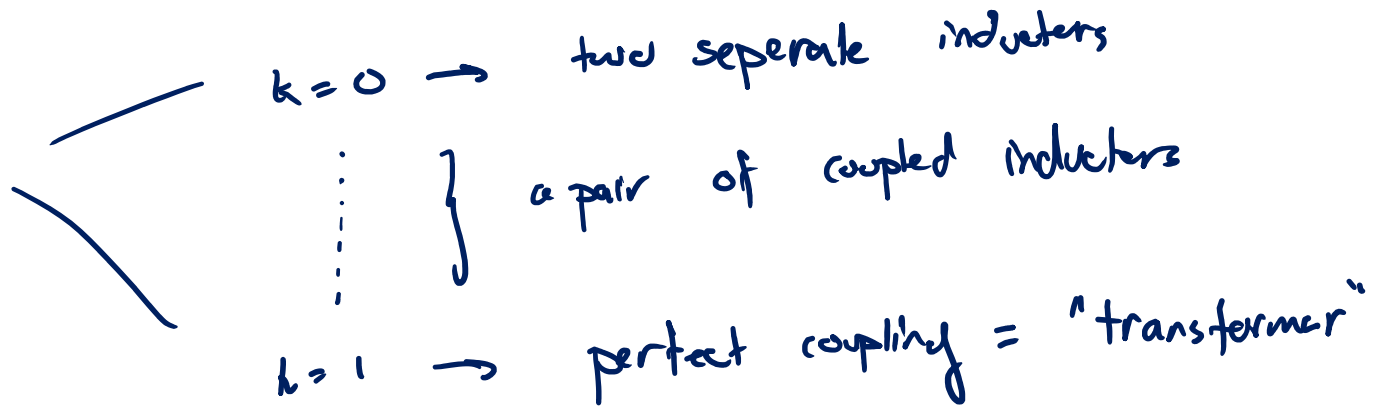

Transformers

Special case when $k=1$

$$\begin{cases} V_1 = L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt} \\ V_2 = \pm M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

$k=1 \iff$ perfect coupling $\iff M = \sqrt{L_1 L_2}$

$$\begin{cases} V_1 = L_1 \frac{di_1}{dt} \pm \sqrt{L_1 L_2} \frac{di_2}{dt} \\ V_2 = \pm \sqrt{L_1 L_2} \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$


$$\downarrow V_1 = V_2 \sqrt{\frac{L_1}{L_2}}$$

$$V_1 = V_2 \sqrt{\frac{\cancel{\alpha_1} N_1^2}{\cancel{\alpha_2} N_2^2}} \quad \alpha_1 = \alpha_2 \text{ if } k=1$$


$$\boxed{V_1 = V_2 \frac{N_1}{N_2}}$$

"turns ratio"

Symbol for transformer

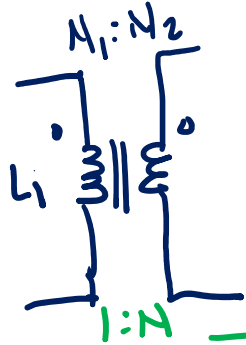

$$N = \frac{N_2}{N_1}$$

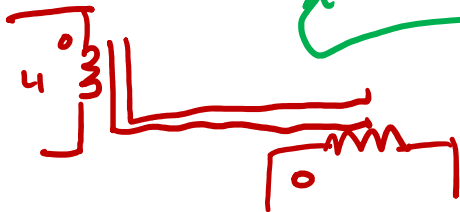


Ideal Transformer

$L_1 \neq L_2$ are "bige" $\hookrightarrow k=1$

Recall: Inductors (\neq transformers) cannot have DC voltage applied so current goes to ∞

- $V = L \frac{di}{dt} \rightarrow i = \frac{1}{L} \int V dt$
- Materials: core materials saturate at high flux causing inductance to drop to nearly zero.
- $V = N \frac{d\phi}{dt} \rightarrow$ Need to have time-varying (non-DC signals)

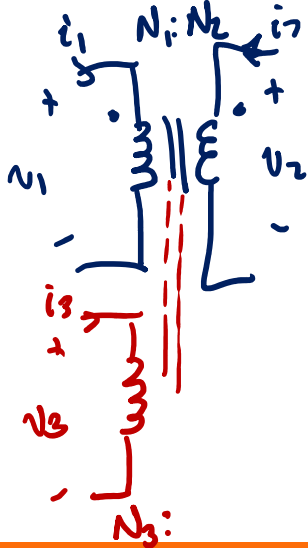When $L_1 \neq L_2$ are in the transformer i_1, i_2 are negligible \neq no energy



$$N_1 = N_2 \frac{N_1}{N_2}$$

$$v_1 i_1 + N_2 i_2 = \phi$$

$$v_2 \frac{N_1}{N_2} i_1 + v_2 i_2 = \phi$$

$$N_1 i_1 + N_2 i_2 = \phi$$

$$\frac{v_1}{N_1} = \frac{v_2}{N_2} = \frac{v_3}{N_3}$$

$$i_1 N_1 + i_2 N_2 + i_3 N_3 = 0$$