


# Announcements

- Homework 1 is posted, due 2/4 before 10:30am
  - Submitted to canvas as a single pdf
  - First two problems are ECE 201 review
- Can begin self-assigning lab groups of 2-3 in Canvas (people → Groups tab)
- No in-person office hours today
  - e-mail to set up alternative time or meet on Zoom

# Coupled Inductor Example

unknowns ~~111~~  
equations ~~111~~

Solve for  $v_o(t)$

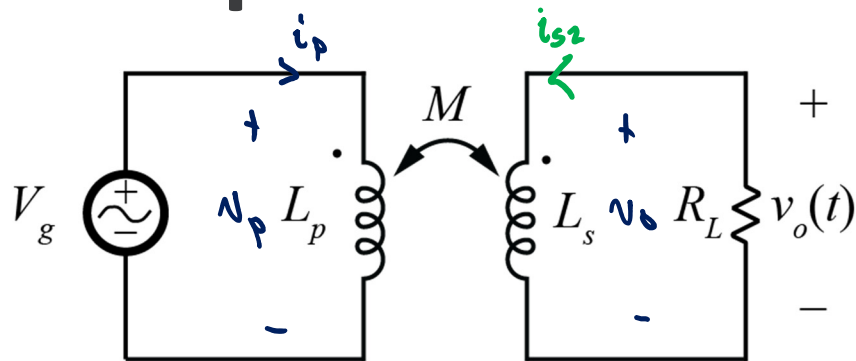

$$\begin{cases} v_p = L_p \frac{di_p}{dt} + M \frac{di_s}{dt} \\ v_s = M \frac{di_p}{dt} + L_s \frac{di_s}{dt} \end{cases}$$

$$v_g = N_p \phi$$

$$N_s = N_o$$

$$v_o = -i_s R_L$$

$$\frac{di_p}{dt} = \frac{v_g - M \frac{di_s}{dt}}{L_p}$$


$$\begin{cases} v_g = L_p \frac{di_p}{dt} + M \frac{di_s}{dt} \\ -i_s R_L = M \frac{di_p}{dt} + L_s \frac{di_s}{dt} \end{cases}$$

$$-i_s R_L = \frac{M}{L_p} \left( N_g \phi - M \frac{di_s}{dt} \right) + L_s \frac{di_s}{dt}$$

$$\phi = \frac{M}{L_p} N_g \phi + i_s R_L + \left( L_s - \frac{M^2}{L_p} \right) \frac{di_s}{dt}$$

$$i_s = -i_{s2}$$

# Ideal Transformer Example

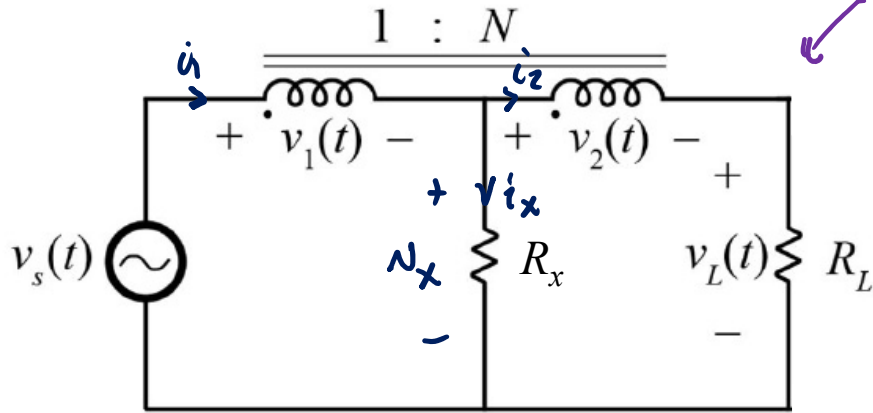

"Autotransformer" → e.g. a variac  
Solve for  $v_L(t)$

Transformer Equations:

$$\frac{v_1}{1} = \frac{v_2}{N} \quad \& \quad i_1 + Ni_2 = 0$$

KCL

$$i_2 = i_L$$

Node:

$$i_1 = i_x + i_2$$

$$-Ni_2 - i_2 = i_x$$

$$-i_2(N+1) = i_x$$

$$-\frac{v_L}{R_L}(N+1) = \frac{v_x}{R_x} = \frac{v_L + v_2}{R_x}$$

$$N_2' = -\frac{R_x}{R_L}(N+1)v_L - v_2$$

KVL  
Loop:  $N_x = N_2 + N_L$   
 $N_s = N_1 + N_2 + N_L$   
 $N_s = N_2 \left( \frac{1}{N} + 1 \right) + N_L$

$$N_s = v_2 + \left( \frac{1}{N} + 1 \right) \left( -v_L - \frac{R_x}{R_L}(N+1)v_L \right)$$

$$N_s = v_L \left[ 1 - \left( \frac{1}{N} \right) (N+1) \left( 1 + \frac{R_x}{R_L}(N+1) \right) \right]$$

$$N_s = v_L \left[ \cancel{1} - \frac{1}{N} - \frac{R_x}{R_L} \frac{1}{N} (N+1)^2 \right] \rightarrow$$

$$v_L = N_s \frac{-N}{1 + \frac{R_x}{R_L}(N+1)^2}$$

# 15W USB Adapter Reference Design

Flyback Converter






Fold Bridge Rectifier

$170 \sin(2\pi 60t)$


$170 \frac{\sqrt{2}}{2}$  volts squarewave  
at @ 100kHz

12:1

2

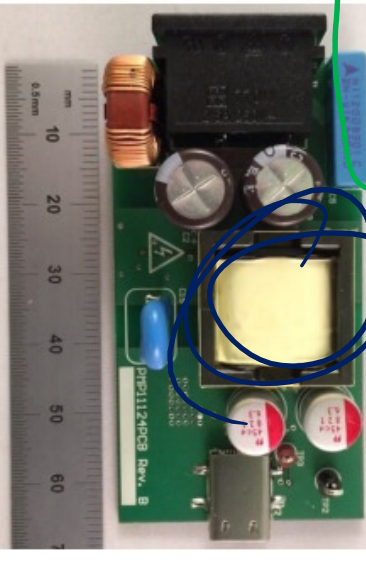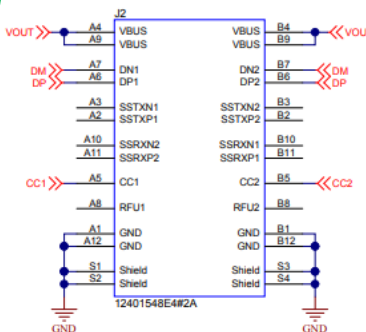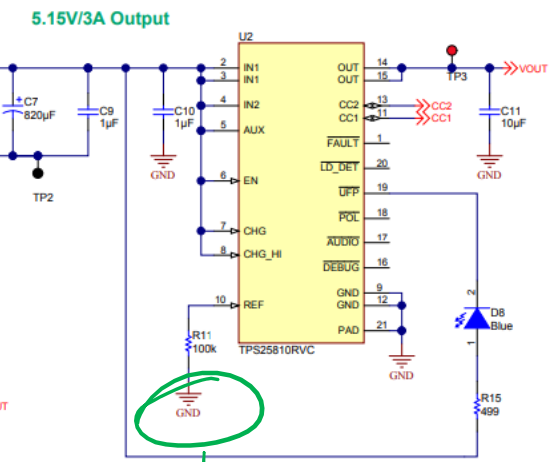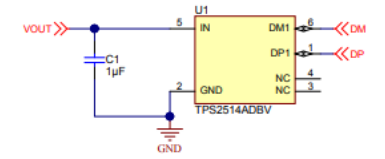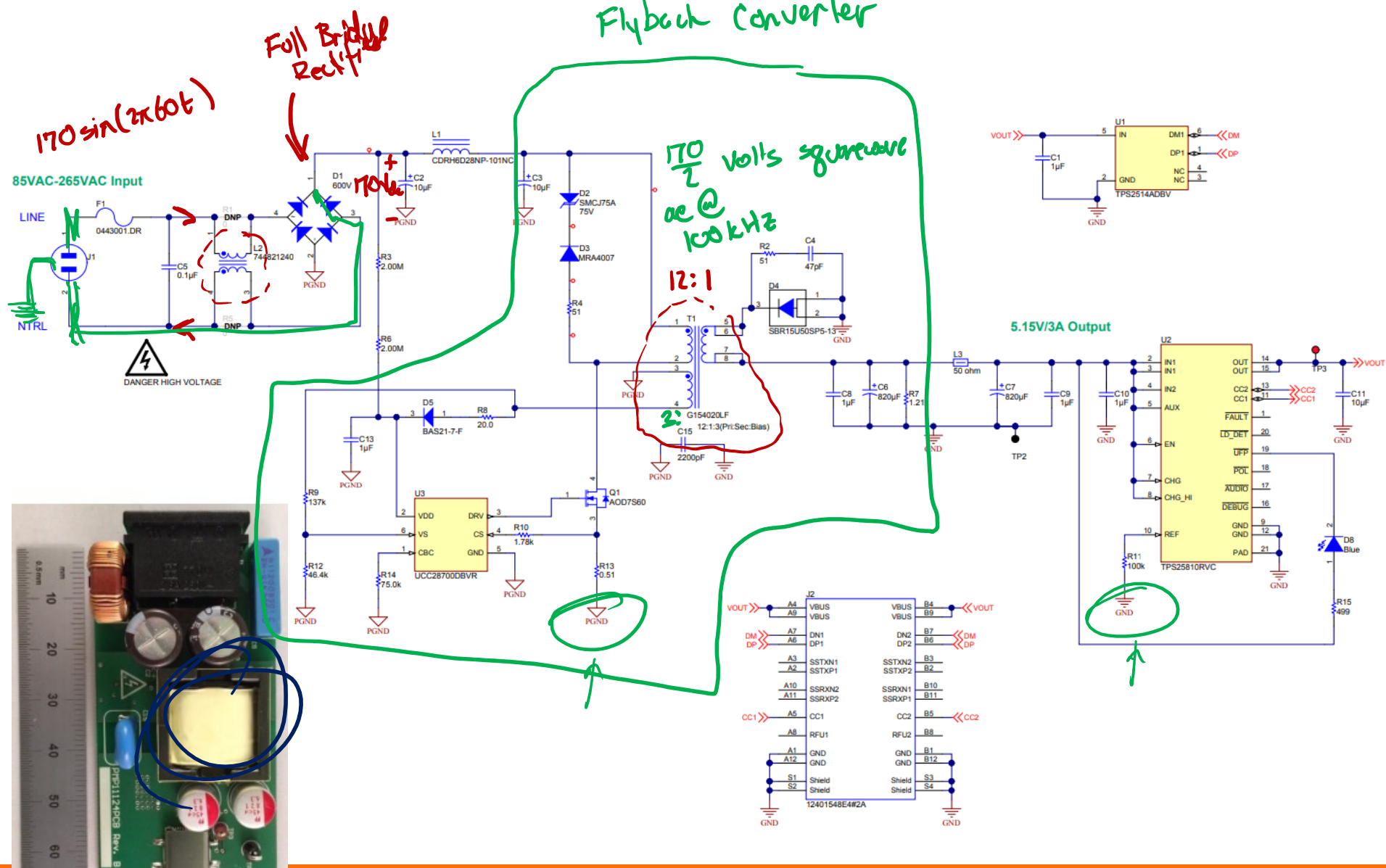

Flyback transformer

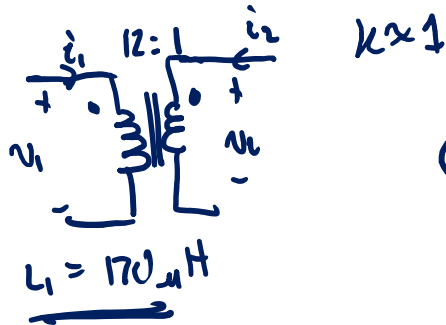

Full details of Flyback in FRED8!

Assume  $v_1 = \frac{\pi 0}{2} \sin(2\pi f_s t)$   $f_s = 100 \text{ kHz}$

① Ideal Transformer:

$v_2 = \frac{1}{12} v_1 = \frac{170}{24} \sin(2\pi f_s t) \approx 7 \sin(2\pi f_s t)$

if  $i_2 = 0$ ,  $i_1 = \phi$

② Non-ideal (still  $k=1$ )

$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

consider no phone connected  
 $i_2 = \phi$

$$i_1 = \frac{1}{L_1} \int_0^+ v_1 dt = i_1 = -\frac{1}{L_1} \frac{1}{2\pi f_s} \frac{170}{2} \cos(2\pi f_s t)$$

$$i_1 = -\left( \frac{1}{L_1} \frac{1}{2\pi f_s} \frac{170}{2} \right) \cos(2\pi f_s t)$$

$I_{IA} = 796 \text{ mA}$

If we run 60 Hz onto the transformer

$$I_{IA} = \left( \frac{1}{L_1} \frac{1}{2\pi \cdot 60} \frac{170}{2} \right) = 1.3 \text{ kA} !!$$

Definitely not ideal