

Announcements

- No Phasor analysis expected in HW2
- HW1 graded
 - 9.56 & 9.57 – review solutions
 - 13.5: $L_1 = 0.5L_2 = 1 \text{ mH}$
 $L_1 = 1 \text{ mH}$
 $L_2 = 2 \text{ mH}$
- Quiz on Wednesday 2/16
 - Covers Chapter 13, HW 1&2, Mutual inductance and transformers

Phasor Notation

$$v(t) = A \cos(\omega t + \phi) = \text{Re} \{ A e^{j\omega t} e^{j\phi} \}$$

↑ phasor transform @ ω

$$\underline{V} = A e^{j\phi} \iff A \angle \phi$$

(short hand notation)

bold in book
underbar in lecture

$$i(t) = B \sin(\omega t + \theta) = B \cos(\omega t + \theta - 90^\circ)$$

↓ phasor transform

$$\underline{I} = B e^{j(\theta - \frac{\pi}{2})} \iff B \angle (\theta - \frac{\pi}{2})$$


Comments:

- Phasor transform works for volt/current sources & signals
- Everything in the circuit must be at a single frequency ω
- Complex numbers:
 - No imaginary numbers in $v(t)$ or $i(t)$ (in time domain)
 - No time in the phasor domain \rightarrow no "t" in \underline{V} or \underline{I}


Phasor Circuit Elements

Time Domain


Phasor Domain

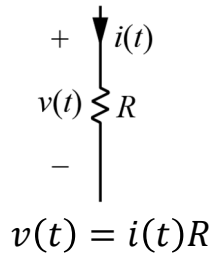

$\underline{V} = \underline{I} R$

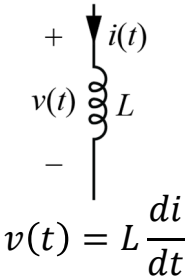

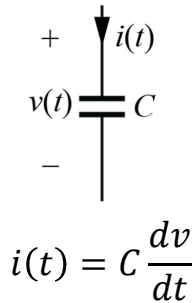$\underline{V} = L j\omega \underline{I}$



$\underline{I} = C j\omega \underline{V}$

$v(t) = A \cos(\omega t + \varphi)$
 $i(t) = \frac{A}{R} \cos(\omega t + \varphi)$
 $v(t) = i(t)R$

phasor transform



$\underline{V} = A e^{j\varphi}$
 $\underline{I} = \frac{A}{R} e^{j\varphi}$



$\underline{V} = \underline{I} R$

$i(t) = A \cos(\omega t + \varphi)$
 $v(t) = L A \omega \cos(\omega t + \varphi + 90^\circ)$
 $v(t) = L \frac{di}{dt}$



$\underline{I} = A e^{j\varphi}$
 $\underline{V} = L A \omega e^{j(\varphi + \frac{\pi}{2})}$
 $\underline{V} = j\omega L A e^{j\varphi}$



$\underline{V} = j\omega L \underline{I}$

$v(t) = A \cos(\omega t + \varphi)$
 $i(t) = C A \omega \cos(\omega t + \varphi + 90^\circ)$
 $i(t) = C \frac{dv}{dt}$




$\underline{V} = A e^{j\varphi}$
 $\underline{I} = C A \omega e^{j(\varphi + \frac{\pi}{2})}$
 $\underline{I} = j\omega C A e^{j\varphi}$



$\underline{V} = \frac{-j}{\omega C} \underline{I}$


$\underline{V} = \frac{1}{j\omega C} \underline{I}$

Time Domain

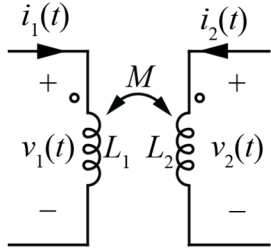

$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

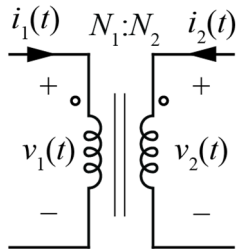
$$v_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



$$\frac{v_1(t)}{N_1} = \frac{v_2(t)}{N_2}$$


$$N_1 i_1(t) + N_2 i_2(t) = 0$$

Phasor Domain

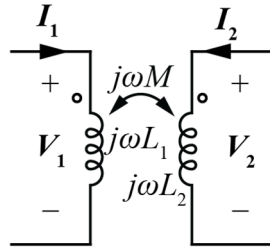

$$\underline{V}_1 = j\omega L_1 \underline{I}_1 + j\omega M \underline{I}_2$$
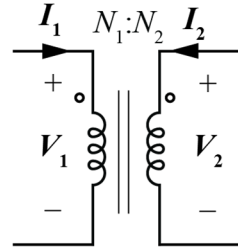
$$\underline{V}_2 = j\omega M \underline{I}_1 + j\omega L_2 \underline{I}_2$$



$$\frac{\underline{V}_1}{N_1} = \frac{\underline{V}_2}{N_2}$$

$$N_1 \underline{I}_1 + N_2 \underline{I}_2 = 0$$

Impedance

Phasor equivalent of ohm's law

$$\underline{V} = \underline{I} \underline{Z}$$

$\underline{z} = \text{"Impedance"} = R + jX$
 $\text{Re}\{\underline{z}\} = R$ "Resistance"

$\text{Im}\{\underline{z}\} = X$ "Reactance"

$$\begin{cases} z_R = R & \text{Resistor} \\ z_L = j\omega L & \text{Inductor} \\ z_C = \frac{-j}{\omega C} & \text{Capacitor} \end{cases}$$

All have units of Ohms (z, R, X)

$\underline{Y} = \text{"Admittance"} = \frac{1}{\underline{z}} = G + jB$
 G conductance
 B susceptance

→ All units of Siemens

$Y = \frac{1}{z} = \frac{1}{R + jX} \neq \frac{1}{R} + j\frac{1}{X}$ No.

Yes! $\hookrightarrow \frac{1}{R + jX} \frac{(R - jX)}{(R - jX)} = \frac{R - jX}{R^2 + X^2} = \frac{R}{R^2 + X^2} - j \frac{X}{R^2 + X^2}$