

Phasor Circuit Analysis

Start: LTI circuit with single-frequency sinusoidal source(s) & want to find steady-state solution


1: Transform all sources & signals into their phasor equivalents

2: Transform all passives into their impedances

3: Solve the circuit


- Can use all 201 analysis techniques for DC, resistor-only circuits

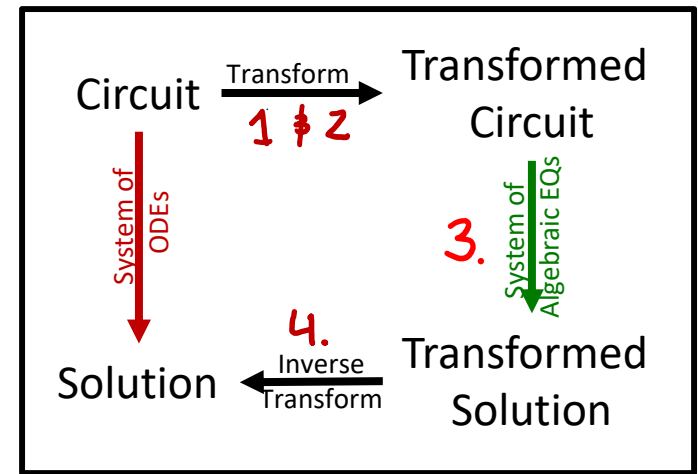4: Transform phasor voltage or current back into the time domain



Example Problem

$$\omega = 2\pi 60$$

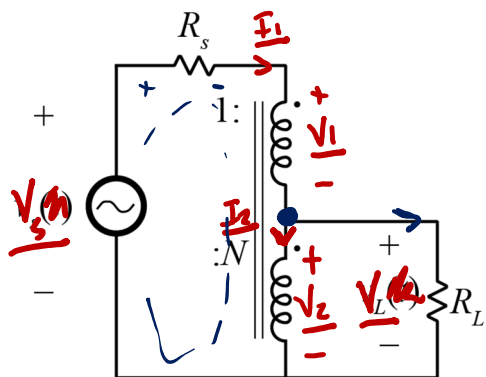

Find $v_L(t)$ for $v_s(t) = 170\cos(2\pi 60t)$ and for $R_s = 10 \Omega$, $N = 0.1$, and $R_L = 50 \Omega$

No differential equations, so no benefit to phasors

$$\textcircled{1} \quad v_s(t) \rightarrow \underline{V}_s = 170 \angle 0^\circ \text{ or } 170e^{j0} = 170$$

$$v_L(t) \rightarrow \underline{V}_L = V_A \angle \phi$$

$$\textcircled{2} \quad R_s \rightarrow R_s \quad R_L \rightarrow R_L$$

$$\frac{V_1}{1} = \frac{V_2}{N}$$

B

$$\underline{I}_1 + N\underline{I}_2 = 0 \rightarrow \underline{I}_2 = -\frac{1}{N}\underline{I}_1$$

$\textcircled{3}$

loop

$$\underline{V}_s = \underline{V}_1 + \underline{V}_2 + \underline{I}_1 R_s$$

$$\underline{V}_s = \left(\frac{1}{N} + 1\right)\underline{V}_L + \underline{I}_1 R_s$$

node

$$\underline{I}_1 = \underline{I}_L + \frac{V_L}{R_L}$$

$$\underline{I}_1 \left(1 + \frac{1}{N}\right) = \frac{V_L}{R_L}$$

$$\underline{V}_s = \left(\frac{1}{N} + 1\right)\underline{V}_L + R_s \frac{V_L}{R_L} \frac{1}{1 + \frac{1}{N}}$$

$$\underline{V}_s = \underline{V}_L \left[\frac{N+1}{N} + \frac{Z_s}{R_L} \frac{N}{N+1} \right]$$


$$\underline{V}_L = \underline{V}_s \frac{1}{\frac{N+1}{N} + \frac{Z_s}{R_L} \frac{N}{N+1}}$$

plug in all #'s : $\underline{V}_L = 15.5 e^{j\omega t} = 15.5$

④ $v_L(t) = 15.5 \cos(2\pi 60 t + 0^\circ)$

FYI: if $R_s \rightarrow \phi$ $V_L = \underline{V}_s \frac{N}{N+1}$


Resonance Example

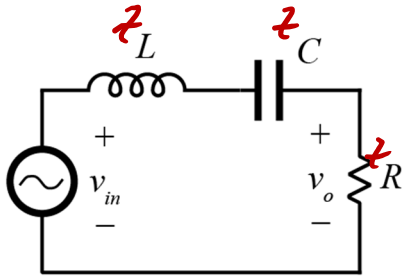

$$= 10 \cos(\omega t - 90^\circ)$$

Find $v_o(t)$ for $v_{in}(t) = 10 \sin(\omega t)$ and $\omega = 2\pi 100 \text{ kHz}$,
 $R = 10 \Omega$, $L = 10 \mu\text{H}$, and $C = 253 \text{ nF}$

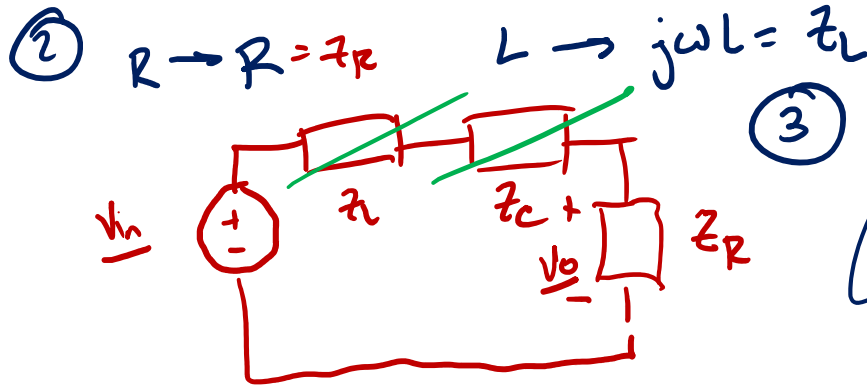① $v_{in}(t) \rightarrow \underline{v_{in}} = 10 \angle -90^\circ$ or $10 e^{j\frac{-\pi}{2}}$
 $v_o(t) \rightarrow \underline{v_o}$



$$C \rightarrow \frac{-j}{\omega C} = Z_C$$

③

$$\underline{v_o} = \underline{v_{in}} \frac{Z_R}{Z_R + Z_L + Z_C}$$

④ $\underline{v_o} = 10 e^{j\frac{-\pi}{2}}$
 $v_o(t) = 10 \cos(\omega t - 90^\circ)$
 $= 10 \sin(\omega t)$

$$R = R = 10 \Omega$$

$$Z_L = j\omega L = j(2\pi 100 \times 10^3)(10 \times 10^{-6}) = j(2\pi)$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{(2\pi 100 \times 10^3)(253 \times 10^{-9})} = -j(2\pi)$$

Reactance and Resonance

Back at the end of 201

$$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow \text{resonant frequency}$$

Now:

$$Z_L = j\omega L$$

$$Z_C = \frac{-j}{\omega C}$$


$$Z_L = -Z_C$$

$$j\omega L = -\left(\frac{-j}{\omega C}\right)$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

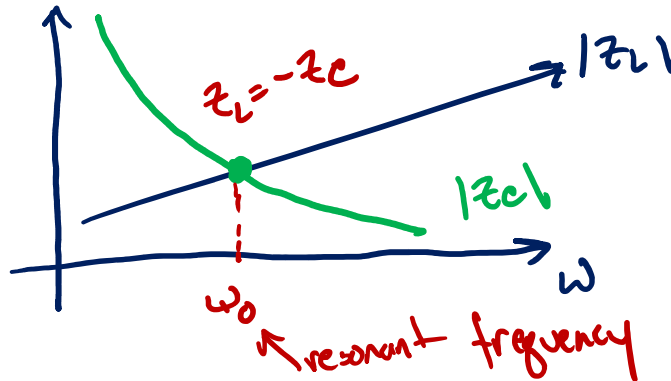

Lim
 $\omega \rightarrow 0 \approx DC$


as $\omega \rightarrow 0 \approx DC$

$Z_C \rightarrow \infty$ cap \rightarrow open
 $Z_L \rightarrow 0$ inductor \rightarrow short

as $\omega \rightarrow \infty$


$Z_C \rightarrow 0$ cap \rightarrow short
 $Z_L \rightarrow \infty$ inductor \rightarrow open

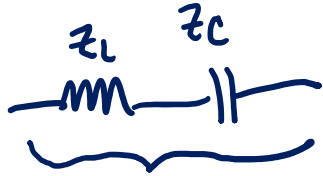Q $\omega_0 = \frac{1}{\sqrt{LC}}$ $Z_L = -Z_C$



$$Z_{eq} = Z_L + Z_C$$

$$= \phi \text{ @ resonance (short)}$$

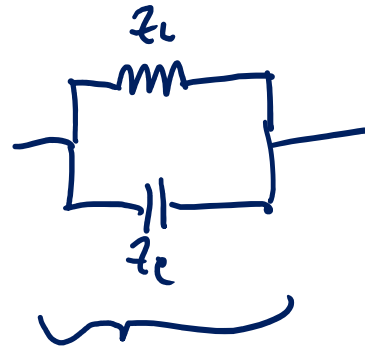

$$Z_{eq} = \frac{Z_L Z_C}{Z_L + Z_C} \rightarrow \phi$$


$$Z_{eq} \rightarrow \infty \text{ (open)}$$

@ resonance

Phasor Superposition

3 frequencies

phasor analysis doesn't apply

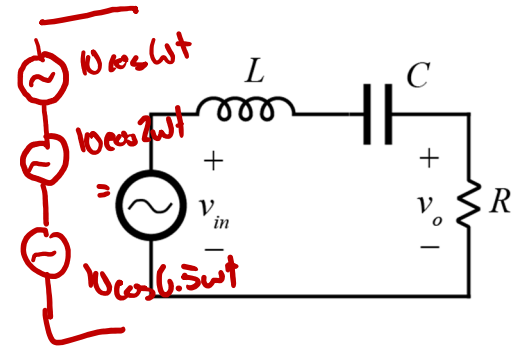

Find $v_o(t)$ for $v_{in}(t) = 10\cos(\omega t) + 10\cos(2\omega t) + 10\cos(0.5\omega t)$
and $\omega = 2\pi 100$ kHz, $R = 10 \Omega$, $L = 10 \mu\text{H}$, and $C = 253$ nF