
 


# DESIGNING FPGAS & ASICS



## HDL Examples

 

Prof. Don Bouldin, Ph.D.



  Electrical & Computer Engineering  
University of Tennessee  
TEL: (865)-974-5444  
FAX: (865)-974-5483  
dbouldin@tennessee.edu



© 2003 -- Don Bouldin

# COURSE OUTLINE

- Overview of FPGAs and ASICs
- Using Synthesis
- HDL Examples
- Simulation and Testing
- Physical Place and Route
- Testing ASICs
- Component Reuse

© 2003 -- Don Bouldin

# TRUTH TABLE OR EQUATIONS USING VHDL

Row number	x <sub>1</sub>	x <sub>2</sub>	x <sub>3</sub>	f
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

The function  $f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6)$ .

EQUATION

END LogicFunc;

© 2003 -- Don Bouldin

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY func3 IS
    PORT ( x1, x2, x3 : IN      STD_LOGIC ;
          f : OUT   STD_LOGIC ) ;
END func3 ;
ARCHITECTURE LogicFunc OF func3 IS
BEGIN
    f <= (NOT x1 AND NOT x2 AND NOT x3) OR
        (NOT x1 AND x2 AND NOT x3) OR
        (x1 AND NOT x2 AND NOT x3) OR
        (x1 AND NOT x2 AND x3) OR
        (x1 AND x2 AND NOT x3) ;
END LogicFunc ;
```

# IEEE STD\_LOGIC\_1164 PACKAGE

library IEEE; use IEEE.std\_logic\_1164.all; -- to use the IEEE package  
package Part STD\_LOGIC\_1164 is  
type STD\_LOGIC is ('U' -- Uninitialized  
'X' -- Forcing Unknown  
'0' -- Forcing 0  
'1' -- Forcing 1  
'Z' -- High Impedance  
'W' -- Weak Unknown  
'L' -- Weak 0  
'H' -- Weak 1  
'-' -- Don't Care);  
type STD\_LOGIC\_VECTOR is array (NATURAL range <>) of STD\_LOGIC;  
function resolved (s : STD\_LOGIC\_VECTOR) return STD\_LOGIC;  
subtype STD\_LOGIC\_VECTOR is array (NATURAL range <>) of STD\_LOGIC;  
subtype X01 is resolved STD\_LOGIC range 'X' to '1';  
subtype X01Z is resolved STD\_LOGIC range 'X' to 'Z';  
subtype UX01 is resolved STD\_LOGIC range 'U' to '1';  
subtype UX01Z is resolved STD\_LOGIC range 'U' to 'Z';

-- Vectorized overloaded logical operators:  
function "and" (L : STD\_LOGIC; R : STD\_LOGIC) return U0X1;  
-- Logical operators not, and, nand, or, nor, xor, xnor (VHDL-93),  
-- overloaded for STD\_LOGIC\_VECTOR  
STD\_LOGIC\_VECTOR;  
-- Strength strippers and type conversion functions:  
-- function To\_T (X : F) return T;  
-- defined for types, T and F, where  
-- F=BIT\_VECTOR STD\_LOGIC\_VECTOR STD\_LOGIC\_VECTOR  
STD\_LOGIC\_VECTOR  
-- T=Types F plus types X01 X01Z UX01 (but not type UX01Z)  
-- Exclude 's in T in name: TO\_STDLOGICvec TO\_STD\_LOGIC  
Page 401  
ASICS by M. Smith  
© 1997 A-W-L, Inc.  
Used by permission.

function rising\_edge (signal s: STD\_LOGIC) return BOOLEAN;  
function falling\_edge (signal s: STD\_LOGIC) return BOOLEAN;  
-- Unknown detection (returns true if s = U, X, Z, W);  
-- function Is\_X(s: T) return BOOLEAN;  
-- defined for T = STD\_LOGIC STD\_LOGIC\_VECTOR  
STD\_LOGIC\_VECTOR.  
end Part STD\_LOGIC\_1164;

© 2003 -- Don Bouldin

# MUX USING IF-THEN-ELSE IN VHDL

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY mux2to1 IS
    PORT (w0, w1, s : IN
          STD_LOGIC ;
          f : OUT   STD_LOGIC ) ;
END mux2to1 ;
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        IF s = '0' THEN
            f <= w0 ;
        ELSE
            f <= w1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```



© 2003 -- Don Bouldin

# DEC2TO4 USING CASE IN VHDL


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY dec2to4 IS
    PORT (w : IN
          STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En : IN
          STD_LOGIC ;
          y : OUT
          STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;
```

```
ARCHITECTURE Behavior OF dec2to4 IS
BEGIN
    PROCESS ( w, En )
    BEGIN
        IF En = '1' THEN
            CASE w IS
                WHEN "00" => y <= "1000" ;
                WHEN "01" => y <= "0100" ;
                WHEN "10" => y <= "0010" ;
                WHEN OTHERS => y <= "0001" ;
            END CASE ;
        ELSE
            y <= "0000" ;
        END IF ;
    END PROCESS ;
END Behavior ;
```



© 2003 -- Don Bouldin

## BCD-TO-7SEG CONVERTER USING VHDL

 

(a) Code converter (b) 7-segment display

$w_3 w_2 w_1 w_0$	a	b	c	d	e	f	g
0 0 0 0	1	1	1	1	1	1	0
0 0 0 1	0	1	1	0	0	0	0
0 0 1 0	1	1	0	1	1	0	1
0 0 1 1	1	1	1	0	0	1	1
0 1 0 0	0	1	1	0	0	1	1
0 1 0 1	1	0	1	1	0	1	1
0 1 1 0	1	1	1	1	0	1	1
0 1 1 1	1	1	1	0	0	0	0
1 0 0 0	1	1	1	1	1	1	1
1 0 0 1	1	1	1	1	0	1	1

(c) Truth table

```

ARCHITECTURE Behavior OF seg7 IS
BEGIN
  PROCESS (bcd)
  BEGIN
    CASE bcd IS
      --      abcdefg
      WHEN "0000" => leds <= "1111110";
      WHEN "0001" => leds <= "0110000";
      WHEN "0010" => leds <= "1101101";
      WHEN "0011" => leds <= "1111001";
      WHEN "0100" => leds <= "0110011";
      WHEN "0101" => leds <= "1011011";
      WHEN "0110" => leds <= "1011111";
      WHEN "0111" => leds <= "1110000";
      WHEN "1000" => leds <= "1111111";
      WHEN "1001" => leds <= "1110011";
      WHEN OTHERS => leds <= "-----";
    END CASE;
  END PROCESS;
END Behavior;
  
```


© 2003 -- Don Bouldin

## BINARY UP-COUNTER USING VHDL

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;

 ENTITY upcount IS
  PORT ( Clock, Resetn, E : IN STD_LOGIC;
        Q : OUT
        STD_LOGIC_VECTOR (3 DOWNTO 0));
END upcount;
  
```



```


ARCHITECTURE Behavior OF upcount IS
  SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNTO 0);
  BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
      IF Resetn = '0' THEN
        Count <= "0000";
      ELSIF (Clock'EVENT AND Clock = '1') THEN
        IF E = '1' THEN
          Count <= Count + 1;
        ELSE
          Count <= Count;
        END IF;
      END IF;
    END PROCESS;
    Q <= Count;
  END Behavior;
  
```

© 2003 -- Don Bouldin
 
## TWO-DIGIT BCD COUNTER

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
ENTITY BCDcount IS
  PORT (Clock : IN STD_LOGIC;
        Clear, E : IN STD_LOGIC;
        BCD1, BCD0 : BUFFER
        STD_LOGIC_VECTOR(3 DOWNTO 0));
END BCDcount;
  
```




```

ARCHITECTURE Behavior OF BCDcount IS
  BEGIN
    PROCESS (Clock)
    BEGIN
      IF Clock'EVENT AND Clock = '1' THEN
        IF Clear = '1' THEN
          BCD1 <= "0000"; BCD0 <= "0000";
        ELSIF E = '1' THEN
          IF BCD0 = "1001" THEN
            BCD0 <= "0000";
            IF BCD1 = "1001" THEN
              BCD1 <= "0000";
            ELSE
              BCD1 <= BCD1 + '1';
            END IF;
          ELSE
            BCD0 <= BCD0 + '1';
          END IF;
        END IF;
      END PROCESS;
    END Behavior;
  
```

© 2003 -- Don Bouldin
 
## STATE DIAGRAM AND STATE TABLE WITH BINARY ASSIGNMENT



Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

Present state	Next state		Output z
	$w_2 w_1$	$w_2 w_1$	
A	00	01	0
B	01	00	0
10	00	10	1
11	dd	dd	d

© 2003 -- Don Bouldin


## LOGIC MINIMIZATION USING K-MAPS

$$Y_1 = w Y_1' Y_2'$$

$$Y_2 = w Y_1 \text{ OR } w Y_2$$

$$= w (Y_1 \text{ OR } Y_2)$$

$$Z = Y_2$$

 


© 2003 -- Don Bouldin

## LOGIC EQUATIONS AND SCHEMATIC


$$Y_2 = w (Y_1 \text{ OR } Y_2)$$

$$Y_1 = w Y_1' Y_2'$$

 


© 2003 -- Don Bouldin

## STATE DIAGRAM AND FINAL SCHEMATIC

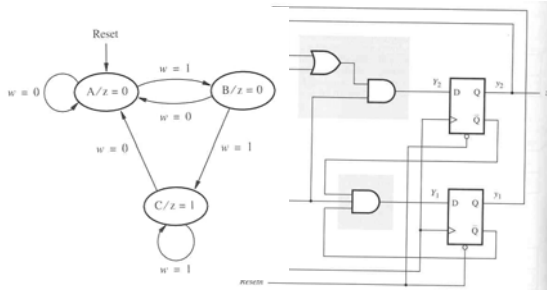

© 2003 -- Don Bouldin

## STATE DIAGRAM USING VHDL (part 1)

 


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY simple IS
PORT (Clock, Resetn, w : IN
STD_LOGIC ;
z : OUTSTD_LOGIC ) ;
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
TYPE State_type IS (A, B, C) ;
SIGNAL y_present, y_next : State_type ;
```

© 2003 -- Don Bouldin


## STATE DIAGRAM USING VHDL (part 2)

 

```
BEGIN
PROCESS ( w, y_present )
BEGIN
CASE y_present IS
WHEN A =>
IF w = '0' THEN y_next <= A ;
ELSE y_next <= B ;
END IF ;
WHEN B =>
IF w = '0' THEN y_next <= A ;
ELSE y_next <= C ;
END IF ;
WHEN C =>
IF w = '0' THEN y_next <= A ;
ELSE y_next <= C ;
END IF ;
END CASE ;
END PROCESS ;
END Behavior ;
```

© 2003 -- Don Bouldin

## STATE DIAGRAM USING VHDL (part 3)

 


```
PROCESS (Clock, Resetn)
BEGIN
IF Resetn = '0' THEN
y_present <= A ;
ELSIF (Clock'EVENT AND Clock = '1') THEN
y_present <= y_next ;
END IF ;
END PROCESS ;

z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;
```

© 2003 -- Don Bouldin
 
## STATE DIAGRAM USING ONE VHDL PROCESS

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY simple IS
PORT (Clock, Resetn, w : IN
z : OUT) ;
END simple ;
ARCHITECTURE Behavior OF simple IS
TYPE State_type IS (A, B, C) ;
SIGNAL y : State_type ;
```




```
BEGIN
PROCESS ( Resetn, Clock )
BEGIN
IF Resetn = '0' THEN
y <= A ;
ELSIF (Clock'EVENT AND Clock = '1') THEN
CASE y IS
WHEN A =>
IF w = '0' THEN y <= A ;
ELSE y <= B ;
END IF ;
WHEN B =>
IF w = '0' THEN y <= A ;
ELSE y <= C ;
END IF ;
WHEN C =>
IF w = '0' THEN y <= A ;
ELSE y <= C ;
END IF ;
END CASE ;
END IF ;
END PROCESS ;
z <= '1' WHEN y = C ELSE '0' ;
END Behavior ;
```

© 2003 -- Don Bouldin

## GRAPHICS CAN SPECIFY STRUCTURE
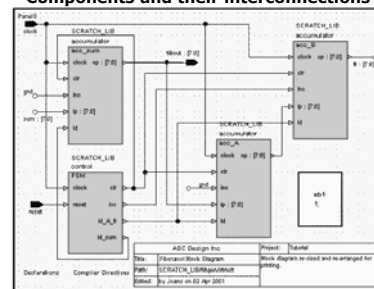
### Components and their interconnections




© 2003 -- Don Bouldin
 
## VHDL CAN SPECIFY STRUCTURE (part 1)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```


```
ENTITY adder IS
    PORT ( Cin : IN STD_LOGIC ;
          X, Y : IN STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S : OUT STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout : OUT STD_LOGIC ) ;
END adder ;
```



© 2003 -- Don Bouldin
 
## VHDL CAN SPECIFY STRUCTURE (part 2)

```
ARCHITECTURE Structure OF adder IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 3) ;
    COMPONENT fulladd
    PORT ( Cin, x, y : IN STD_LOGIC ;
          s, Cout : OUT STD_LOGIC ) ;
    END COMPONENT ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP (
        x => X(3), y => Y(3), Cin => C(3), s => S(3), Cout => Cout ) ;
END Structure ;
```



© 2003 -- Don Bouldin


## VHDL CAN SPECIFY STRUCTURE (part 3)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY fulladd IS
    PORT ( Cin, x, y : IN STD_LOGIC ;
          s, Cout : OUT STD_LOGIC ) ;
END fulladd ;
```

```
ARCHITECTURE LogicFunc OF fulladd IS
```
 
```
BEGIN
    s <= x XOR y XOR Cin ;
    Cout <= (x AND y) OR (x AND Cin) OR (y AND Cin) ;
END LogicFunc ;
```



© 2003 -- Don Bouldin

## USE HDL AND GRAPHICS WISELY

- Use HDL:
  - Most straightforward transcription of control (if-then).
  - Can be technology-independent.
  - Can be optimized and retargeted by synthesis.
  - Can be used to describe structure if needed.
- Use Graphics:
  - Most straightforward transcription of structure/flow.
  - Best for visualization and even animation.
  - May be slower to enter/modify.
  - May be more difficult to manage large designs.
- Capture design using either and then convert to the other.

© 2003 -- Don Bouldin