

DESIGNING FPGAS & ASICS

Simulation and Testing

Prof. Don Bouldin, Ph.D.




Electrical & Computer Engineering

University of Tennessee

TEL: (865)-974-5444

FAX: (865)-974-5483

dbouldin@tennessee.edu

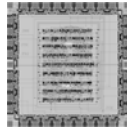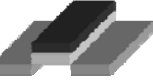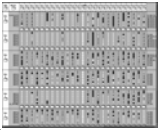

© 2007 -- Don Bouldin

COURSE OUTLINE

- Overview of FPGAs and ASICs
- Using Synthesis
- HDL Examples
- Simulation and Testing
- Physical Place and Route
- Testing ASICs
- Component Reuse

© 2007 -- Don Bouldin

SEMI-CUSTOM DESIGN FLOW OF DIGITAL FPGAS/ASICS

1—HDL


```

CASE w IS
  WHEN "00" => y <= "1000";
  WHEN "01" => y <= "0100";
  WHEN "10" => y <= "0010";
  WHEN OTHERS => y <= "0001";
END CASE;
    
```

2--PRE-SYNTHESIS SIMULATION



3--SYNTHESIS/AUTO LAYOUT

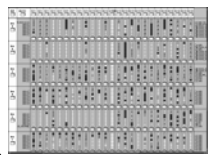


4--POST-LAYOUT SIMULATION



© 2007 -- Don Bouldin

PRE-SYNTHESIS SIMULATION IS TECHNOLOGY-INDEPENDENT

Note the "zero" delay at 2450 ns:

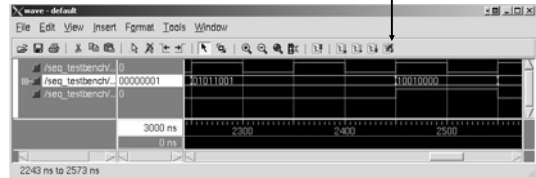

© 2007 -- Don Bouldin

POST-LAYOUT SIMULATION INCLUDES COMPONENT AND WIRING DELAYS


Note the "14ns" delay at 2464 ns:




© 2007 -- Don Bouldin

Simulation of fulladd.vhd

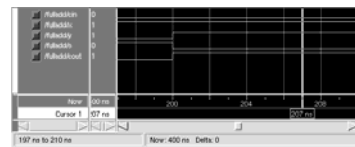- Pre-synthesis: outputs change instantly at 200 ns.



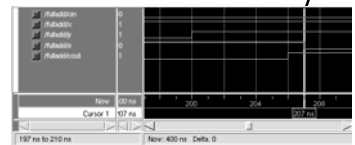- Post-layout: outputs change at 206-207 ns.




© 2007 -- Don Bouldin

RECOMMENDED METHOD FOR LEARNING VHDL

- Copy a known working file to use as a template with reserved words and syntax. Simulate it.
- Modify the VHDL source code to perform your intended operations and then simulate the revised code.
- Be wary of examples in textbooks and on the internet since not all VHDL code is synthesizable with a particular synthesis tool and software environment.
- Avoid use of the “FOR” statement which is confusing.
- Avoid using technology-dependent statements like “WAIT until 14 ns”. Instead, use “WAIT_CLOCK(16)”.

© 2007 -- Don Bouldin

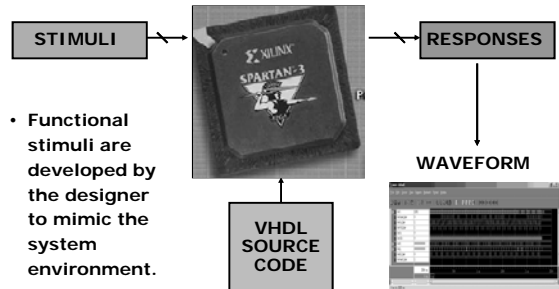SIMULATION SHOWS THE RESPONSES OF THE VHDL TO STIMULI




- Functional stimuli are developed by the designer to mimic the system environment.

© 2007 -- Don Bouldin

THE TESTBENCH CONTAINS THE STIMULI, RESPONSES AND UUT

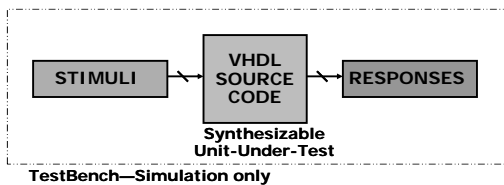- The testbench is written in VHDL but is not synthesized into the FPGA/ASIC.



© 2007 -- Don Bouldin

EXPECTED RESPONSES ARE COMPARED TO ACTUAL ONES

- “Failure” stops simulation while “warning” does not.
- “Note” is used to document a correct response.

```

wait_clock(16);
IF (left_seg = X"6")
  -- check second state of 7-segment display
  THEN
    ASSERT false
    REPORT "Output signals set correctly (7-segment second state)"
    SEVERITY note;
  ELSE
    ASSERT false
    REPORT "Output not set correctly (7-segment second state)"
    SEVERITY warning;
  END IF;
  
```

© 2007 -- Don Bouldin


ALL VHDL SOURCE LINES SHOULD BE TESTED

The simulator can produce coverage reports.

Pathname	Lines	Hits	%	Coverage
tel tech/bin/./suinos5	228	0	0.0	
tel tech/bin/./suinos5	502	0	0.0	
tel tech/bin/./suinos5	20	0	0.0	
ky/bist_mod.vhd	126	104	82.5	
ky/debounce.vhd	6	6	100.0	
ky/mainlogic.vhd	193	170	88.1	
ky/out_7seg.vhd	71	43	60.6	
ky/out_leds.vhd	42	30	71.4	
ky/prng.vhd	24	22	91.7	
ky/registers.vhd	13	13	100.0	
ky/translate_job.vhd	12	12	100.0	
bench/main_test.vhd	87	80	92.0	
Total	1359	480	35.3	

© 2007 -- Don Bouldin

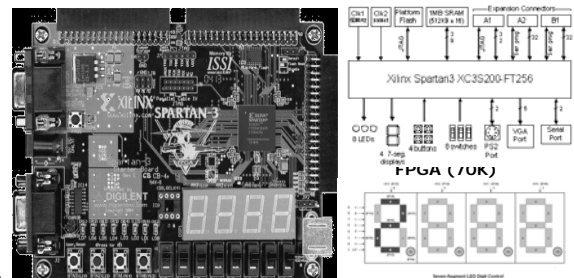FINAL VERIFICATION IS PERFORMED USING A PROTYPING BOARD



© 2007 -- Don Bouldin

XILINX TOOLS ARE FREE BUT TARGET ONLY XILINX PARTS

- Anyone can download Xilinx WebPACK tools for free from www.xilinx.com

Free ISE WebPACK 7.1i



The free ISE WebPACK™ 7.1i is the most complete, easy-to-use software solution to complete a Xilinx CPLD or medium-density FPGA design. ISE WebPACK is the ideal downloadable desktop solution offering free software modules from ABEL and HDL, synthesis to device filing and JTAG programming. ISE WebPACK is a subset of our award winning ISE Foundation™ design tools providing instant access to the ISE tools at no cost. Xilinx has created a solution that allows convenient productivity by providing a design solution that is always up to date with error-free downloading and single file installation.

ModelSim™ Xilinx Edition-III



The ModelSim-III Family of Products

Product Name	Available From
ModelSim-III Starter	Free from Xilinx
CPL	Full

- WebPACK includes a free version of ModelSim that works only for Xilinx parts but you must register at www.mentor.com


© 2007 -- Don Bouldin

IMPLEMENTING A PROJECT

- Determine I/O Requirements
- Partition into 5-9 submodules and test individually before combining.
- Use/Enhance Built-In Self-Test
- Debounce Pushbutton Switches
- Filter an Input to Produce a Single Pulse
- Use hierarchy with Submodule Components
- Synchronize Externally Clocked Inputs


© 2007 -- Don Bouldin

DETERMINE SYSTEM I/O REQUIREMENTS

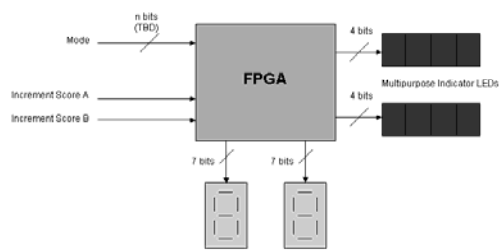


© 2007 -- Don Bouldin

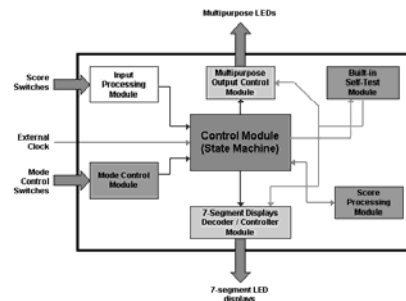DECOMPOSE EACH LEVEL INTO 7 +/- 2 SUBMODULES



© 2007 -- Don Bouldin

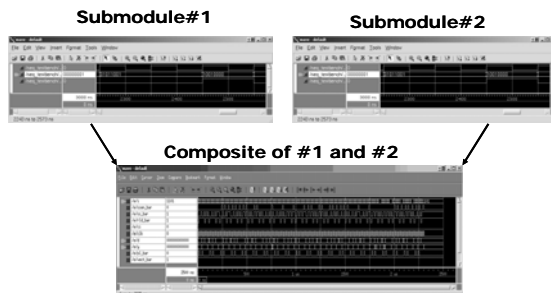SIMULATE EACH SUBMODULE AND THEN INTEGRATE THEM



© 2007 -- Don Bouldin

BUILT-IN SELF-TEST

- Downloading hw3a (BIST) ensures the integrity of the connection between the CPU and the Spartan3 prototyping board AND then checks the input switches and the 7-segment displays.
- More thorough checks could be added to ensure the integrity of the board I/O for a specific project.



© 2007 -- Don Bouldin

INTERNAL FREQUENCIES CAN BE DERIVED FROM THE EXTERNAL CLOCK

- A crystal oscillator on the Spartan3 prototyping board produces a 50 MHz clock.
- Counters can be used to divide down a frequency into a slower synchronized one:

Divide By	Frequency	Duration
1	clock_50MHz	20 ns
2	clock_25 MHz	40 ns
25	clock_1MHz	1000 ns = 1us
10	clock_100KHz	10 us
10	clock_10KHz	100 us
10	clock_1KHz	1000 us = 1 ms
10	clock_100Hz	10 ms
10	clock_10Hz	100 ms
10	clock_1Hz	1000 ms = 1 s
10	clock_tenthHz	10 s

© 2007 -- Don Bouldin

Simulation of clk_div.vhd (part 1)

- 50 MHz divided by 2 → 25 MHz:




- 25 MHz divided by 25 → 1 MHz:



© 2007 -- Don Bouldin

Simulation of clk_div.vhd (part 2)

- 10 KHz divided by 10 → 1 KHz:

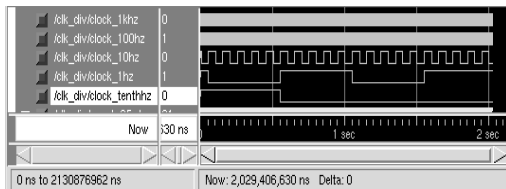

© 2007 -- Don Bouldin

clk_div.vhd (part 1)

```

in#          sim:clk_div: clk_div.vhd
1  -- original from sim:modules at verilog Test
2  -- created on 3/25/07 by Don Bouldin, Civ 5000 and TestLab
3  LIBRARY IEEE;
4  USE IEEE.STD_LOGIC_1164.ALL;
5  USE IEEE.STD_LOGIC_ARITH.ALL;
6  USE IEEE.STD_LOGIC_UNSIGNED.ALL;
7
8  ENTITY clk_div IS
9
10     port
11     (
12         clock_50MHz      : IN  STD_LOGIC;
13         clock_25MHz      : OUT  STD_LOGIC;
14         clock_1MHz       : OUT  STD_LOGIC;
15         clock_100KHz     : OUT  STD_LOGIC;
16         clock_10KHz      : OUT  STD_LOGIC;
17         clock_1KHz       : OUT  STD_LOGIC;
18         clock_10Hz       : OUT  STD_LOGIC;
19         clock_1Hz        : OUT  STD_LOGIC;
20         clock_tenthHz    : OUT  STD_LOGIC);
21
22 END clk_div;
23
24 ARCHITECTURE OF clk_div IS
25
26     SIGNAL count_25MHz : STD_LOGIC_VECTOR( 000000 );
27     SIGNAL count_1MHz  : STD_LOGIC_VECTOR( 000000 );
28     SIGNAL count_100KHz : STD_LOGIC_VECTOR( 000000 );
29     SIGNAL count_10KHz : STD_LOGIC_VECTOR( 000000 );
30     SIGNAL count_1KHz : STD_LOGIC_VECTOR( 000000 );
31     SIGNAL count_10Hz : STD_LOGIC_VECTOR( 000000 );
32     SIGNAL count_1Hz : STD_LOGIC_VECTOR( 000000 );
33     SIGNAL count_tenthHz : STD_LOGIC_VECTOR( 000000 );
34
35 BEGIN

```

© 2007 -- Don Bouldin

clk_div.vhd (part 2)

```

in#          sim:clk_div: clk_div.vhd
33 BEGIN
34     PROCESS
35     BEGIN
36         -- Divide by 2
37         WAIT UNTIL clock_50MHz'EVENT and clock_50MHz = '1';
38         IF count_25MHz < 1 THEN
39             count_25MHz <= count_25MHz + 1;
40         ELSE
41             count_25MHz <= "00";
42         END IF;
43         IF count_25MHz < 1 THEN
44             clock_25MHz_int <= '0';
45         ELSE
46             clock_25MHz_int <= '1';
47         END IF;
48
49         -- Riggle clocks are used in this code to save prescaler hardware
50         -- Sync all clock prescaler outputs back to master clock signal
51         clock_1Hz <= clock_25MHz_int;
52         clock_10Hz <= clock_1Hz_int;
53         clock_100Hz <= clock_10Hz_int;
54         clock_1KHz <= clock_1KHz_int;
55         clock_10KHz <= clock_10KHz_int;
56         clock_100KHz <= clock_100KHz_int;
57         clock_1Hz <= clock_1Hz_int;
58         clock_10Hz <= clock_10Hz_int;
59         clock_1KHz <= clock_1KHz_int;
60         clock_tenthHz <= clock_tenthHz_int;
61
62     END PROCESS;

```

© 2007 -- Don Bouldin

clk_div.vhd (part 3)

```

in#          sim:clk_div: clk_div.vhd
62     PROCESS
63     BEGIN
64         -- Divide by 25
65         WAIT UNTIL clock_1MHz_int'EVENT and clock_1MHz_int = '1';
66         IF count_10Hz < 1 THEN
67             count_10Hz <= count_10Hz + 1;
68         ELSE
69             count_10Hz <= "00000";
70         END IF;
71         IF count_10Hz < 1 THEN
72             clock_10Hz_int <= '0';
73         ELSE
74             clock_10Hz_int <= '1';
75         END IF;
76     END PROCESS;
77
78     PROCESS
79     BEGIN
80         -- Divide by 10
81         WAIT UNTIL clock_10Hz_int'EVENT and clock_10Hz_int = '1';
82         IF count_100KHz < 1 THEN
83             count_100KHz <= count_100KHz + 1;
84         ELSE
85             count_100KHz <= "0000";
86         END IF;
87         IF count_100KHz < 1 THEN
88             clock_100KHz_int <= '0';
89         ELSE
90             clock_100KHz_int <= '1';
91         END IF;
92     END PROCESS;
93
94 END clk_div;

```

© 2007 -- Don Bouldin

clk_div.vhd (part 4)

```

136
137
138
1000

```

© 2007 -- Don Bouldin

clk_div.vhd (part 5)

```

136
137
138
500

```

© 2007 -- Don Bouldin

clk_div.vhd (part 6)

```

136
137
138
500

```

© 2007 -- Don Bouldin

AN INPUT PUSHBUTTON SWITCH MAY BOUNCE

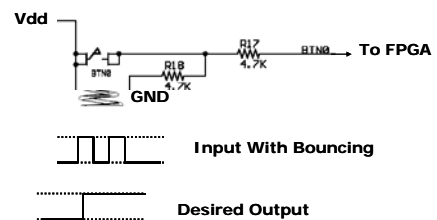


Fig. 5.11, Page 243
© 1997 A-W-L, Inc.
Used by permission.

© 2007 -- Don Bouldin

debounce.vhd

```


1
2
3
500

```

© 2007 -- Don Bouldin

Simulation of debounce.vhd (part 1)

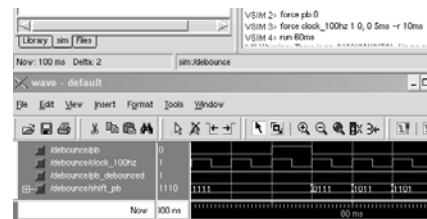
- PB has been 0 (inactive), then is 1 (active) but only for 10 ms (too short to be valid) so PB_debounced stays 1 (inactive):



© 2007 -- Don Bouldin

Simulation of debounce.vhd (part 2)

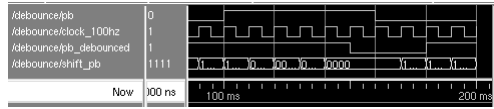
- This time PB is 1 (active) for 60 ms (which is valid since it is at least 40ms) so PB_debounced becomes 0 (active):



© 2007 -- Don Bouldin

FILTER AN INPUT TO PRODUCE A SINGLE PULSE

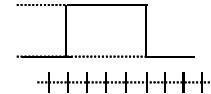An External Pushbutton Switch May Be Pressed For Multiple Clock Ticks




A Circuit Can Be Implemented to Produce Only a Single Pulse



© 2007 -- Don Bouldin

Simulation of onepulse.vhd

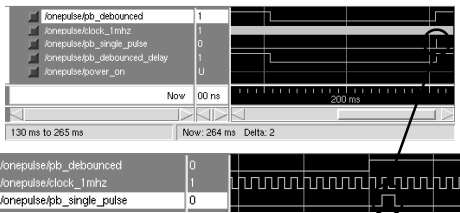- PB_debounced has been 0 (active) for 100 ms but only a single 1 ms pulse is produced:



© 2007 -- Don Bouldin

onepulse.vhd (part 1)

```

in #                                sim:/onepulse : onepulse.vhd
1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.all;
3  USE IEEE.STD_LOGIC_ARITH.all;
4  USE IEEE.STD_LOGIC_UNSIGNED.all;
5
6  -- Single Pulse circuit
7  -- the output will go high for only one clock cycle
8
9  ENTITY onepulse IS
10
11     PORT (PB_debounced, clock_1mhz : IN STD_LOGIC;
12          PB_single_pulse : OUT STD_LOGIC);
13
14 END onepulse;
15
16
    
```

© 2007 -- Don Bouldin

onepulse.vhd (part 2)

```

--
16 ARCHITECTURE a OF onepulse IS
17     SIGNAL PB_debounced_delay, Power_on : STD_LOGIC;
18
19
20 BEGIN
21     PROCESS
22     BEGIN
23         WAIT UNTIL (CLOCK_1mhz'event) AND (CLOCK_1mhz='1');
24         -- Power_on will be initialized to '0' at power up
25         IF Power_on='0' THEN
26             -- This code resets the critical signals once at power up
27             PB_single_pulse <= '0';
28             PB_debounced_delay <= '1';
29             Power_on <= '1';
30         ELSE
31             -- A single clock cycle pulse is produced when the switch is hit
32             -- No matter how long the switch is held down
33             -- The switch input must already be debounced
34             IF PB_debounced = '1' AND PB_debounced_delay = '0' THEN
35                 PB_single_pulse <= '1';
36             ELSE
37                 PB_single_pulse <= '0';
38             END IF;
39             PB_debounced_delay <= PB_debounced;
40         END IF;
41     END PROCESS;
42
43 END a;
44
45 END PROCESS;
46
47 END a;
    
```

© 2007 -- Don Bouldin

onepulse.vhd (part 1) (modified)

Original

```

in #                                sim:/onepulse : onepulse.vhd
1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.all;
3  USE IEEE.STD_LOGIC_ARITH.all;
4  USE IEEE.STD_LOGIC_UNSIGNED.all;
5
6  -- Single Pulse circuit
7  -- the output will go high for only one clock cycle
8
9  ENTITY onepulse IS
10
11     PORT (PB_debounced, clock_1mhz : IN STD_LOGIC;
12          PB_single_pulse : OUT STD_LOGIC);
13
14 END onepulse;
15
16
    
```

Modified:

```

in #                                sim:/onepulse : onepulse.vhd
1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.all;
3  USE IEEE.STD_LOGIC_ARITH.all;
4  USE IEEE.STD_LOGIC_UNSIGNED.all;
5
6  -- Single Pulse circuit
7  -- the output will go high for only one clock cycle
8
9  ENTITY onepulse IS
10
11     PORT (PB_debounced, reset_pb_flag, clock_1mhz : IN STD_LOGIC;
12          PB_single_pulse, pb_flag : OUT STD_LOGIC);
13
14 END onepulse;
15
16
    
```

© 2007 -- Don Bouldin

onepulse.vhd (part 2) (modified)

```

17 ARCHITECTURE a OF onepulse IS
18     SIGNAL pb_debounced_delay, Power_on : STD_LOGIC;
19
20 BEGIN
21     PROCESS
22     BEGIN
23         WAIT UNTIL (clock_10Hz='HIGH') AND (clock_10Hz='1');
24         Power_on will be initialized to '0' at power up
25
26         IF Power_on='0' THEN -- This code creates the critical signals once at power up
27             pb_single_pulse <= '0';
28             pb_debounced_delay <= "1";
29             pb_flag <= "1";
30             Power_on
31         ELSE
32             -- A single clock cycle pulse is produced when the switch is hit
33             -- No matter how long the switch is held down
34             -- The switch bounces must always be debounced
35             IF pb_debounced = '1' AND pb_debounced_delay = '0' THEN
36                 pb_single_pulse <= "1";
37                 pb_flag <= "1";
38             ELSE
39                 pb_single_pulse <= "0";
40                 IF reset_pb_flag = "1" THEN pb_flag <= "0";
41                 ELSE
42                     END IF;
43             END IF;
44             pb_debounced_delay <= pb_debounced;
45
46         END IF;
47     END PROCESS;
48 END a;

```

© 2007 -- Don Bouldin


Simulation of onepulse.vhd (modified)

- PB_debounced has been 0 (active) for 100 ms but only a single 1 ms pulse is produced and pb_flag is set. After being read, pb_flag is reset.



© 2007 -- Don Bouldin


HIERARCHY WITH SUBMODULE COMPONENTS

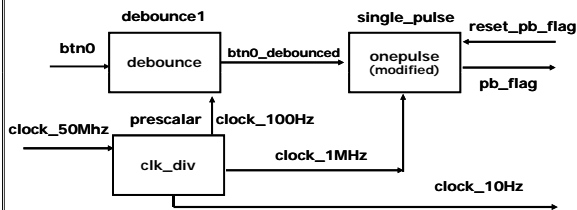

© 2007 -- Don Bouldin

Simulation of hierarch.vhd

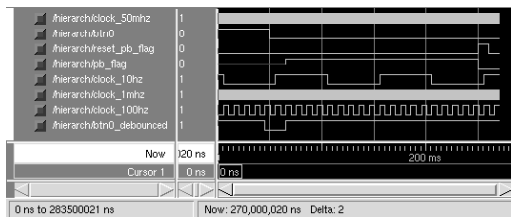- A proper pressing of btn0 sets pb_flag to HIGH.
- Once pb_flag is read, it is reset to LOW.



© 2007 -- Don Bouldin

hierarch.vhd (part 1)

```

1 LIBRARY IEEE;
2 USE IEEE.STD_LOGIC_1164.ALL;
3 USE IEEE.STD_LOGIC_ARITH.ALL;
4 USE IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6 ENTITY hierarch IS
7     PORT (clock_50MHz, btn0, reset_pb_flag : IN STD_LOGIC;
8           pb_flag, clock_10Hz : OUT STD_LOGIC);
9 END ENTITY hierarch;
10 ARCHITECTURE a OF hierarch IS
11     -- Delay signals needed to connect submodules
12     SIGNAL clock_100Hz, clock_100ms, btn0_debounced : STD_LOGIC;
13     -- Use components to define submodules and parameters
14     COMPONENT debounce
15     PORT (pb : IN STD_LOGIC;
16           pb_debounced : OUT STD_LOGIC);
17     END COMPONENT;
18     COMPONENT onepulse
19     PORT (pb_debounced, reset_pb_flag, clock_10Hz : IN STD_LOGIC;
20           pb_single_pulse, pb_flag : OUT STD_LOGIC);
21     END COMPONENT;
22     COMPONENT clk_div
23     PORT (clock_50MHz : IN STD_LOGIC;
24           clock_100Hz : OUT STD_LOGIC;
25           clock_10Hz : OUT STD_LOGIC);
26     END COMPONENT;
27     clk_div : clk_div PORT MAP (clock_50MHz => clock_50MHz, clock_10Hz => clock_10Hz,
28                                clock_100Hz => clock_100Hz);
29     debounce : debounce PORT MAP (pb => btn0, clock_100Hz => clock_100Hz);
30     onepulse : onepulse PORT MAP (pb_debounced => btn0_debounced,
31                                  reset_pb_flag => reset_pb_flag,
32                                  pb_flag => pb_flag,
33                                  clock_10Hz => clock_10Hz);
34 END ARCHITECTURE a;

```

© 2007 -- Don Bouldin

hierarch.vhd (part 2)

```


36 BEGIN
37
38 -- Use Port Map to connect signals between components in the hierarchy
39 debounce1 : debounce PORT MAP (pb => btn0, clock_100Hz => clock_100Hz,
40                                pb_debounced => btn0_debounced);
41
42 prescaler : clk_div PORT MAP (clock_50MHz => clock_50MHz, clock_10Hz => clock_10Hz,
43                                clock_100Hz => clock_100Hz, clock_10Hz => clock_10Hz);
44
45 single_pulse : onepulse PORT MAP (pb_debounced => btn0_debounced,
46                                   reset_pb_flag => reset_pb_flag,
47                                   pb_flag => pb_flag,
48                                   clock_10Hz => clock_10Hz);
49
50 END a;
51

```

© 2007 -- Don Bouldin

Detailed Layout of hw3a


- Pin M13 is connected to btn0:

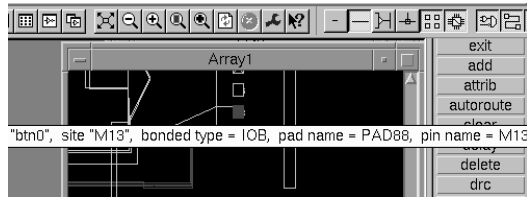

© 2007 -- Don Bouldin

SYNCHRONIZER REDUCES RISK OF METASTABILITY PROBLEMS

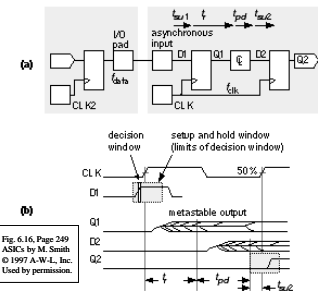- Signals from external circuits whose clock is independent must be synchronized with our internal clock.
- If not, the external input may occur during the decision window of our flip-flop and cause it to go into a metastable state.
- To reduce the likelihood of this occurring, the input can be double-buffered.



© 2007 -- Don Bouldin