 




CMOS Digital Integrated Circuits



Chapter 5 MOS Inverters: Static Characteristics

S.M. Kang and Y. Leblebici

Ideal Inverter

 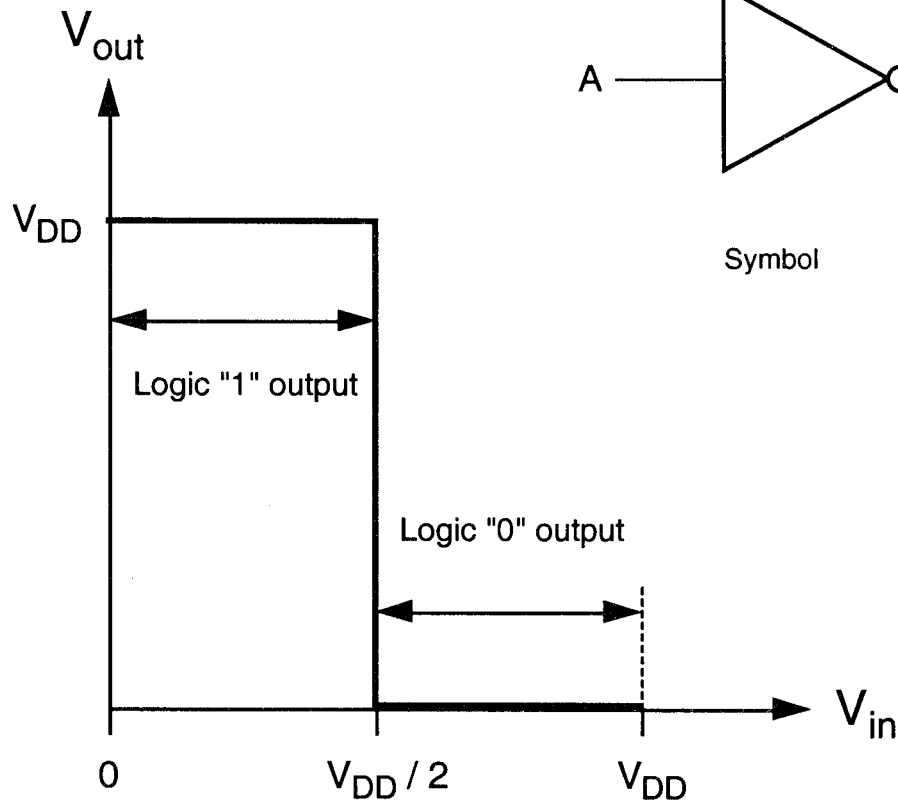


Symbol

A	B
0	1
1	0

Truth Table


Voltage Transfer Characteristic (VTC) of the ideal inverter

Generic Inverter VTC

 


Voltage Transfer Characteristic (VTC) of a typical inverter

Noise Margins

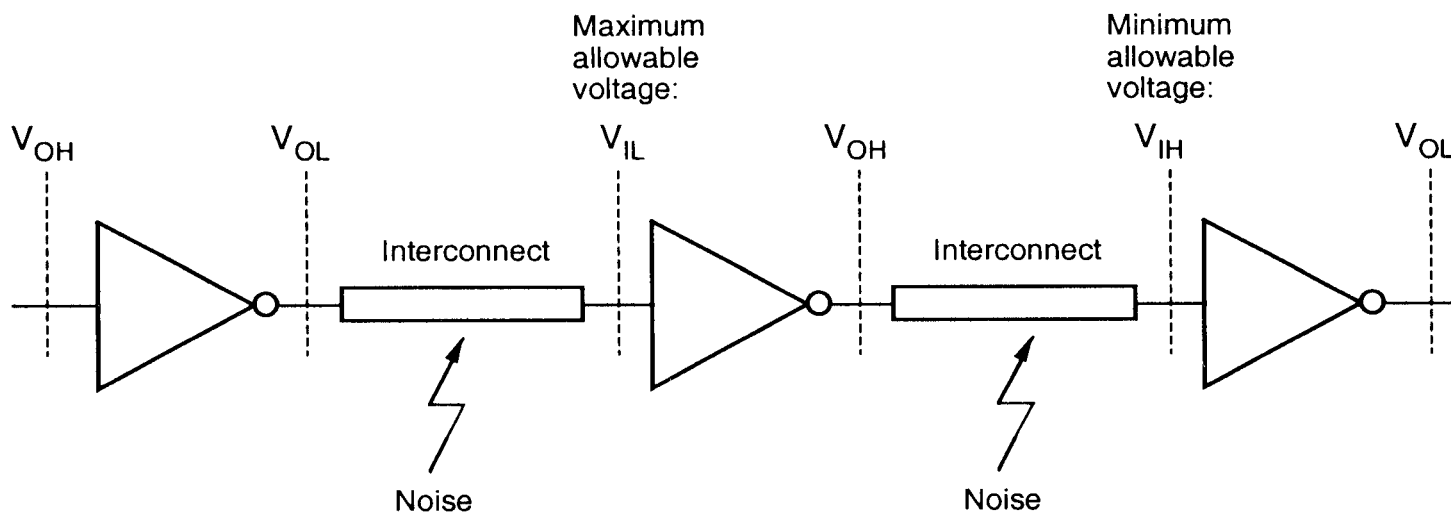

Propagation of digital signals under the influence of noise

Noise Margins

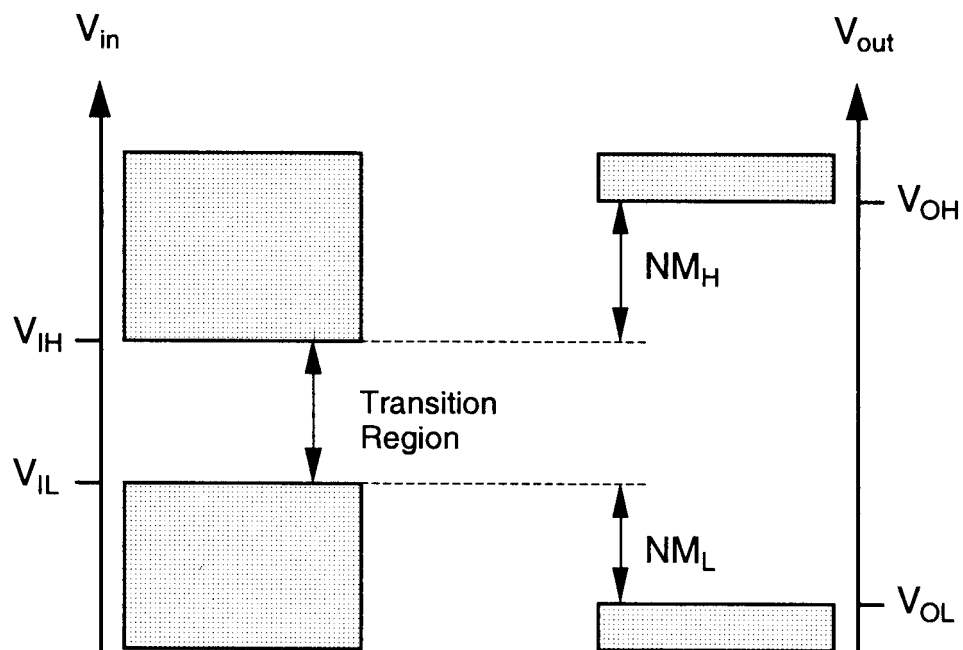

Definition of
noise margins

$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

Noise Margins

Nominal output $V_{out} = f(V_{in})$ (5.5)


Output under noise $V'_{out} = f(V_{in} + \Delta V_{noise})$ (5.6)

$$V'_{out} = f(V_{in}) + \frac{dV_{out}}{dV_{in}} \cdot \Delta V_{noise} + \text{higher order terms (neglected)} \quad (5.7)$$


The nominal operating region is defined as the region where the gain is less than unity !

$$\text{Perturbed Output} = \text{Nominal Output} + \text{Gain} \times \text{External Perturbation} \quad (5.8)$$

CMOS Inverter Circuit

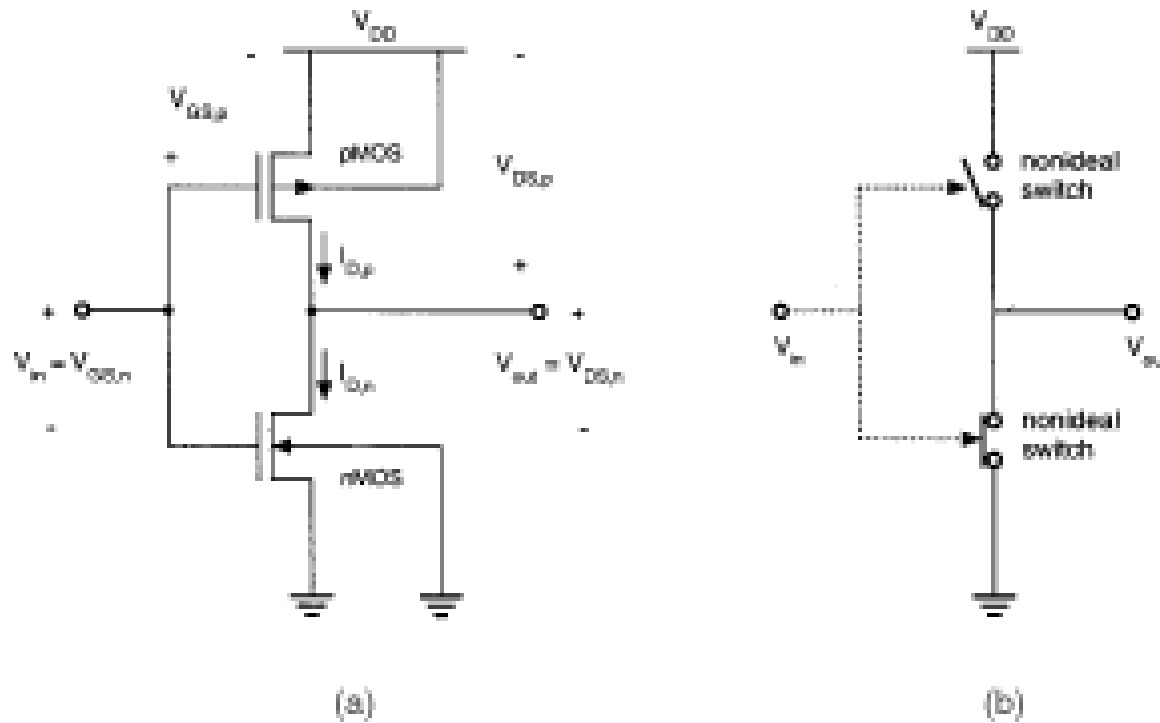

CMOS Inverter Circuit

 

CMOS Inverter Circuit

determine noise margins


$$V_{IL} = \frac{2V_{out} + V_{T0,p} - V_{DD} + k_R V_{T0,n}}{1 + k_R} \quad (5.62)$$

$$V_{IH} = \frac{V_{DD} + V_{T0,p} + k_R \cdot (2V_{out} + V_{T0,n})}{1 + k_R} \quad (5.67)$$

inversion (switching) threshold voltage


$$V_{th} = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R}} \cdot (V_{DD} + V_{T0,p})}{\left(1 + \sqrt{\frac{1}{k_R}}\right)} \quad (5.71)$$

CMOS Inverter Circuit

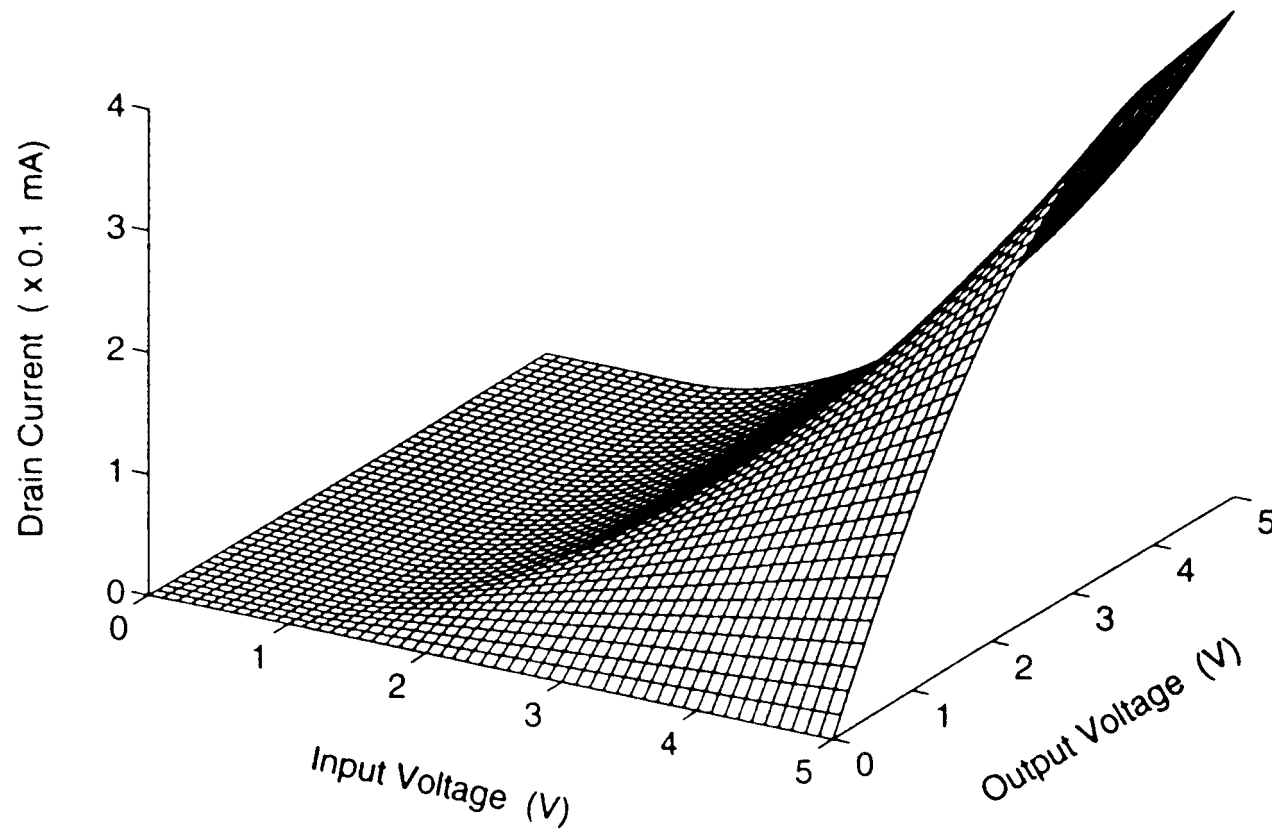


nMOS transistor current-voltage characteristics

CMOS Inverter Circuit

 


pMOS transistor current-voltage characteristics

CMOS Inverter Circuit

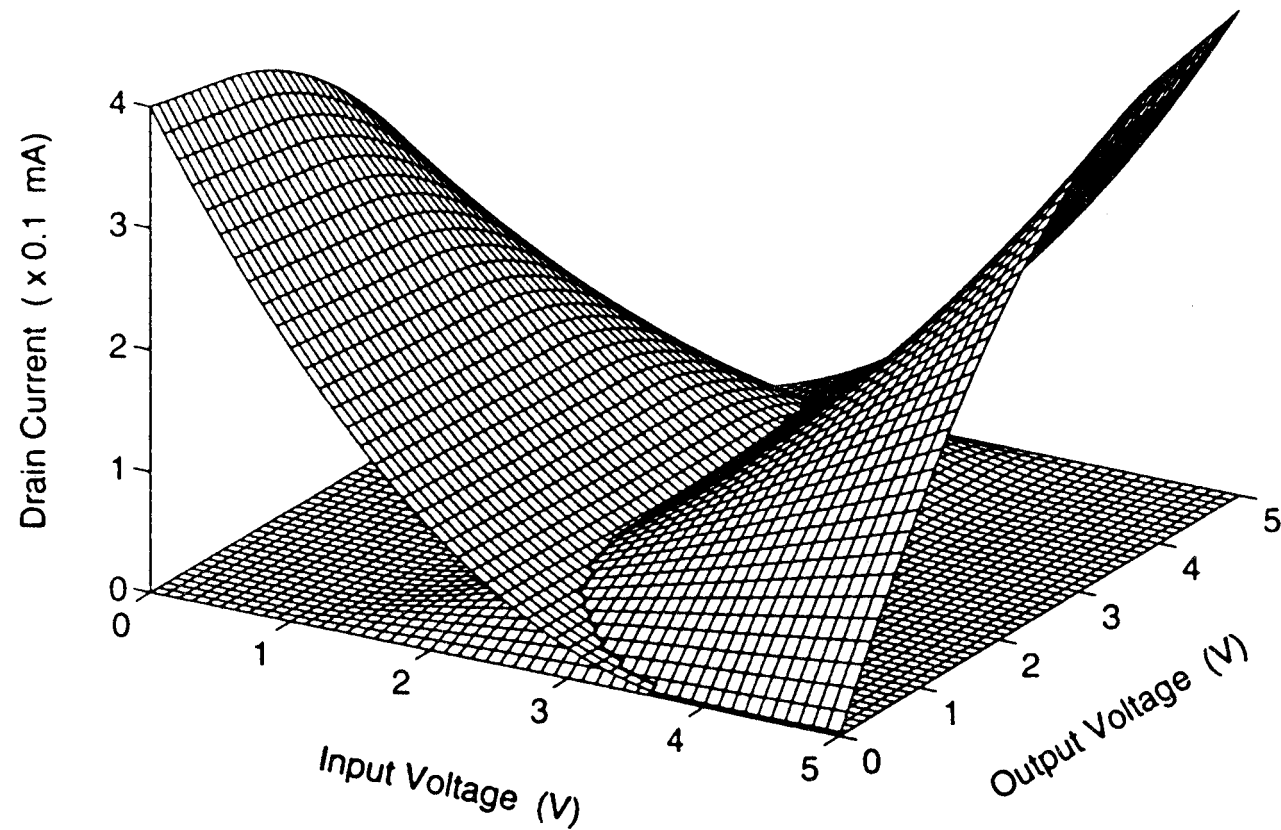


Intersection of current-voltage surfaces of nMOS and pMOS transistors

CMOS Inverter Circuit

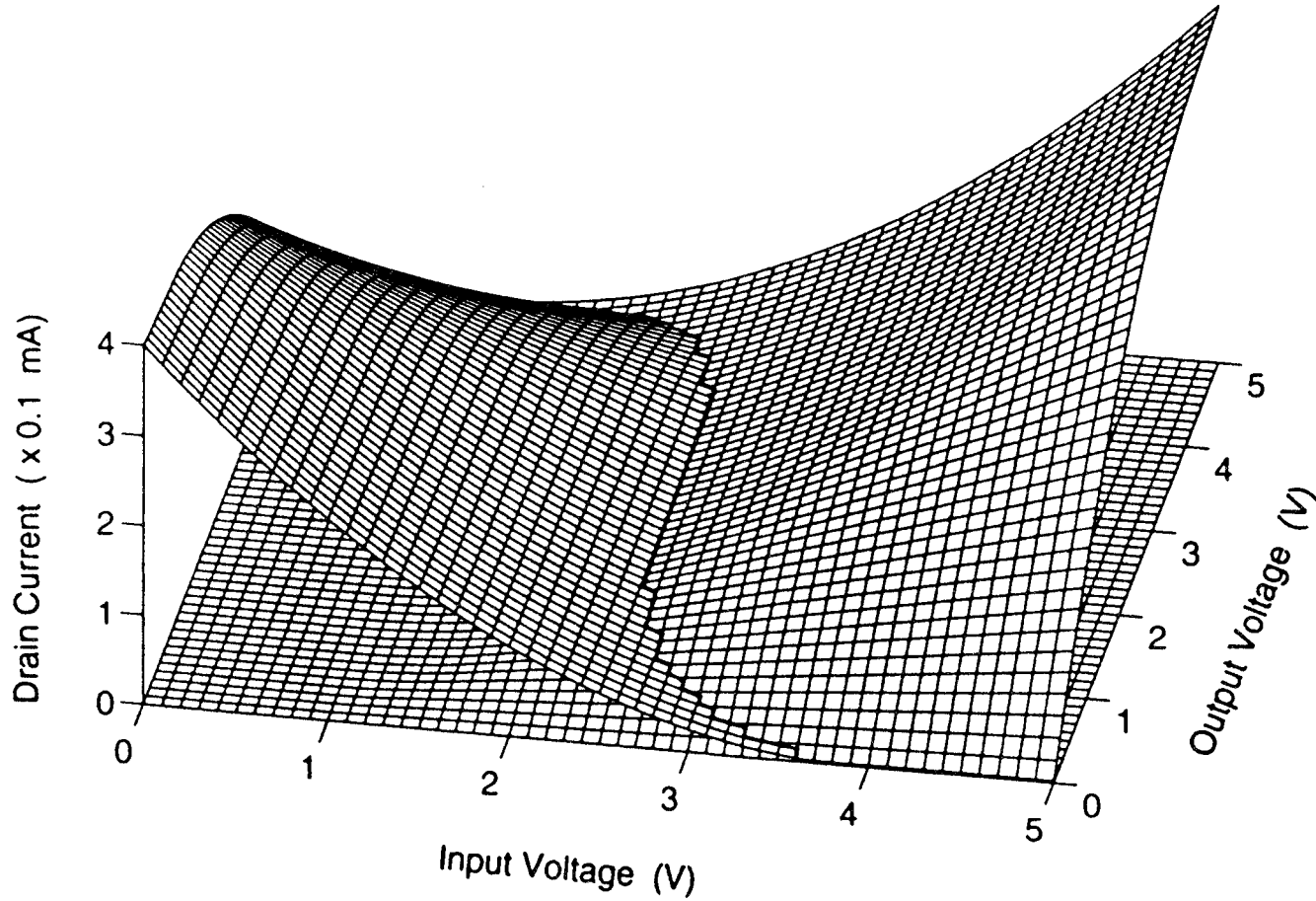

Intersection of current-voltage surfaces gives the VTC in the voltage plane

CMOS Inverter Circuit

 


CMOS Inverter Circuit

How to choose the k_R ratio to achieve a desired inversion threshold voltage:


$$k_R = \frac{k_n}{k_p} = \left(\frac{V_{DD} + V_{T0,p} - V_{th}}{V_{th} - V_{T0,n}} \right)^2 \quad (5.73)$$

$$\frac{k_n}{k_p} = \frac{\mu_n C_{ox} \cdot \left(\frac{W}{L} \right)_n}{\mu_p C_{ox} \cdot \left(\frac{W}{L} \right)_p} = \frac{\mu_n \cdot \left(\frac{W}{L} \right)_n}{\mu_p \cdot \left(\frac{W}{L} \right)_p} \quad (5.77)$$

CMOS Inverter Circuit

 


Supply Voltage Scaling

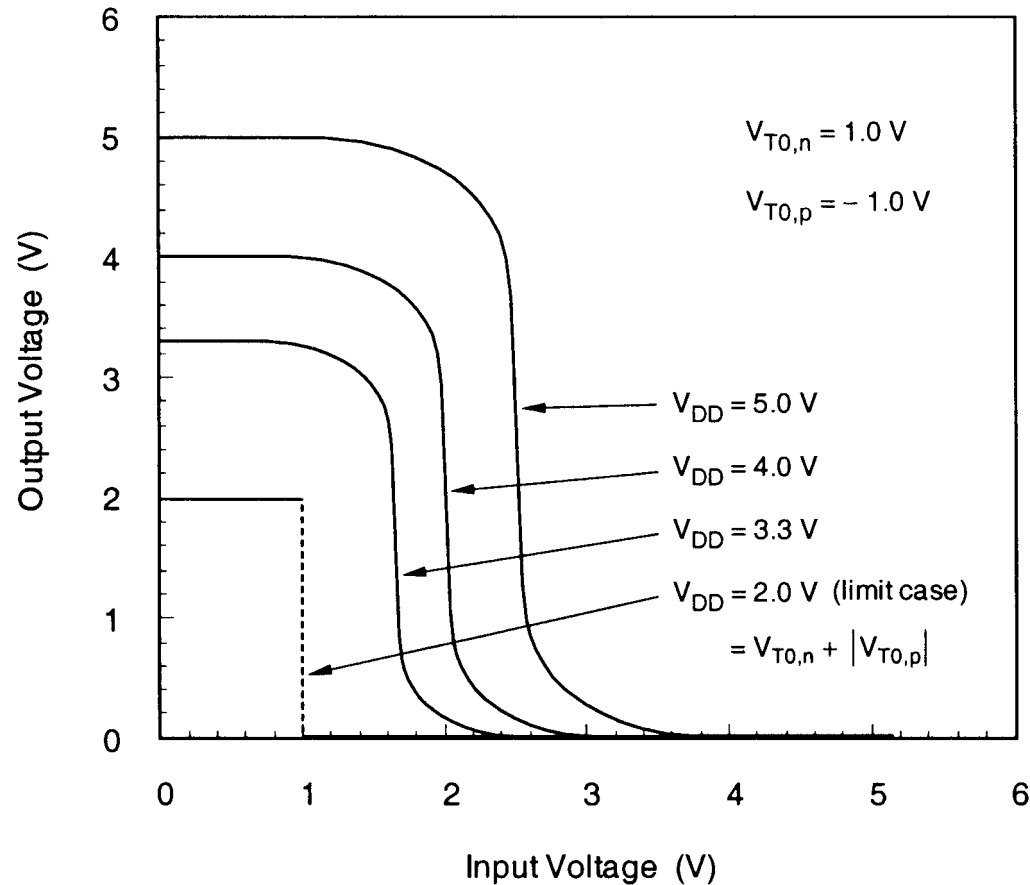

VTC of a CMOS inverter for different power supply voltage values.


Supply Voltage Scaling

 


VTC of a CMOS inverter, when operated with a supply voltage that is smaller than $(V_{Tn} + |V_{Tp}|)$.

→ Hysteresis behavior !


CMOS Inverter Layout

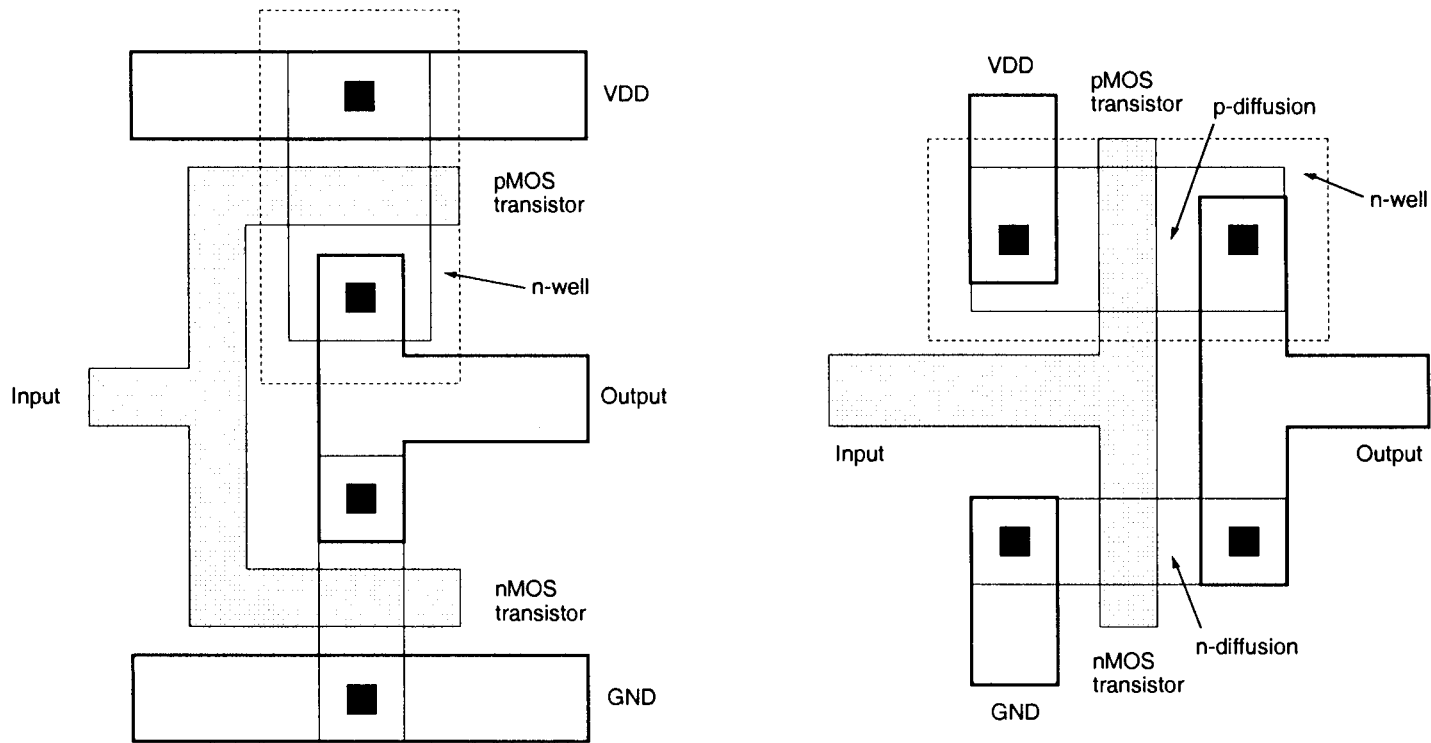

CMOS Inverter Layout

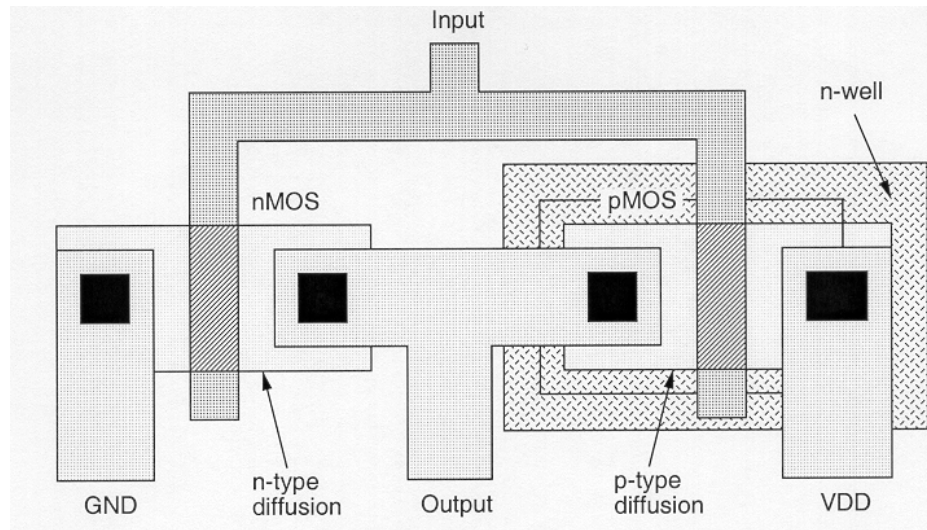

Mask layout of the inverter

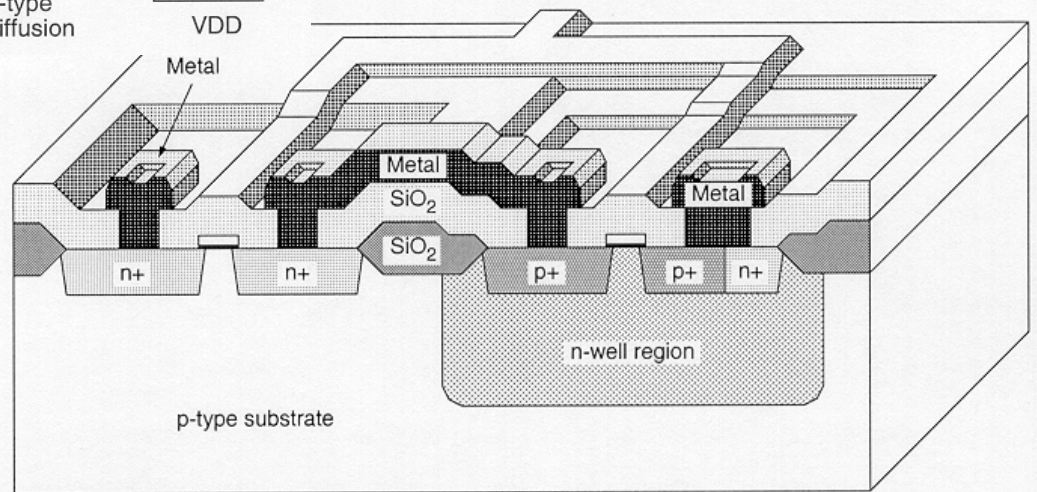

Simplified cross-section