 


## DESIGNING FPGAs & ASICs



### HDL-Synthesis



  **Prof. Don Bouldin, Ph.D.**




Electrical & Computer Engineering  
University of Tennessee  
TEL: (865)-974-5444  
FAX: (865)-974-5483  
dbouldin@tennessee.edu



© 2005 -- Don Bouldin

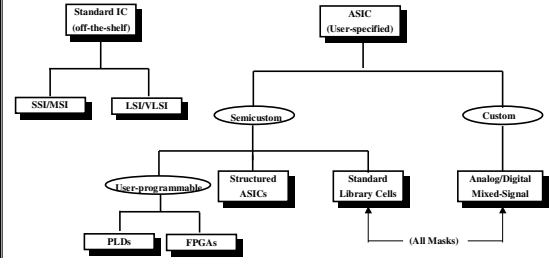
## APPLICATIONS MAY USE STANDARD ICs or FPGAs/ASICs



© 2005 -- Don Bouldin
 
## SYSTEM FUNCTIONS ARE OFTEN SPLIT BETWEEN THE CPU AND AN ASIC

- The most economical means of implementing logic functions is to use a microprocessor.
- When the microprocessor is too slow or too busy to handle some fast inputs and outputs, an ASIC can be used to implement "random" logic.




© 2005 -- Don Bouldin

## PROGRAMMABLE LOGIC DEVICES ARE BEST FOR SMALL DESIGNS WITH I/O

- Vendor prefabricates multiple sets of ANDs and ORs with programmable connections
- User specifies connections to implement desired logic functions
- Replaces 200 to 8,000 gates with single package of 20-84 pins
- Electrically programmable (and erasable) by the user one at a time within minutes


### PLDs

 

© 2005 -- Don Bouldin

## FPGAs ARE BEST FOR ADAPTABLE SITUATIONS

### FPGAs

 

- Vendor prefabricates parts with rows of gates and programmable connections
- User specifies connections to implement logic functions
- Replaces 8,000 to 200,000 gates (or more)
- Electrically programmable (and erasable) by the user one at a time within minutes
- Production quantity < 200,000
- PC-based development system costs \$10K

© 2005 -- Don Bouldin


## ALTERA FPGA LAYOUT

Vendor prefabricates parts with rows of gates (look-up tables) and programmable connections (not shown).

© 2005 -- Don Bouldin
 
## DETAILED LAYOUT OF XILINX FPGA


Programmable switches (*puddles* which have RC delay) determine which wiring segments (short, medium, long) are connected.



© 2005 -- Don Bouldin

 
## RECONFIGURABLE COMPONENTS ARE ADAPTABLE

The internal logic and interconnect of a reconfigurable component (FPGA) may be specified by the user and changed at any time.




© 2005 -- Don Bouldin
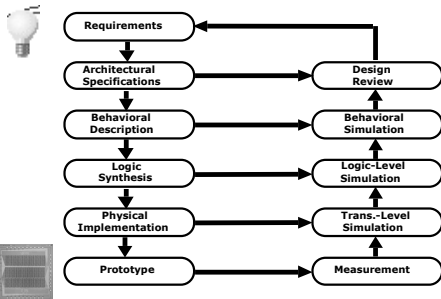
## MICROELECTRONIC SYSTEM DESIGN CONSISTS OF ITERATIVE REFINEMENTS OF SYNTHESIS AND VERIFICATION



© 2005 -- Don Bouldin
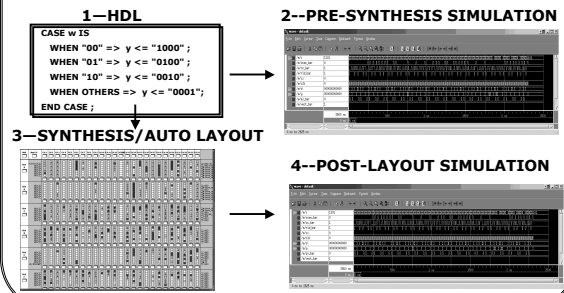
## SEMI-CUSTOM DESIGN FLOW OF DIGITAL FPGAs/ASICs




© 2005 -- Don Bouldin

## A HARDWARE DESCRIPTION LANGUAGE CAN BE SYNTHESIZED

- The desired functionality and timing may be described using a *hardware description language* such as VHDL or Verilog and then *synthesized* into the structural level for a specified device.
- Synthesis* involves:
  - (1) translation into Boolean equations,
  - (2) optimization for area/delay, and then
  - (3) mapping to a FPGA or ASIC process (library).
- The physical level is then implemented automatically using a placement and routing program.

© 2005 -- Don Bouldin

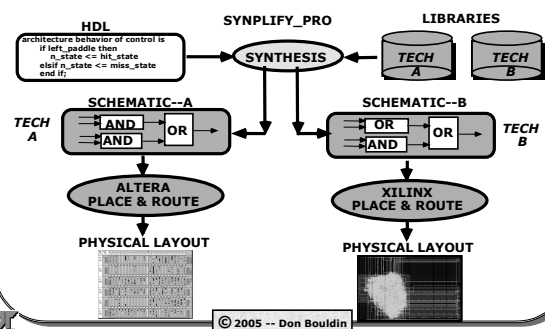
## HDL DESIGNS CAN BE TARGETED TO MULTIPLE LAYOUTS



© 2005 -- Don Bouldin
 
## SYNTHESIS AND FPGAS CAN REDUCE TIME-TO-MARKET

- Synthesis can reduce the design time required to achieve and verify a given functionality since many candidate solutions can be constructed quickly and accurately.
- Simulation is required for verification and risk reduction but is time-consuming and may not be entirely representative of the full system environment.
- Prototyping with FPGAs can speed verification and reduce risk.
- Synthesis facilitates retargeting a design from one FPGA to another or to an ASIC when the requirements are frozen and the production quantity is sufficient.



© 2005 -- Don Bouldin

13

## TIME-TO-MARKET AFFECTS PRODUCT REVENUE

 


Fig. 1.13, Page 24 ASICs by M. Smith © 1997 A-D-W, Inc. Used by permission.

© 2005 -- Don Bouldin

14

## REDUCTION IN TIME-TO-MARKET INCREASES PROFITS

METHODOLOGY	Design Capture	Design Verification	Production and Profit
TRADITIONAL:	CAP	VER	\$\$\$
SYNTHESIS:	CAP	VER	\$\$\$\$\$\$\$\$
SYNTHESIS AND FPGAs:	CAP	VER	\$\$\$\$\$\$\$\$\$\$\$\$\$\$\$\$

© 2005 -- Don Bouldin

15

## DRIVING THE DESIGN FLOW



- Graphical User Interface (GUI)

Presents only valid choices and can guide user. May improve productivity by reducing errors. May degrade productivity by taking longer to enter.

- Command Line Interface (CLI)

Command lines (script) are generally faster. Can use old script as a guide. Best for iterations.

`vsim -coverage Seq_TestBench -do stim.do`

© 2005 -- Don Bouldin

16

## PRINCIPLES OF SYSTEM OPTIMIZATION

- A global figure of merit for the entire system should be determined and optimized.
- This figure of merit involves multiple dimensions including cost, area, speed, power, design time, risk, etc.
- Optimization of a particular level or component of a system may not constitute a good return on investment.
- Decisions made at the higher levels of the design are often more significant than at the lower levels.
- Designers should pinpoint and concentrate on sensitive components for which small changes yield big payoffs.

© 2005 -- Don Bouldin

17

## THE ORIGINAL AND PRESENT USES OF VHDL

- VHDL = VHSIC HDL = Very High-Speed Integrated Circuit Hardware Description Language
- In 1981 VHDL was developed by the US Dept. of Defense to standardize documentation for maintenance or possible redesign.
- In 1987 IEEE approved a VHDL standard.
- Since then, CAE companies have been using VHDL with enhancements for synthesis.
- In 1992, a new IEEE standard with many of these synthesis enhancements was approved.

© 2005 -- Don Bouldin

18

## VERILOG

- VERILOG is a hardware description language originally developed by Gateway Automation (Cadence) for verification of logic.
- Cadence and other CAE companies have been using Verilog with enhancements for synthesis.
- Most users say Verilog is easier to learn than VHDL.
- VERILOG is no longer proprietary.

© 2005 -- Don Bouldin

19

## TRUTH TABLE OR EQUATIONS USING VHDL

Row number	x <sub>1</sub>	x <sub>2</sub>	x <sub>3</sub>	f
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

The function  $f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6)$

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY func3 IS
    PORT ( x1, x2, x3 : IN      STD_LOGIC ;
          f : OUT   STD_LOGIC ) ;
END func3 ;
ARCHITECTURE LogicFunc OF func3 IS
    BEGIN
        f <= (NOT x1 AND NOT x2 AND NOT x3) OR
              (NOT x1 AND x2 AND NOT x3) OR
              (x1 AND NOT x2 AND NOT x3) OR
              (x1 AND x2 AND NOT x3) ;
    END LogicFunc ;
    
```

© 2005 -- Don Bouldin

20

## IEEE STD\_LOGIC\_1164 PACKAGE

```

library IEEE; use IEEE.std_logic_1164.all; -- to use the IEEE package
package Part_STD_LOGIC_1164 is
    type STD_ULOGIC is ('U', -- Uninitialized
                        'X', -- Forcing Unknown
                        '0', -- Forcing 0
                        '1', -- Forcing 1
                        'Z', -- High Impedance
                        'W', -- Weak Unknown
                        'L', -- Weak 0
                        'H', -- Weak 1
                        '-- Don't Care);
    type STD_ULOGIC_VECTOR is array (NATURAL range <>) of STD_ULOGIC;
    function resolved (s : STD_ULOGIC_VECTOR) return STD_ULOGIC;
    type STD_LOGIC is resolved STD_ULOGIC;
    type STD_LOGIC_VECTOR is array (NATURAL range <>) of STD_LOGIC;
    subtype X01 is resolved STD_ULOGIC range 'X' to '1';
    subtype X01Z is resolved STD_ULOGIC range 'X' to 'Z';
    subtype UX01 is resolved STD_ULOGIC range 'U' to '1';
    subtype UX01Z is resolved STD_ULOGIC range 'U' to 'Z';
    
```

```

-- Vectorized overloaded logical operators:
function "and" (L : STD_ULOGIC; R : STD_ULOGIC) return STD_ULOGIC;
-- Logical operators not_and, named, or, nor, xor, xnor (VHDL-93),
-- overloaded for STD_ULOGIC STD_ULOGIC_VECTOR
STD_ULOGIC_VECTOR;
-- Strength strippers and type conversion functions:
-- function To_T (K : T) return T;
-- defined for types, T and F, where
-- F=BIT_VECTOR STD_ULOGIC STD_ULOGIC_VECTOR
STD_ULOGIC_VECTOR;
-- Exclude _s in T in name: TO_STDULOGIC not TO STD_ULOGIC
-- To_X01 : L->0, H->1 others->X
-- To_X01Z : Z->Z, others as To_X01
-- To_UX01 : U->U, others as To_X01
-- Edge detection functions:
function rising_edge (signal s : STD_ULOGIC) return BOOLEAN;
function falling_edge (signal s : STD_ULOGIC) return BOOLEAN;
-- Unknown detection (returns true if s = U, X, Z, W);
-- function Is_X (s : T) return BOOLEAN;
-- defined for T = STD_ULOGIC STD_ULOGIC_VECTOR
STD_ULOGIC_VECTOR;
end Part_STD_LOGIC_1164;
    
```

Page 401  
ASCS by M. Smith  
© 1997 A-W-L, Inc.  
Used by permission.


© 2005 -- Don Bouldin

21
 
## MUX USING IF-THEN-ELSE IN VHDL

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY mux2to1 IS
    PORT (w0, w1, s : IN      STD_LOGIC ;
          f : OUT   STD_LOGIC ) ;
END mux2to1 ;
ARCHITECTURE Behavior OF mux2to1 IS
    BEGIN
        PROCESS (w0, w1, s)
        BEGIN
            IF s = '0' THEN
                f <= w0 ;
            ELSE
                f <= w1 ;
            END IF ;
        END PROCESS ;
    END Behavior ;
    
```




© 2005 -- Don Bouldin

22
 
## DEC2TO4 USING CASE IN VHDL

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY dec2to4 IS
    PORT
        (w : IN      STD_LOGIC_VECTOR(1 DOWNTO 0);
         En : IN    STD_LOGIC;
         y : OUT    STD_LOGIC_VECTOR(0 TO 3) );
END dec2to4 ;
ARCHITECTURE Behavior OF dec2to4 IS
    BEGIN
        PROCESS (w, En)
        BEGIN
            IF En = '1' THEN
                CASE w IS
                    WHEN "00" => y <= "1000" ;
                    WHEN "01" => y <= "0100" ;
                    WHEN "10" => y <= "0010" ;
                    WHEN OTHERS => y <= "0001" ;
                END CASE ;
            ELSE
                y <= "0000" ;
            END IF ;
        END PROCESS ;
    END Behavior ;
    
```




© 2005 -- Don Bouldin

23
 
## BCD-TO-7SEG CONVERTER USING VHDL

```

ARCHITECTURE Behavior OF seg7 IS
    BEGIN
        PROCESS (bcd)
        BEGIN
            CASE bcd IS
                WHEN "0000" => leds <= "1111110" ;
                WHEN "0001" => leds <= "0110000" ;
                WHEN "0010" => leds <= "1101101" ;
                WHEN "0011" => leds <= "1111001" ;
                WHEN "0100" => leds <= "0110011" ;
                WHEN "0101" => leds <= "1011011" ;
                WHEN "0110" => leds <= "1011111" ;
                WHEN "0111" => leds <= "1110000" ;
                WHEN "1000" => leds <= "1111111" ;
                WHEN "1001" => leds <= "1110011" ;
                WHEN OTHERS => leds <= "-----" ;
            END CASE ;
        END PROCESS ;
    END Behavior ;
    
```



w <sub>3</sub>	w <sub>2</sub>	w <sub>1</sub>	w <sub>0</sub>	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	1	0	1	1	1	0	0
0	0	1	0	1	1	0	0	0	0	1
0	0	1	1	1	1	0	0	0	1	1
0	1	0	0	1	1	0	0	1	1	1
0	1	0	1	1	0	1	0	1	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	1
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	1	1	0
1	0	1	0	1	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1	1	0

(c) Truth table

© 2005 -- Don Bouldin

24

## BINARY UP-COUNTER USING VHDL

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY upcount IS
PORT ( Clock, Resetn, E : IN STD_LOGIC ;
      Q : OUT STD_LOGIC_VECTOR (3 DOWNTO 0) );
END upcount ;

ARCHITECTURE Behavior OF upcount IS
SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNTO 0) ;
BEGIN
PROCESS ( Clock, Resetn )
BEGIN
IF Resetn = '0' THEN
Count <= "0000" ;
ELSIF (Clock'EVENT AND Clock = '1') THEN
IF E = '1' THEN
Count <= Count + 1 ;
ELSE
Count <= Count ;
END IF ;
END IF ;
END PROCESS ;
Q <= Count ;
END Behavior ;
    
```

© 2005 -- Don Bouldin 25

## TWO-DIGIT BCD COUNTER

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY BCDcount IS
PORT ( Clock : IN STD_LOGIC ;
      Clear, E : IN STD_LOGIC ;
      BCD1, BCD0 : BUFFER STD_LOGIC_VECTOR(3 DOWNTO 0) );
END BCDcount ;

ARCHITECTURE Behavior OF BCDcount IS
BEGIN
PROCESS ( Clock )
BEGIN
IF Clock'EVENT AND Clock = '1' THEN
IF Clear = '1' THEN
BCD1 <= "0000" ; BCD0 <= "0000" ;
IF BCD1 = "1001" THEN
BCD1 <= "0000" ;
IF BCD1 = "1001" THEN
BCD1 <= "0000" ;
ELSE
BCD1 <= BCD1 + '1' ;
END IF ;
END IF ;
BCD0 <= BCD0 + '1' ;
ELSE
BCD0 <= BCD0 ;
END IF ;
END IF ;
END PROCESS ;
END Behavior ;
    
```

© 2005 -- Don Bouldin 26

## STATE DIAGRAM AND STATE TABLE WITH BINARY ASSIGNMENT

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

Present state	Next state		Output z	
	y2y1	y2y1		y2y1
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

© 2005 -- Don Bouldin 27

## LOGIC MINIMIZATION USING K-MAPS

$$Y1 = w Y1' Y2'$$

$$Y2 = w Y1 \text{ OR } w Y2 = w (Y1 \text{ OR } Y2)$$

$$Z = Y2$$

© 2005 -- Don Bouldin 28

## LOGIC EQUATIONS AND SCHEMATIC

$$Y2 = w (Y1 \text{ OR } Y2)$$


$$Y1 = w Y1' Y2'$$

© 2005 -- Don Bouldin 29

## STATE DIAGRAM AND FINAL SCHEMATIC

© 2005 -- Don Bouldin 30

## STATE DIAGRAM USING VHDL (part 1)

 


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY simple IS
PORT (Clock, Resetn, w : IN
STD_LOGIC;
z : OUTSTD_LOGIC ) ;
END simple ;


ARCHITECTURE Behavior OF simple IS
TYPE State_type IS (A, B, C) ;
SIGNAL y_present, y_next : State_type ;
```

## STATE DIAGRAM USING VHDL (part 2)

 

```
BEGIN
PROCESS ( w, y_present )
BEGIN
CASE y_present IS
WHEN A =>
IF w = '0' THEN y_next <= A ;
ELSE y_next <= B ;
END IF ;
WHEN B =>
IF w = '0' THEN y_next <= A ;
ELSE y_next <= C ;
END IF ;
WHEN C =>
IF w = '0' THEN y_next <= A ;
ELSE y_next <= C ;
END IF ;
END CASE ;
END PROCESS ;
END Behavior ;
```


## STATE DIAGRAM USING VHDL (part 3)

 

```
PROCESS (Clock, Resetn)
BEGIN
IF Resetn = '0' THEN
y_present <= A ;
ELSIF (Clock'EVENT AND Clock = '1') THEN
y_present <= y_next ;
END IF ;
END PROCESS ;

z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;
```

## STATE DIAGRAM USING ONE VHDL PROCESS

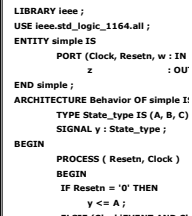


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY simple IS
PORT (Clock, Resetn, w : IN
: OUT
z : OUT) ;
END simple ;

ARCHITECTURE Behavior OF simple IS
TYPE State_type IS (A, B, C) ;
SIGNAL y : State_type ;
BEGIN
PROCESS ( Resetn, Clock )
BEGIN
IF Resetn = '0' THEN
y <= A ;
ELSIF (Clock'EVENT AND Clock = '1') THEN
END IF ;
END PROCESS ;
z <= '1' WHEN y = C ELSE '0' ;
END Behavior ;
```


## GRAPHICS CAN SPECIFY STRUCTURE

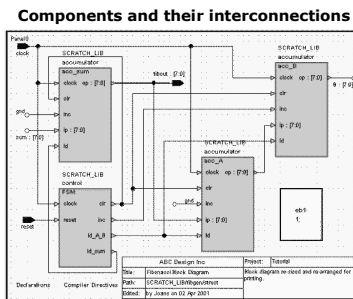
 
## VHDL CAN SPECIFY STRUCTURE (part 1)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY adder IS
PORT ( Cin : IN STD_LOGIC ;
X, Y : IN STD_LOGIC_VECTOR(3 DOWNTO 0) ;
S : OUT STD_LOGIC_VECTOR(3 DOWNTO 0) ;
Cout : OUT STD_LOGIC ) ;
END adder ;
```




## VHDL CAN SPECIFY STRUCTURE (part 2)

```

ARCHITECTURE Structure OF adder IS
  SIGNAL C : STD_LOGIC_VECTOR(1 TO 3);
  COMPONENT fulladd
  PORT ( Cin, x, y : IN  STD_LOGIC;
        s, Cout  : OUT  STD_LOGIC);
  END COMPONENT;
BEGIN
  stage0: fulladd PORT MAP ( Cin , X(0), Y(0), S(0), C(1) );
  stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) );
  stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) );
  stage3: fulladd PORT MAP (
    x => X(3), y => Y(3), Cin => C(3), s => S(3), Cout => Cout );
END Structure;

```

 


## VHDL CAN SPECIFY STRUCTURE (part 3)

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY fulladd IS
  PORT ( Cin, x, y : IN  STD_LOGIC;
        s, Cout  : OUT  STD_LOGIC );
END fulladd;
ARCHITECTURE LogicFunc OF fulladd IS
BEGIN
  s <= x XOR y XOR Cin;
  Cout <= (x AND y) OR (x AND Cin) OR (y AND Cin);
END LogicFunc;

```

 

## USE HDL AND GRAPHICS WISELY

- **Use HDL:**
  - Most straightforward transcription of control (if-then).
  - Can be technology-independent.
  - Can be optimized and retargeted by synthesis.
  - Can be used to describe structure if needed.
- **Use Graphics:**
  - Most straightforward transcription of structure/flow.
  - Best for visualization and even animation.
  - May be slower to enter/modify.
  - May be more difficult to manage large designs.
- **Capture design using either and then convert to the other.**