 


DESIGNING FPGAS & ASICS

Simulation and Testing

Prof. Don Bouldin, Ph.D.




Electrical & Computer Engineering

University of Tennessee

TEL: (865)-974-5444

FAX: (865)-974-5483

dbouldin@tennessee.edu

 A timing diagram showing multiple digital signals over time. The signals are represented by horizontal lines that are either high (black) or low (white). The diagram is organized into columns and rows, with a vertical axis on the left labeled 'Time' and a horizontal axis at the top labeled 'Signal Name'.

COURSE OUTLINE

- Overview of FPGAs and ASICs
- Using Synthesis
- HDL Examples
- Simulation and Testing
- Physical Place and Route
- Testing ASICs
- Component Reuse

SEMI-CUSTOM DESIGN FLOW OF DIGITAL FPGAS/ASICS

1—HDL

CASE w IS


```
WHEN "00" => y <= "1000" ;  
WHEN "01" => y <= "0100" ;  
WHEN "10" => y <= "0010" ;  
WHEN OTHERS => y <= "0001" ;  
END CASE ;
```




2--PRE-SYNTHESIS SIMULATION



3—SYNTHESIS/AUTO LAYOUT

 


4--POST-LAYOUT SIMULATION

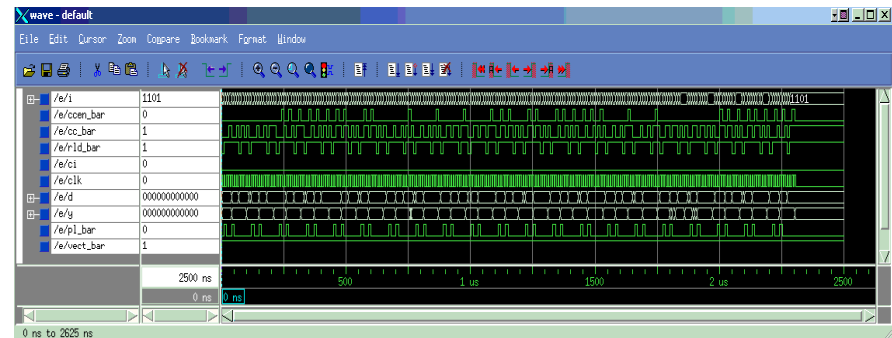


PRE-SYNTHESIS SIMULATION IS TECHNOLOGY-INDEPENDENT

Note the "zero" delay at 2450 ns:

 


POST-LAYOUT SIMULATION INCLUDES COMPONENT AND WIRING DELAYS

Note the "14ns" delay at 2464 ns:

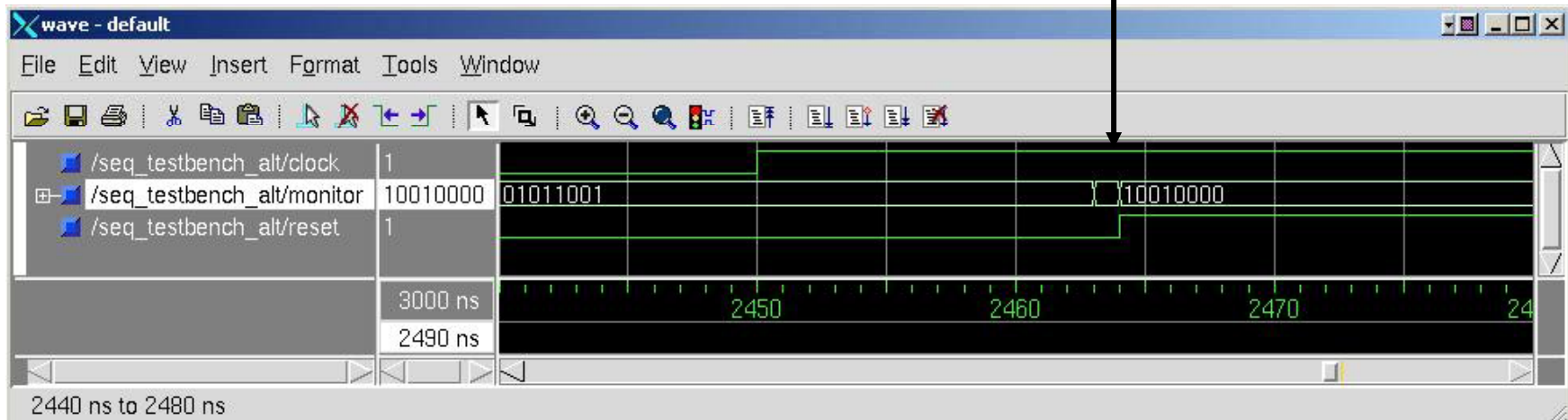


Simulation of fulladd.vhd

 - **Pre-synthesis:**
outputs change instantly at 200 ns.



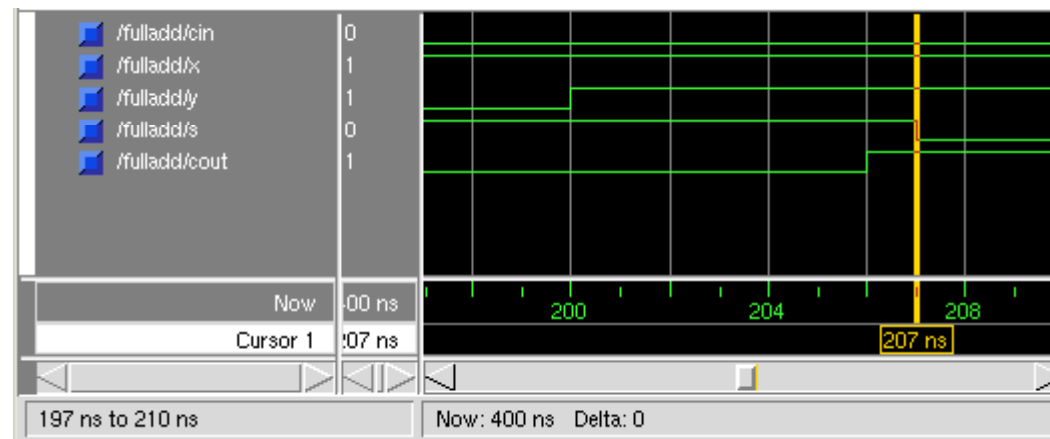
- **Post-layout:**
outputs change at 206-207 ns.



RECOMMENDED METHOD FOR LEARNING VHDL


- Copy a known working file to use as a template with reserved words and syntax. Simulate it.
- Modify the VHDL source code to perform your intended operations and then simulate the revised code.
- Be wary of examples in textbooks and on the internet since not all VHDL code is synthesizable with a particular synthesis tool and software environment.
- Avoid use of the "FOR" statement which is confusing.
- Avoid using technology-dependent statements like "WAIT until 14 ns". Instead, use "WAIT_CLOCK(16)".

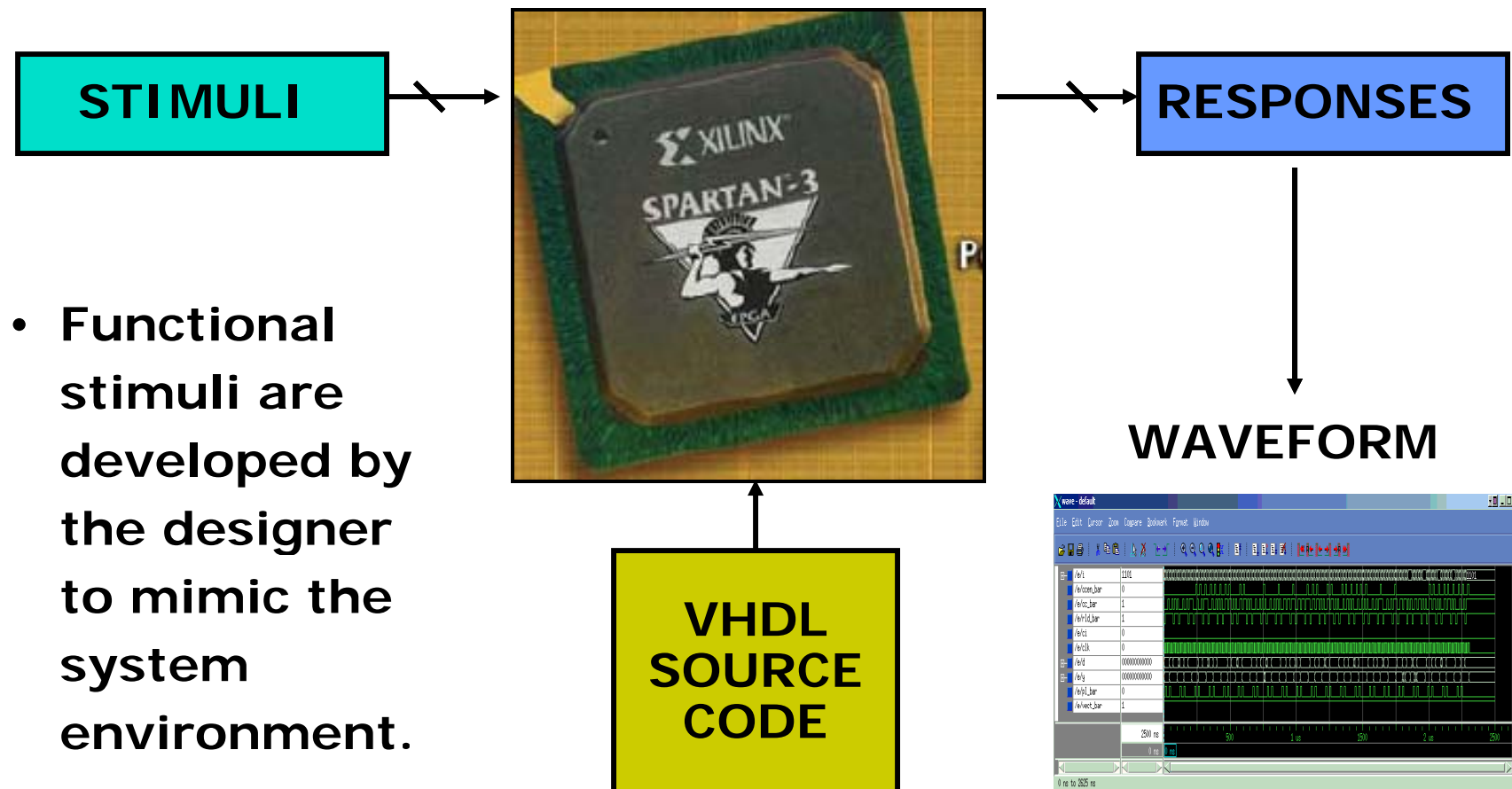SIMULATION SHOWS THE RESPONSES OF THE VHDL TO STIMULI



THE TESTBENCH CONTAINS THE STIMULI , RESPONSES AND UUT

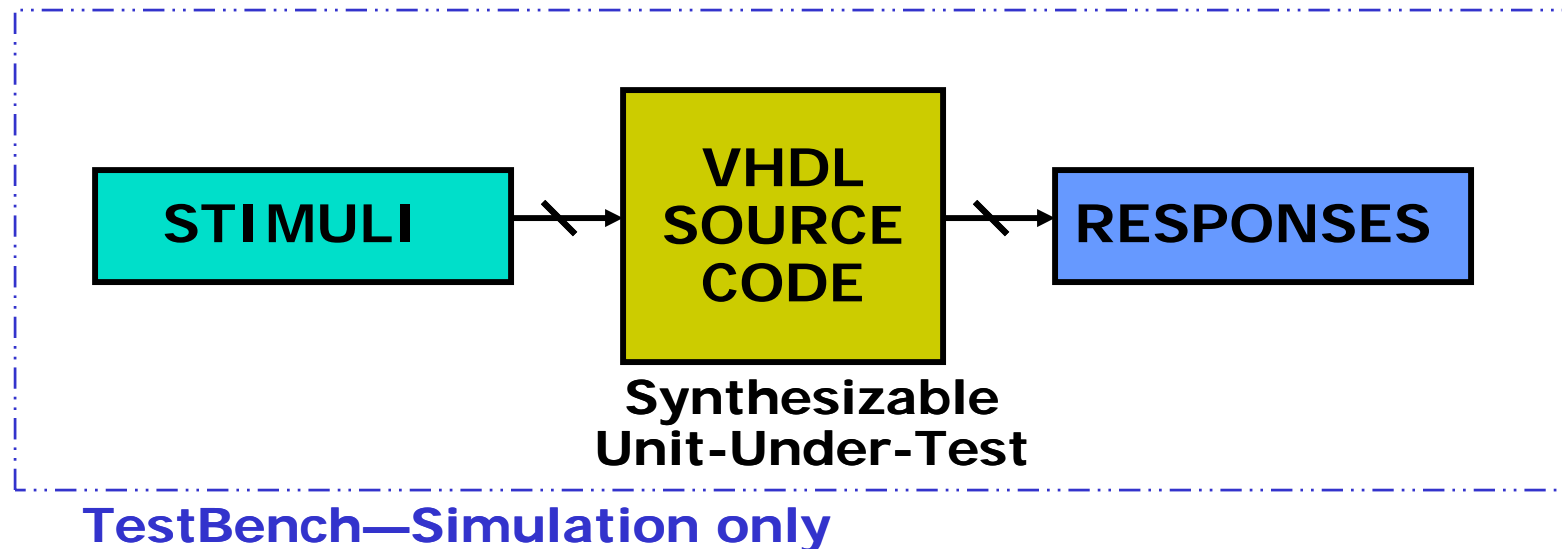- The testbench is written in VHDL but is **not** synthesized into the FPGA/ASIC.



EXPECTED RESPONSES ARE COMPARED TO ACTUAL ONES


"Failure" stops simulation while **"warning"** does not.

"Note" is used to document a correct response.



```
wait_clock(16);  
IF (left_seg = X"6")  
-- check second state of 7-segment display  
THEN  
ASSERT false  
REPORT "Output signals set correctly (7-segment second state)"  
SEVERITY note;  
ELSE  
ASSERT false  
REPORT "Output not set correctly (7-segment second state)"  
SEVERITY warning;  
END IF;
```

ALL VHDL SOURCE LINES SHOULD BE TESTED

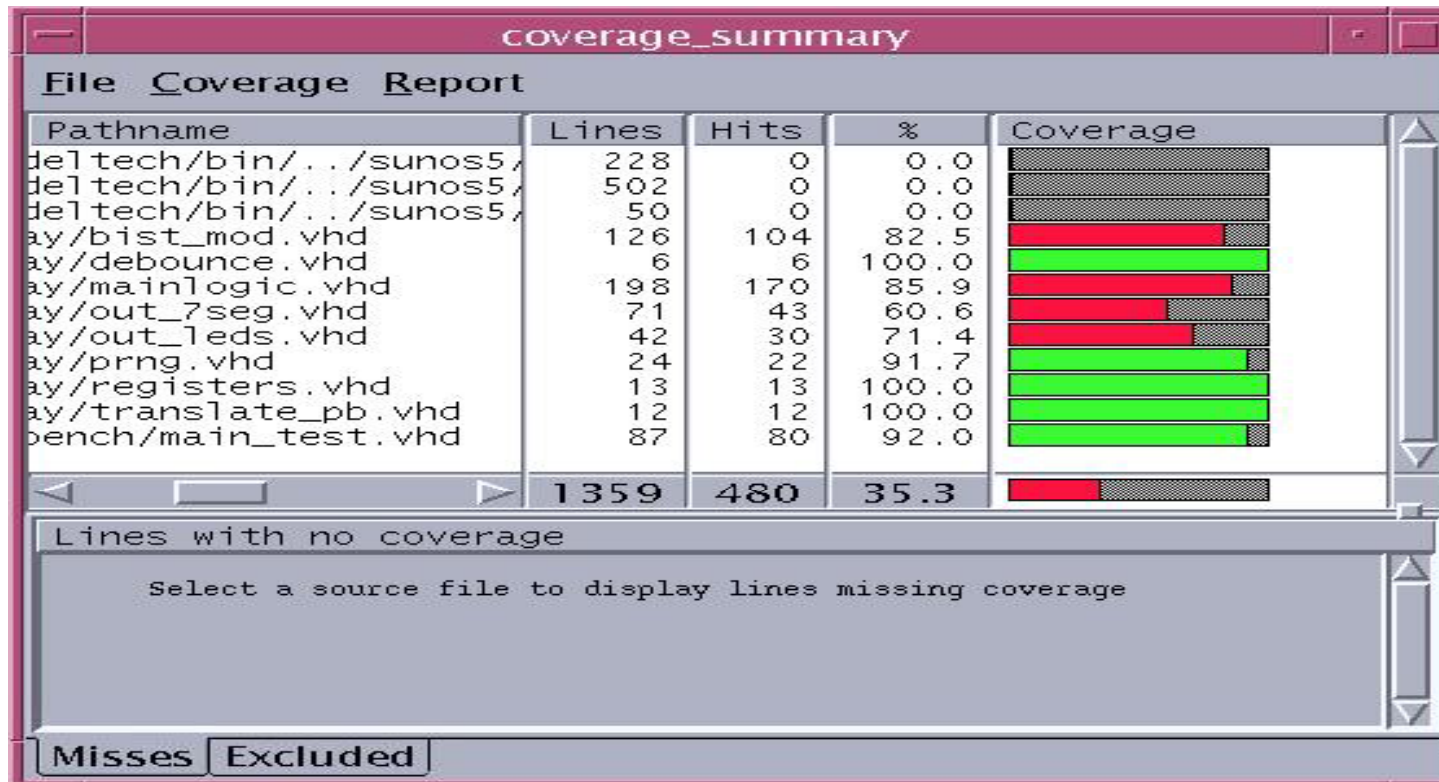The simulator can produce coverage reports.



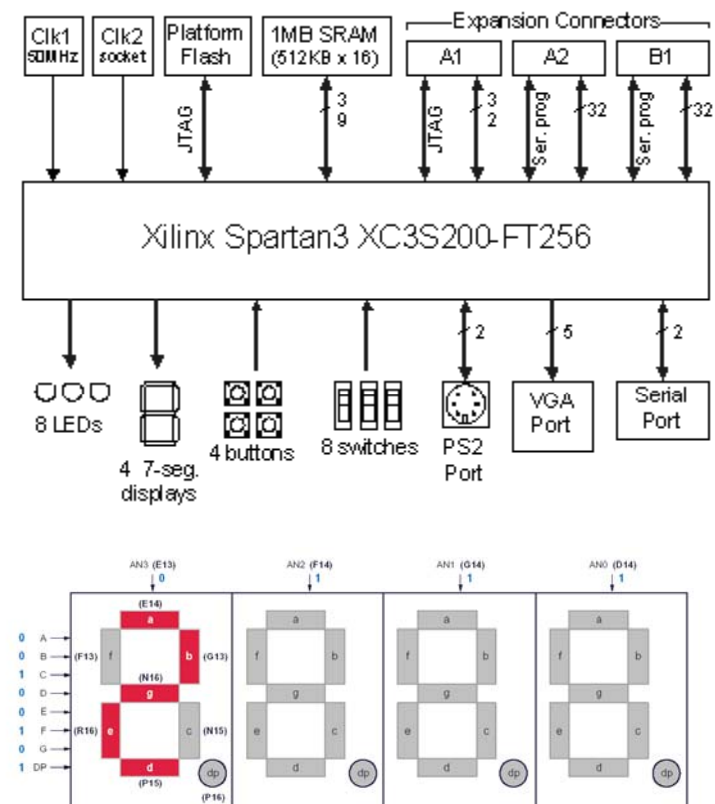 FINAL VERIFICATION IS PERFORMED USING A PROTOTYPING BOARD



Seven-Segment LED Digit Control

XILINX TOOLS ARE FREE BUT TARGET ONLY XILINX PARTS

- Anyone can download Xilinx WebPACK tools for free from www.xilinx.com

Free ISE WebPACK 7.1i



The free ISE WebPACK™ 7.1i is the most complete, easy-to-use software solution to complete a Xilinx CPLD or medium-density FPGA design

ISE WebPACK is the ideal downloadable desktop solution offering free software modules from ABEL and HDL synthesis to device fitting and JTAG programming. ISE WebPACK is a subset of our award winning ISE Foundation™ design tools providing instant access to the ISE tools at no cost. Xilinx has created a solution that allows convenient productivity by providing a design solution that is always up to date with error-free downloading and single file installation.

> Register

> Add to Cart

- WebPACK includes a free version of ModelSim that works only for Xilinx parts but you must register at www.mentor.com

ModelSim™ Xilinx Edition-III




The ModelSim-III Family of Products

Product Name	Available From	
ModelSim XE-III Starter	Free from Xilinx	CPL sub-


IMPLEMENTING A PROJECT

- **Determine I/O Requirements**
- **Partition into 5-9 submodules and test individually before combining.**
- **Use/Enhance Built-In Self-Test**
- **Debounce Pushbutton Switches**
- **Filter an Input to Produce a Single Pulse**
- **Use hierarchy with Submodule Components**
- **Synchronize Externally Clocked Inputs**

DETERMINE SYSTEM I/O REQUIREMENTS

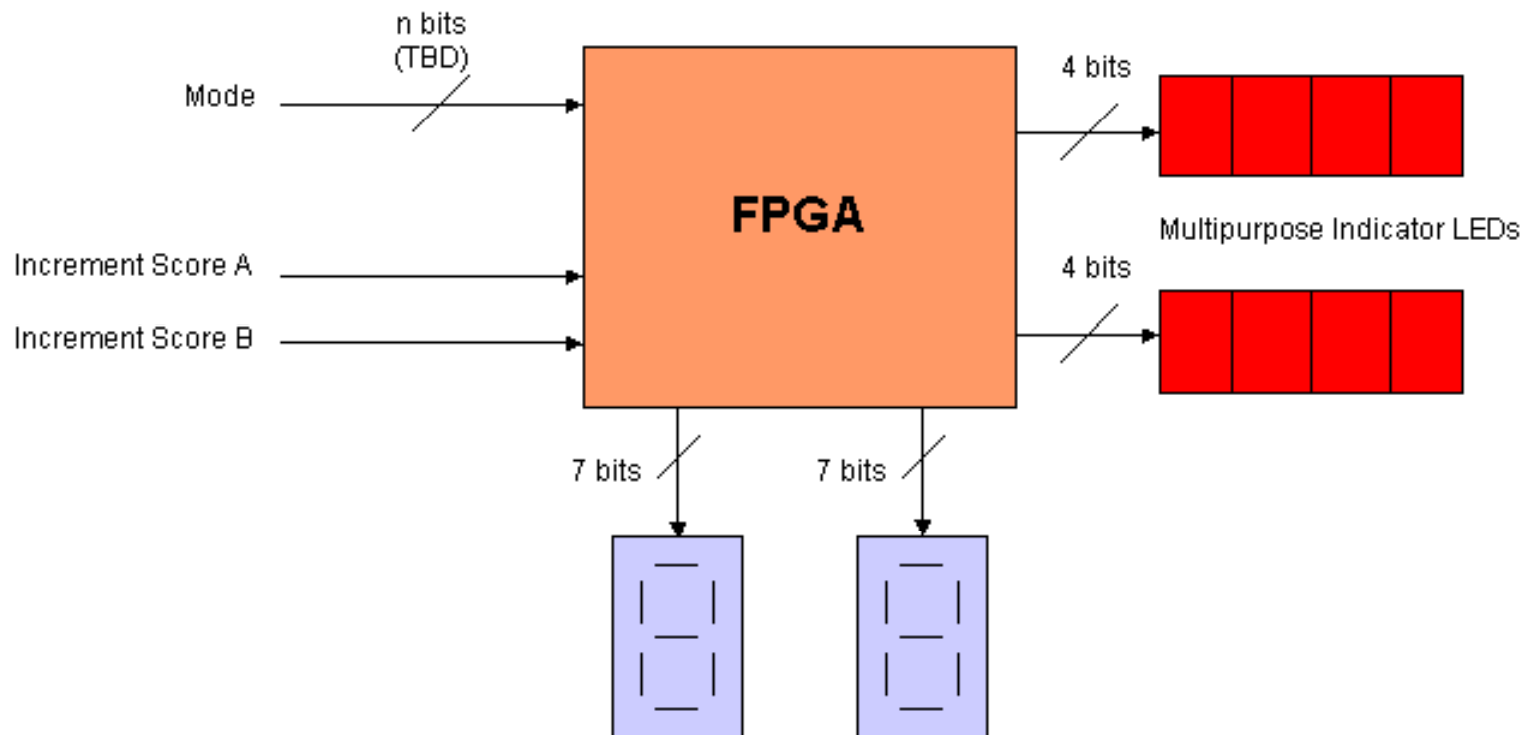


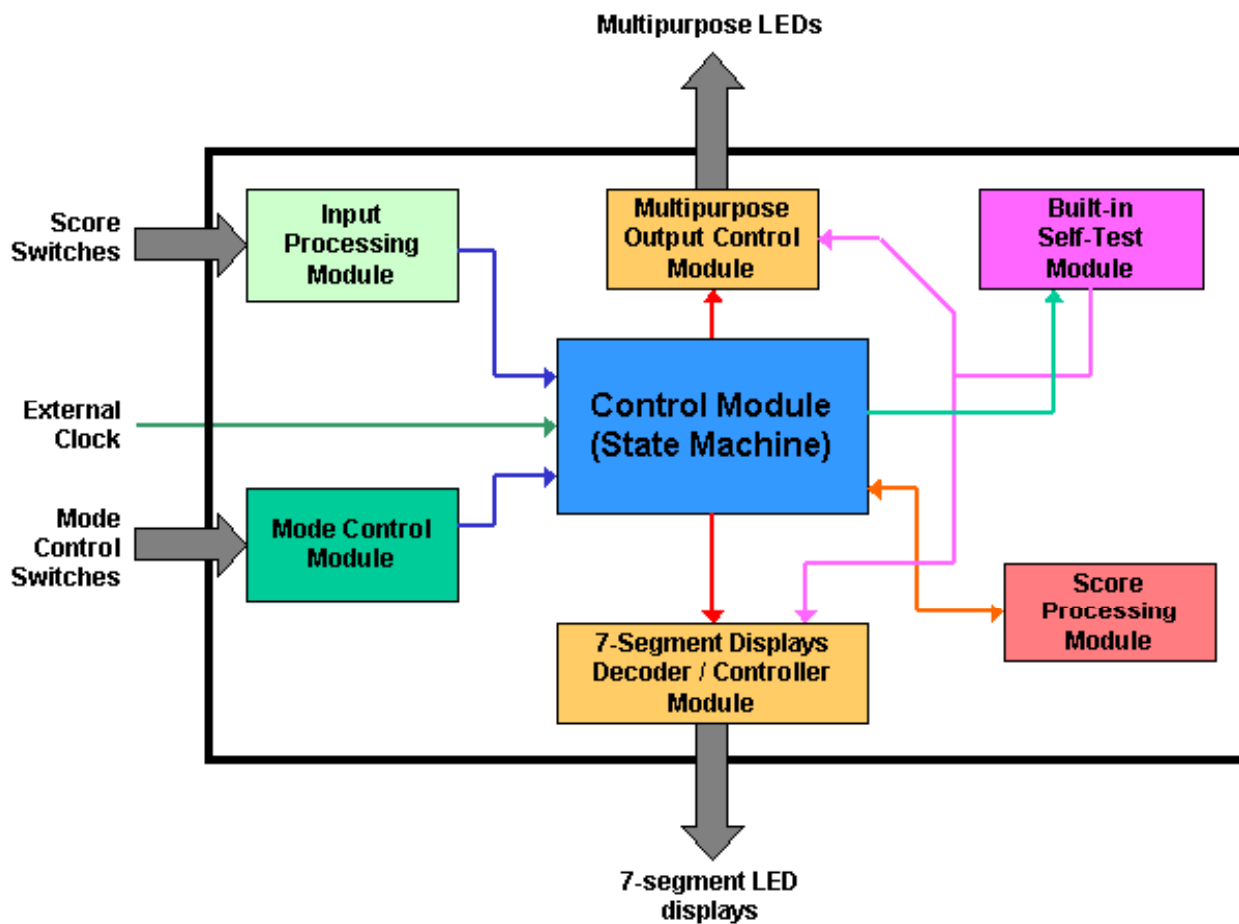DECOMPOSE EACH LEVEL INTO 7+/-2 SUBMODULES




SIMULATE EACH SUBMODULE AND THEN INTEGRATE THEM

Submodule#1

 

Submodule#2

 


Composite of #1 and #2



BUILT-IN SELF-TEST

 - Downloading hw3a (BIST) ensures the integrity of the connection between the CPU and the Spartan3 prototyping board AND then checks the input switches and the 7-segment displays.
- More thorough checks could be added to ensure the integrity of the board I/O for a specific project.




INTERNAL FREQUENCIES CAN BE DERIVED FROM THE EXTERNAL CLOCK

- A crystal oscillator on the Spartan3 prototyping board produces a 50 MHz clock.
- Counters can be used to divide down a frequency into a slower synchronized one:

<u>Divide By</u>	<u>Frequency</u>	<u>Duration</u>
1	clock_50MHz	20 ns
2	clock_25 MHz	40 ns
25	clock_1MHz	1000 ns = 1us
10	clock_100KHz	10 us
10	clock_10KHz	100 us
10	clock_1KHz	1000 us = 1 ms
10	clock_100Hz	10 ms
10	clock_10Hz	100 ms
10	clock_1Hz	1000 ms = 1 s
10	clock_tenthHz	10 s

Simulation of clk_div.vhd (part 1)

- 50 MHz divided by 2 → 25 MHz:

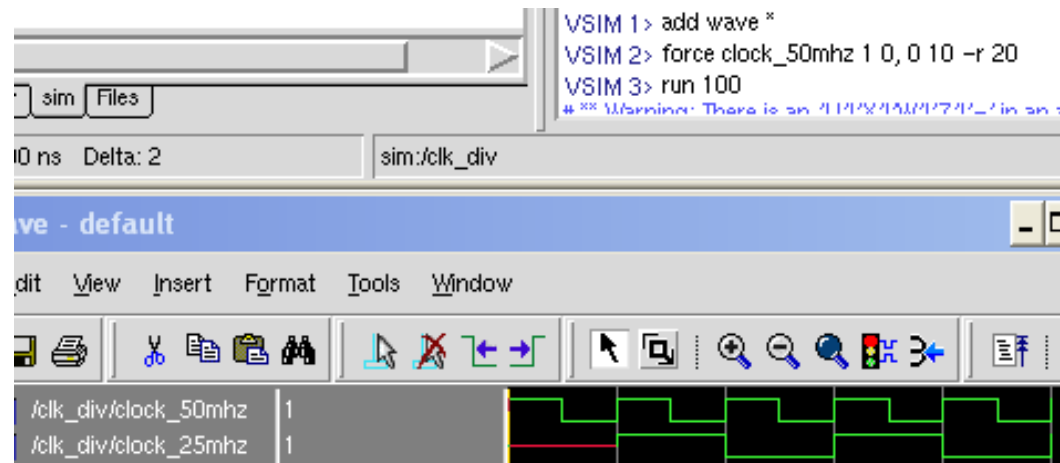


- 25 MHz divided by 25 → 1 MHz:



Simulation of clk_div.vhd (part 2)

- 10 KHz divided by 10 → 1 KHz:

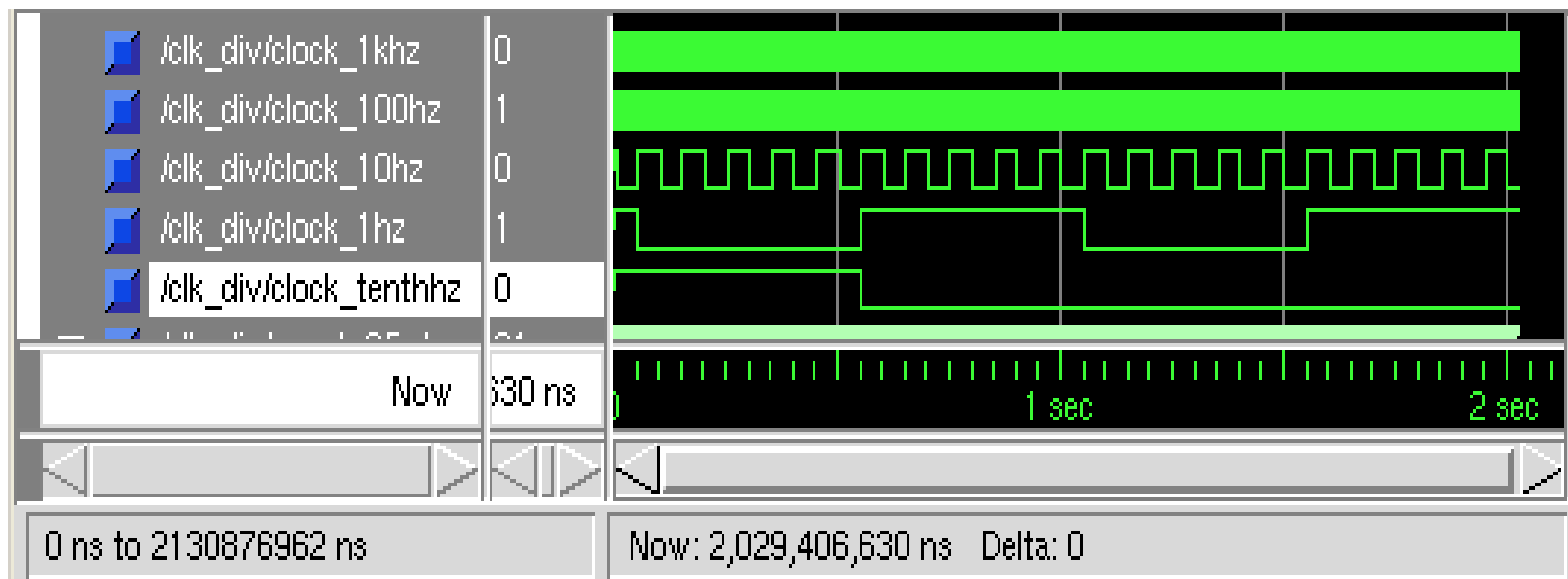

clk_div.vhd (part 1)

```
ln # sim:/clk_div : clk_div.vhd
1 -- original from Jim Hamblen at Georgia Tech
2 -- revised on 9/15/05 by Don Bouldin for 50MHz and TenthHz
3 LIBRARY IEEE;
4 USE IEEE.STD_LOGIC_1164.all;
5 USE IEEE.STD_LOGIC_ARITH.all;
6 USE IEEE.STD_LOGIC_UNSIGNED.all;
7
8 ENTITY clk_div IS
9
10     PORT
11     (
12         clock_50mhz          : IN    STD_LOGIC;
13         clock_25mhz          : OUT   STD_LOGIC;
14         clock_1mhz           : OUT   STD_LOGIC;
15         clock_100KHz         : OUT   STD_LOGIC;
16         clock_10KHz          : OUT   STD_LOGIC;
17         clock_1KHz           : OUT   STD_LOGIC;
18         clock_100Hz          : OUT   STD_LOGIC;
19         clock_10Hz           : OUT   STD_LOGIC;
20         clock_1Hz            : OUT   STD_LOGIC;
21         clock_tenthHz        : OUT   STD_LOGIC);
22
23 END clk_div;
24
25 ARCHITECTURE a OF clk_div IS
26
27     SIGNAL count_25mhz: STD_LOGIC_VECTOR(1 DOWNTO 0);
28     SIGNAL count_1mhz: STD_LOGIC_VECTOR(4 DOWNTO 0);
29     SIGNAL count_100khz, count_10khz, count_1khz: STD_LOGIC_VECTOR(3 DOWNTO 0);
30     SIGNAL count_100hz, count_10hz, count_1hz, count_tenthhz : STD_LOGIC_VECTOR(3 DOWNTO 0);
31     SIGNAL clock_25mhz_int, clock_1mhz_int, clock_100KHz_int, clock_10KHz_int, clock_1KHz_int: STD_LOGIC;
32     SIGNAL clock_100hz_int, clock_10Hz_int, clock_1Hz_int, clock_tenthHz_int : STD_LOGIC;
33 BEGIN
```

clk_div.vhd (part 2)

```

In #          sim:/clk_div : clk_div.vhd
33 BEGIN
34     PROCESS
35     BEGIN
36     -- Divide by 2
37     WAIT UNTIL clock_50Mhz'EVENT and clock_50Mhz = '1';
38     IF count_25Mhz < 1 THEN
39         count_25Mhz <= count_25Mhz + 1;
40     ELSE
41         count_25Mhz <= "00";
42     END IF;
43     IF count_25Mhz < 1 THEN
44         clock_25Mhz_int <= '0';
45     ELSE
46         clock_25Mhz_int <= '1';
47     END IF;
48
49     -- Ripple clocks are used in this code to save prescaler hardware
50     -- Sync all clock prescaler outputs back to master clock signal
51     clock_25Mhz <= clock_25Mhz_int;
52     clock_1Mhz <= clock_1Mhz_int;
53     clock_100Khz <= clock_100Khz_int;
54     clock_10Khz <= clock_10Khz_int;
55     clock_1Khz <= clock_1Khz_int;
56     clock_100hz <= clock_100hz_int;
57     clock_10hz <= clock_10hz_int;
58     clock_1hz <= clock_1hz_int;
59     clock_tenthhz <= clock_tenthhz_int;
60     END PROCESS;
61

```

clk_div.vhd (part 3)

```
ln #      sim:/clk_div : clk_div.vhd
61
62     PROCESS
63     BEGIN
64     -- Divide by 25
65     WAIT UNTIL clock_25mhz_int'EVENT and clock_25mhz_int = '1';
66     IF count_1mhz < 24 THEN
67     count_1mhz <= count_1mhz + 1;
68     ELSE
69     count_1mhz <= "00000";
70     END IF;
71     IF count_1mhz < 12 THEN
72     clock_1mhz_int <= '0';
73     ELSE
74     clock_1mhz_int <= '1';
75     END IF;
76     END PROCESS;
77
78     PROCESS
79     BEGIN
80     -- Divide by 10
81     WAIT UNTIL clock_1mhz_int'EVENT and clock_1mhz_int = '1';
82     IF count_100khz < 9 THEN
83     count_100khz <= count_100khz + 1;
84     ELSE
85     count_100khz <= "0000";
86     END IF;
87     IF count_100khz < 5 THEN
88     clock_100khz_int <= '0';
89     ELSE
90     clock_100khz_int <= '1';
91     END IF;
92
93     END PROCESS;
94
```


clk_div.vhd (part 4)

```
ln # | sim:/clk_div : clk_div.vhd
94
95
96     PROCESS
97     BEGIN
98     -- Divide by 10
99         WAIT UNTIL clock_100Khz_int'EVENT and clock_100Khz_int = '1';
100         IF count_10khz < 9 THEN
101             count_10khz <= count_10khz + 1;
102         ELSE
103             count_10khz <= "0000";
104         END IF;
105         IF count_10khz < 5 THEN
106             clock_10khz_int <= '0';
107         ELSE
108             clock_10khz_int <= '1';
109         END IF;
110
111     END PROCESS;
112
113
114     PROCESS
115     BEGIN
116     -- Divide by 10
117         WAIT UNTIL clock_10Khz_int'EVENT and clock_10Khz_int = '1';
118         IF count_1khz < 9 THEN
119             count_1khz <= count_1khz + 1;
120         ELSE
121             count_1khz <= "0000";
122         END IF;
123         IF count_1khz < 5 THEN
124             clock_1khz_int <= '0';
125         ELSE
126             clock_1khz_int <= '1';
127         END IF;
128
129     END PROCESS;
130
```

clk_div.vhd (part 5)


```
ln # | sim:/clk_div : clk_div.vhd
130
131
132     PROCESS
133     BEGIN
134 -- Divide by 10
135         WAIT UNTIL clock_1Khz_int'EVENT and clock_1Khz_int = '1';
136         IF count_100hz < 9 THEN
137             count_100hz <= count_100hz + 1;
138         ELSE
139             count_100hz <= "0000";
140         END IF;
141         IF count_100hz < 5 THEN
142             clock_100hz_int <= '0';
143         ELSE
144             clock_100hz_int <= '1';
145         END IF;
146
147     END PROCESS;
148
149
150     PROCESS
151     BEGIN
152 -- Divide by 10
153         WAIT UNTIL clock_100hz_int'EVENT and clock_100hz_int = '1';
154         IF count_10hz < 9 THEN
155             count_10hz <= count_10hz + 1;
156         ELSE
157             count_10hz <= "0000";
158         END IF;
159         IF count_10hz < 5 THEN
160             clock_10hz_int <= '0';
161         ELSE
162             clock_10hz_int <= '1';
163         END IF;
164
165     END PROCESS;
166
```

clk_div.vhd (part 6)


```
ln # | sim:/clk_div : clk_div.vhd
167
168     PROCESS
169     BEGIN
170 -- Divide by 10
171         WAIT UNTIL clock_10hz_int'EVENT and clock_10hz_int = '1';
172         IF count_1hz < 9 THEN
173             count_1hz <= count_1hz + 1;
174         ELSE
175             count_1hz <= "0000";
176         END IF;
177         IF count_1hz < 5 THEN
178             clock_1hz_int <= '0';
179         ELSE
180             clock_1hz_int <= '1';
181         END IF;
182
183     END PROCESS;
184
185     PROCESS
186     BEGIN
187 -- Divide by 10
188         WAIT UNTIL clock_1hz_int'EVENT and clock_1hz_int = '1';
189         IF count_tenthhz < 9 THEN
190             count_tenthhz <= count_tenthhz + 1;
191         ELSE
192             count_tenthhz <= "0000";
193         END IF;
194         IF count_tenthhz < 5 THEN
195             clock_tenthhz_int <= '0';
196         ELSE
197             clock_tenthhz_int <= '1';
198         END IF;
199
200     END PROCESS;
201
202
203
204 END a;
```

clk_div.vhd

AN INPUT PUSHBUTTON SWITCH MAY BOUNCE

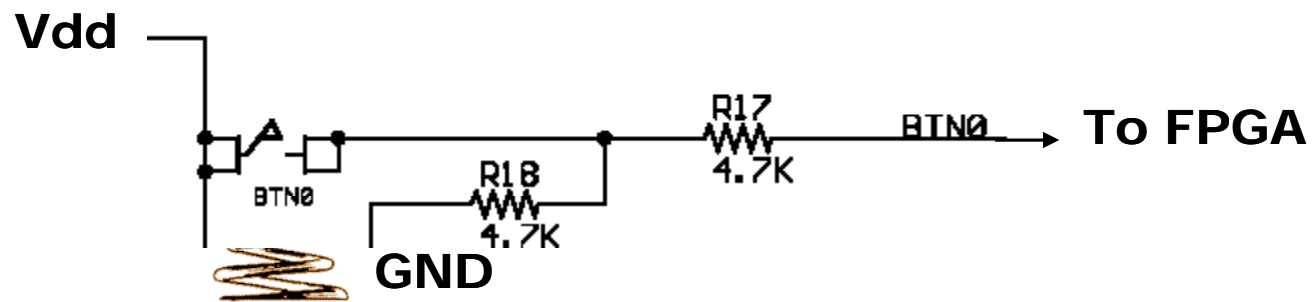

Input With Bouncing

 

Desired Output


Fig. 6.11, Page 243
ASICs by M. Smith
© 1997 A-W-L, Inc.
Used by permission.

debounce.vhd

```
ln # sim:/debounce : debounce.vhd
1 LIBRARY IEEE;
2 USE IEEE.STD_LOGIC_1164.all;
3 USE IEEE.STD_LOGIC_ARITH.all;
4 USE IEEE.STD_LOGIC_UNSIGNED.all;
5
6     -- Debounce Pushbutton: Filters out mechanical switch bounce for around 40Ms.
7 ENTITY debounce IS
8     PORT(pb, clock_100Hz : IN STD_LOGIC;
9          pb_debounced   : OUT  STD_LOGIC);
10 END debounce;
11
12 ARCHITECTURE a OF debounce IS
13     SIGNAL SHIFT_PB   : STD_LOGIC_VECTOR(3 DOWNTO 0);
14
15
16 BEGIN
17
18     -- Debounce clock should be approximately 10ms or 100Hz
19     PROCESS
20     BEGIN
21         WAIT UNTIL (clock_100Hz'EVENT) AND (clock_100Hz = '1');
22         -- Use a shift register to filter switch contact bounce
23         SHIFT_PB(2 DOWNTO 0) <= SHIFT_PB(3 DOWNTO 1);
24         SHIFT_PB(3) <= NOT PB;
25         IF SHIFT_PB(3 DOWNTO 0) = "0000" THEN
26             PB_DEBOUNCED <= '0';
27         ELSE
28             PB_DEBOUNCED <= '1';
29         END IF;
30     END PROCESS;
31 END a;
```


Simulation of debounce.vhd (part 1)

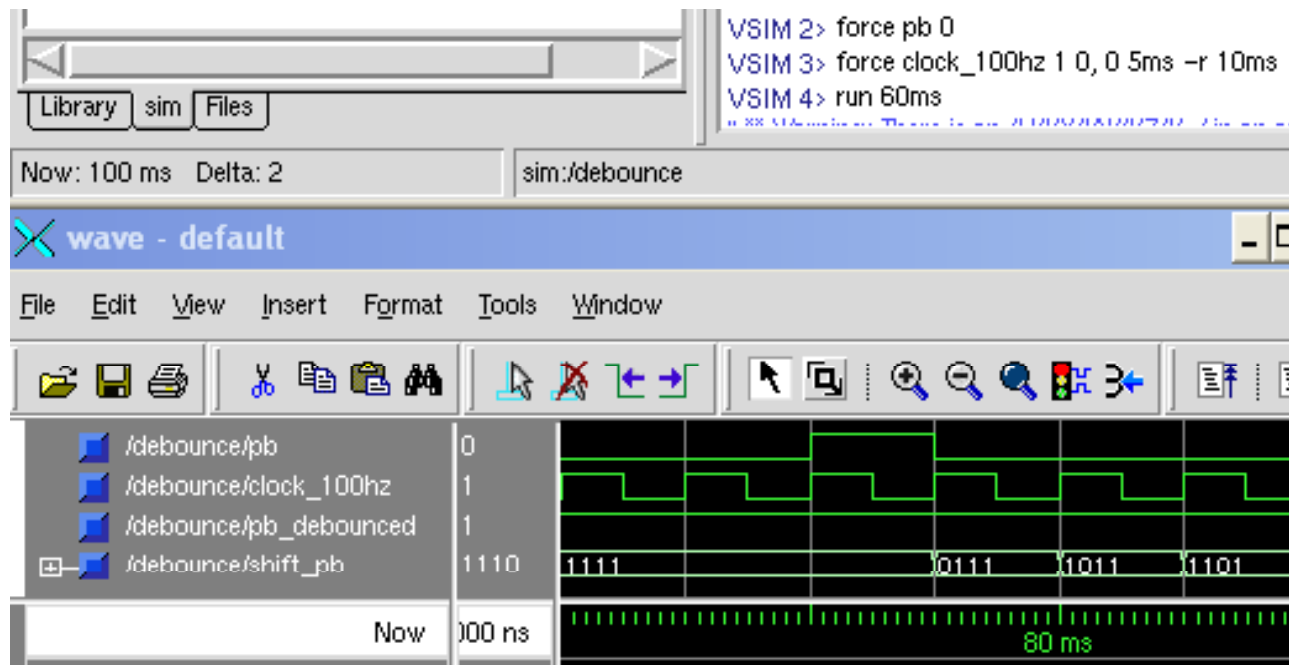- **PB has been 0 (inactive), then is 1 (active) but only for 10 ms (too short to be valid) so PB_debounced stays 1 (inactive):**




Simulation of debounce.vhd (part 2)

 - This time PB is 1 (active) for 60 ms (which is valid since it is at least 40ms) so PB_debounced becomes 0 (active):




FILTER AN INPUT TO PRODUCE A SINGLE PULSE

 **An External Pushbutton Switch
May Be Pressed For Multiple
Clock Ticks**




 **A Circuit Can Be
Implemented to Produce
Only a Single Pulse**



Simulation of onepulse.vhd

 - **PB_debounced has been 0 (active) for 100 ms but only a single 1 ms pulse is produced:**



onepulse.vhd (part 1)

```
ln #      sim:/onepulse : onepulse.vhd
1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.all;
3  USE IEEE.STD_LOGIC_ARITH.all;
4  USE IEEE.STD_LOGIC_UNSIGNED.all;
5
6  -- Single Pulse circuit
7  -- the output will go high for only one clock cycle
8
9  ENTITY onepulse IS
10
11      PORT (PB_debounced, clock_1MHz : IN STD_LOGIC;
12            PB_single_pulse   : OUT STD_LOGIC);
13
14  END onepulse;
15
16
```

onepulse.vhd (part 2)

```
16
17 ARCHITECTURE a OF onepulse IS
18     SIGNAL PB_debounced_delay, Power_on : STD_LOGIC;
19
20 BEGIN
21     PROCESS
22     BEGIN
23         WAIT UNTIL (CLOCK_1MHz'event) AND (CLOCK_1MHz='1');
24         -- Power_on will be initialized to '0' at power up
25         IF Power_on='0' THEN
26             -- This code resets the critical signals once at power up
27             PB_single_pulse    <= '0';
28             PB_debounced_delay <= '1';
29             Power_on           <= '1';
30
31         ELSE
32             -- A single clock cycle pulse is produced when the switch is hit
33             -- No matter how long the switch is held down
34             -- The switch input must already be debounced
35             IF PB_debounced = '1' AND PB_debounced_delay = '0' THEN
36                 PB_single_pulse <= '1';
37             ELSE
38                 PB_single_pulse <= '0';
39             END IF;
40
41             PB_debounced_delay <= PB_debounced;
42
43         END IF;
44     END PROCESS;
45 END PROCESS;
46
47 END a;
```

onepulse.vhd (part 1) (modified)

Original

```
ln # sim:/onepulse : onepulse.vhd
1 LIBRARY IEEE;
2 USE IEEE.STD_LOGIC_1164.all;
3 USE IEEE.STD_LOGIC_ARITH.all;
4 USE IEEE.STD_LOGIC_UNSIGNED.all;
5
6 -- single Pulse circuit
7 -- the output will go high for only one clock cycle
8
9 ENTITY onepulse IS
10
11     PORT(PB_debounced, clock_1MHz : IN STD_LOGIC;
12         PB_single_pulse : OUT STD_LOGIC);
13
14 END onepulse;
15
16
```

Modified:

```
ln # sim:/onepulse : onepulse.vhd
1 LIBRARY IEEE;
2 USE IEEE.STD_LOGIC_1164.all;
3 USE IEEE.STD_LOGIC_ARITH.all;
4 USE IEEE.STD_LOGIC_UNSIGNED.all;
5
6 -- single Pulse circuit
7 -- the output will go high for only one clock cycle
8
9 ENTITY onepulse IS
10
11     PORT(PB_debounced, reset_pb_flag, clock_1MHz : IN STD_LOGIC;
12         PB_single_pulse, pb_flag : OUT STD_LOGIC);
13
14 END onepulse;
15
16
```

onepulse.vhd (part 2) (modified)


```
--
17 ARCHITECTURE a OF onepulse IS
18     SIGNAL PB_debounced_delay, Power_on : STD_LOGIC;
19
20 BEGIN
21     PROCESS
22     BEGIN
23         WAIT UNTIL (CLOCK_1MHz'event) AND (CLOCK_1MHz='1');
24         -- Power_on will be initialized to '0' at power up
25         IF Power_on='0' THEN
26             -- This code resets the critical signals once at power up
27             PB_single_pulse  <= '0';
28             PB_flag          <= '0';
29             PB_debounced_delay <= '1';
30             Power_on         <= '1';
31
32         ELSE
33             -- A single clock cycle pulse is produced when the switch is hit
34             -- No matter how long the switch is held down
35             -- The switch input must already be debounced
36             IF PB_debounced = '1' AND PB_debounced_delay = '0' THEN
37                 PB_single_pulse <= '1';
38                 pb_flag <= '1';
39             ELSE
40                 PB_single_pulse <= '0';
41                 IF reset_pb_flag = '1' THEN pb_flag <= '0';
42                 ELSE
43                     END IF;
44             END IF;
45
46             PB_debounced_delay <= PB_debounced;
47
48         END IF;
49     END PROCESS;
50 END PROCESS;
51
52 END a;
```

Simulation of onepulse.vhd (modified)

- **PB_debounced** has been 0 (active) for 100 ms but only a single 1 ms pulse is produced and **pb_flag** is set. After being read, **pb_flag** is reset.




HIERARCHY WITH SUBMODULE COMPONENTS

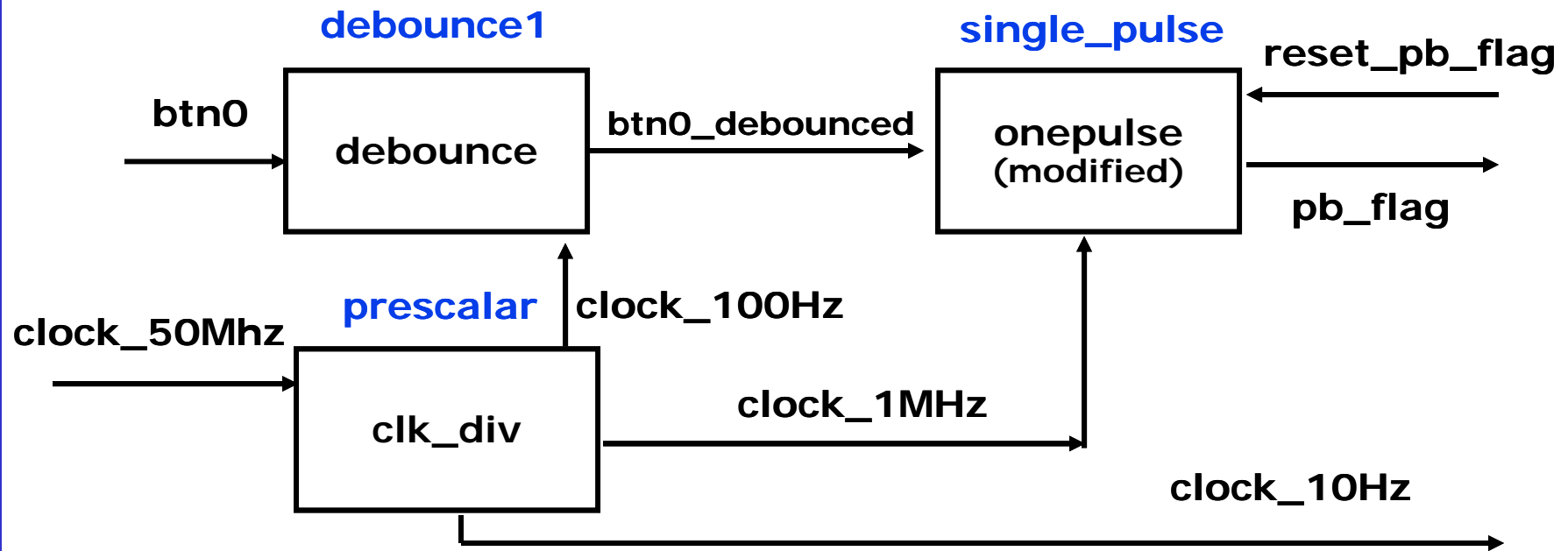

Simulation of hierarch.vhd

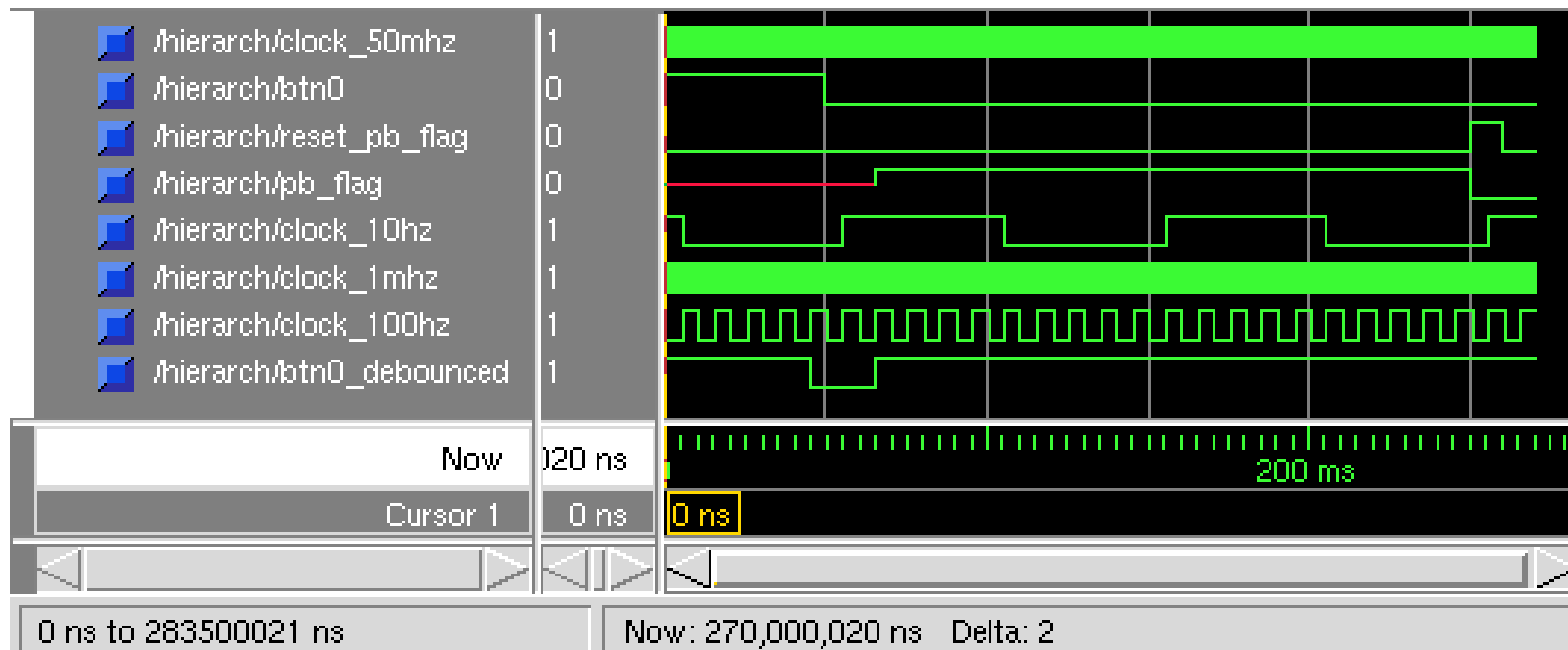- A proper pressing of btn0 sets pb_flag to HIGH.
- Once pb_flag is read, it is reset to LOW.



hierarch.vhd (part 1)

```
ln # sim:/hierarch : hierarch.vhd
1
2 LIBRARY IEEE;
3 USE IEEE.STD_LOGIC_1164.all;
4 USE IEEE.STD_LOGIC_ARITH.all;
5 USE IEEE.STD_LOGIC_UNSIGNED.all;
6
7 ENTITY hierarch IS
8     PORT (clock_50Mhz, btn0, reset_pb_flag : IN STD_LOGIC;
9           pb_flag, clock_10Hz : OUT STD_LOGIC);
10 END hierarch;
11 ARCHITECTURE a OF hierarch IS
12     -- Declare internal signals needed to connect submodules
13     SIGNAL clock_1MHz, clock_100Hz, btn0_debounced : STD_LOGIC;
14     -- Use Components to Define Submodules and Parameters
15     COMPONENT debounce
16         PORT(pb, clock_100Hz : IN STD_LOGIC;
17             pb_debounced : OUT STD_LOGIC);
18     END COMPONENT;
19
20     COMPONENT onepulse
21         PORT(PB_debounced, reset_pb_flag, clock_1MHz : IN STD_LOGIC;
22             PB_single_pulse, pb_flag : OUT STD_LOGIC);
23     END COMPONENT;
24
25     COMPONENT clk_div
26         PORT(clock_50Mhz : IN STD_LOGIC;
27             clock_25MHz : OUT STD_LOGIC;
28             clock_1MHz : OUT STD_LOGIC;
29             clock_100KHz : OUT STD_LOGIC;
30             clock_10KHz : OUT STD_LOGIC;
31             clock_1KHz : OUT STD_LOGIC;
32             clock_100Hz : OUT STD_LOGIC;
33             clock_10Hz : OUT STD_LOGIC;
34             clock_1Hz : OUT STD_LOGIC);
35     END COMPONENT;
```


hierarch.vhd (part 2)

```
-- -----  
36 BEGIN  
37  
38 -- Use Port Map to connect signals between components in the hierarchy  
39 debounced1 : debounce PORT MAP (pb => btn0, clock_100Hz => clock_100Hz,  
40                                pb_debounced => btn0_debounced);  
41  
42 prescalar : clk_div PORT MAP (clock_50MHz => clock_50MHz, clock_1MHz => clock_1MHz,  
43                                clock_100Hz => clock_100Hz, clock_10Hz => clock_10Hz);  
44  
45 single_pulse : onepulse PORT MAP (pb_debounced => btn0_debounced,  
46                                reset_pb_flag => reset_pb_flag,  
47                                pb_flag => pb_flag,  
48                                clock_1MHz => clock_1MHz);  
49  
50 END a;  
51
```

hierarch.vhd

Simulation of hw3a.vhd

- After btn0 is pressed (properly), the pb_flag is set. Then while dig “0111” is displayed , swt<7:0> are read and pb_flag is reset:

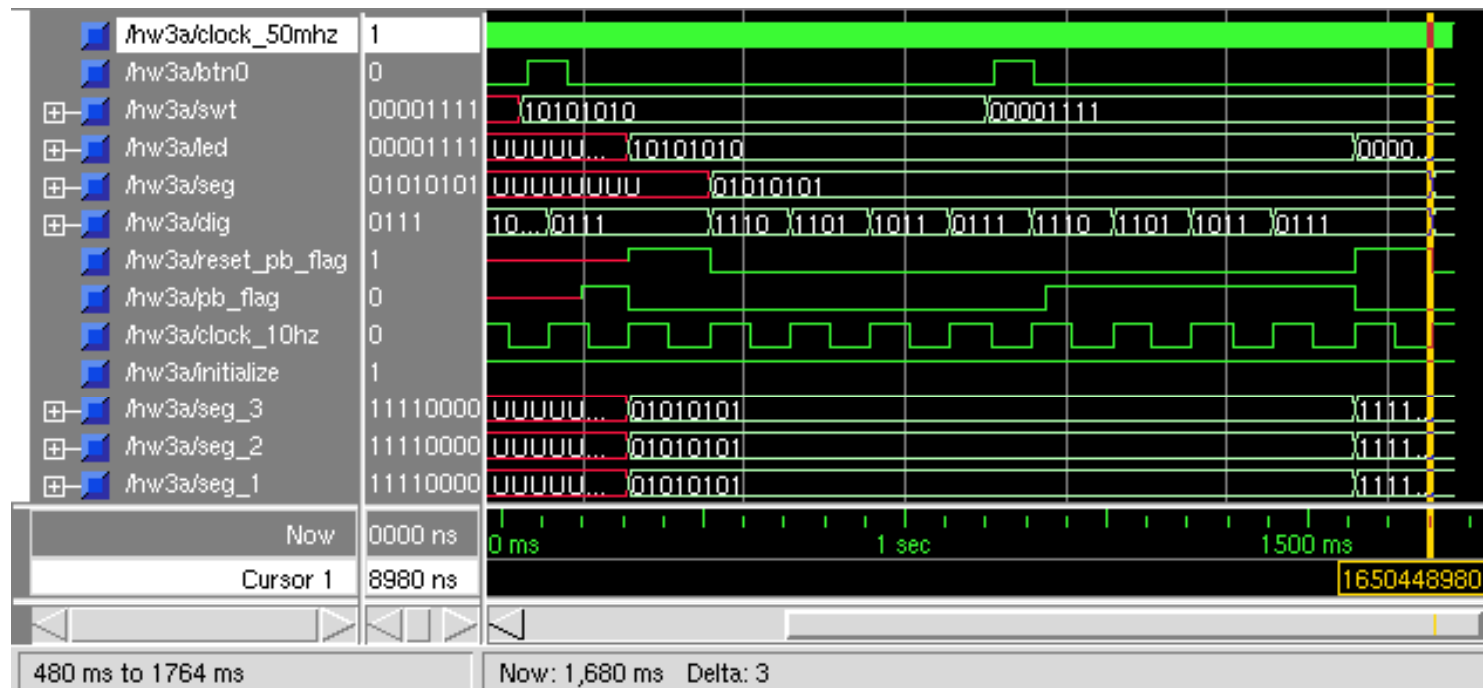

hw3a.vhd (part 1)

```
ln # | sim:hw3a : hw3a.vhd
-----|-----
1 |
2 | -- hw3a.vhd -- Demonstrate basic functions
3 | -----|-----
4 | -- Author: Don Bouldin, Univ. of Tennessee, 9/19/05
5 | -----|-----
6 | -- This module tests basic functions and I/O on the Spartan3 board.
7 | -----|-----
8 |
9 | library IEEE;
10 | use IEEE.STD_LOGIC_1164.ALL;
11 | use IEEE.STD_LOGIC_ARITH.ALL;
12 | use IEEE.STD_LOGIC_UNSIGNED.ALL;
13 |
14 | entity hw3a is
15 | Port (
16 | clock_50MHz : in std_logic;
17 |
18 | btn0: in std_logic;
19 |
20 |
21 | swt : in std_logic_vector(7 downto 0);
22 | -- swt(7) = most significant sliding switch; OFF = LOW; ON = HIGH
23 | -- swt(0) = least significant sliding switch; OFF = LOW; ON = HIGH
24 |
25 |
26 | led : out std_logic_vector(7 downto 0);
27 | -- led(7) = most significant led is ON when active HIGH
28 | -- led(0) = least significant led is ON when active HIGH
29 |
30 |
31 | seg : out std_logic_vector(7 downto 0);
32 | -- segment lights when active LOW
33 | -- seg(0) = seg-a
34 | -- seg(1) = seg-b
35 | -- seg(2) = seg-c
36 | -- seg(3) = seg-d
37 | -- seg(4) = seg-e
38 | -- seg(5) = seg-f
39 | -- seg(6) = seg-g
40 | -- seg(7) = dp
41 |
42 | ..
```

hw3a.vhd (part 2)

```
ln # | sim:/hw3a : hw3a.vhd
41
42
43 dig : out std_logic_vector(3 downto 0)
44 -- dig(3) = most significant digit is displayed when active LOW
45 -- dig(0) = least significant digit is displayed when active LOW
46
47 );
48 end hw3a;
49
50 architecture Behavioral of hw3a is
51
52 SIGNAL reset_pb_flag, pb_flag, clock_10hz: std_logic;
53
54 SIGNAL initialize : STD_LOGIC;
55
56 SIGNAL seg_3 : std_logic_vector(7 downto 0);
57 SIGNAL seg_2 : std_logic_vector(7 downto 0);
58 SIGNAL seg_1 : std_logic_vector(7 downto 0);
59 SIGNAL seg_0 : std_logic_vector(7 downto 0);
60
61 COMPONENT hierarch
62     PORT(
63         clock_50mhz, btn0, reset_pb_flag: IN STD_LOGIC;
64         pb_flag, clock_10Hz : OUT STD_LOGIC
65     );
66 END COMPONENT;
67
68 -- Use Port Map to connect signals between components in the hierarchy
69
70 BEGIN
71
72 hw3a : hierarch PORT MAP (clock_50mhz => clock_50mhz,
73                          btn0 => btn0,
74                          reset_pb_flag => reset_pb_flag,
75                          pb_flag => pb_flag,
76                          clock_10hz => clock_10hz
77                          );
78
```

hw3a.vhd (part 3)


```
ln # sim:/hw3a : hw3a.vhd
79 -- begin loop
80 PROCESS
81 BEGIN
82
83     -- initialize will be initialized to '0' at power up
84     IF initialize = '0' THEN
85         -- This code resets the critical signals once at power
86
87         reset_pb_flag <= '0';
88
89         led(7 downto 0) <= "00000000";
90
91         seg_3(7 downto 0) <= "11111111";
92         seg_2(7 downto 0) <= "11111111";
93         seg_1(7 downto 0) <= "11111111";
94         seg_0(7 downto 0) <= "11111111";
95
96     ELSE
97         initialize <= '1';
98
99     -- display each of the four digits for 0.1 second each forever
100
101
102     seg(7 downto 0) <= seg_0(7 downto 0) ;
103     dig <= "1110" ; --digit(0) is ON
104     --now wait for 0.1 second
105     WAIT UNTIL clock_10hz'EVENT and clock_10hz = '1';
106
107     seg(7 downto 0) <= seg_1(7 downto 0) ;
108     dig(3 downto 0) <= "1101" ; --digit(1) is ON
109     --now wait for 0.1 second
110     WAIT UNTIL clock_10hz'EVENT and clock_10hz = '1';
111
112
113     seg(7 downto 0) <= seg_2(7 downto 0);
114     dig(3 downto 0) <= "1011" ; --digit(2) is ON
115     --now wait for 0.1 second
116     WAIT UNTIL clock_10hz'EVENT and clock_10hz = '1';
117
118     seg(7 downto 0) <= seg_3(7 downto 0);
119     dig(3 downto 0) <= "0111" ; --digit(3) is ON
120     --now wait for 0.1 second
121     WAIT UNTIL clock_10hz'EVENT and clock_10hz = '1';
122
123
```

hw3a.vhd (part 4)

```
123
124 -- repeat display until USER sets sliding switches and then presses btn0
125
126 -- if btn0_pressed has NOT occurred then skip to repeat this loop,
127 -- else copy the switch settings and update the display
128
129   IF pb_flag = '1' THEN
130
131 -- copy the sliding switch settings to the leds
132 led(? downto 0) <= swt(? downto 0);
133
134 -- copy the sliding switch settings to the internal digit segments
135 seg_3(? downto 0) <= not (swt(? downto 0)) ;
136 seg_2(? downto 0) <= not (swt(? downto 0)) ;
137 seg_1(? downto 0) <= not (swt(? downto 0)) ;
138 seg_0(? downto 0) <= not (swt(? downto 0)) ;
139
140 reset_pb_flag <= '1';
141 --now wait for 0.1 second
142     WAIT UNTIL clock_10hz'EVENT and clock_10hz = '1';
143 reset_pb_flag <= '0';
144 ELSE
145 END IF;
146
147 END IF;
148
149 -- repeat loop
150 END PROCESS;
151
152 END Behavioral;
153
```


FPGA Resources for hw3a

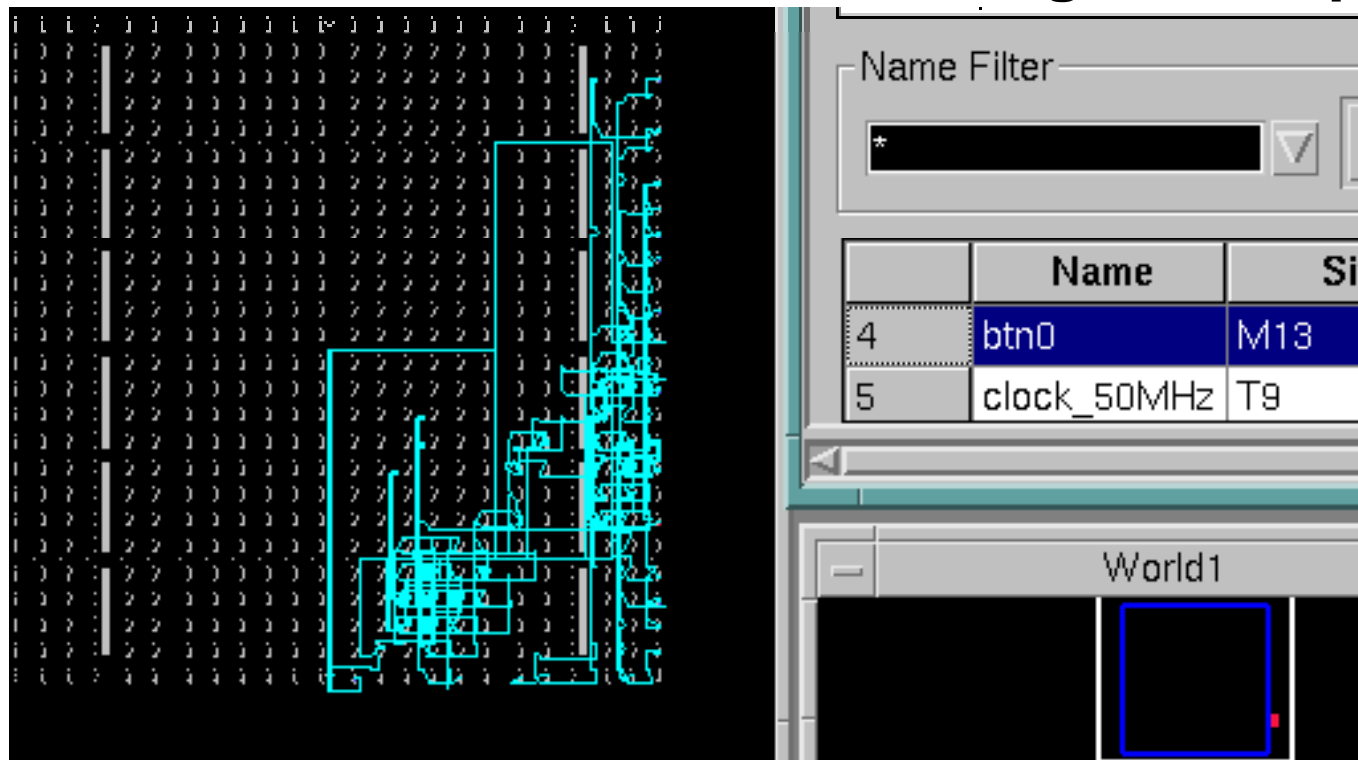- Logic slices used: 58 out of 1920 = 3%
- The constraint file, hw3a.ucf, assigned the pins.



Detailed Layout of hw3a

- Pin M13 is connected to btn0:

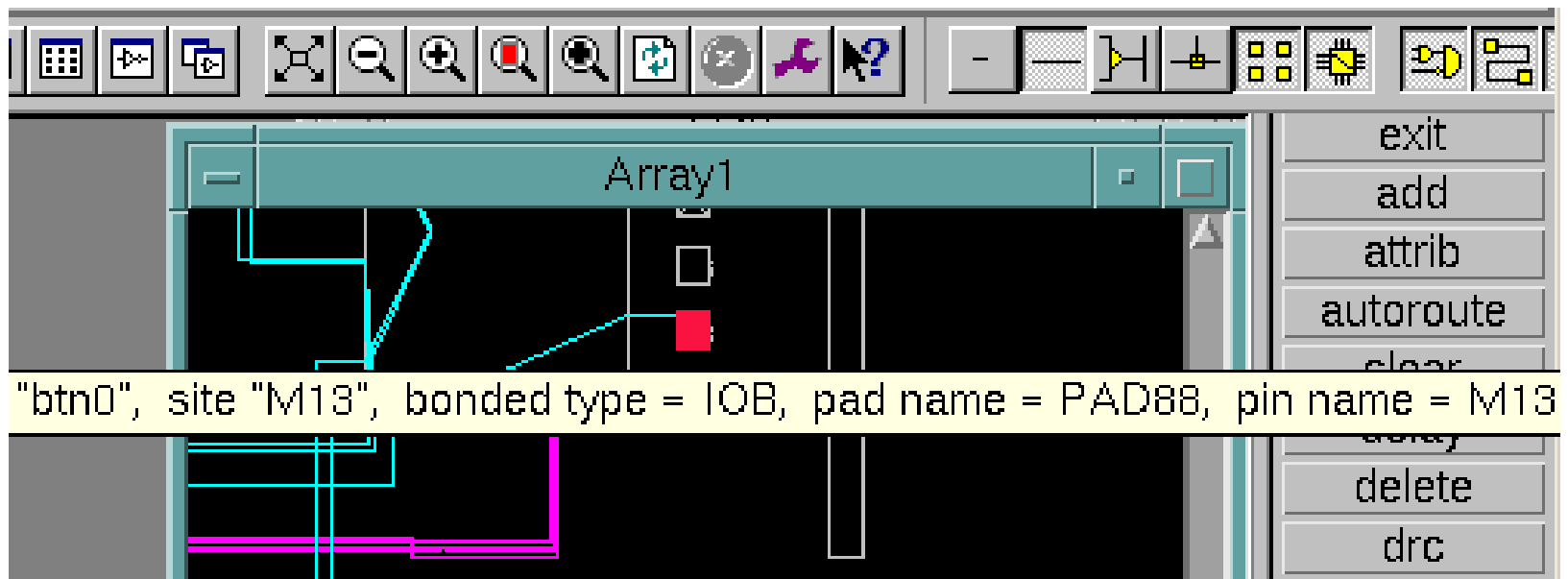

SYNCHRONIZER REDUCES RISK OF METASTABILITY PROBLEMS

- Signals from external circuits whose clock is independent must be synchronized with our internal clock.
- If not, the external input may occur during the decision window of our flip-flop and cause it to go into a metastable state.
- To reduce the likelihood of this occurring, the input can be double-buffered.

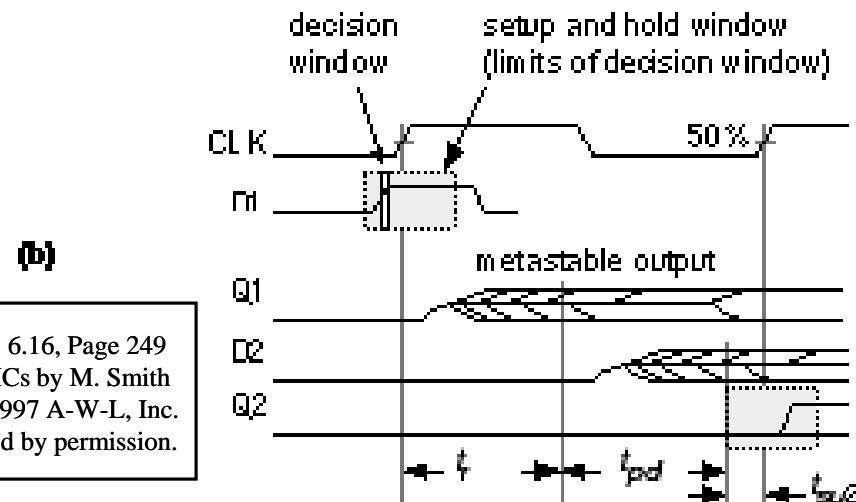
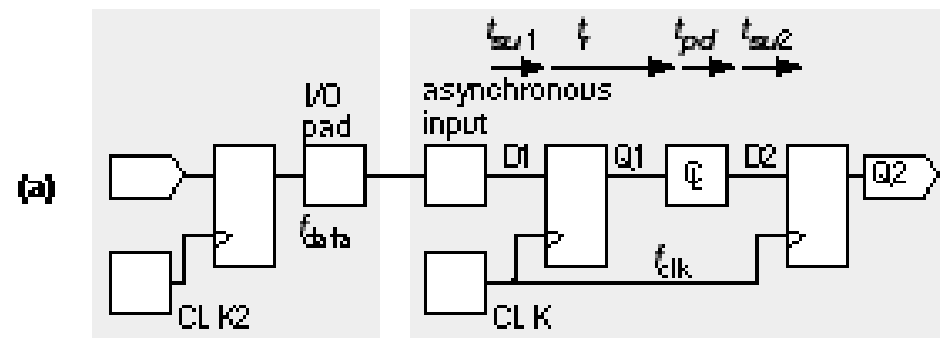


Fig. 6.16, Page 249
ASICs by M. Smith
© 1997 A-W-L, Inc.
Used by permission.