

# Inductance: Review

We know behavior of an inductor


$$V_1 = L_1 \frac{di_1}{dt}$$

More fundamentally

magnetic flux

$$\Phi_{L_1} = \alpha_1 i_1$$

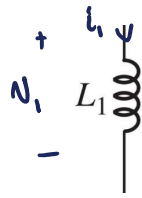$\alpha_1 = \text{some geometric constant}$  (from Ampere's law)




If these are the same loop

$$\Phi_L = \Phi_{L_1}$$

$$V_1 = \frac{d}{dt} \alpha_1 i_1$$

$$V_1 = \alpha_1 \frac{di_1}{dt}$$

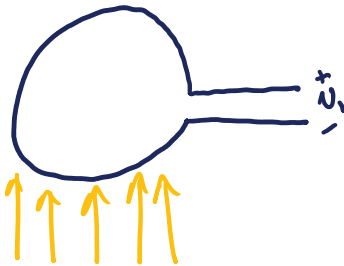

from Faraday's law

$$|V_1| = \frac{d\Phi_{L_1}}{dt}$$




for an N-turn coil

$$\Phi_{L_1} = N \alpha_1 i_1$$


$$|V_1| = N \frac{d\Phi_{L_1}}{dt}$$

$$V_1 = N^2 \alpha_1 \frac{di_1}{dt}$$

## Some Inductor Examples

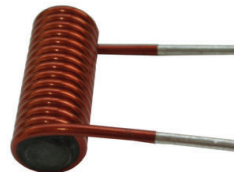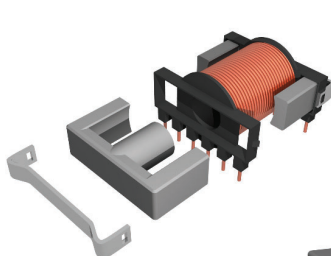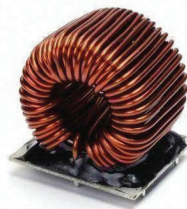


high  $\mu_r$  material  
(ferrite)

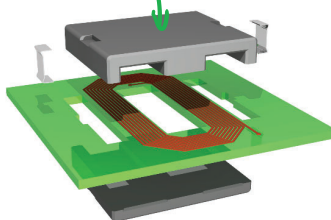

# Magnetic Coupling

occurs when (intentionally or not) flux from one inductance impinges on another

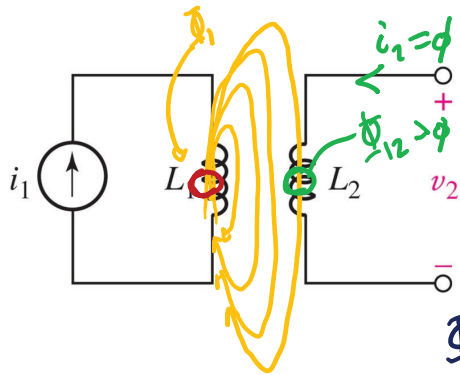

Case 1:  $i_2 = 0$

$$\Phi_1 = \alpha_1 N_1 i_1$$

$$v_1 = N_1 \frac{d\Phi_1}{dt} \rightarrow v_1 = \underbrace{N_1^2 \alpha_1}_{L_1} \frac{di_1}{dt}$$

Looking at  $L_2$ :

$\Phi_{12}$  = portion of  $\Phi_1$  that impinges on  $L_2$ 's windings

$$|v_2| = N_2 \frac{d\Phi_{12}}{dt}$$

$$\Phi_{12} = \alpha_{12} \Phi_1$$


$$\text{Let's say } \Phi_{12} = \alpha_{12} N_1 i_1$$

$$v_2 = \alpha_{12} N_2 N_1 \frac{di_1}{dt}$$

$= M = \text{"Mutual inductance"}$

$$\text{when } i_2 = 0 \quad \begin{cases} v_1 = L_1 \frac{di_1}{dt} \\ v_2 = M \frac{di_1}{dt} \end{cases}$$

# Magnetic Coupling

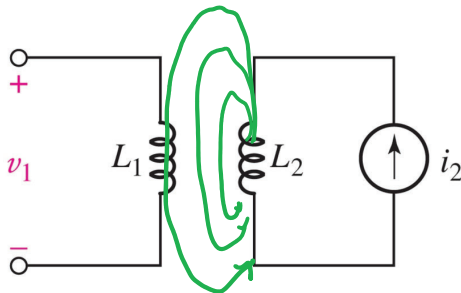


Case 2:  $i_1 = 0$

same circuit as previous, just mirrored & relabeled

$$\text{when } i_1 = 0 \quad \begin{cases} v_2 = L_2 \frac{di_2}{dt} \\ v_1 = M \frac{di_2}{dt} \end{cases}$$

# Mutual Inductance

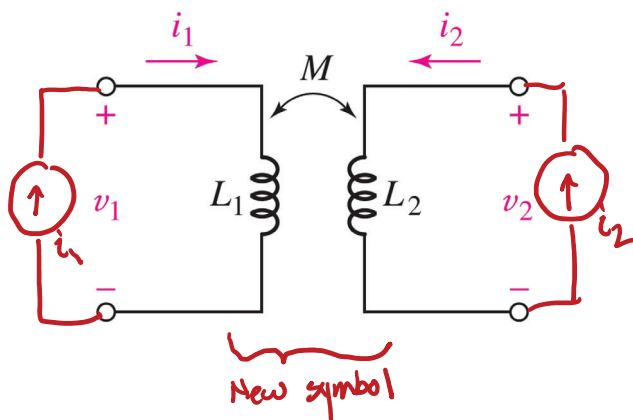

Apply superposition:

when  $i_2 = 0$

$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} \\ v_2 = M \frac{di_1}{dt} \end{cases}$$

when  $i_1 = 0$


$$\begin{cases} v_1 = M \frac{di_2}{dt} \\ v_2 = L_2 \frac{di_2}{dt} \end{cases}$$

$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{cases}$$


sign depends on winding arrangement
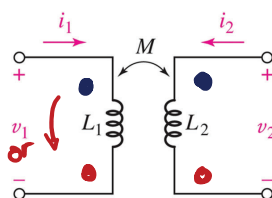
## Symbols and Dot Convention

Note: Always assign passive sign convention



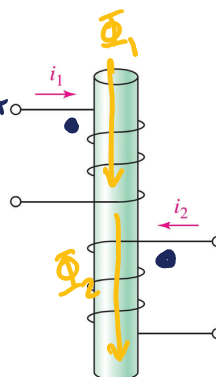
$$v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$




Physically:

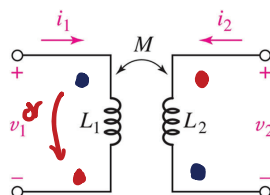If both winding currents enter the dotted terminals, the fluxes are additive


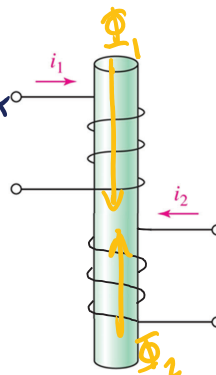
$$v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$



Circuit:

Current flowing into the dotted terminal of one winding will produce an open-circuit voltage that is positive at the dotted terminal of the other