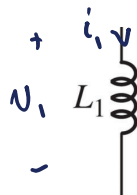


Energy Storage




prior to $t=0$, $i_1 = 0$, @ t_0 , $I_0 = i_1$

$$E_L = \int_0^{t_0} P_L(t) dt = \int_0^{t_0} v_1(t) i_1(t) dt = \int_0^{t_0} L_1 \frac{di_1}{dt} i_1(t) dt$$

$$E_L = L_1 \int_0^{t_0} \left[\frac{d}{dt} i_1(t) \right] \cdot \frac{1}{2} dt = \frac{1}{2} L_1 [i_1(t)^2] \Big|_{i_1(t=0)}^{i_1(t=t_0)} = \frac{1}{2} L_1 I_0^2$$

$E_L = \frac{1}{2} L_1 I_0^2$

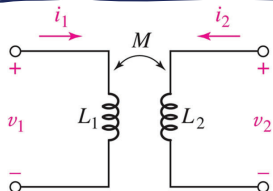

$$E_{12} = \int_0^{t_0} (i_1(t) \cdot v_1(t) + i_2(t) \cdot v_2(t)) dt$$

before $t=0$, $i_1(t)=0$ & $i_2(t)=0$
 @ t_0 , $i_1(t)=I_{01}$, $i_2(t)=I_{02}$

$$E_{12} = \int_0^{t_0} \left(i_1 \left(L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt} \right) + i_2 \left(L_2 \frac{di_2}{dt} \pm M \frac{di_1}{dt} \right) \right) dt$$

$$E_{12} = \int_0^{t_0} \left(L_1 \frac{di_1}{dt} i_1 + L_2 \frac{di_2}{dt} i_2 \pm M \left(i_1 \frac{di_2}{dt} + i_2 \frac{di_1}{dt} \right) \right) dt$$

$$E_{12} = \frac{1}{2} L_1 I_{01}^2 + \frac{1}{2} L_2 I_{02}^2 \pm M \int_0^{t_0} \frac{d}{dt} (i_1 \cdot i_2) dt$$

$E_{12} = \frac{1}{2} L_1 I_{01}^2 + \frac{1}{2} L_2 I_{02}^2 \pm M I_{01} I_{02}$

$$E_{12} = \frac{1}{2} L_1 I_{01}^2 + \frac{1}{2} L_2 I_{02}^2 \pm M I_{01} I_{02} \geq 0$$

pick negative sign for "minimum" $E_{12} \geq 0$

$$M \leq \frac{\frac{1}{2} L_1 I_{01}^2 + \frac{1}{2} L_2 I_{02}^2}{I_{01} I_{02}} = \frac{1}{2} L_1 \frac{I_{01}}{I_{02}} + \frac{1}{2} L_2 \frac{I_{02}}{I_{01}}$$

let $x = \frac{I_{01}}{I_{02}} \rightarrow M \leq \frac{1}{2} L_1 x + \frac{1}{2} L_2 \frac{1}{x}$

find max & min w.r.t. $x = \frac{I_{01}}{I_{02}}$ & make sure inequality holds

$$\frac{dM}{dx} = \frac{1}{2} L_1 - \frac{1}{2} L_2 \frac{1}{x^2} = 0 \rightarrow x = \sqrt{L_2/L_1}$$

$$\frac{\partial^2 M}{\partial x^2} = \frac{1}{2} L_2 \frac{2}{x^3} = \frac{L_2}{x^3} > 0$$

$E_{12} \geq 0$ must hold @ minimum at $x = \sqrt{L_2/L_1}$

$$M \leq \frac{1}{2} L_1 \sqrt{L_2/L_1} + \frac{1}{2} L_2 \sqrt{L_1/L_2}$$

$M \leq \sqrt{L_1 L_2}$

Coupling Coefficient

Define $k = \frac{M}{\sqrt{L_1 L_2}} \equiv \text{"coupling coefficient"}$

Always $0 \leq k \leq 1$

$k=0 \rightarrow$ two separate inductors

\vdots } coupled inductors

$k=1 \rightarrow$ perfect coupling
 \rightarrow "transformer"

Transformers

Special case where $k=1 \Leftrightarrow M = \sqrt{L_1 L_2}$

$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{cases} \xrightarrow{k=1} \begin{cases} v_1 = L_1 \frac{di_1}{dt} + \sqrt{L_1 L_2} \frac{di_2}{dt} \\ v_2 = L_2 \frac{di_2}{dt} + \sqrt{L_1 L_2} \frac{di_1}{dt} \end{cases}$$


\downarrow
assume positive coupling

$$v_2 = v_1 \sqrt{\frac{L_2}{L_1}}$$

$$v_2 = v_1 \sqrt{\frac{\cancel{N_2^2} N_2^2}{\cancel{N_1^2} N_1^2}} \quad \text{if } k=1 \quad v_1 = v_2$$

$$v_2 = v_1 \left(\frac{N_2}{N_1} \right) \rightarrow \text{"turns ratio"}$$

New circuit symbol

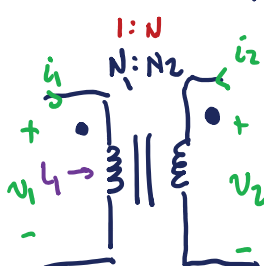

where $N = \frac{N_2}{N_1}$

$$\frac{v_2}{N_2} = \frac{v_1}{N_1}$$