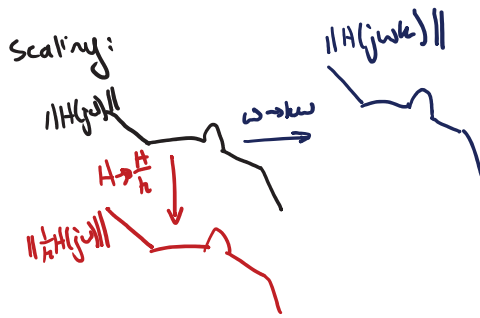


Scaling and Bandwidth




frequency scaling $\|H(s)\| \rightarrow \|H(jkw)\|$

$$\begin{cases} R \rightarrow R \\ C \rightarrow C/k \\ L \rightarrow L/k \end{cases} \quad \text{useful to minimize}$$

$Z_R = R$ (same for all frequencies)

$Z_L = sL \Rightarrow j\omega L$

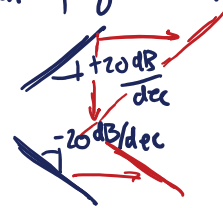$Z_C = \frac{1}{sC} \Rightarrow \frac{-j}{\omega C}$



Magnitude Scaling $\|H(jw)\| \rightarrow \frac{1}{k} \|H(jw)\|$


$$\begin{cases} R \rightarrow R/k \\ C \rightarrow Ck \\ L \rightarrow L/k \end{cases}$$

Bandwidth = $|\omega_2 - \omega_1| \rightarrow$ some range of frequencies
commonly "-3dB bandwidth" or "half power bandwidth"

For 2nd order resonance (complex pair)

$B = BW = \frac{\omega_0}{Q}$

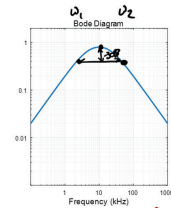Higher $Q =$ Less $B =$ More frequency selective





Filter Design

$H(s) = \underline{\hspace{1cm}}$ \rightarrow How to realize as a circuit

Approximate Graphical Analysis

- $\|H_1 \cdot H_2\|_{dB} = \|H_1\|_{dB} + \|H_2\|_{dB}$ Multiplication (linear) \rightarrow Addition (log)
- $\|\omega^n\|_{dB} = 20(n) \log(\omega) \Rightarrow 20(n) \text{ dB/dec}$ line
- $\|1 + jx\|_{dB} \approx \begin{cases} \|x\|_{dB}, & x \gg 1 \\ -20 \text{ dB}, & x = 1 \\ 1, & x \ll 1 \end{cases}$ Addition (linear) $\approx \max()$ (+ look at intersection)

Series  $\|Z_1 + Z_2\|_{dB} = \begin{cases} \|Z_1\|_{dB}, & |Z_1| \gg |Z_2| \\ \text{look closer}, & |Z_1| = |Z_2| \\ \|Z_2\|_{dB}, & |Z_1| \ll |Z_2| \end{cases}$

Parallel  $\begin{aligned} \|(Z_1 \| Z_2)\|_{dB} &= \begin{cases} \|Z_2\|_{dB}, & |Z_1| \gg |Z_2| \\ \text{look closer}, & |Z_1| = |Z_2| \\ \|Z_1\|_{dB}, & |Z_1| \ll |Z_2| \end{cases} \\ \|\frac{Z_1 Z_2}{Z_1 + Z_2}\|_{dB} & \end{aligned}$

Reactance Paper

