


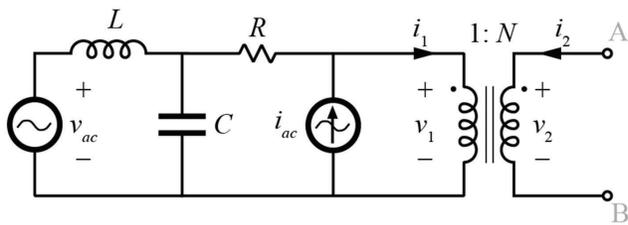
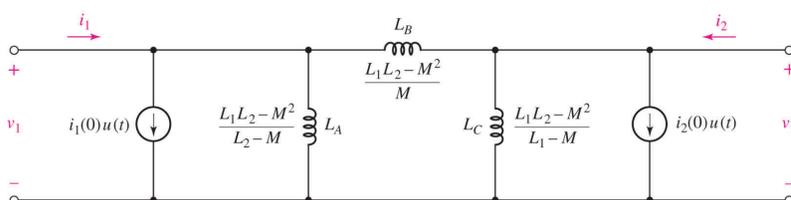
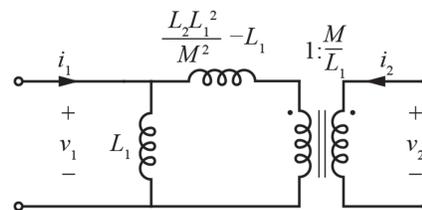
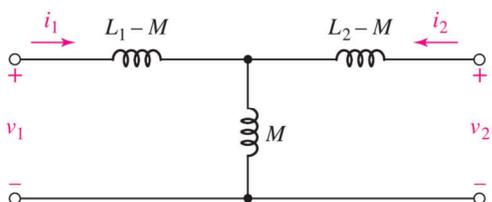
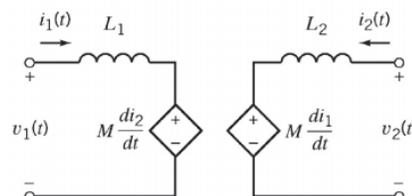


# Example Circuit Simplification

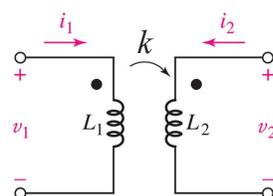

## Equivalent Circuits

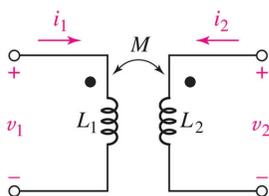

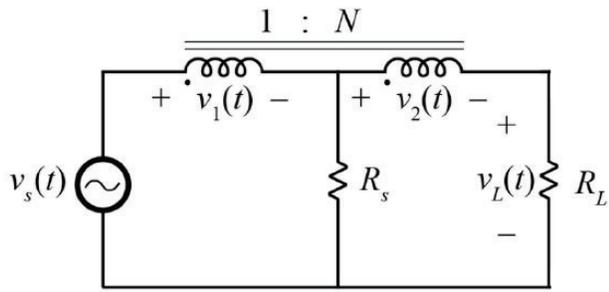

# 15W USB Adapter Reference Design

