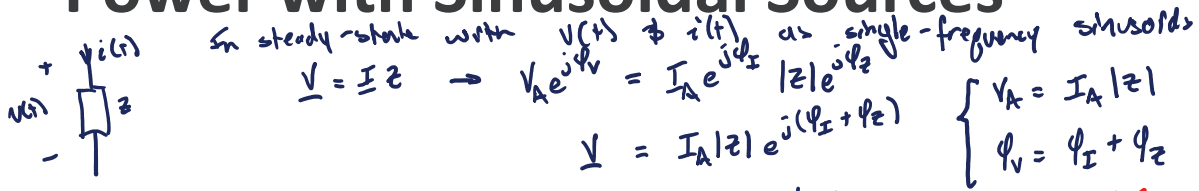


# Power with Sinusoidal Sources



For power, we cannot just multiply  $V$  &  $I$   
 $p(t) = v(t)i(t) = \text{Re}\{V_A e^{j\phi_V} e^{j\omega t}\} \cdot \text{Re}\{I_A e^{j\phi_I} e^{j\omega t}\} \rightarrow \text{Re}\{I_A e^{j\phi_I} e^{j\omega t}\}$  *matter*

Go back to the time domain:

$$p(t) = V_A \cos(\omega t + \phi_V) \cdot I_A \cos(\omega t + \phi_I)$$

$$= V_A I_A \cos(\omega t + \phi_V) \cos(\omega t + \phi_I)$$

$$= \frac{V_A I_A}{2} \cos(2\omega t + \phi_V + \phi_I) + \frac{V_A I_A}{2} \cos(\phi_V - \phi_I)$$

Trig Identity  
 $2 \cos \theta \cos \phi = \cos(\theta + \phi) + \cos(\theta - \phi)$


sinusoid @  $2\omega$   
AC

No time-variation  
DC


In  $\phi_V - \phi_I$ , order doesn't matter

Average Power  $P = \frac{1}{T} \int_0^T p(t) dt = \frac{V_A I_A}{2} \cos(\phi_V - \phi_I) = V_{rms} I_{rms} \cos(\phi_V - \phi_I)$

# Power with Sinusoidal Sources

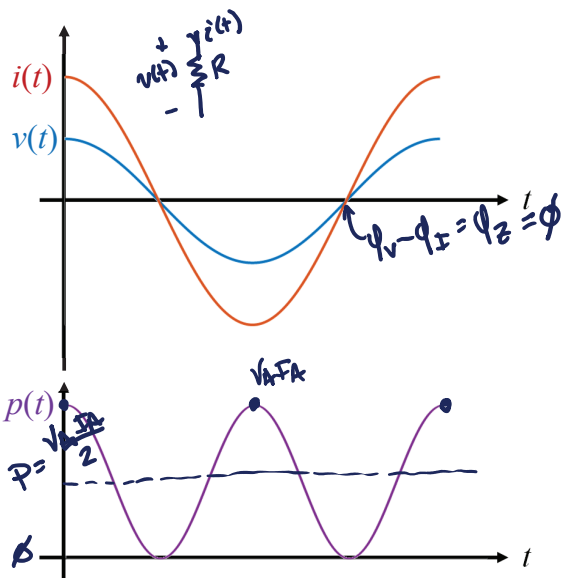
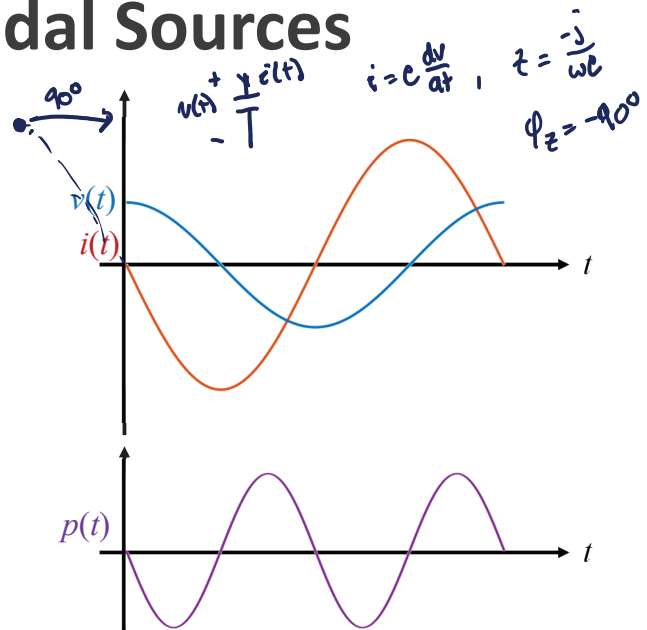
$$P_R = \frac{V_A I_A}{2} = V_{rms} I_{rms}$$



$$\cos(\phi_V - \phi_I) = \cos(90^\circ) = 0$$

so  
 $P = 0$