


Complex Power

Average Power P in sinusoidal steady state

$$P = \frac{V_A I_A}{2} \cos(\phi_V - \phi_I) = \frac{1}{2} \operatorname{Re}\{V \cdot I^*\}$$

$$\begin{aligned} \frac{1}{2} \operatorname{Re}\{V I^*\} &= \frac{1}{2} \operatorname{Re}\{V_A e^{j\phi_V} I_A e^{-j\phi_I}\} \\ &= \frac{1}{2} \operatorname{Re}\{V_A I_A e^{j(\phi_V - \phi_I)}\} \\ &= \frac{1}{2} V_A I_A \cos(\phi_V - \phi_I) \quad \checkmark \end{aligned}$$

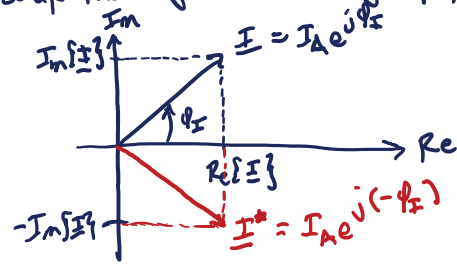complex conjugate (swap the sign of the imaginary part)



$$P = \frac{V_A I_A}{2} \cos(\phi_V - \phi_I) = V_{rms} I_{rms} \cos(\phi_V - \phi_I) = \frac{1}{2} \operatorname{Re}\{V I^*\} = \operatorname{Re}\{V_{rms} I_{rms}^*\}$$

rms phasor exponent

What about the imaginary part of $V I^*$

$$\frac{1}{2} V I^* = V_{rms} I_{rms}^* = S = P + jQ$$

Complex Power [VA]
Real or Average Power [W]
Reactive or Quadrature Power [VAR]

Apparent Power & Power Factor

Apparent Power $|S| = \frac{V_A I_A}{2} = V_{rms} I_{rms}$

→ Maximum value of real power that can be obtained from $V_A \neq I_A$

Power Factor $PF = \frac{P}{|S|} = \frac{P}{V_{rms} I_{rms}} = \frac{\frac{V_A I_A}{2} \cos(\phi_V - \phi_I)}{\frac{V_A I_A}{2}} = \cos(\phi_V - \phi_I)$

↓
general for non-sinusoids

$0 \leq PF \leq 1$

① How over-stressed is the circuit

② Regulated for connection to the grid for any loads above 65W