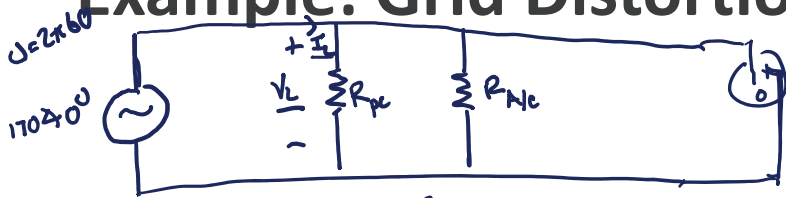


# Example: Grid Distortion



PC: about 1kW } power consumption  
A/c: 3.5 kW }

ohm's law for impedances

$$V = I Z$$

for resistor  $I = \frac{V}{R}$

what are  $R_{pc}$  &  $R_{A/c}$ ?  $\phi_z = 0$  for resistor

$$P_R = \frac{|V_R| |I_R|}{2} \cos(\phi_V - \phi_I) = \frac{|V_R| |I_R|}{2}$$

$$P_R = \frac{|V_R|^2}{2R}$$

then

$$R_{pc} = \frac{|V_L|^2}{2P_{pc}} = \frac{170^2}{2 \cdot 1kW} = 14.5 \Omega$$

$$R_{A/c} = \frac{170^2}{2 \cdot 3.5kW} = 4.1 \Omega$$


$$|I_R| = \frac{|V_R|}{R}$$

$$R_{eq} = R_{pc} \parallel R_{A/c} = 3.2 \Omega$$

$$I_L = \frac{V_s}{R_{eq}} = 53.4 \angle 0^\circ \text{ A}$$

$$S = \frac{1}{2} V_s I_L^* = \frac{1}{2} (170 e^{j0}) (53.4 e^{j0}) = 4.5 \text{ kW} + 0j \text{ VAR}$$

$$PF = \frac{P}{|S|} = 1$$

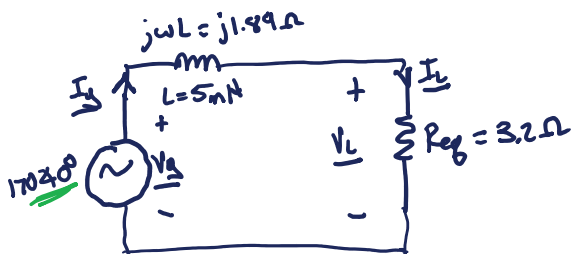

$$I_g = I_L = \frac{V_s}{R_{eq} + j\omega L} = 45.4 \angle -30^\circ$$

$$V_L = I_g R_{eq} = 146.5 \angle -30^\circ$$

$$P_L = \frac{|V_L| |I_L|}{2} \cos(0^\circ) = 3.3 \text{ kW}$$

In a more realistic model  $R_{eq}$  might change to keep the same power  
- Neglect for now.

Complex power from grid

$$P_g = \frac{1}{2} V_s I_g^* = \frac{1}{2} (170 \angle 0^\circ) (45.4 \angle 30^\circ) = 3.8 \text{ kW} \angle 30^\circ$$

$$S = 3.3 \text{ kW} + j1.9 \text{ kW}$$

↑ P      ↑ Q



$$PF = \frac{P}{|S|} = 0.87 \text{ lagging}$$

could also use

$$PF = \cos(\phi_V - \phi_I)$$

defined for current relative to voltage  
"lagging" indicates our load is inductive, "leading" capacitive

Can we return the power factor to unity

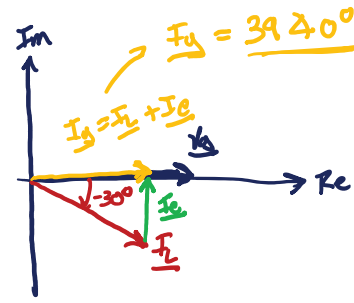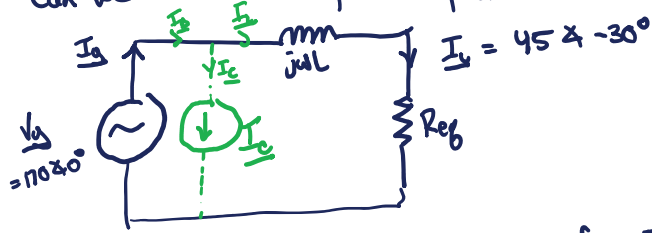


Try to add  $I_C$  such that phase of  $I_g = 0^\circ$

$$I_C = 45 \sin(30^\circ) \angle 90^\circ = 22.5 \angle 90^\circ = j22.5$$

$$\frac{V_s}{I_C} = Z = \frac{170 e^{j0}}{22.5 e^{j90}} = \frac{170}{22.5} e^{-j\frac{\pi}{2}} = 7.56 \angle -90^\circ = \frac{-j}{1/7.56} \Rightarrow \frac{-j}{\omega C}$$

$$C = \frac{1}{\omega 7.56} = 350 \mu\text{F}$$

this can be a capacitor with

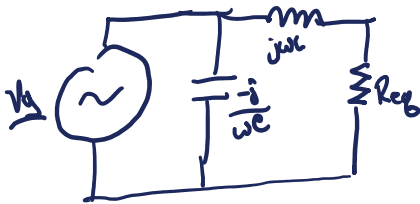

$$Z_{eq} = \frac{-j}{\omega C} \parallel (j\omega L + R_{eq}) = 4.3 + 0j \Omega$$

$$S = V_s I_g^* = \frac{170 \parallel 170}{2} \cos(\theta_v - \theta_i) \text{ transformed the impedance}$$

$$= 3.31 \text{W} + 0j$$

$$\downarrow \text{PF} = 1$$