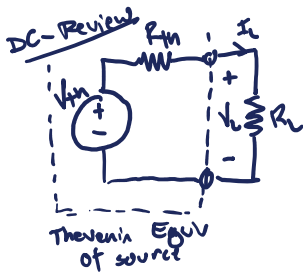


Maximum Power Transfer



What resistance R_L results in maximum $P_L = I_L V_L$?


$$P_L = V_{th} \frac{R_L}{R_L + R_{th}} \frac{V_{th}}{R_L + R_{th}} = V_{th}^2 \frac{R_L}{(R_L + R_{th})^2}$$

$$\frac{dP_L}{dR_L} = 0 = V_{th}^2 \left[\frac{1}{(R_L + R_{th})^2} + \frac{-2R_L}{(R_L + R_{th})^3} \right]$$

$$R_L = \frac{1}{2} (R_L + R_{th}) \rightarrow \boxed{R_L = R_{th}}$$

Note: maximizing power may not always be a good idea.

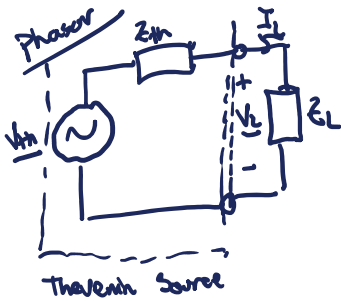Efficiency $\frac{P_{out}}{P_{in}} = \eta = \frac{I_L^2 R_L}{I_L^2 Z_{th} + I_L^2 R_L} = \frac{R_L}{R_L + R_{th}} \rightarrow 50\%$ at maximum power




what value of Z_L maximizes real power to the load?

If we set $Z_L = R_e\{Z_{th}\} - j \text{Im}\{Z_{th}\}$


$$\boxed{Z_L = Z_{th}^*}$$

Impedance Matching

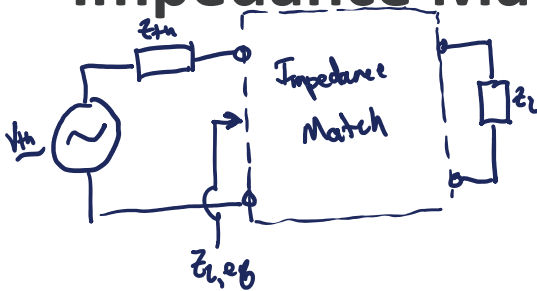

- Signals \rightarrow RF $\rightarrow Z_{L,eq} = Z_{th}^*$
- Signals \rightarrow comm $\rightarrow Z_{L,eq} = Z_{th}$
- power converters $\rightarrow R_{L,eq} \rightarrow \infty \rightarrow R_{th}$
- grid applications \rightarrow periodically correct PF

Example Matching Circuits

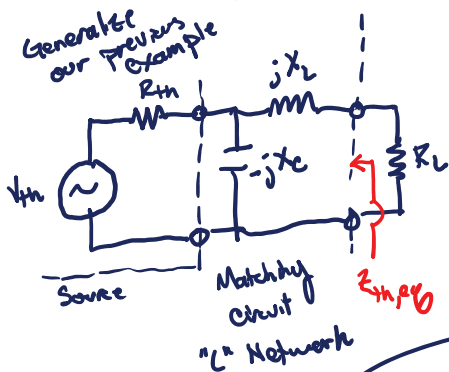

$$Z_{in,eq} = R_{th} \parallel (-jX_C) + jX_L$$


$$= \frac{-jX_C R_{th}}{R_{th} - jX_C} + jX_L$$

$$= \left[\frac{X_C^2 R_{th}}{R_{th}^2 + X_C^2} \right] + j \left[\frac{-X_C R_{th}^2}{R_{th}^2 + X_C^2} \right] + jX_L$$

cancel reactance to zero

for max power transfer

set to R_L

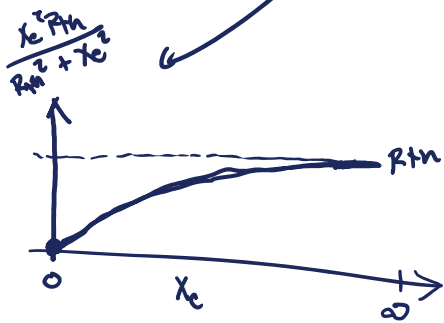

works if $R_{th} > R_L \rightarrow$ this configuration
Lower source resistance



If I swap L & C?
 same result