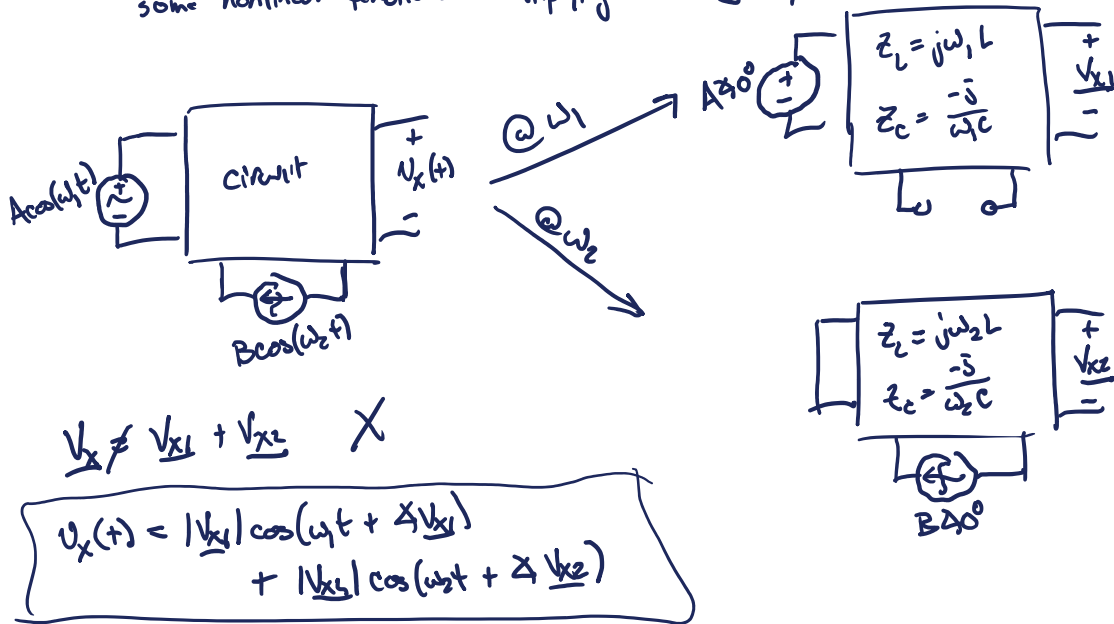


Phasor Superposition \rightarrow Problem 10-63 on HW #4

- Phasor Transformation valid only for a single frequency
 - Superposition can be applied if we compute the transform at each frequency.
- Superposition is guaranteed to work for linear functions \rightarrow $f(x_1) = y_1$ } $f(x_1, x_2) = y_1 + y_2$
 $f(x_2) = y_2$
- Linear functions include $r/-$, $\frac{d}{dt}$, \int multiplication by constant
 some nonlinear functions: multiplying two signals, $(x)^2$, ...




Power Spectrum

Power calculations are nonlinear

End of 11.4

\rightarrow superposition not guaranteed.

example

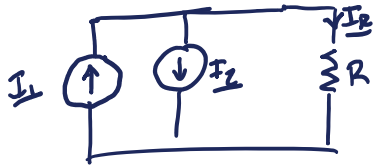

If $I_1 = I_2$
 by inspection $I_R = \emptyset$ so $P_R = \emptyset$
 But if we (incorrectly) apply superposition

$$P_1 = \frac{|I_1|^2 R}{2}, \quad P_2 = \frac{|I_2|^2 R}{2} \quad \} \times$$

$$P_1 + P_2 = |I_1|^2 R$$

But, superposition of powers does work if all sources are at different frequency.

$$P_R(t) = i_R(t)^2 R = [|I_1| \cos(\omega_1 t) - |I_2| \cos(\omega_2 t)]^2 R$$

$$\text{average } P_R = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} [|I_1| \cos(\omega_1 t) - |I_2| \cos(\omega_2 t)]^2 R dt$$

$$= \lim_{T \rightarrow \infty} \frac{R}{T} \int_{-T/2}^{T/2} |I_1|^2 \cos^2(\omega_1 t) + |I_2|^2 \cos^2(\omega_2 t) - 2|I_1||I_2| \cos(\omega_1 t) \cos(\omega_2 t) dt$$

$$\downarrow$$

$$2|I_1||I_2| \frac{1}{2} (\cos(\omega_1 t + \omega_2 t) + \cos(\omega_1 t - \omega_2 t))$$

Average = 0 if $\omega_1 \neq \omega_2$

Limitations of Phasor Analysis

- ① Single frequency
- ② Only steady-state response
- ③ sinusoidal inputs & waveforms only

} Developed for particular solutions to ODE
 Pattern matching & know that for sinusoids in, we get sinusoids out, only mag & phase change.

want to develop analysis techniques w/out these limitations

① Superposition can help

frequency response \rightarrow valid for all ω (chapter 15)

③ Fourier series & transform can express arbitrary* waveforms as a sum of sinusoids

Ch 17

② Homogeneous solution needed

Need exponentials \rightarrow Ch 14, Laplace Transforms

Frequency Response

solve with ω as a variable

$$\underline{V}_o = \underline{V}_I \frac{-j/\omega C}{R - j/\omega C} = \underline{V}_I \frac{1}{j\omega RC + 1}$$

\downarrow some complex number
 $H(j\omega)$
 \downarrow Frequency Response

