

Inverse Transforms

often we're interested in $\mathcal{L}^{-1}\{F(s)\}$ of signals that look like a ratio of polynomials (uniqueness)
 if $F(s)$ is $\mathcal{L}\{f(t)\}$, $\mathcal{L}^{-1}\{F(s)\} = f(t)$
 if $m \leq n \rightarrow$ physically realizable system (causal system)

$$F(s) = \frac{a_n s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}$$

often, we'll need to factor the polynomials

ex/ $F(s) = \frac{10}{s^2 + 4s + 4} = \frac{10}{(s+2)^2}$

$$\mathcal{L}^{-1}\left\{\frac{10}{(s+2)^2}\right\} = 10 \mathcal{L}^{-1}\left\{\frac{1}{(s+2)^2}\right\} = \boxed{10 t e^{-2t} u(t) = f(t)}$$

ex/ $F(s) = \frac{5s+1}{s+1}$ here $m \geq n$, so use long division

$$\begin{array}{r} 5 \\ s+1 \overline{) 5s+1} \\ \underline{-(5s+5)} \\ -4 \end{array} \quad \frac{5s+1}{s+1} = 5 - \frac{4}{s+1}$$

$$\mathcal{L}^{-1}\left\{5 - \frac{4}{s+1}\right\} = 5 \mathcal{L}^{-1}\{1\} - 4 \mathcal{L}^{-1}\left\{\frac{1}{s+1}\right\} = \boxed{5 \delta(t) - 4 e^{-t} u(t) = f(t)}$$

Partial Fraction Expansion / Decomposition

$$\frac{(s-z_1)(s-z_2)\dots(s-z_m)}{(s-p_1)(s-p_2)\dots(s-p_n)} = \frac{k_1}{s-p_1} + \frac{k_2}{s-p_2} + \dots + \frac{k_n}{s-p_n}$$

where all p_i are unique & $n \geq m$
 k_i are called "residuals"

Find k_i by multiplying both sides by $(s-p_i)$ & evaluating at $s=p_i$

e.g. @ $i=2$

$$(s-p_2) \frac{(s-z_1)(s-z_2)\dots(s-z_m)}{(s-p_1)(s-p_2)\dots(s-p_n)} = \frac{k_1 \cancel{(s-p_2)}}{s-p_1} + \frac{k_2 \cancel{(s-p_2)}}{s-p_2} + \dots + \frac{k_n \cancel{(s-p_2)}}{s-p_n} = k_2$$

ex/ $F(s) = \frac{4(s+2)}{s^2 + 4s + 3} = \frac{4(s+2)}{(s+1)(s+3)} = \frac{k_1}{s+1} + \frac{k_2}{s+3} = \frac{2}{s+1} + \frac{2}{s+3}$


$$\left\{ \begin{array}{l} \text{for } k_1 \Rightarrow k_1 = \frac{4(s+2)}{s+3} \Big|_{s=-1} = 2 \\ \text{for } k_2 \Rightarrow k_2 = \frac{4(s+2)}{s+1} \Big|_{s=-3} = 2 \end{array} \right.$$

$$f(t) = 2 \mathcal{L}^{-1}\left\{\frac{1}{s+1}\right\} + 2 \mathcal{L}^{-1}\left\{\frac{1}{s+3}\right\} = 2(e^{-t} + e^{-3t})u(t)$$


if p_i are not unique, polynomial residual e.g. $\frac{k_1 s + k_2}{(s-p_i)^2}$

Circuit Laplace Transform


Time Domain

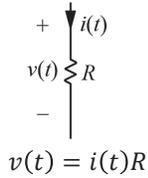

Phasor Domain

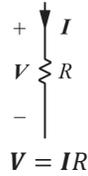




s-Domain

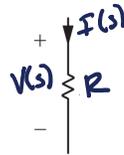

$Z_R = R$ still use "Impedance"

$$\mathcal{L}\{v(t)\} = \mathcal{L}\{i(t)R\}$$

$$V(s) = I(s)R$$

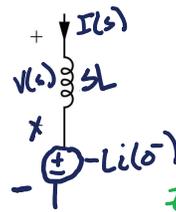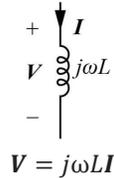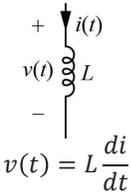




$Z_L = sL$

$$\mathcal{L}\{v(t)\} = \mathcal{L}\left\{L \frac{di}{dt}\right\}$$

$$V(s) = \mathcal{L}\left[sI(s) - i(0^-)\right]$$

$$V(s) = sL I(s) - L i(0^-)$$
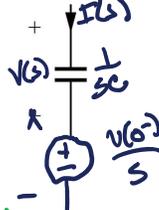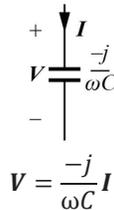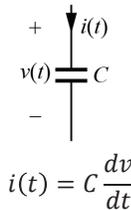
$$I(s) = \frac{1}{sL} V(s) + \frac{1}{sL} i(0^-)$$



$Z_C = \frac{1}{sC}$


$Z_C = \frac{1}{sC}$

$$I(s) = C \left[sV(s) - v(0^-) \right]$$

$$I(s) = sC V(s) - C v(0^-)$$

$$V(s) = \frac{1}{sC} I(s) + \frac{v(0^-)}{s}$$


Time Domain

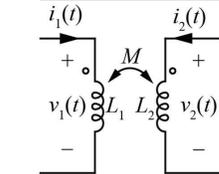

$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$


Phasor Domain

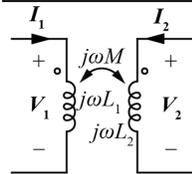

$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$

s-Domain

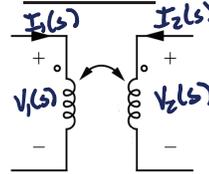

$$V_1(s) = L_1 [sI_1(s) - i_1(0^-)] + M [sI_2(s) - i_2(0^-)]$$

$$V_2(s) = M [sI_1(s) - i_1(0^-)] + L_2 [sI_2(s) - i_2(0^-)]$$

Alternatively replace w/ equivalent circuit first.

Ideal XF's (ie L=1 & L0 -> infinity)

No change

$$\frac{V_1(s)}{N_1} = \frac{V_2(s)}{N_2}$$

$$N_1 I_1(s) + N_2 I_2(s) = \phi$$