
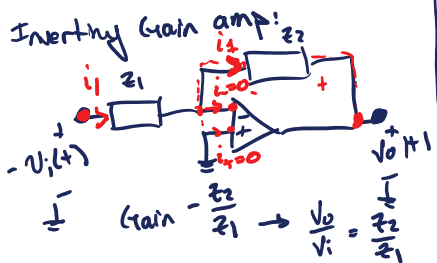
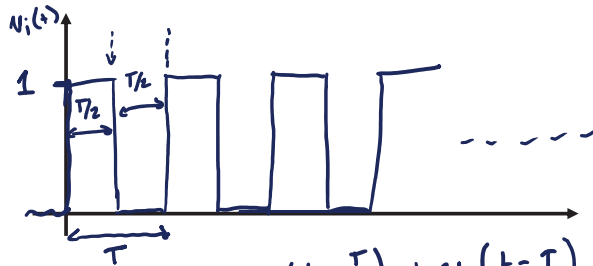


Example Problem

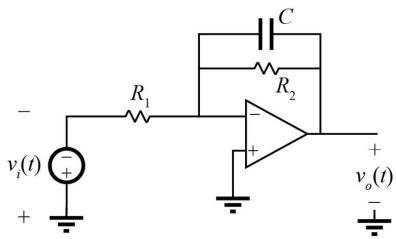

Inverting gain amp:
 (i) (if negative feedback) → virtual short
 $v_- = v_+$

(ii) $i_+ = i_- = 0$

$i_1 = \frac{-v_i}{z_1}$ $v_o = -i_1 z_2$
 $v_o = -\left(\frac{-v_i}{z_1}\right) z_2 = \frac{z_2}{z_1} v_i$

$$v_i(t) = u(t) - u(t - \frac{T}{2}) + u(t - T) - u(t - \frac{3T}{2}) + \dots$$

$$= \sum_{k=0}^{\infty} u(t - kT) - u(t - kT - \frac{T}{2})$$

$$= \sum_{k=0}^{\infty} u(t - k\frac{T}{2}) (-1)^k$$

$$V_I(s) = \mathcal{L}\{v_i(t)\}$$

$$= \int_0^{\infty} e^{-st} \sum_{k=0}^{\infty} u(t - k\frac{T}{2}) (-1)^k dt$$

↓ next page

$z_1 = R_1$
 $z_2 = \frac{1}{sC} \parallel R_2$

$$H(s) = \frac{R_2 / sC}{R_1 + \frac{1}{sC}} = \frac{R_2 / R_1}{sCR_2 + 1} = H(s)$$

Slido: #Q711

$$H(s) = \frac{R_2}{R_1} \frac{1}{sR_2C + 1}$$

$$V_o(s) = H(s) \cdot V_I(s) = \frac{R_2}{R_1} \frac{1}{sR_2C + 1} \left(\sum_{k=0}^{\infty} \frac{1}{s} e^{-sk\frac{T}{2}} (-1)^k \right)$$



$$V_o(s) = \sum_{k=0}^{\infty} (-1)^k \frac{R_2}{R_1} e^{-sk\frac{T}{2}} \frac{1}{s} \frac{1}{sR_2C + 1}$$

scale factor s-domain time delay


$$\frac{1}{s} \frac{1}{sR_2C + 1} = \frac{1}{s} + \frac{-R_2C}{sR_2C + 1} = \frac{1}{s} + \frac{-1}{s + \frac{1}{R_2C}}$$

$$v_o(t) = \mathcal{L}^{-1}\{V_o(s)\}$$
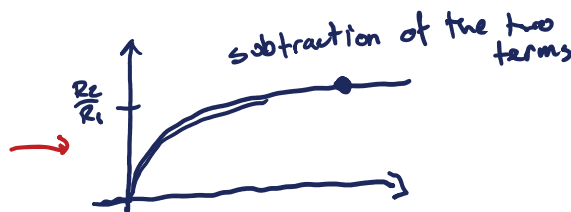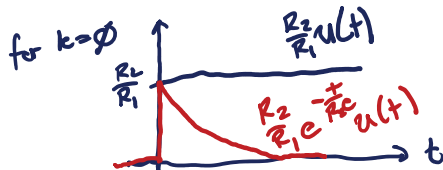
$$= \sum_{k=0}^{\infty} (-1)^k \frac{R_2}{R_1} \left(u(t - k\frac{T}{2}) - e^{-\frac{t - k\frac{T}{2}}{R_2C}} u(t - k\frac{T}{2}) \right) = \sum_{k=0}^{\infty} (-1)^k \frac{R_2}{R_1} \left(1 - e^{-\frac{t - k\frac{T}{2}}{R_2C}} \right) u(t - k\frac{T}{2})$$




Slido: #Q711

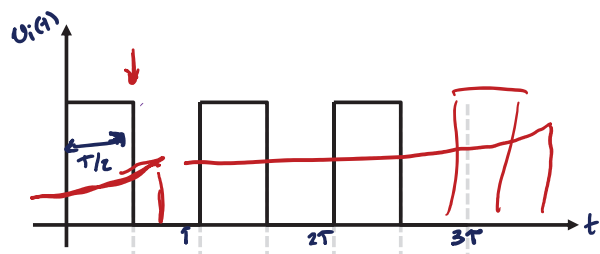

$$v_o(t) = \sum_{k=0}^{\infty} (-1)^k \frac{R_2}{R_1} (1 - e^{-\frac{t-kT}{R_2C}}) u(t - k\frac{T}{2})$$

if $\frac{T}{2} \gg R_2C \rightarrow$ exponential goes through multiple time constants

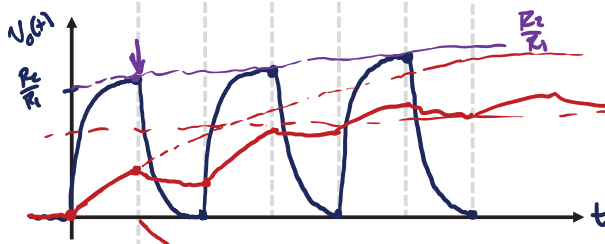if $\frac{T}{2} \ll R_2C \rightarrow$ exponential gets through less than 1 time constant



$$\frac{R_2}{R_1} \left(\frac{1}{2}\right)$$

$$H(s) = \frac{R_2}{R_1} \frac{1}{sR_2C + 1} = \frac{R_2}{R_1} \frac{\frac{1}{R_2C}}{s + \frac{1}{R_2C}}$$

$$h(t) = \mathcal{L}^{-1}\{H(s)\} = \frac{1}{R_1C} e^{-\frac{t}{R_2C}} u(t)$$

$$v_o(t) = \int_0^{\infty} h(t-\tau) v_i(\tau) d\tau$$

