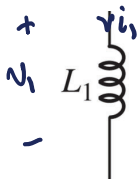


Energy Storage




Inductor: if $i_1 = \phi$ for $t < \phi$, then goes to I_x @ t_x

$$E_x = \int_0^{t_x} P_c(t) dt = \int_0^{t_x} v_1(t) i_1(t) dt = \int_0^{t_x} L_1 i_1(t) \frac{di_1(t)}{dt} dt$$

$$= L_1 \int_0^{t_x} \frac{1}{2} \left[\frac{d}{dt} i_1(t)^2 \right] dt = \frac{1}{2} L_1 \left[i_1(t)^2 \right] \Big|_0 = i_1(t=0)$$

$$= \frac{1}{2} L_1 I_x^2$$

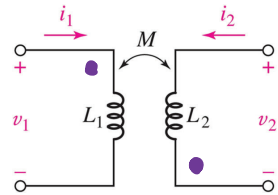

prior to time $t=0$
 $i_1 = 0$ & $i_2 = 0$
 then @ $t = t_x$
 $i_1 = I_{x1}$ & $i_2 = I_{x2}$

$$E_x = \int_0^{t_x} (i_1 v_1 + i_2 v_2) dt =$$

$$= \int_0^{t_x} \left(i_1 L_1 \frac{di_1}{dt} \pm i_1 M \frac{di_2}{dt} + i_2 L_2 \frac{di_2}{dt} \pm i_2 M \frac{di_1}{dt} \right) dt$$

$$= \frac{1}{2} L_1 I_{x1}^2 + \frac{1}{2} L_2 I_{x2}^2 \pm M \int_0^{t_x} \left(i_1 \frac{di_2}{dt} + i_2 \frac{di_1}{dt} \right) dt$$

$$= \frac{1}{2} L_1 I_{x1}^2 + \frac{1}{2} L_2 I_{x2}^2 \pm M \int_0^{t_x} \frac{d}{dt} (i_1 \cdot i_2) dt$$

$$E_x = \frac{1}{2} L_1 I_{x1}^2 + \frac{1}{2} L_2 I_{x2}^2 \pm M I_{x1} I_{x2}$$

\hookrightarrow depends on dot notation.

$$E_x = \frac{1}{2} L_1 I_{x1}^2 + \frac{1}{2} L_2 I_{x2}^2 - M I_{x1} I_{x2}$$

- Assume inverting winding polarity for the scenario described $E_x \geq \phi$ (otherwise its a source)

then

$$E_x = \frac{1}{2} L_1 I_{x1}^2 + \frac{1}{2} L_2 I_{x2}^2 - M I_{x1} I_{x2} \geq \phi$$

$$M \leq \frac{\frac{1}{2} L_1 I_{x1}^2 + \frac{1}{2} L_2 I_{x2}^2}{I_{x1} I_{x2}} = \frac{1}{2} L_1 \frac{I_{x1}}{I_{x2}} + \frac{1}{2} L_2 \frac{I_{x2}}{I_{x1}}$$

Must hold $\forall (I_{x1}, I_{x2})$

lets' substitute $x = \frac{I_{x1}}{I_{x2}}$

find $x = x_{min}$ to minimize $f(x)$

$$f(x) = \frac{1}{2} L_1 x + \frac{1}{2} L_2 \frac{1}{x}$$

$$f'(x) = \frac{1}{2} L_1 - \frac{1}{2} L_2 \frac{1}{x^2} = 0 \rightarrow x_{min} = \sqrt{\frac{L_2}{L_1}}$$

$$f''(x) = L_2 \frac{1}{x^3}$$

$$M \leq \frac{1}{2} L_1 \sqrt{\frac{L_2}{L_1}} + \frac{1}{2} L_2 \frac{1}{\sqrt{\frac{L_2}{L_1}}} \rightarrow M \leq \sqrt{L_1 L_2}$$

Coupling Coefficient

$M \leq \sqrt{L_1 L_2}$ → must hold for any physically realizable element
 one check: let's consider two identical inductors perfectly overlapped

→ $L_1 = L_2 = L$ $M \leq \sqrt{L_1 L_2} = \sqrt{L \cdot L} = L$

justification: recall $L_1 = k_{11} N_1^2$, $L_2 = k_{22} N_2^2$, $M = k_{12} N_1 N_2$

In this perfectly matched case, $L_1 = L_2 = M$

Define $k = \frac{M}{\sqrt{L_1 L_2}}$ → "coupling coefficient"

$0 \leq k \leq 1$ {
 $k = 0$ → two separate inductors
 \vdots → partial coupling
 $k = 1$ → perfect coupling → "transformer"

Transformers

special case of coupled inductors where $k \approx 1 \Leftrightarrow M \approx \sqrt{L_1 L_2}$

$$\left. \begin{aligned} V_1 &= L_1 \frac{di_1}{dt} \pm \sqrt{L_1 L_2} \frac{di_2}{dt} \\ V_2 &= L_2 \frac{di_2}{dt} \pm \sqrt{L_1 L_2} \frac{di_1}{dt} \end{aligned} \right\} V_1 = V_2 \left(\frac{\sqrt{L_1 L_2}}{L_2} \right)$$

$$V_1 = V_2 \sqrt{\frac{L_1}{L_2}}$$

$$V_1 = V_2 \sqrt{\frac{L_1 N_1^2}{L_2 N_2^2}}$$

if $k = 1$, $k_{11} = k_{22}$

$$V_1 = V_2 \frac{N_1}{N_2}$$