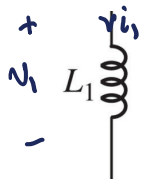


Energy Storage




Inductor: if $i_1 = 0$ for $t < 0$, then goes to I_x @ t_x

$$E_x = \int_0^{t_x} P_1(t) dt = \int_0^{t_x} v_1(t) i_1(t) dt = \int_0^{t_x} L_1 i_1(t) \frac{di_1(t)}{dt} dt$$

$$= L_1 \int_0^{t_x} \frac{1}{2} \left[\frac{d}{dt} i_1(t)^2 \right] dt = \frac{1}{2} L_1 \left[i_1(t)^2 \right] \Big|_0 = i_1(t_x)$$

$$= \frac{1}{2} L_1 I_x^2$$

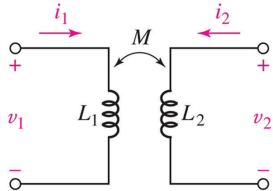







Coupling Coefficient

Transformers

Ideal Transformer

Equivalent Circuits

Equivalent Circuits

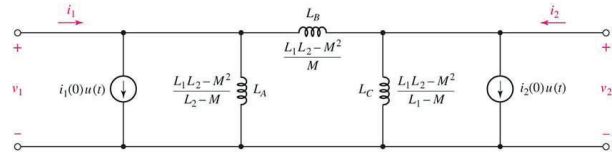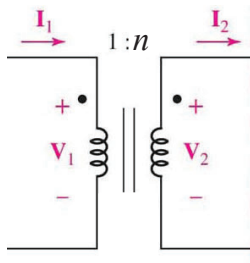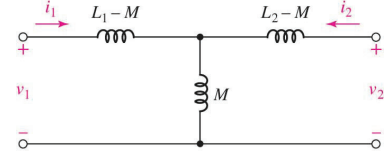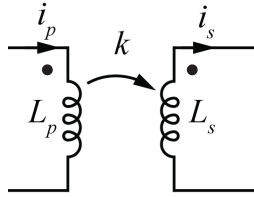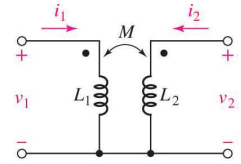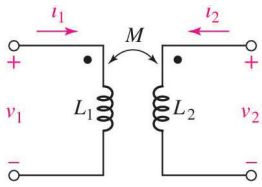

Transformer Reflection

Applications of Coupled Inductors

