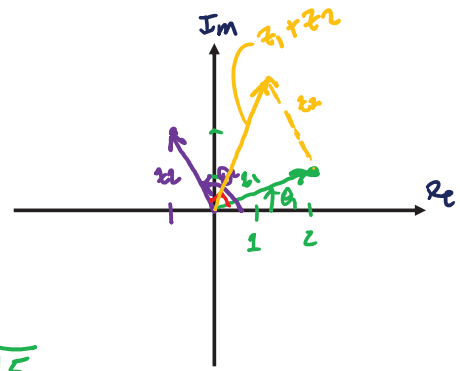


Complex Numbers

$$z = x + jy = r e^{j\theta}$$

$x = \text{Re}\{z\}$ "real part" $y = \text{Im}\{z\}$ "imaginary part"
 $r = |z|$ magnitude $\theta = \angle z$ phase



Complex numbers can represent vectors in 2D

Rect: (x, y)

Polar: (r, θ)

$$z_1 = 2 + j1 = \sqrt{5} e^{j \tan^{-1}(\frac{1}{2})}$$

$$\theta_1 = \tan^{-1}(\frac{1}{2}) \quad r = \sqrt{5}$$

$$z_2 = jz_1 = z_1 \cdot j = (-1 + j2)$$

$$j = 0 + j1 = 1 e^{j \tan^{-1}(\frac{1}{0})} = e^{j \frac{\pi}{2}}$$

$$z_2 = jz_1 = e^{j \frac{\pi}{2}} \cdot z_1 = e^{j \frac{\pi}{2}} \sqrt{5} e^{j \theta_1} = \sqrt{5} e^{j(\frac{\pi}{2} + \theta_1)}$$

→ multiplying a complex number by j is a 90° phase shift

Addition:

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

Multiply

$$z_1 \cdot z_2 = (r_1 e^{j\theta_1}) (r_2 e^{j\theta_2}) = r_1 r_2 e^{j(\theta_1 + \theta_2)}$$



Sinusoids as Complex Numbers

$$v(t) = A \cos(\omega t + \phi)$$

$$= \text{Re} \{ A e^{j(\omega t + \phi)} \}$$

$$= \text{Re} \{ A e^{j\phi} e^{j\omega t} \}$$

project onto Real axis = cos
 amplitude
 phase
 sinusoid


Euler: $e^{j\theta} = \cos\theta + j\sin\theta$
 $\cos\theta = \text{Re} \{ e^{j\theta} \}$


$$\frac{d}{dt} v(t) = -A\omega \sin(\omega t + \phi) = \omega A \cos(\omega t + \phi + 90^\circ)$$

$$= \text{Re} \{ \omega A e^{j(\omega t + \phi + \frac{\pi}{2})} \}$$

$$= \text{Re} \{ \omega A e^{j\frac{\pi}{2}} e^{j\phi} e^{j\omega t} \}$$
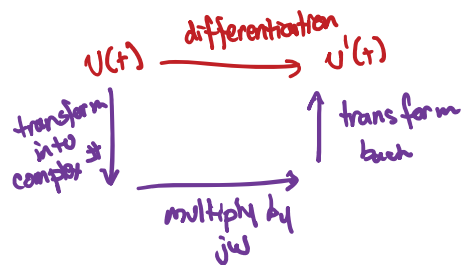
$$= \text{Re} \{ j\omega A e^{j\phi} e^{j\omega t} \}$$



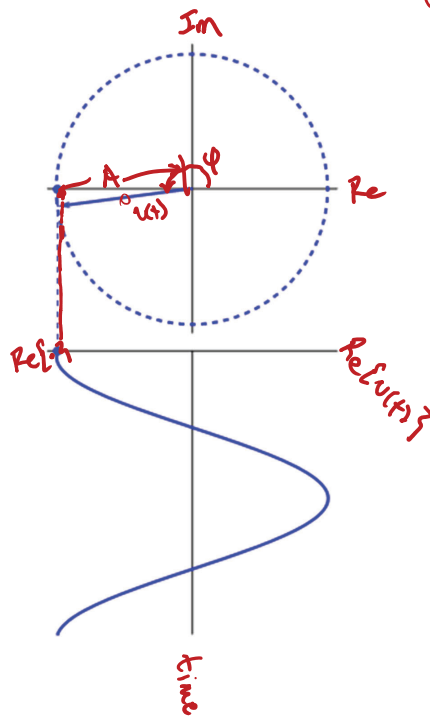

$u(t) = \text{Re}\{Ae^{j\omega t}e^{j\phi}\}$
 at $t=0$ $e^{j\omega 0} = 1$
 $e^{j\omega t} \rightarrow$ has magnitude 1
 phase is zero @ $t=0$
 as t goes $0 \rightarrow \frac{2\pi}{\omega} = \frac{1}{f} = T$
 phase of $e^{j\omega t}$: $0 \rightarrow 2\pi$

Phasor Transformation

Phasor: A complex vector that represents a sinusoid

$A \cos(\omega t + \phi)$

- Amplitude A
- Phase ϕ
- ~~frequency ω~~ \rightarrow known for single-frequency problem
- ~~function \cos/\sin~~ \rightarrow by convention, everything is a cos


$u(t) = A \cos(\omega t + \phi) = \text{Re}\{Ae^{j\phi}e^{j\omega t}\}$

phasor transform
 $\underline{V} = Ae^{j\phi}$ \longleftrightarrow $A \angle \phi$
 (Bold in book)

$v_2(t) = B \sin(\omega t + \theta)$
 $= B \cos(\omega t + \theta - 90^\circ)$

$\underline{V}_2 = B e^{j(\theta - \frac{\pi}{2})} \Leftrightarrow B \angle (\theta - \frac{\pi}{2})$

Phasor Circuit Elements

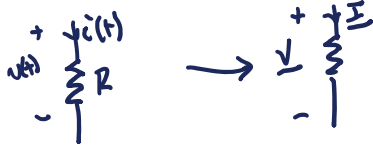

$$v(t) = A \cos(\omega t + \phi)$$


$$i(t) = \frac{A}{R} \cos(\omega t + \phi)$$

$$v(t) = i(t)R$$

$$\underline{V} = A e^{j\phi}$$

$$\underline{I} = \frac{A}{R} e^{j\phi}$$

$$\underline{V} = \underline{I} R$$

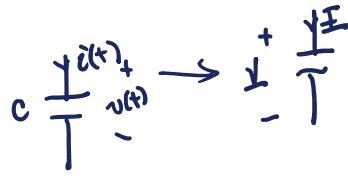

$$v(t) = A \cos(\omega t + \phi)$$

$$i(t) = -CA\omega \sin(\omega t + \phi)$$

$$= CA\omega \cos(\omega t + \phi + 90^\circ)$$

$$i(t) = C \frac{dv}{dt}$$

$$\underline{V} = A e^{j\phi}$$


$$\underline{I} = CA\omega e^{j(\phi + \frac{\pi}{2})}$$

$$= CA\omega e^{j\phi} e^{j\frac{\pi}{2}}$$

$$= CA\omega j e^{j\phi}$$

$$\underline{V} = \underline{I} \frac{1}{j\omega C}$$

same process

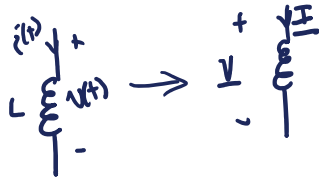

$$\underline{V} = \underline{I} j\omega L$$