

Extra Credit Problem #1:

An ideal boost converter is shown in Fig. 1.

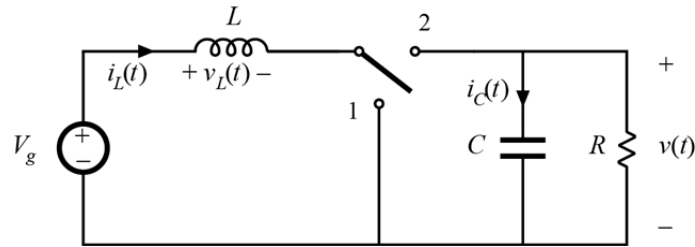


Fig. 1: Ideal Boost Converter

For the converter operating in steady-state, derive *exact* (i.e. without approximation) analytical expressions for the following in terms of the circuit parameters V_g , R , T_s , L , C and duty cycle D .

- The DC component of the output voltage
- The peak-to-peak inductor current ripple
- The peak-to-peak capacitor voltage ripple

No partial credit will be awarded. Answers which employ the small-ripple approximation will not receive credit on this problem.