

Chapter 8: Converter Transfer Functions

8.1. Review of Bode plots

- 8.1.1. Single pole response
- 8.1.2. Single zero response
- 8.1.3. Right half-plane zero
- 8.1.4. Frequency inversion
- 8.1.5. Combinations
- 8.1.6. Double pole response: resonance
- 8.1.7. The low-Q approximation
- 8.1.8. Approximate roots of an arbitrary-degree polynomial

8.2. Analysis of converter transfer functions

- 8.2.1. Example: transfer functions of the buck-boost converter
- 8.2.2. Transfer functions of some basic CCM converters
- 8.2.3. Physical origins of the right half-plane zero in converters

Converter Transfer Functions

8.3. Graphical construction of converter transfer functions

8.3.1. Series impedances: addition of asymptotes

8.3.2. Parallel impedances: inverse addition of asymptotes


8.3.3. Another example

8.3.4. Voltage divider transfer functions: division of asymptotes

8.4. Measurement of ac transfer functions and impedances

8.5. Summary of key points


Buck Boost Model

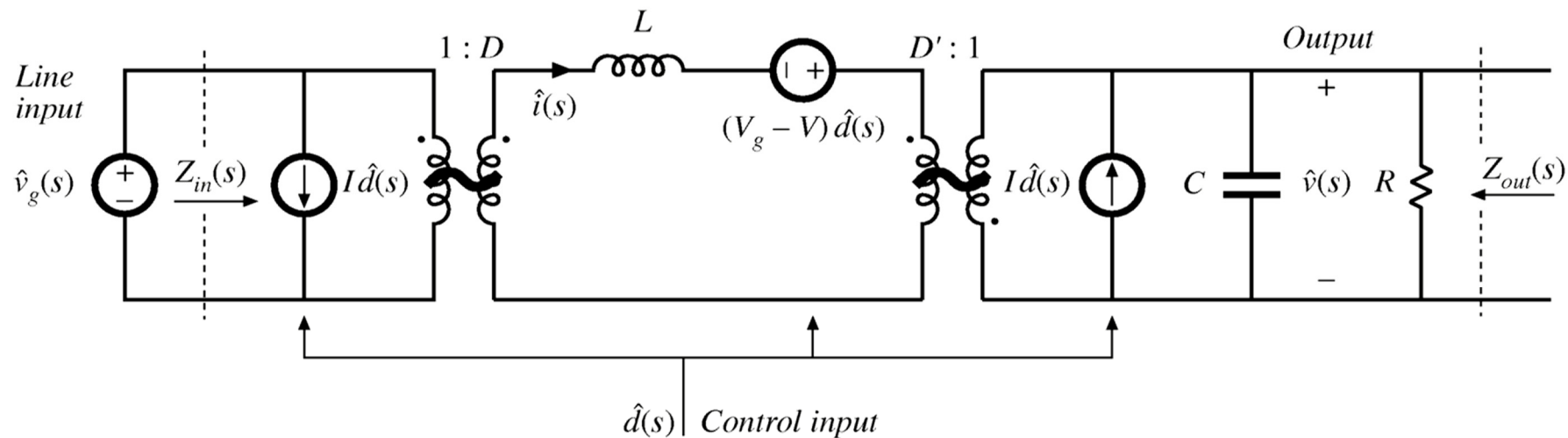

$$G_{vg}(s) = \left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\hat{d}(s)=0}$$


$$G_{vd}(s) = \left. \frac{\hat{v}(s)}{\hat{d}(s)} \right|_{\hat{v}_g(s)=0}$$

Buck-Boost Control-to-Output TF

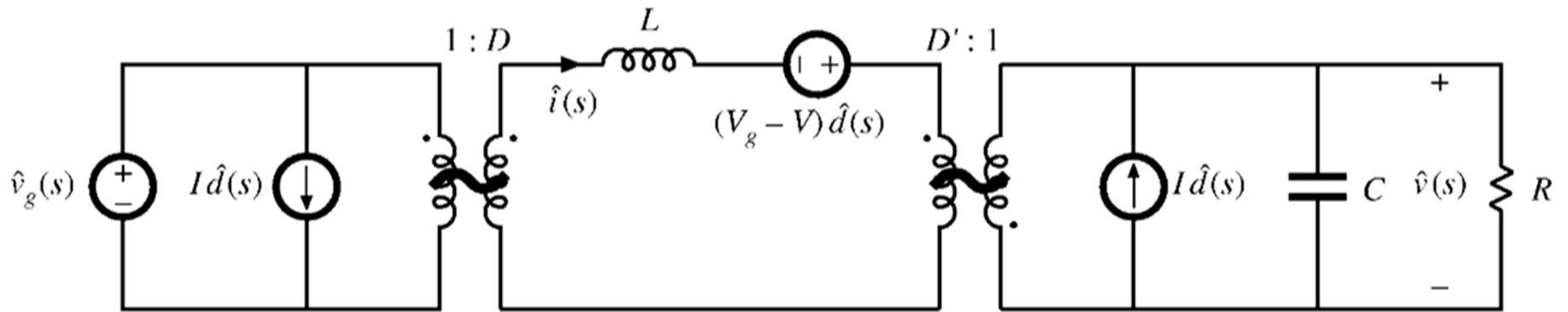

Buck-Boost Control-to-Output TF

Control-to-output Transfer Function

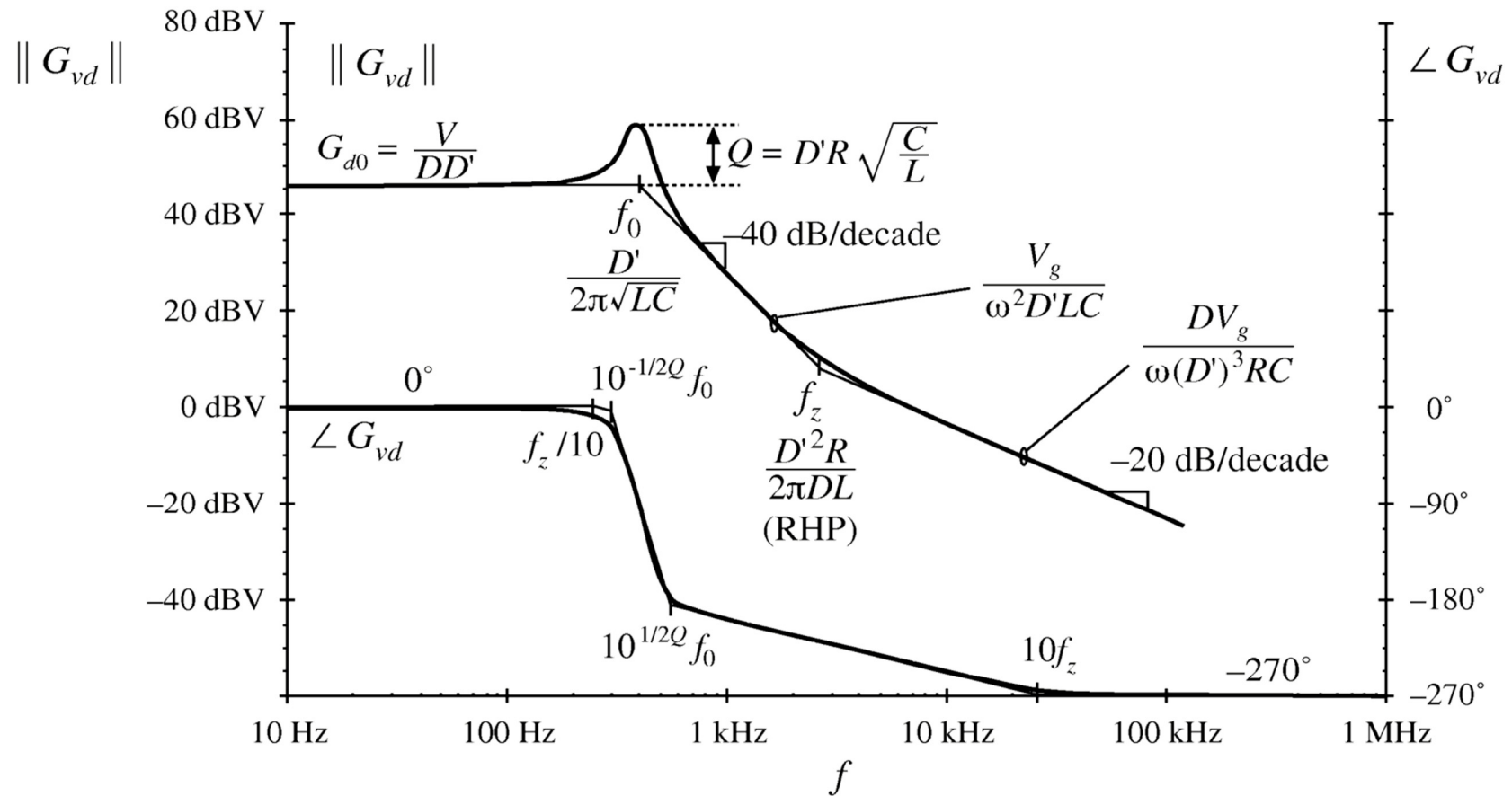

Design-Oriented Analysis

How to approach a real (and hence, complicated) system

Problems:

- Complicated derivations

- Long equations

- Algebra mistakes

Design objectives:

- Obtain physical insight which leads engineer to synthesis of a good design

- Obtain simple equations that can be inverted, so that element values can be chosen to obtain desired behavior. Equations that cannot be inverted are useless for design!

Design-oriented analysis is a structured approach to analysis, which attempts to avoid the above problems

Chapter 8: Design-Oriented Analysis

- Writing transfer functions in normalized form, to directly expose salient features
- Obtaining simple analytical expressions for asymptotes, corner frequencies, and other salient features, allows element values to be selected such that a given desired behavior is obtained
- Use of inverted poles and zeroes, to refer transfer function gains to the most important asymptote
- Analytical approximation of roots of high-order polynomials
- Graphical construction of Bode plots of transfer functions and polynomials, to
 - avoid algebra mistakes
 - approximate transfer functions
 - obtain insight into origins of salient features

8.1 Review of Bode Plots

Decibels

$$\|G\|_{\text{dB}} = 20 \log_{10}(\|G\|)$$

Decibels of quantities having units (impedance example): normalize before taking log

$$\|Z\|_{\text{dB}} = 20 \log_{10}\left(\frac{\|Z\|}{R_{\text{base}}}\right)$$

Table 8.1. Expressing magnitudes in decibels

<i>Actual magnitude</i>	<i>Magnitude in dB</i>
1/2	- 6dB
1	0 dB
2	6 dB
5 = 10/2	20 dB - 6 dB = 14 dB
10	20dB
1000 = 10 ³	3 · 20dB = 60 dB

5Ω is equivalent to 14dB with respect to a base impedance of $R_{\text{base}} = 1\Omega$, also known as 14dBΩ.


60dBμA is a current 60dB greater than a base current of 1μA, or 1mA.

Logarithm Review

Plotting on Logarithmic Axes



Single Pole Response

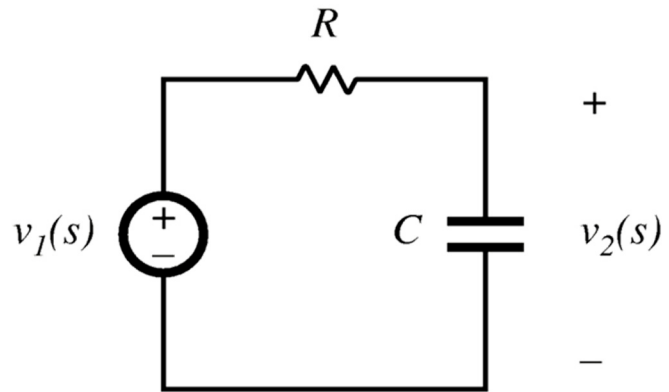


Magnitude of Single Pole Response

Plotting a Single Pole Response



Exact response near $f = f_0$


Summary: Single Pole Magnitude

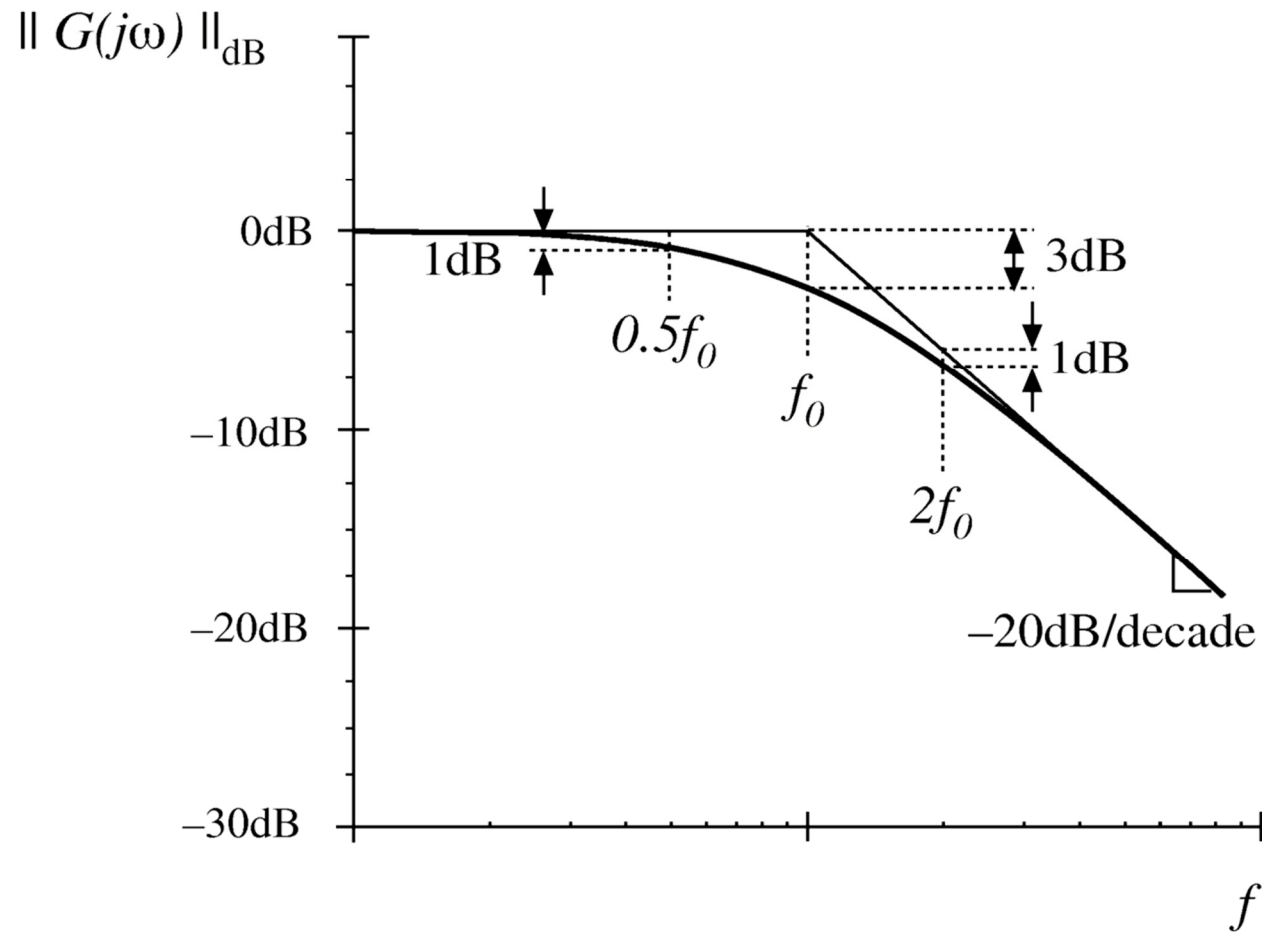


Phase of Single Pole

Phase Asymptotes

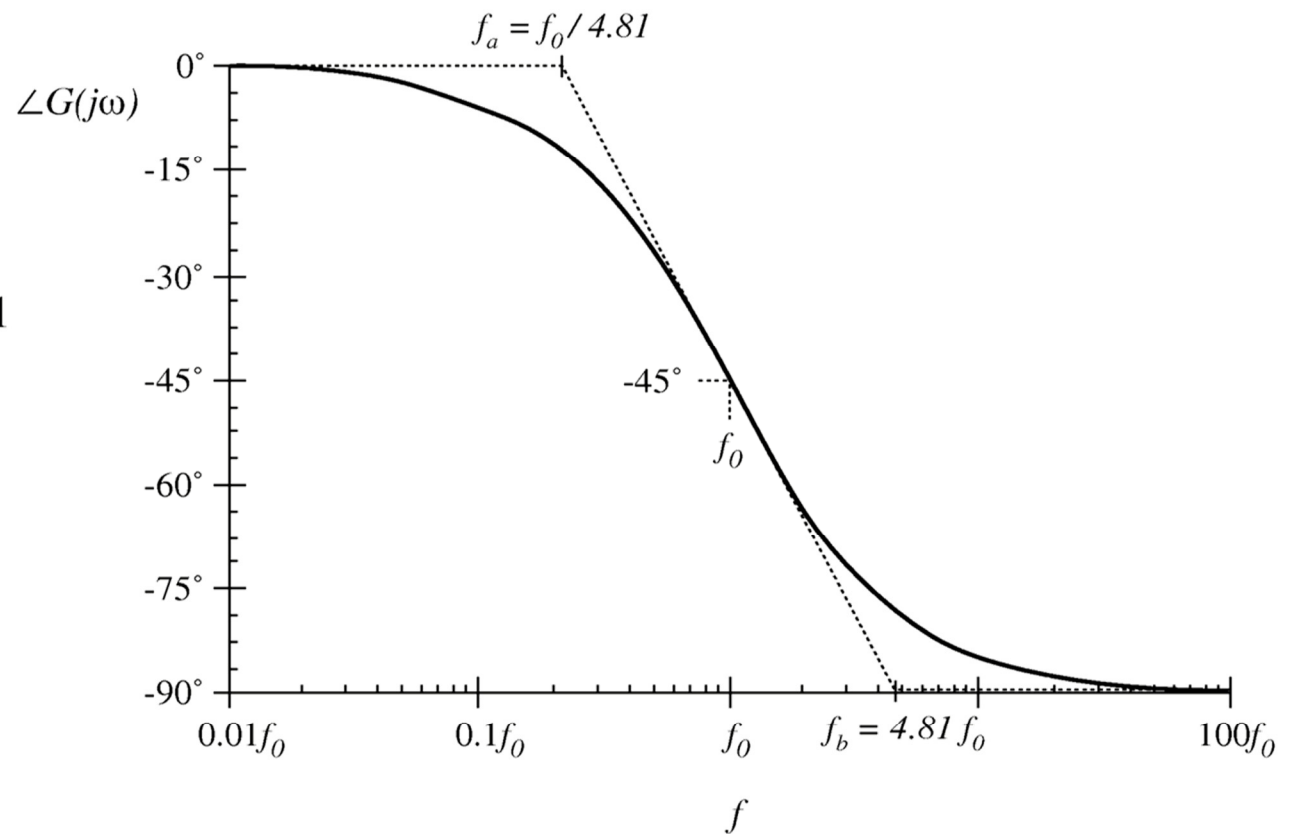
$$f_a = f_0 e^{-\pi/2} \approx f_0 / 4.81$$
$$f_b = f_0 e^{\pi/2} \approx 4.81 f_0$$



Phase Asymptotes: A Simpler Choice

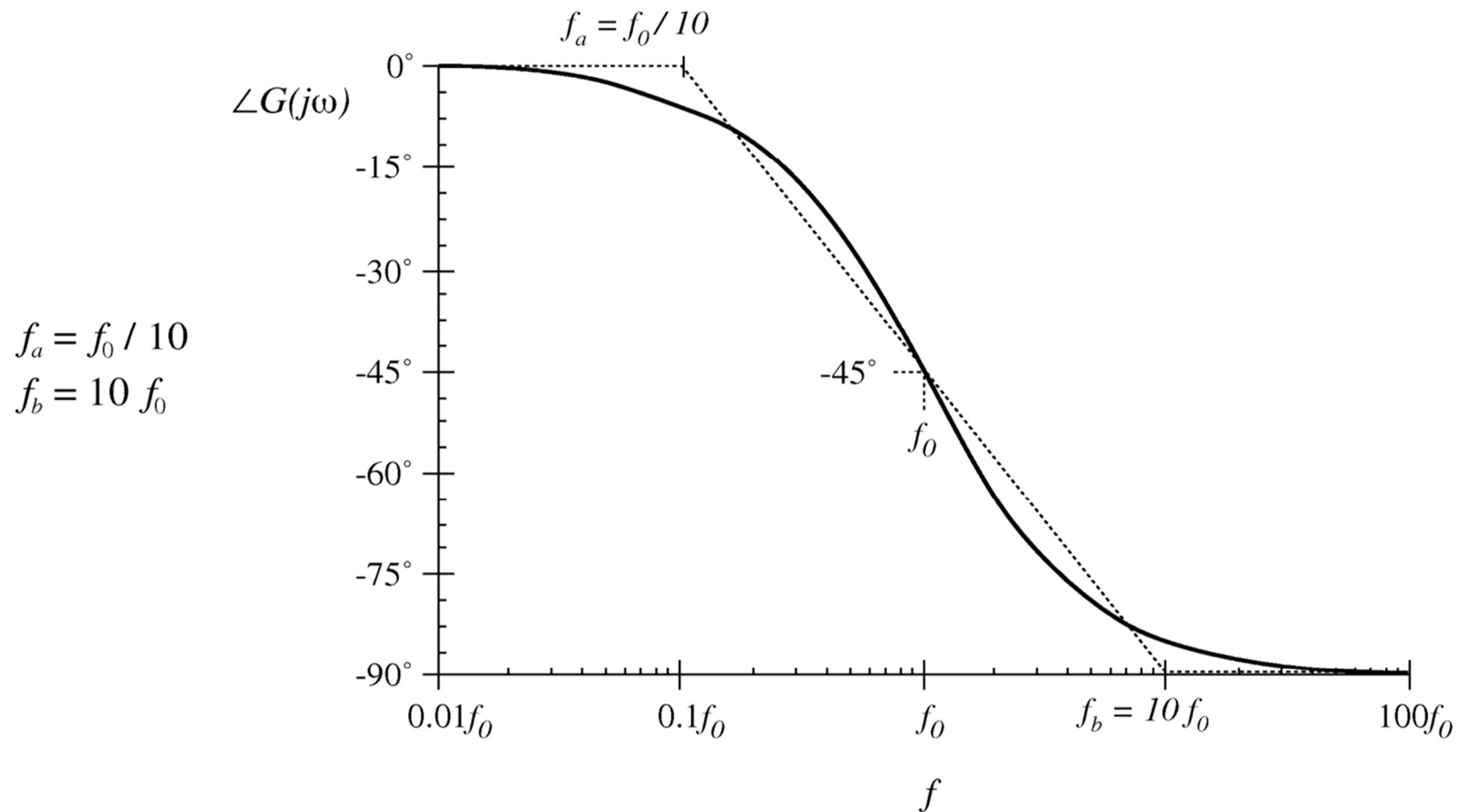


Summary: Single Real Pole

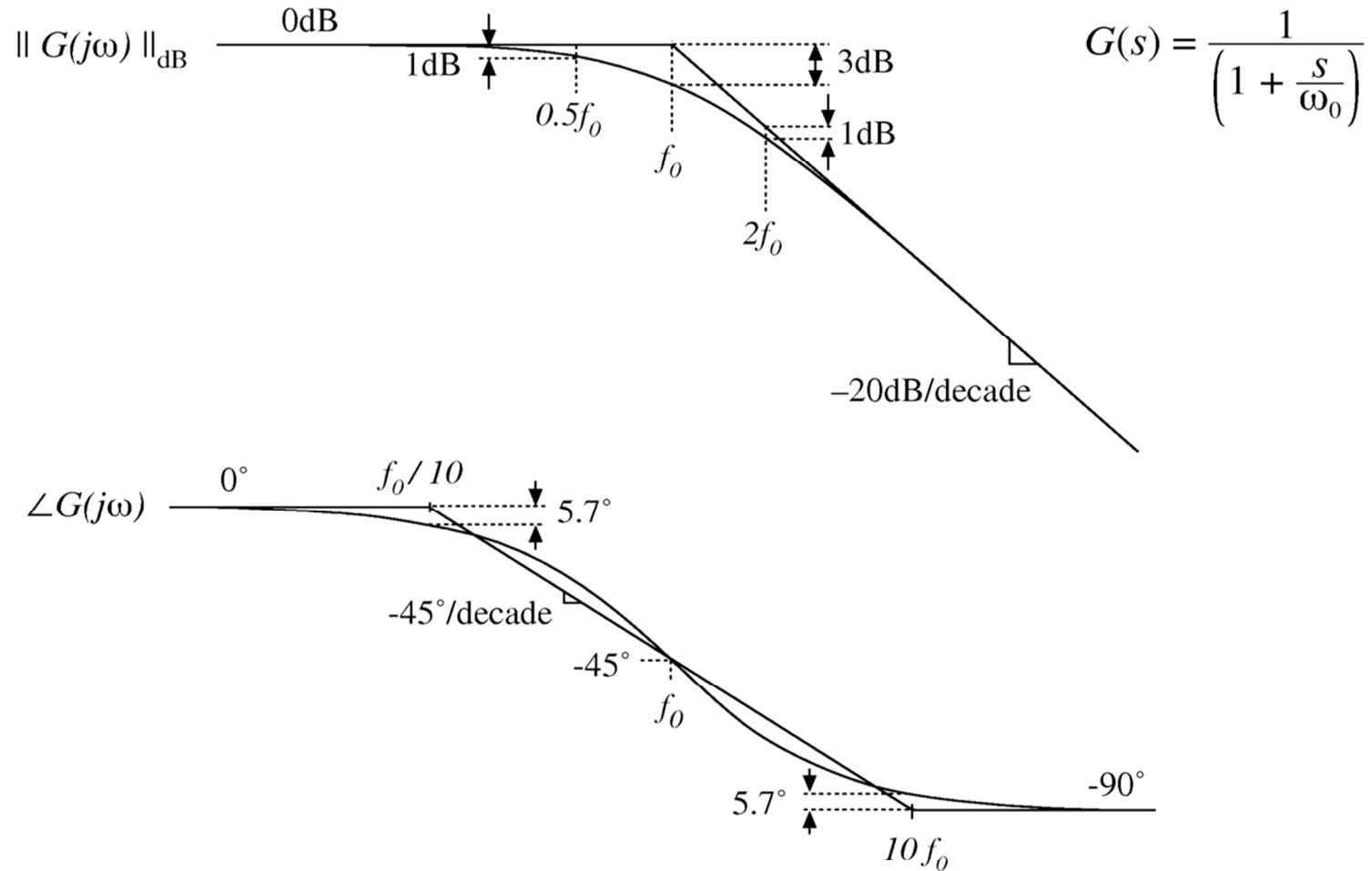


Bode Plot: Real Zero
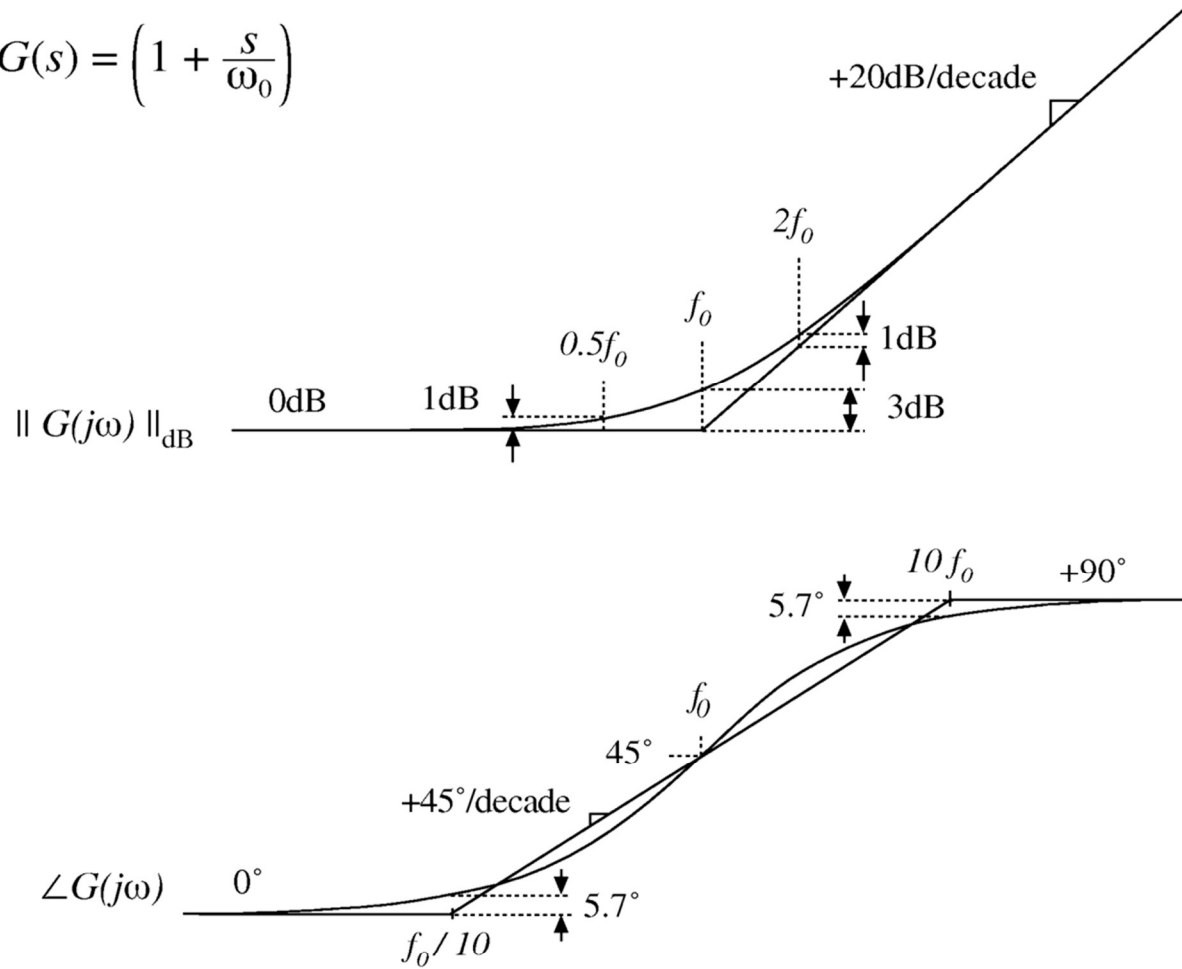
$$G(s) = \left(1 + \frac{s}{\omega_0}\right)$$




RHP Zero
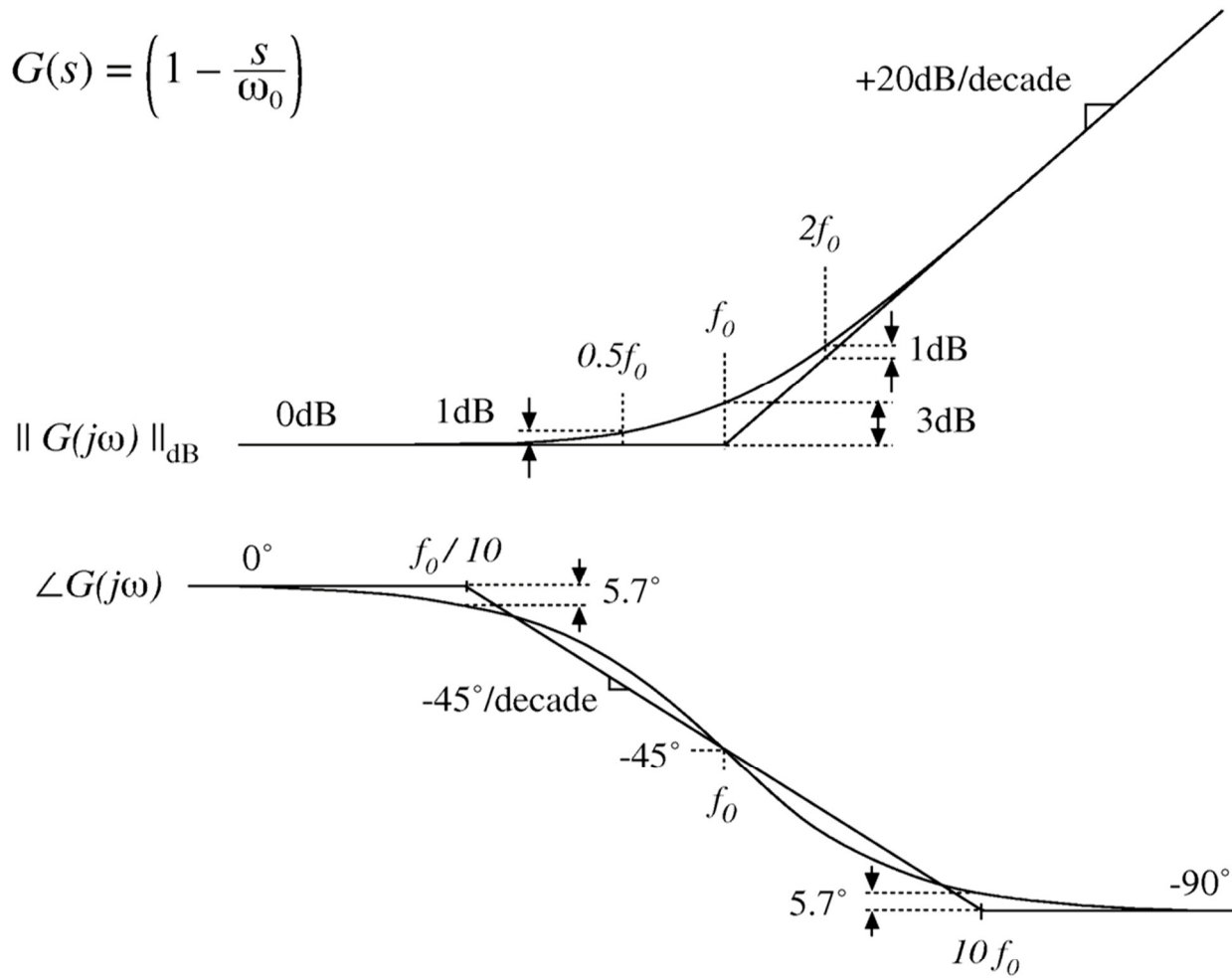
$$G(s) = \left(1 - \frac{s}{\omega_0}\right)$$



Inverted Pole

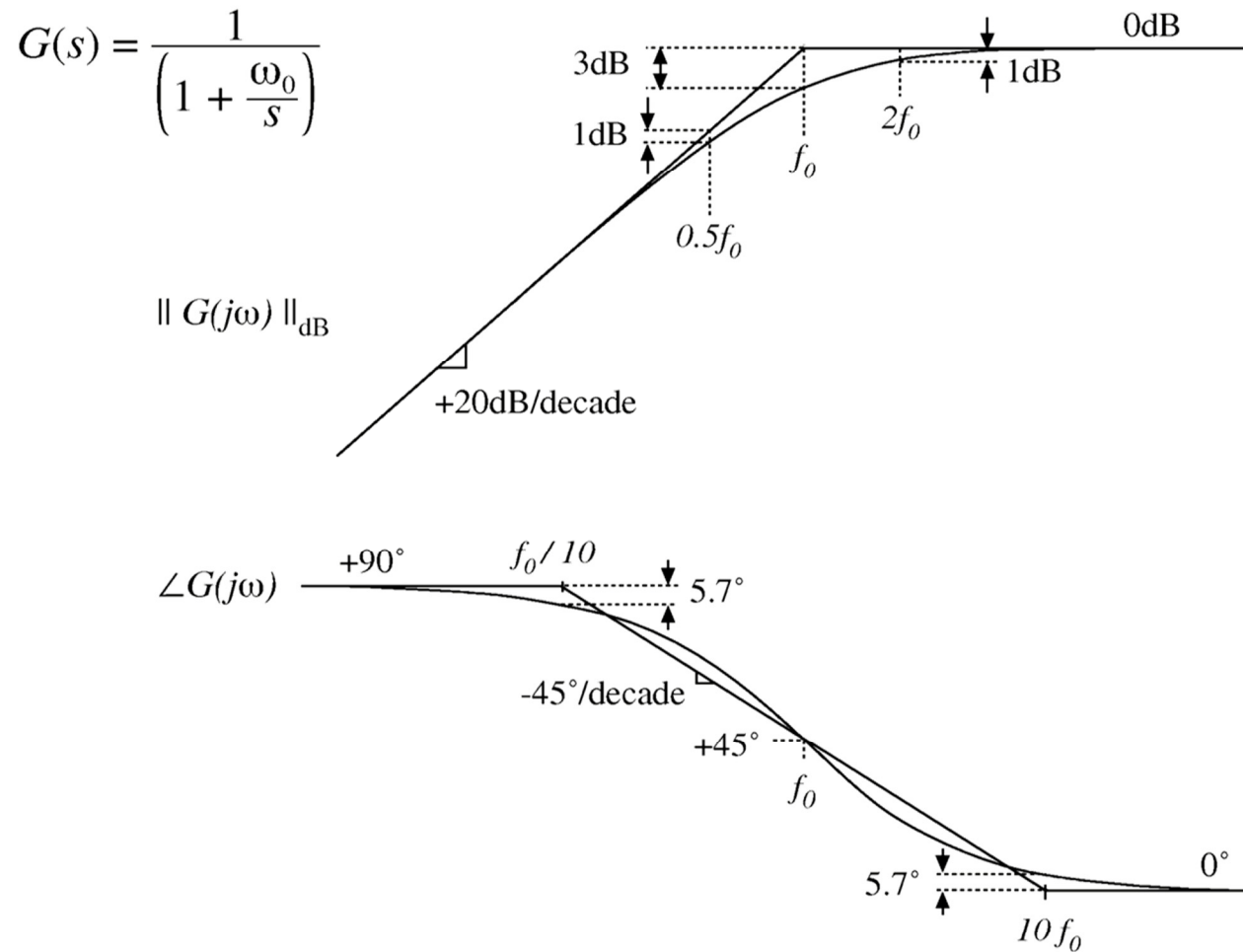

Inverted Zero

