

# Derivation of Volt-second Balance

Inductor defining relation:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Integrate over one complete switching period:

$$i_L(T_s) - i_L(0) = \frac{1}{L} \int_0^{T_s} v_L(t) dt$$

In periodic steady state, the net change in inductor current is zero:

$$0 = \int_0^{T_s} v_L(t) dt$$


Hence, the total area (or volt-seconds) under the inductor voltage waveform is zero whenever the converter operates in steady state.

An equivalent form:


$$0 = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \langle v_L \rangle$$

The average inductor voltage is zero in steady state.
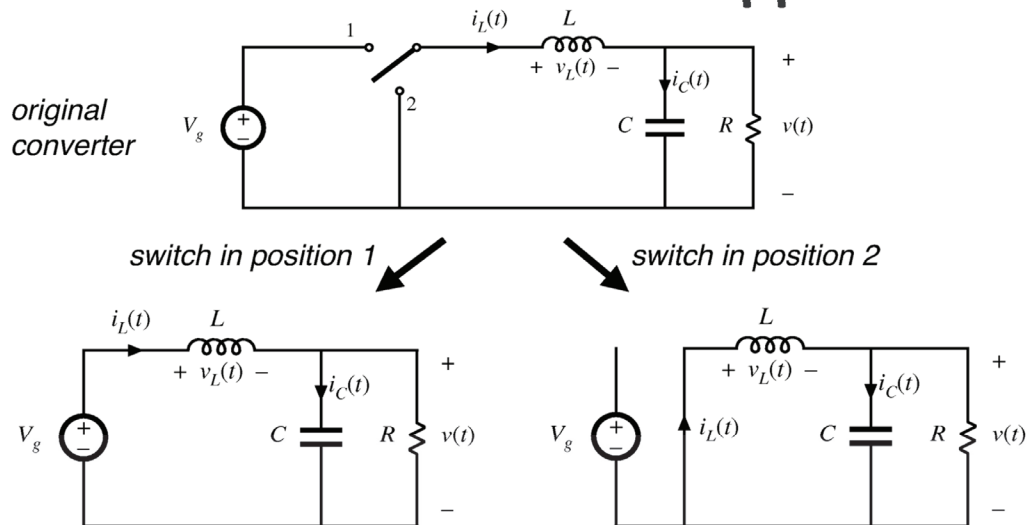
## Volt-Second Balance: Direct Application




# Current Ripple Magnitude

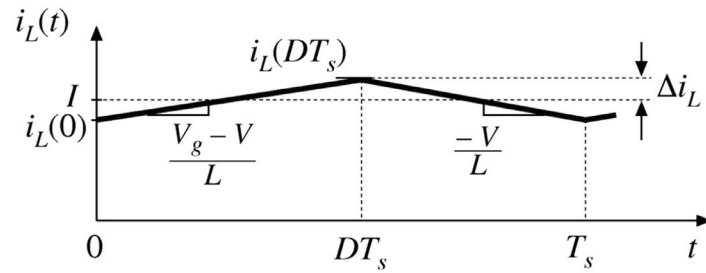

$$(\text{change in } i_L) = (\text{slope})(\text{length of subinterval})$$

# Buck Cap Charge Balance

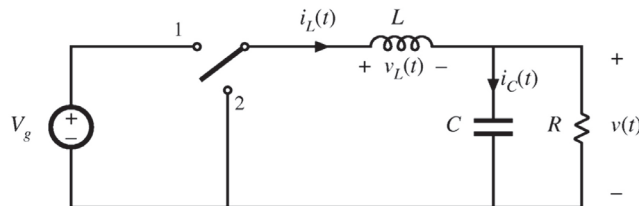

# Derivation of Capacitor Charge Balance

Capacitor defining relation:

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

Integrate over one complete switching period:

$$v_c(T_s) - v_c(0) = \frac{1}{C} \int_0^{T_s} i_c(t) dt$$


In periodic steady state, the net change in capacitor voltage is zero:

$$0 = \frac{1}{T_s} \int_0^{T_s} i_c(t) dt = \langle i_c \rangle$$


Hence, the total area (or charge) under the capacitor current waveform is zero whenever the converter operates in steady state. The average capacitor current is then zero.

## The Boost Converter


Boost converter  
with ideal switch

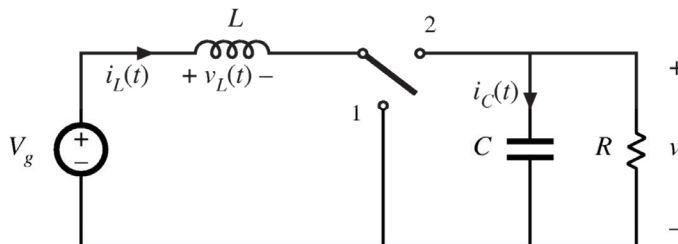

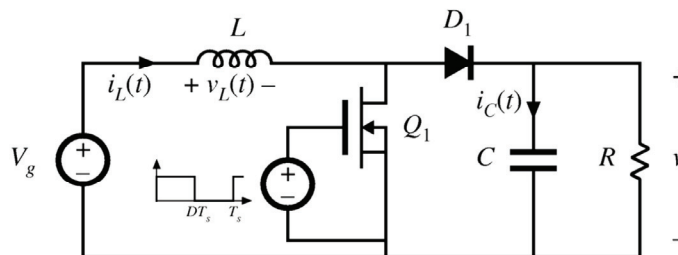
Realization using  
power MOSFET  
and diode




# Boost Subintervals

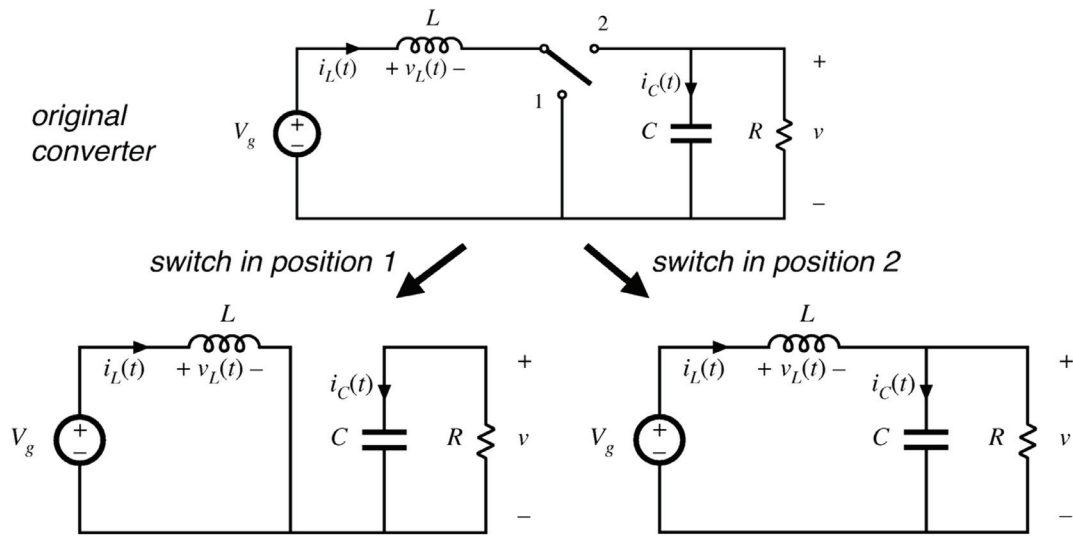



## Boost: Subinterval 1

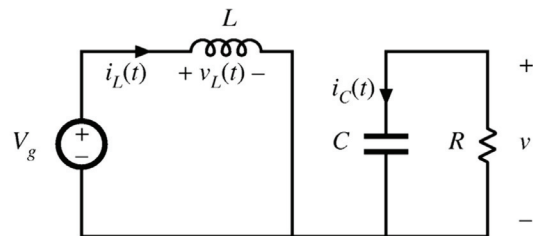

# Boost: Subinterval 2

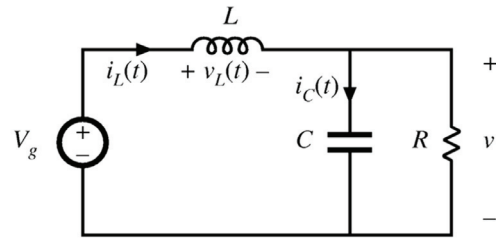

## Waveforms

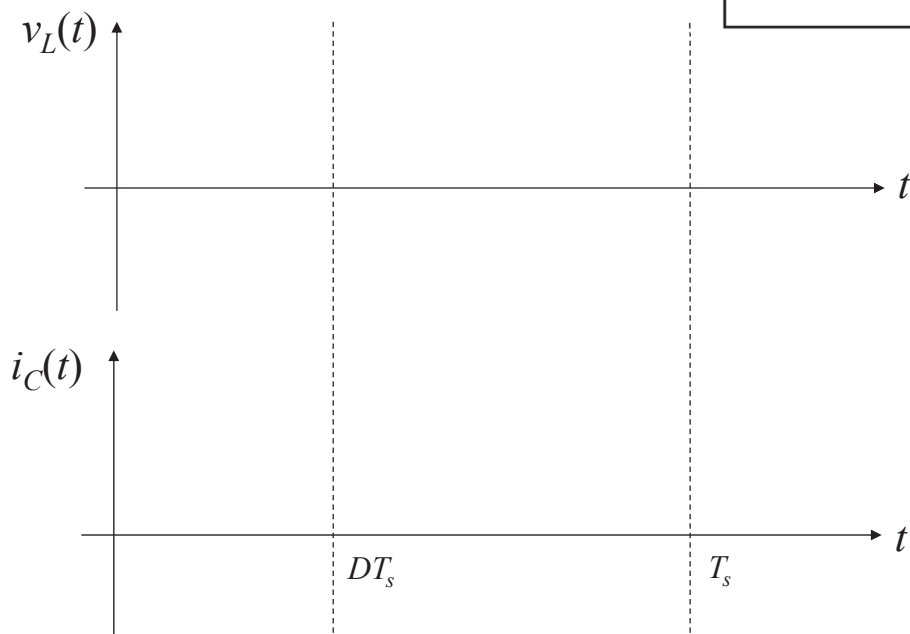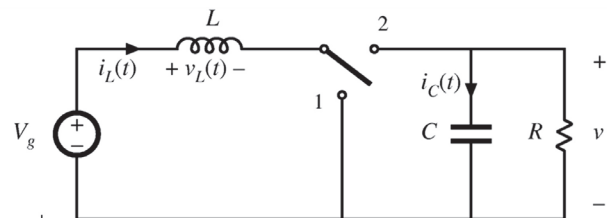

# Steady State Solution

## Boost: Conversion Ratio

