



---

# PCB Layout



ECE 482 Lecture 10  
February 28, 2014






---
 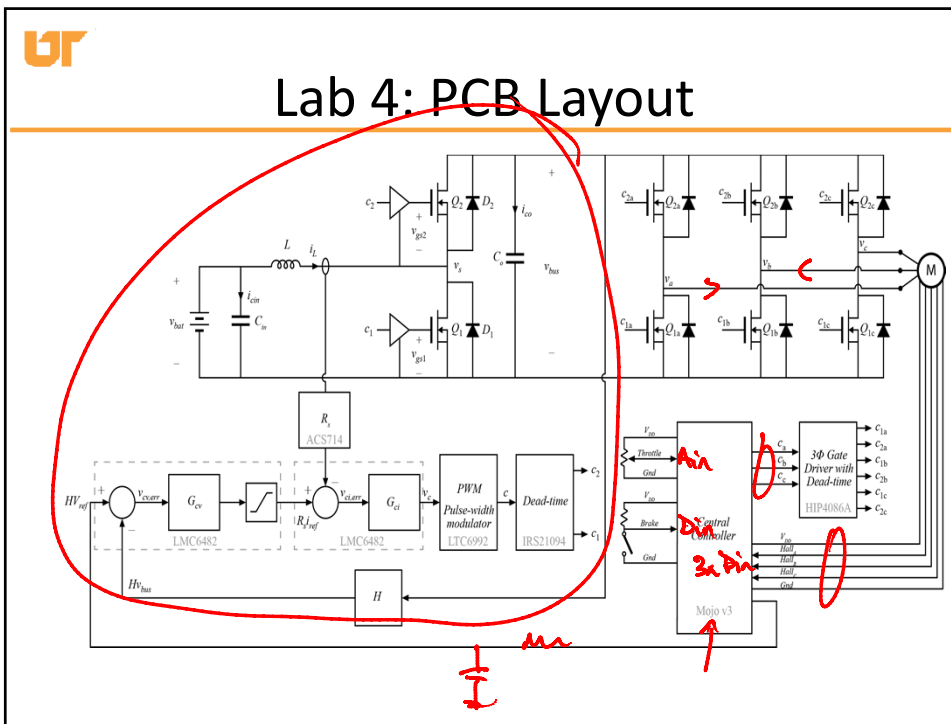
# Announcements

- Prelab 4 due Friday
  - Decide on System Improvements
- Next week:
  - Demo closed-loop Voltage Regulation
  - Begin PCB Layout ASAP. Designs due Wed. Mar 12<sup>th</sup>.



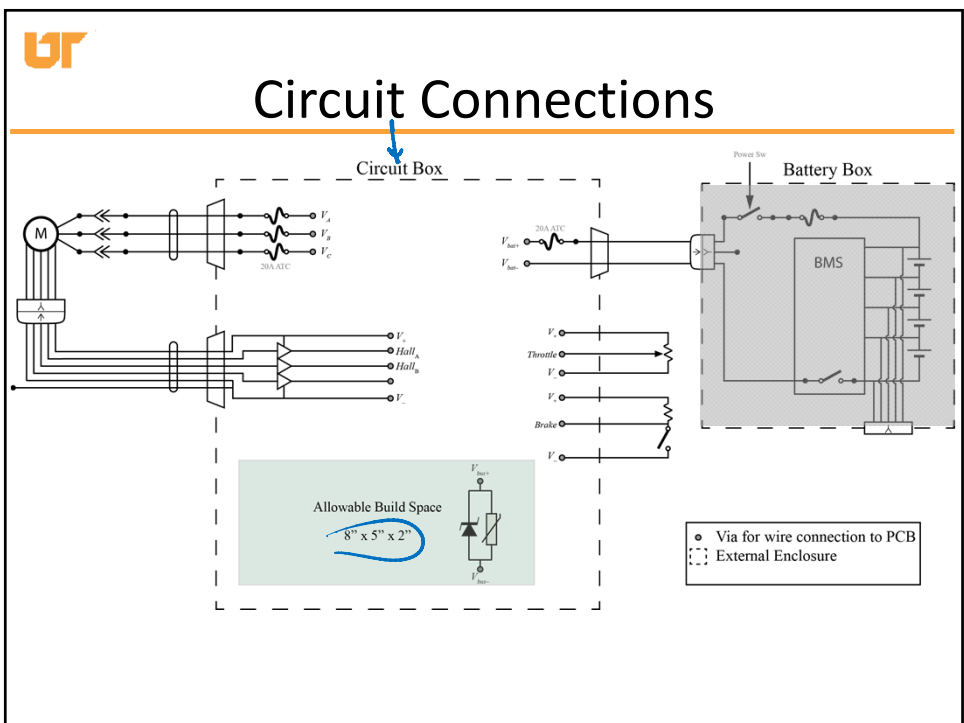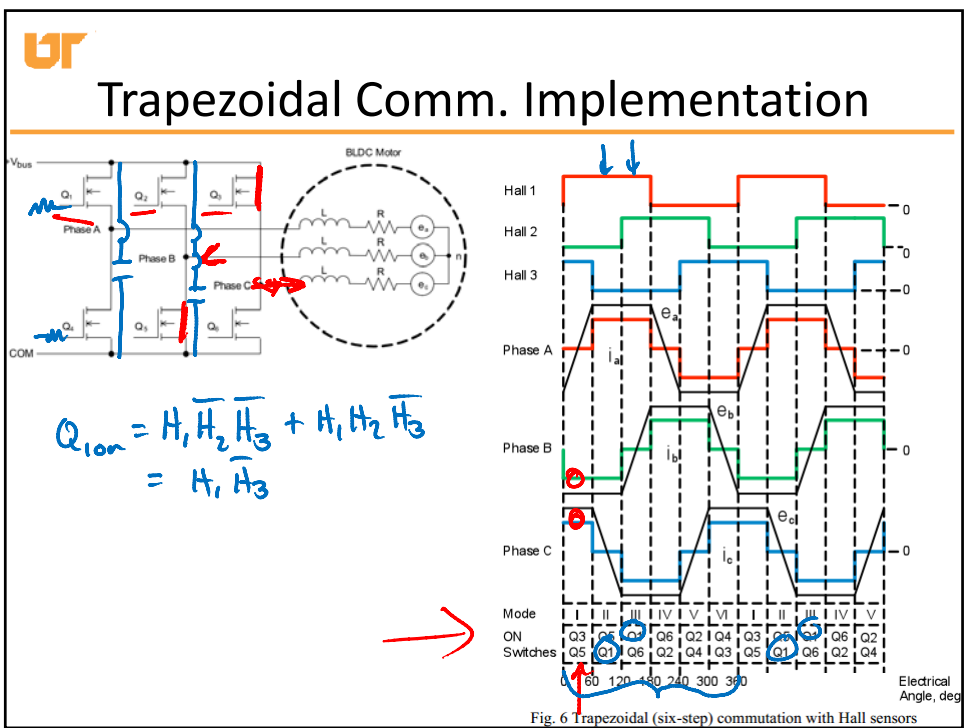

 

## Basic PCB Layout Concepts


- Trace Resistances
- Kelvin Sensing
- Loop Inductances / Decoupling
- Ground Plane / Return Currents
- Partitioning



## Trace Resistance

$$R = \frac{\rho Z}{XY}$$

$\rho$  = RESISTIVITY

 

SHEET RESISTANCE CALCULATION FOR  
1 OZ. COPPER CONDUCTOR:

$$\rho = 1.724 \times 10^{-6} \Omega \text{cm} \quad Y = 0.0036 \text{cm}$$

$$R = 0.48 \frac{\text{m}\Omega}{X}$$

$$\frac{Z}{X} = \text{NUMBER OF SQUARES}$$

$$R = \text{SHEET RESISTANCE OF 1 SQUARE (Z=X)} \\ = 0.48 \text{m}\Omega/\text{SQUARE}$$

Figure 12.2: Calculation of Sheet Resistance and Linear Resistance  
for Standard Copper PCB Conductors



## Trace Sizing Rough Guidelines

### 2.2 PCB Etch

Table 1 is helpful to determine the current carrying capacity of PCB etches. The table assumes:



- 1oz/sq foot copper (0.035mm thickness).
- 10°C rise on outer layers, ~~20°C inner layers~~ *2-layer PCB*
- Groups of high current tracks are de-rated
- Tracks are not near or over heat sink areas

Table 1. Current Capacity PCB Etch

WIDTH	CURRENT CAPACITY
0.010"	0.8 A
0.015"	1.2 A
0.020"	1.5 A
0.050"	3.2 A
0.100"	6.0 A
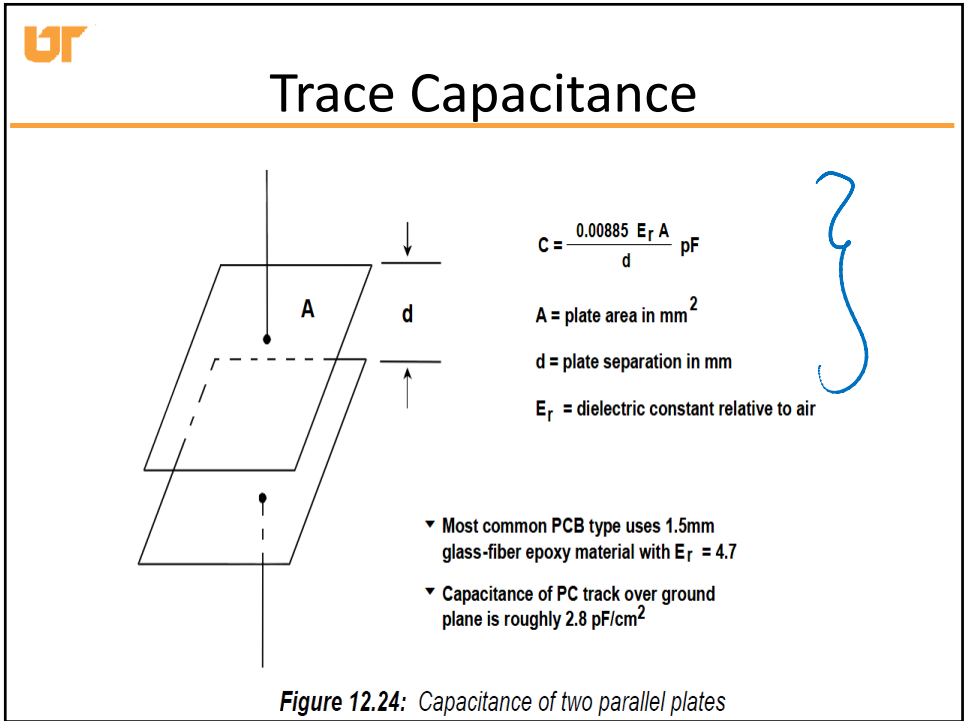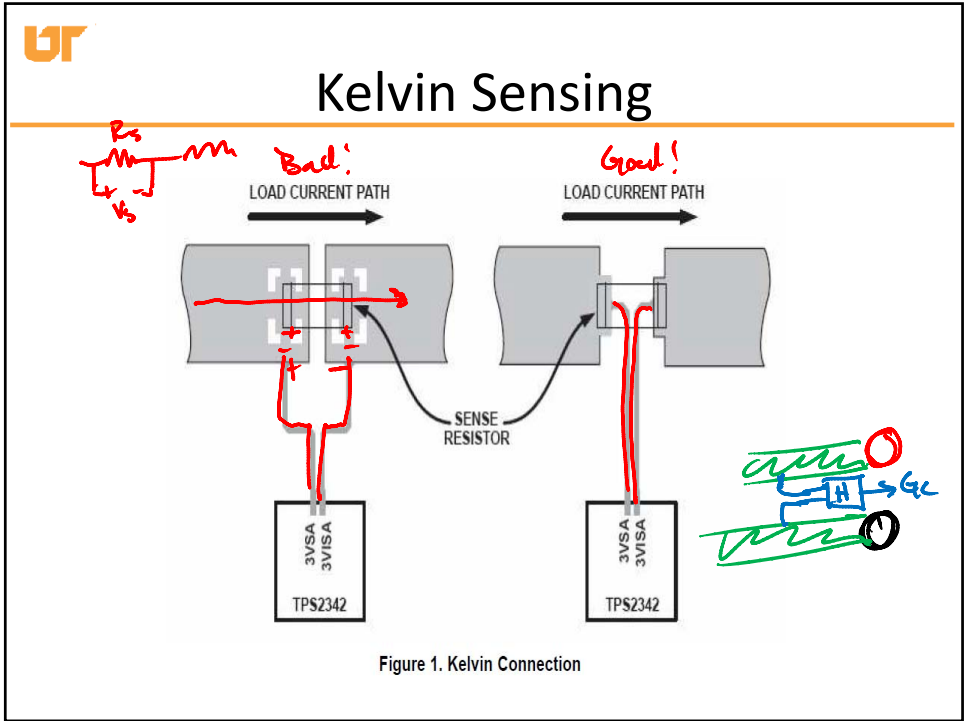
### 2.3 Vias or Feedthrus

Vias limit the current and add inductance between the power supply and load. Layouts are usually done with 10-mil inner ring feedthrus. At this size, current capability is about 1 A per feedthru.





## High Impedance Nodes and Capacitive Coupling

 


Figure 12.29 High Circuit Impedances Increase Susceptibility to Noise Pickup



## Capacitive Shielding

 


Figure 12.26: An Operational Model of a Faraday Shield




## Trace Inductance



$$\text{WIRE INDUCTANCE} = 0.0002L \left[ \ln \left( \frac{2L}{R} \right) - 0.75 \right] \mu\text{H}$$

 EXAMPLE: 1cm of 0.5mm o.d. wire has an inductance of 7.26nH  
( $2R = 0.5\text{mm}$ ,  $L = 1\text{cm}$ )




$$\text{STRIP INDUCTANCE} = 0.0002L \left[ \ln \left( \frac{2L}{W+H} \right) + 0.2235 \left( \frac{W+H}{L} \right) + 0.5 \right] \mu\text{H}$$

EXAMPLE: 1cm of 0.25 mm PC track has an inductance of 9.59 nH  
( $H = 0.038\text{mm}$ ,  $W = 0.25\text{mm}$ ,  $L = 1\text{cm}$ )


Figure 12.18: Wire and Strip Inductance Calculations



## Loop Inductances

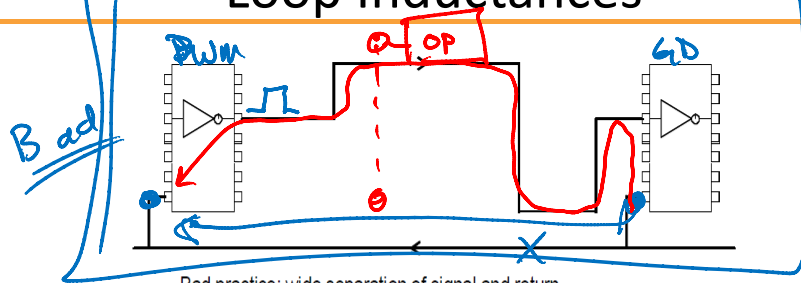

 Bad practice: wide separation of signal and return




Good practice: close coupling of signal and return






## Loop Inductance: Experiment

 

**Figure 12.60:** Schematic and Layout of Current Source with U-shaped Trace on PC Board and Return through Ground Plane.



## Loop Inductance: Experiment

 

**Figure 12.61:** DC Current Flow for Figure 12.60



# Loop Inductance: Experiment


 



Figure 12.63: AC Current Path Without (left) and with (right) Resistance in the Ground Plane

 

Parasitic inductances of input loop explicitly shown:



 
Addition of bypass capacitor confines the pulsating current to a smaller loop:




high frequency currents are shunted through capacitor instead of input source



 Even better: minimize area of the high frequency loop, thereby minimizing its inductance



 Solution: bypass capacitor and close coupling of gate and return leads



High frequency components of gate drive current are confined to a small loop

A dc component of current is still drawn output of 15V supply, and flows past the control chips. Hence, return conductor size must be sufficiently large




## Op-amp Pulsed Decoupling

PROPER DECOUPLING



NO DECOUPLING

 


VERTICAL SCALE: 100mV/div  
HORIZONTAL SCALE: 10ns/div

Figure 12.68: Effects of Inadequate Decoupling on the Phase Response of the AD9631 Op Amp



## Star-Grounding Vs. Daisy Chain

Undesired

 

Desired




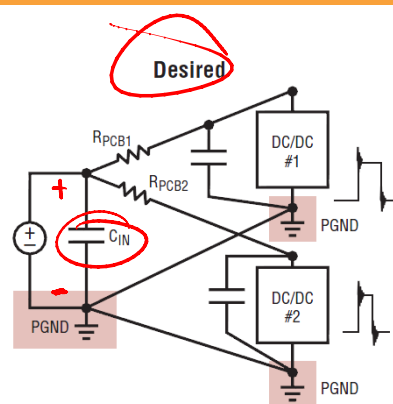
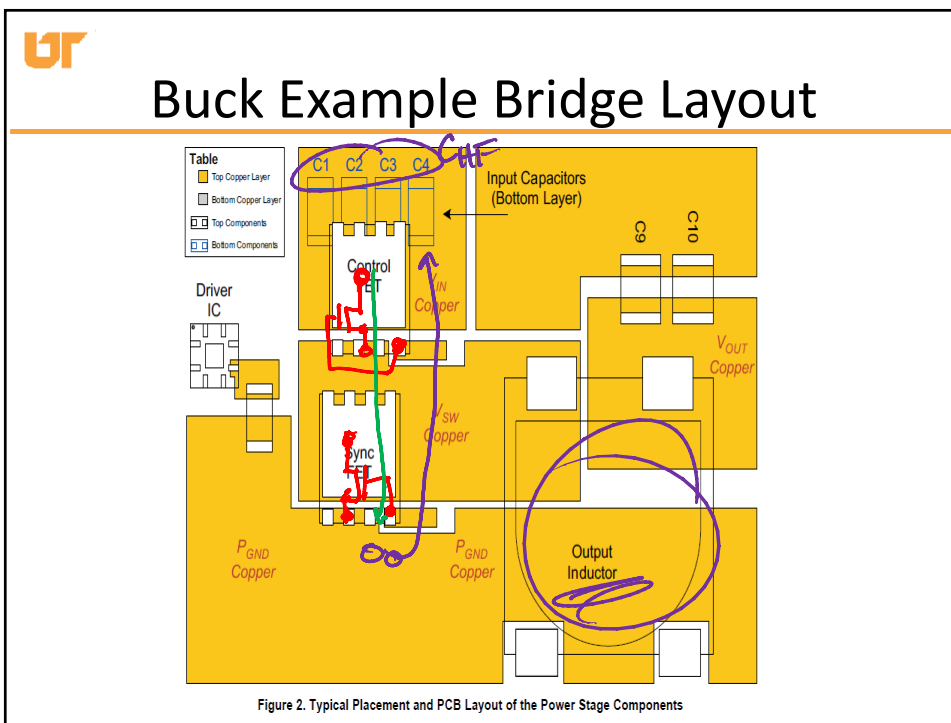


Figure 9. Separate the Input Current Paths Among Supplies

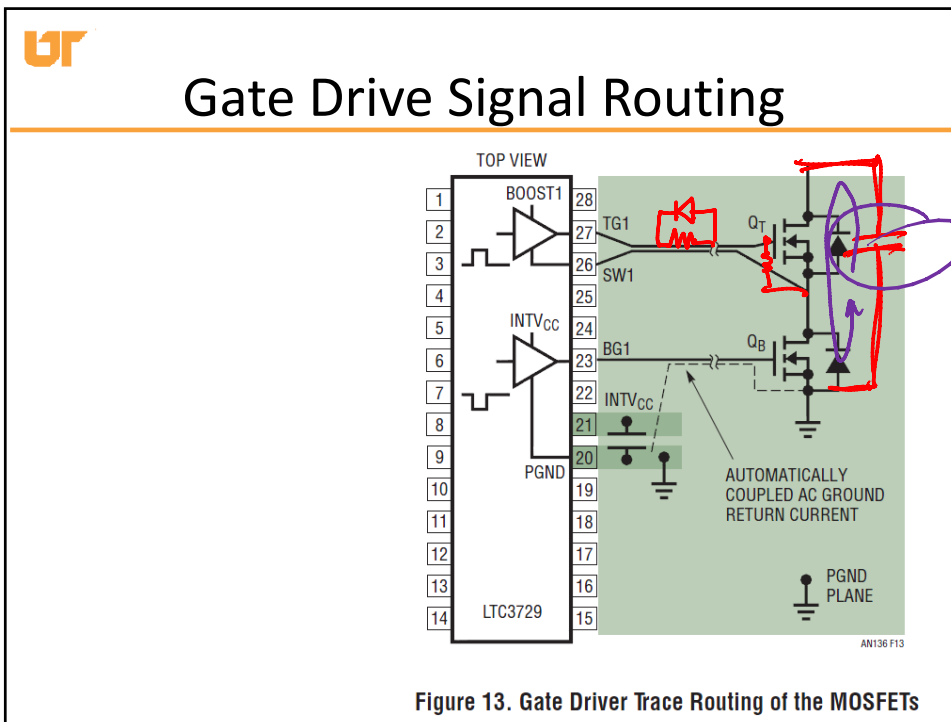

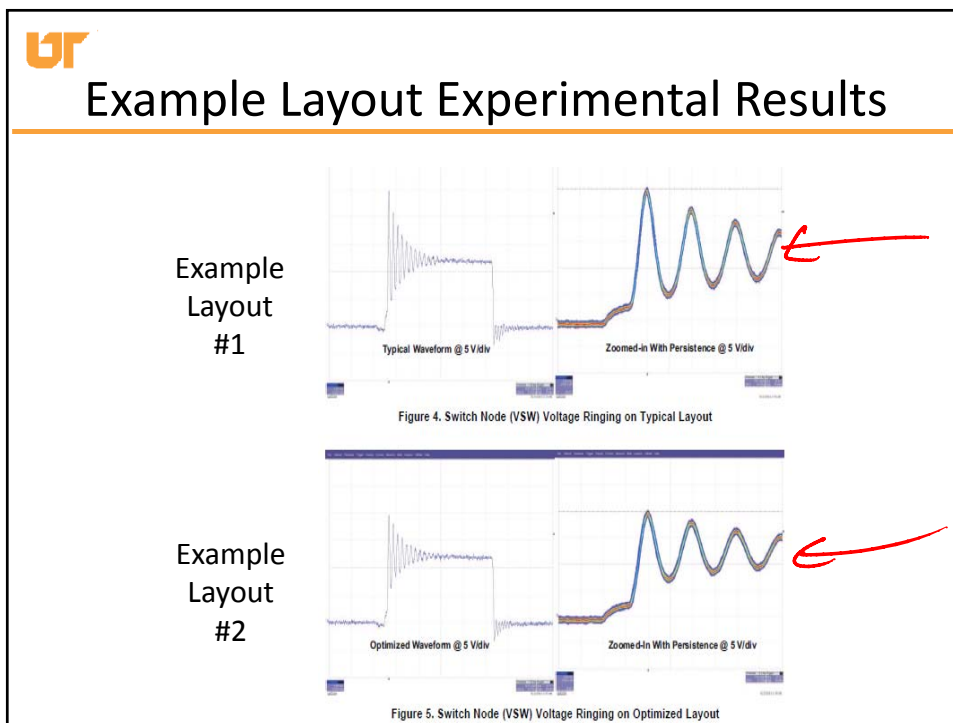

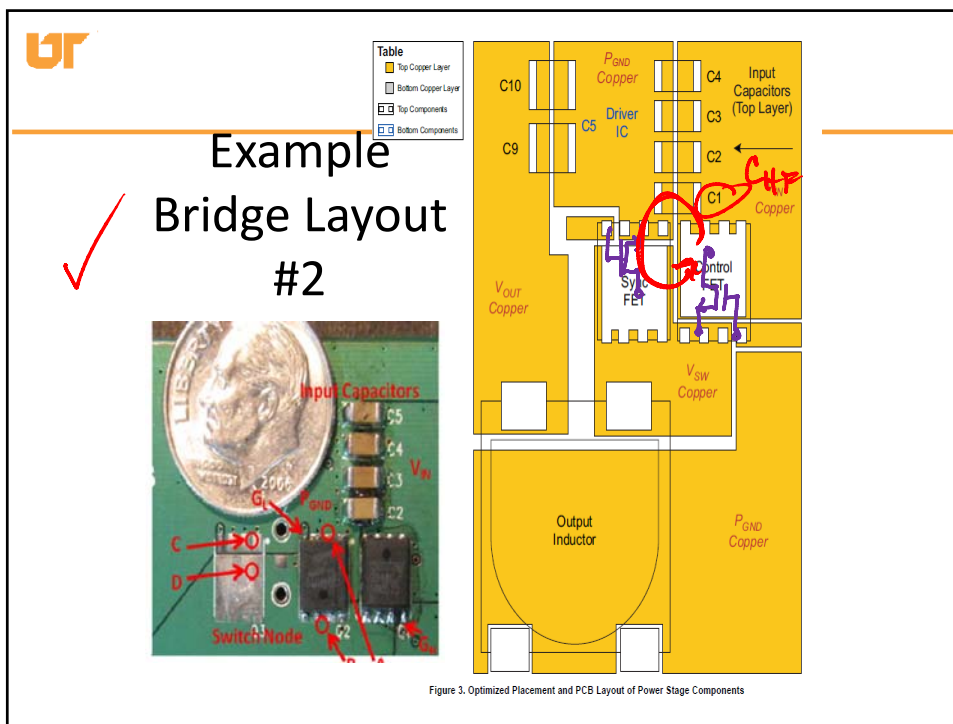

# Decoupling Capacitance


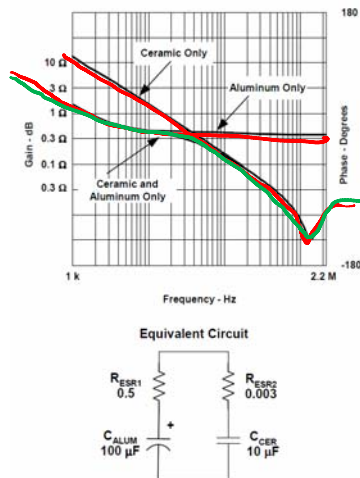


Fig. 8. Paralleled capacitors minimize impedance over frequency.

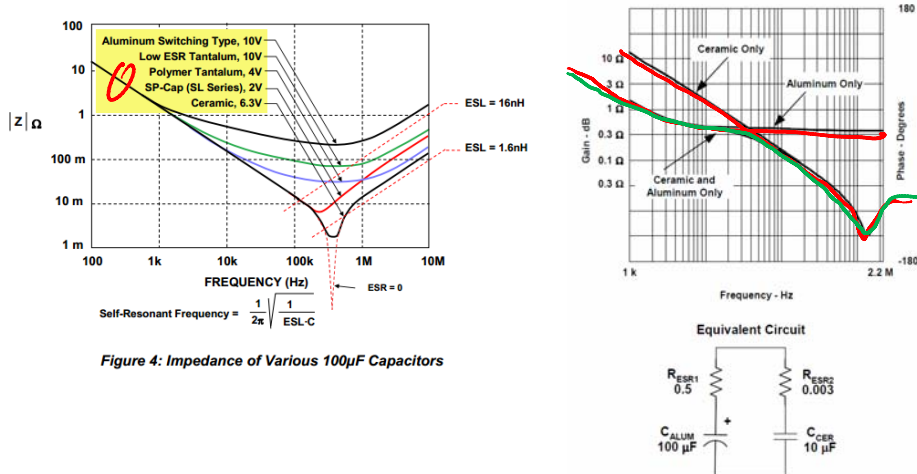

# Capacitor Packaging

 
 


FIGURE 8. IMPEDANCE OF AN ACTUAL CAPACITOR (NON-IDEAL)

FIGURE 9. IMPEDANCE OF AN ACTUAL CAPACITOR (NON-IDEAL) IN DIFFERENT SURFACE-MOUNT PACKAGES


 


FIGURE 10. IMPEDANCE OF THREE CAPACITORS, THE SAME SURFACE-MOUNT PACKAGES

FIGURE 11. IMPEDANCE OF THREE CAPACITORS, SCALED SURFACE-MOUNT PACKAGES

 


## Ground Plane



- Benefits:
  - Common reference voltage
  - Shielding
  - Heat dissipation
  - Reduced inductance (increased capacitance)
- Resist urge to cut ground plane as much as possible; consider paths of return currents when cuts are unavoidable





## Ground Currents

 

  No split: high mutual inductance,  
low ground inductance



Extra return path adds ground inductance

  





## Acceptable Cuts in Ground Plane

- Cuts that are necessary should be kept short and out of the path of any significant (high frequency) return paths
- Cuts can be used effectively for isolation, and to reduce noise coupled between digital/analog/power circuitry
- Reducing parasitic capacitance in sensitive signal locations (i.e. op-amp circuitry)



## Partitioning

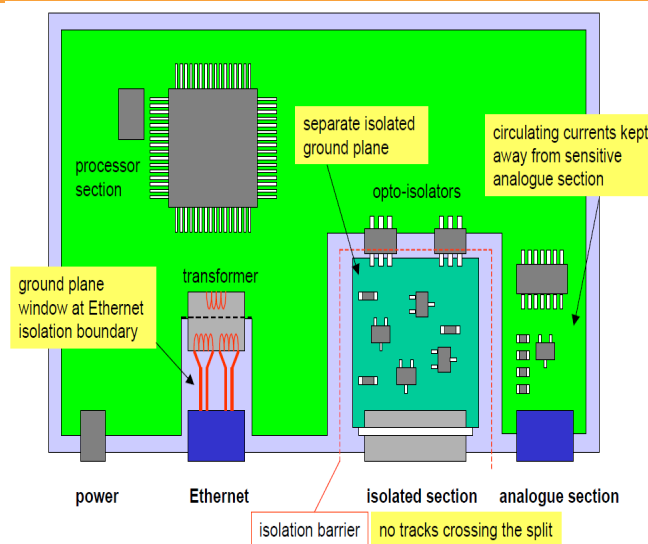


Figure 4 Uses of ground plane windows



## Effective Ground Plane Cuts

