



Converter Loss Analysis

ECE 482 Lecture 4
January 17, 2014



Announcements

- Finish Experiment 1: report due Monday, 1/27
- This week: Experiment 2
 - Boost open-loop construction and modeling
 - Prelab: Inductor design and switch selection
- Component kits available in circuits store
 - \$80 *per group* for components for Labs 2 and 3
 - Plan to spend additional <\$5.00 on resistors




Analytical Loss Modeling



- High efficiency approximation is acceptable for hand calculations, as long as it is justified
 - Solve waveforms of lossless converter, then calculate losses
- Alternate approach: average circuit
 - Uses average, rather than RMS currents
 - Difficult to include losses other than conduction
- Argue which losses need to be included, and which may be neglected



Boost Converter Loss Analysis

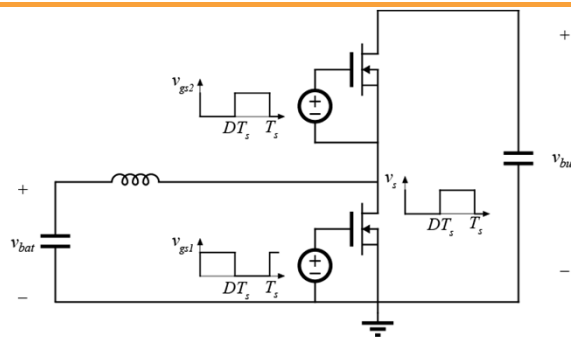


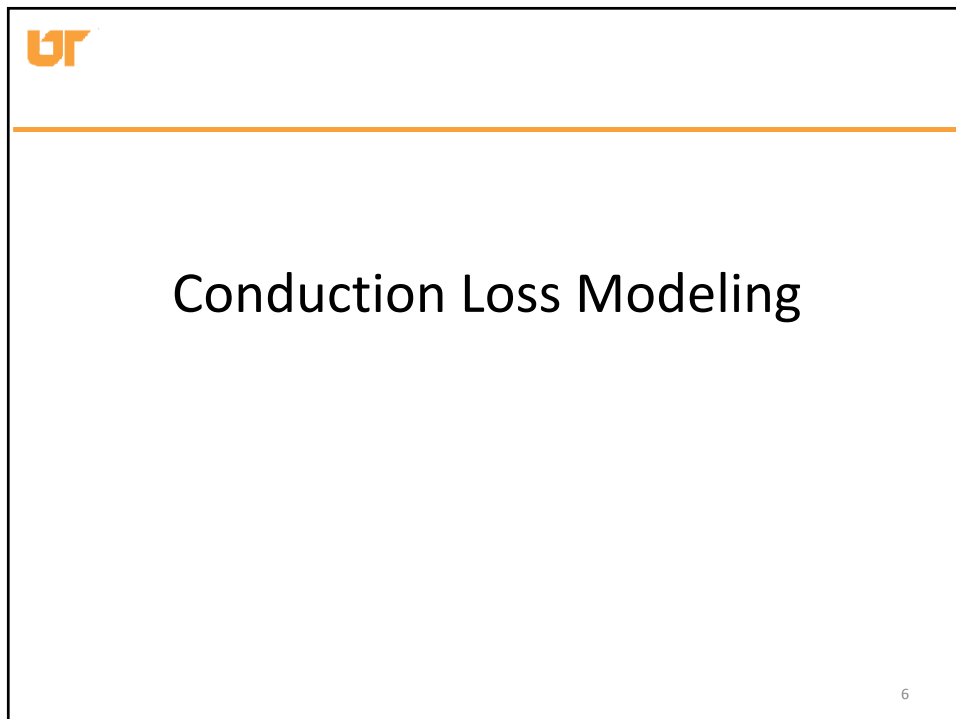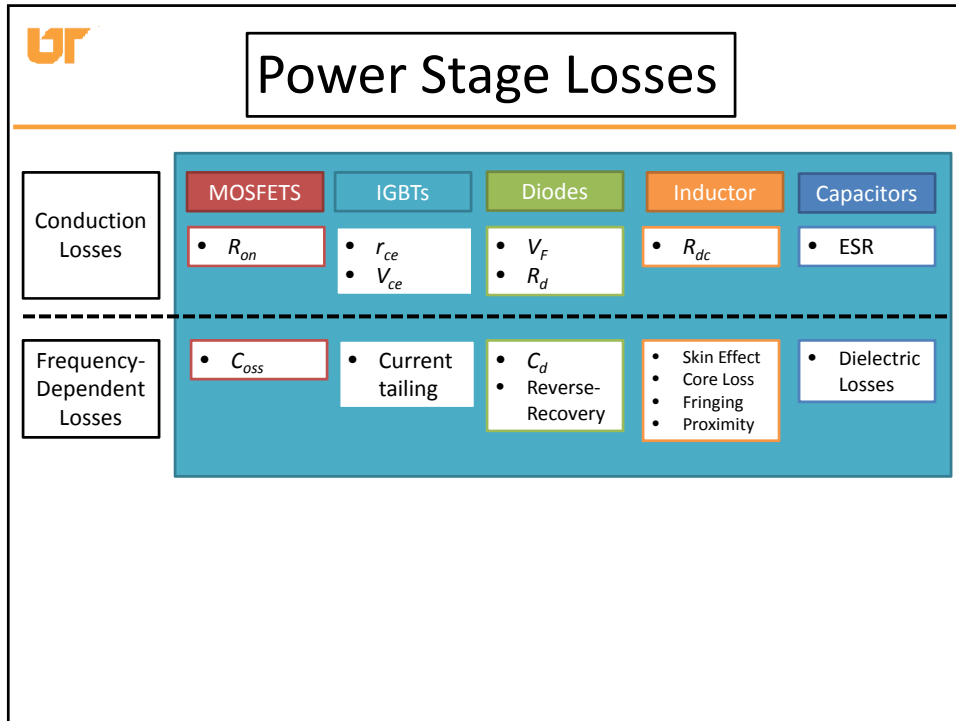- Begin by solving important waveforms throughout converter assuming lossless operation





MOSFET Equivalent Circuit

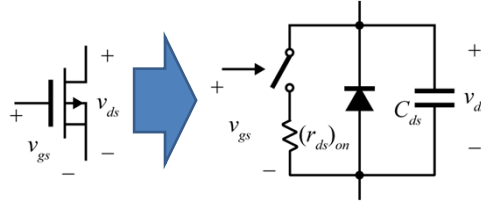


- Considering only power stage losses (gate drive neglected)
- MOSFET operated as power switch
- Intrinsic body diode behaviors considered using normal diode analysis



MOSFET On Resistance


5 Typ. output characteristics

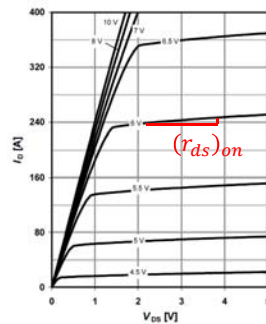$I_D = f(V_{DS})$; $T_J = 25^\circ\text{C}$
parameter: V_{GS}




6 Typ. drain-source on resistance

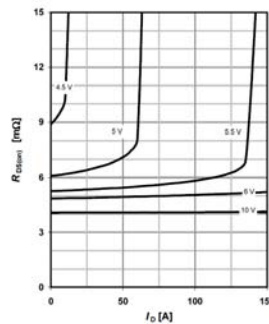$R_{DS(on)} = f(I_D)$; $T_J = 25^\circ\text{C}$
parameter: V_{GS}



9 Drain-source on-state resistance

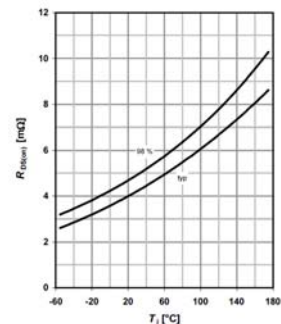
$R_{DS(on)} = f(T_J)$; $I_D = 100\text{ A}$; $V_{GS} = 10\text{ V}$



- On resistance extracted from datasheet waveforms
- Significantly dependent on V_{GS} amplitude, temperature



Boost Converter RMS Currents

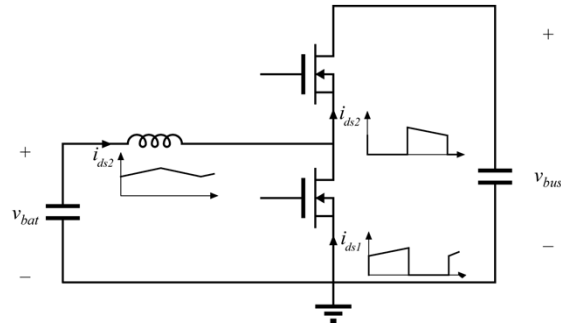

- MOSFET conduction losses due to $(r_{ds})_{on}$ depend given as

$$P_{cond,FET} = I_{d,rms}^2 (r_{ds})_{on}$$



MOSFET Conduction Losses

Pulsating waveform with linear ripple, Fig. A.6:

$$r_{ms} = I\sqrt{D} \sqrt{1 + \frac{1}{3} \left(\frac{\Delta i}{I}\right)^2} \quad (\text{A.6})$$


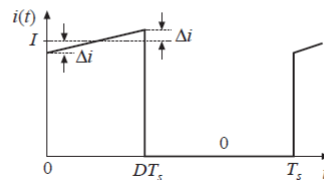


Fig. A.6

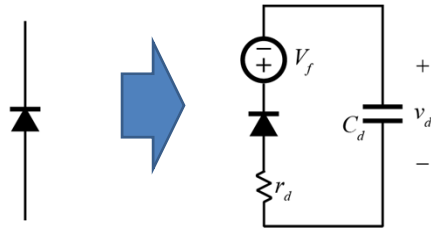
- RMS values of commonly observed waveforms appendix from Power Book




Diode Loss Model



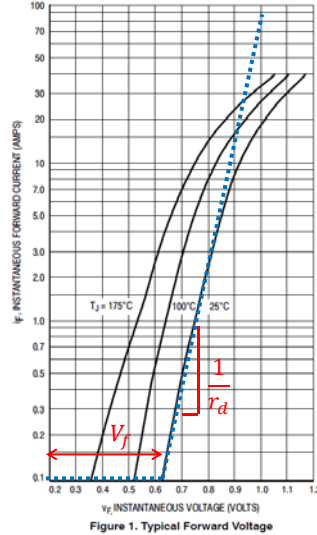- Example loss model includes resistance and forward voltage drop extracted from datasheet




IGBT Loss Model

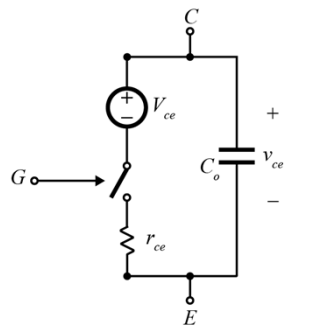


$$P_{cond} = I_{c,rms}^2 r_{ce} + V_{ce} I_{c,avg}$$

Figure 1. Typical Output Characteristics

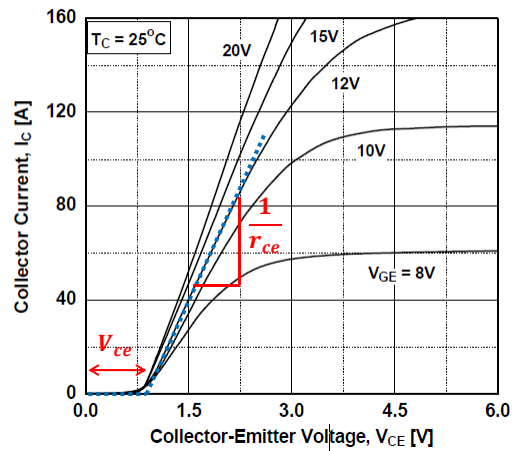

UF Semiconductor Switch Conduction Loss

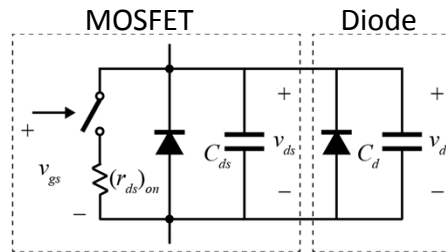



- Equivalent circuit of MOSFET with external antiparallel diode has two, non-ideal diodes
- Diodes, even when matched, will not share current equally, but $v_d = v_{ds}$ must remain true
- Silicon rectifier diodes are minority carrier devices
 - Concentration of minority carriers depends heavily on temperature

UF Diode Paralleling

12 Forward characteristics of reverse diode


$$I_F = f(V_{SD})$$

parameter: T_j

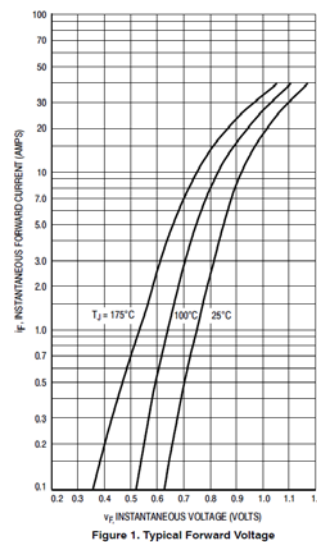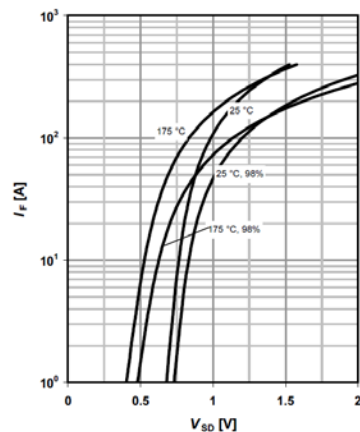



DC Inductor Resistance

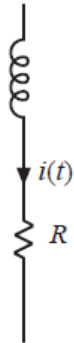

- DC Resistance given by

$$R_{DC} = \rho \frac{l_b}{A_w}$$

- At room temp, $\rho = 1.724 \cdot 10^{-6} \Omega\text{-cm}$
- At 100°C, $\rho = 2.3 \cdot 10^{-6} \Omega\text{-cm}$
- Losses due to DC current:

$$P_{cu,DC} = I_{L,rms}^2 R_{DC}$$



Inductor Conduction Losses

DC plus linear ripple, Fig. A.2:

$$r_{ms} = I \sqrt{1 + \frac{1}{3} \left(\frac{\Delta i}{I} \right)^2} \quad (\text{A.2})$$


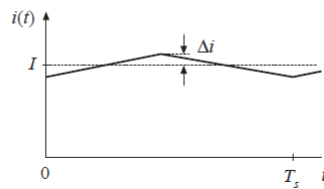


Fig. A.2

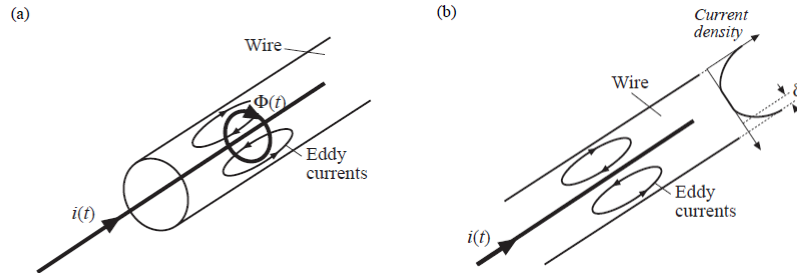- Conduction losses dependent on RMS current through inductor



Skin Effect in Copper Wire



- Current profile at high frequency is exponential function of distance from center with characteristic length δ



Skin Depth


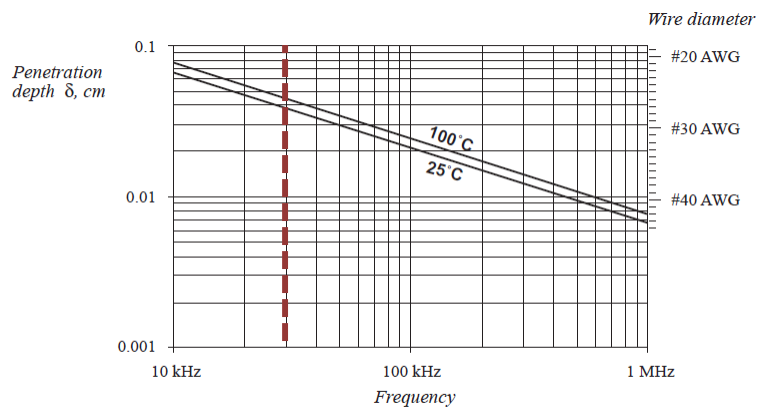


Fig. 13.23 Penetration depth δ , as a function of frequency f , for copper wire.

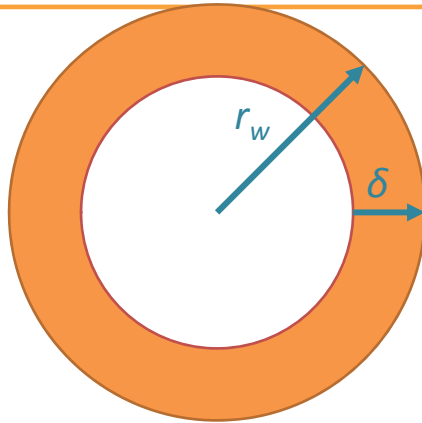


AC Resistance



$$A_{w,eff} = \pi r_w^2 - \pi (r_w - \delta)^2$$

$$R_{ac} = \rho \frac{l_b}{A_{w,eff}}$$

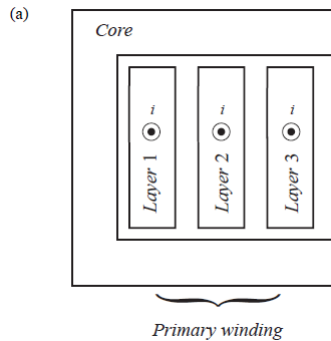

Proximity Effect

- In *foil* conductor closely spaced with $h \gg \delta$, flux between layers generates additional current according to Lenz's law.


$$P_1 = I_{L,rms}^2 R_{ac}$$

- Power loss in layer 2:

$$P_2 = I_{L,rms}^2 R_{ac} + (2I_{L,rms})^2 R_{ac}$$


$$P_2 = 5P_1$$

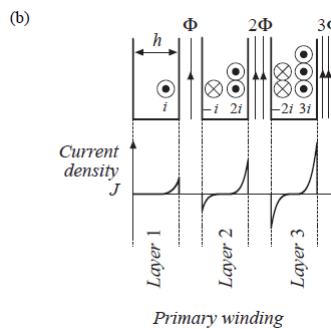- Needs modification for non-foil conductors






Capacitor Loss Model

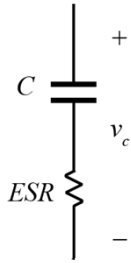

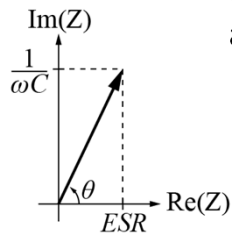- Operation well below resonance
- All loss mechanisms in a capacitor are generally lumped into an empirical loss model
- Equivalent Series Resistance (ESR) is *highly* frequency dependent
- Datasheets may give effective impedance at a frequency, or loss factor:



$$\delta = \frac{\pi}{2} - \theta$$

$$D = \tan(\delta)$$



Capacitor ESR Extraction



WV (Vdc)	Cap (µF)	Case size ϕD×L(mm)	Impedance (Ωmax/100kHz)		Rated ripple current (mA rms/105°C, 100kHz)	Part No.
			20°C	-10°C		
6.8	5×11	1.4	5.6	125	EKZE101E□□6R8ME11D	
15	6.3×11	0.57	2.3	205	EKZE101E□□150MF11D	
27	8×11.5	0.36	1.4	355	EKZE101E□□270MHB5D	
39	8×15	0.25	1.0	450	EKZE101E□□390MH16D	
47	10×12.5	0.17	0.66	480	EKZE101E□□470MJCS	
56	8×20	0.19	0.76	565	EKZE101E□□560MH20D	
68	10×16	0.11	0.47	600	EKZE101E□□680MJ16S	
82	10×20	0.084	0.34	800	EKZE101E□□820MJ20S	
100	12.5×16	0.11	0.34	750	EKZE101E□□101MK16S	
120	10×25	0.069	0.28	900	EKZE101E□□121MJ25S	
150	12.5×20	0.062	0.18	1,100	EKZE101E□□151MK20S	
220	12.5×25	0.047	0.14	1,250	EKZE101E□□221MK25S	
220	16×20	0.048	0.15	1,350	EKZE101E□□221ML20S	
270	12.5×30	0.042	0.13	1,500	EKZE101E□□271MK30S	



Dissipation Factor: 1% Max. (25 °C, 1kHz)

Dissipation Factor (tan δ)	Rated voltage (Vdc)	6.3V	10V	16V	25V	35V	50V	63V	80V	100V
		tan δ (Max.)	0.22	0.19	0.16	0.14	0.12	0.10	0.09	0.09

When nominal capacitance exceeds 1,000µF, add 0.02 to the value above for each 1,000µF increase. (at 20°C, 120Hz)




Switching Loss Modeling



23





Lump Switched Node Capacitance

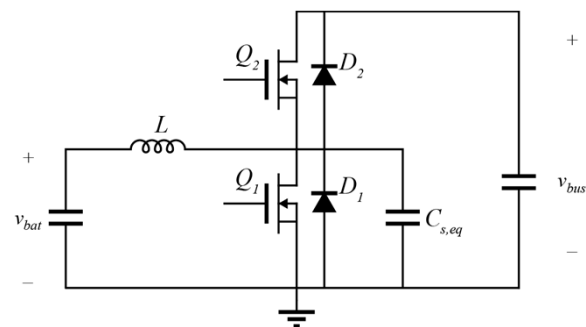

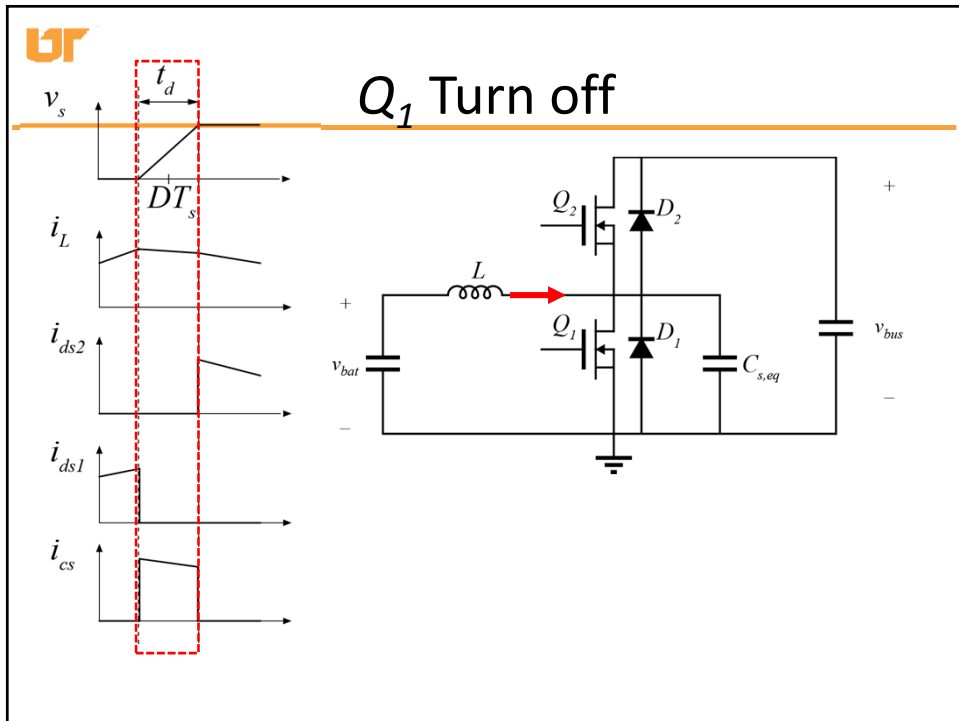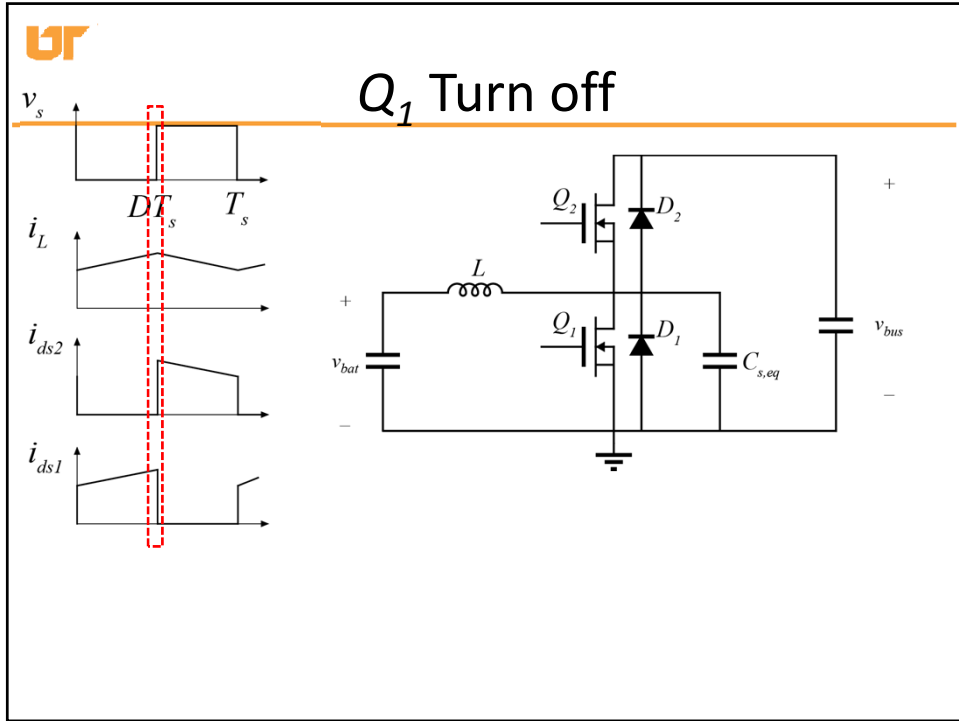- Consider a single equivalent capacitor at switched node which combines energy storage due to all four semiconductor devices



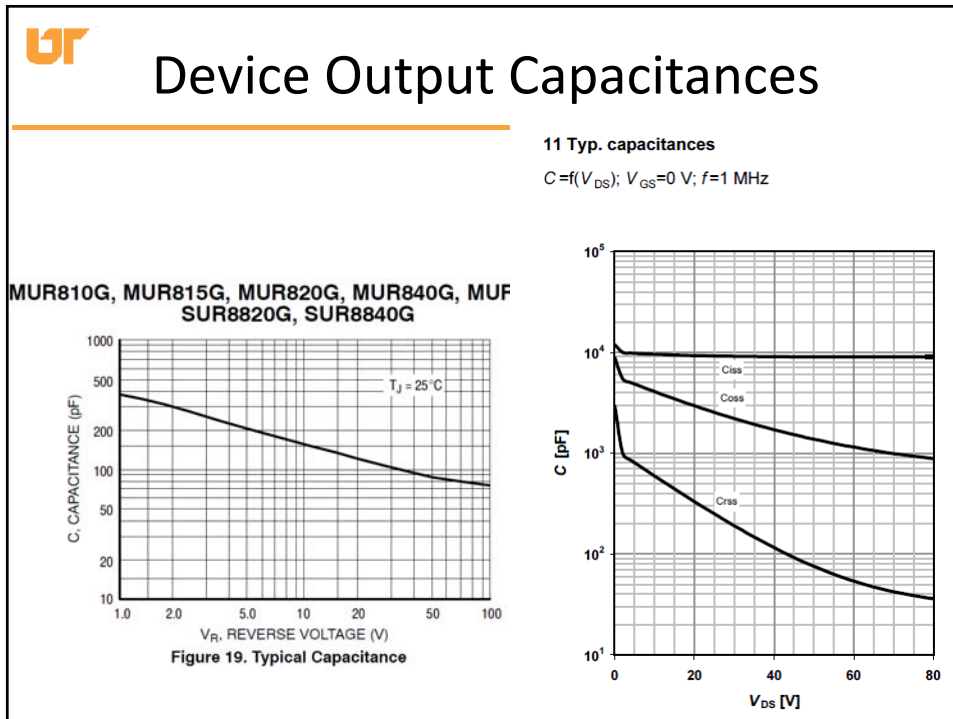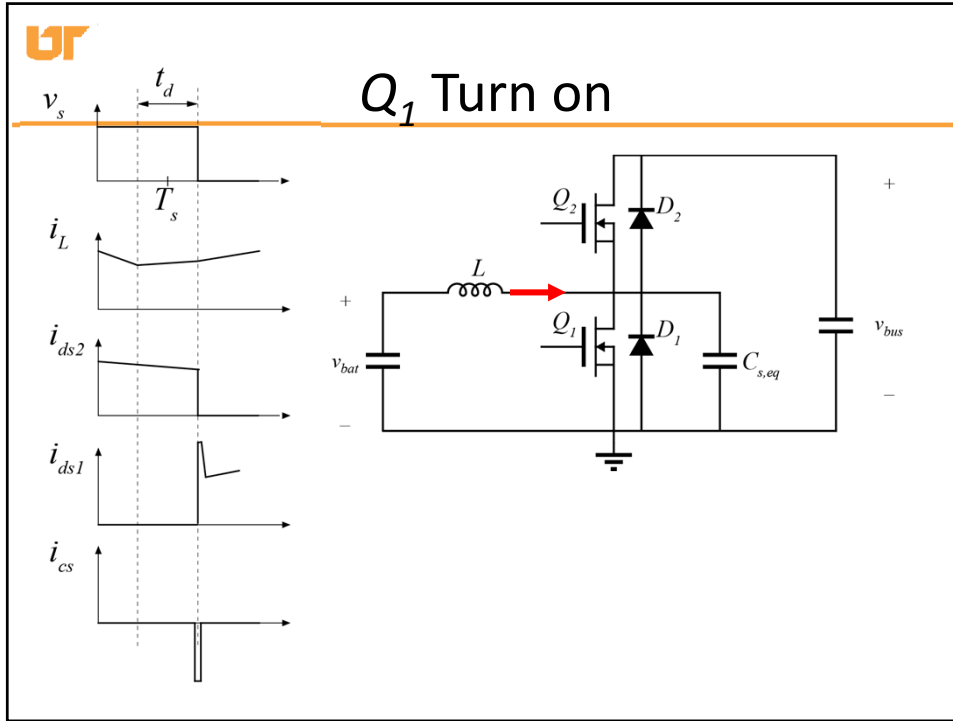



Energy Equivalent Capacitor

- Measurements are small-signal
- At any voltage:

$$\hat{i}_{ds} = C_{oss} \Big|_{V_{ds}} \frac{d\hat{v}_{ds}}{dt}$$

- Total energy is then:

$$E_{ds}(V) = \int_0^t \hat{i}_{ds}(\tau) \hat{v}_{ds}(\tau) d\tau$$


$$E_{ds}(V) = \int_0^t C_{oss} \Big|_{\hat{v}_{ds}(\tau)} \frac{d\hat{v}_{ds}(\tau)}{d\tau} \hat{v}_{ds}(\tau) d\tau$$

$$E_{ds}(V) = \int_0^V v_{ds} C_{ds}(v_{ds}) dv_{ds}$$

$$C_{eq,E}(V) = \frac{2E_{ds}(V)}{V^2}$$

11 Typ. capacitances

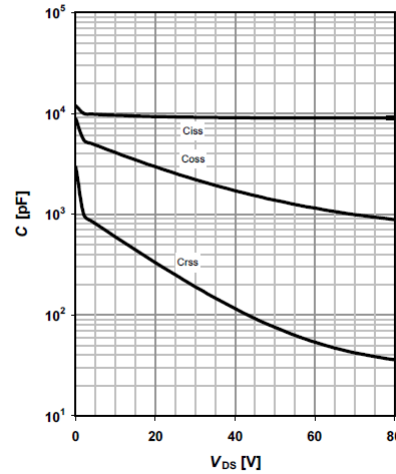$C=f(V_{DS}); V_{GS}=0\text{ V}; f=1\text{ MHz}$



Energy Storage Example


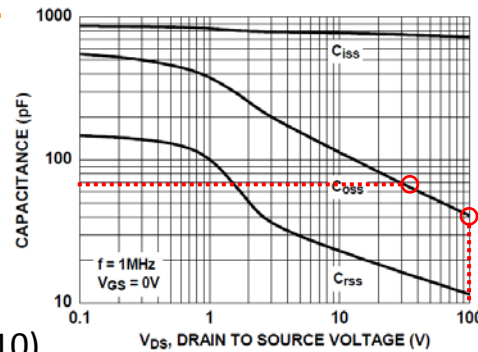


Figure 8. Capacitance vs Drain to Source Voltage

- Different device (FDMC2610)
- Charged to 100 V, capacitance stores same energy as 67pF linear capacitor


$$E = \text{trapz}(vx(\text{range}), Cx(\text{range}).*\text{abs}((vx(\text{range}))));$$

$$C_{per} = 2*(E)/Vg^2;$$

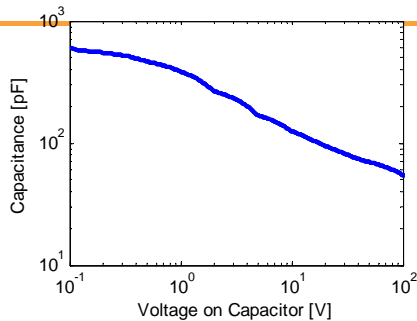

Diode Reverse Recovery




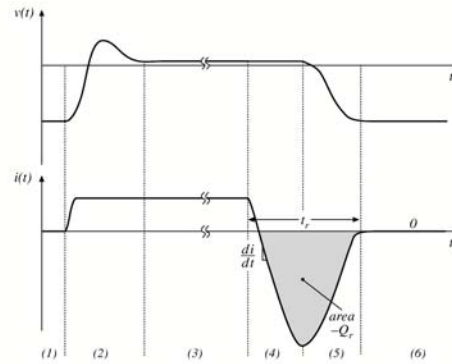
- Diodes will turn on during dead time intervals
- Significant reverse recovery possible on both body diode and external diode





$$E_{on,rr} = ((I_L - \Delta i_L)t_{rr} + Q_{rr})V_{bus}$$



IGBT Switching

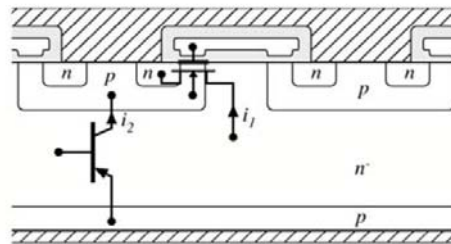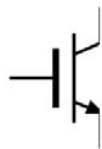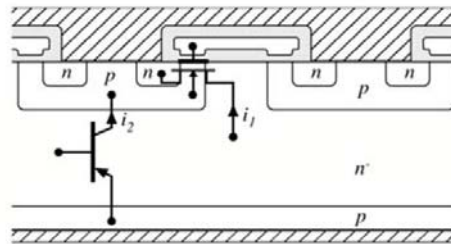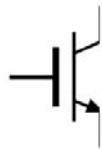

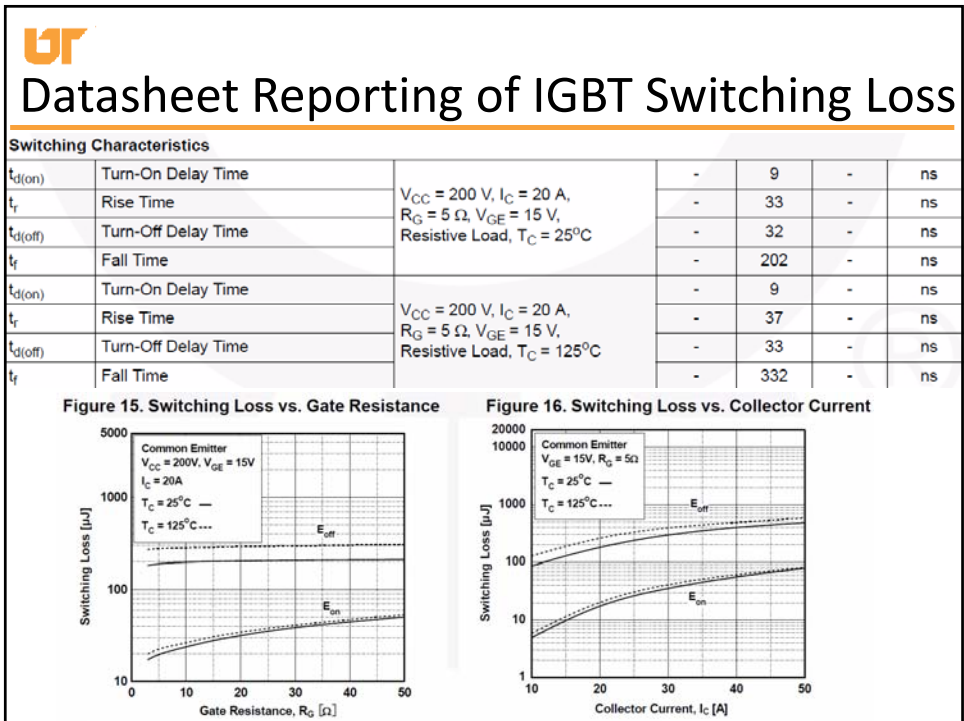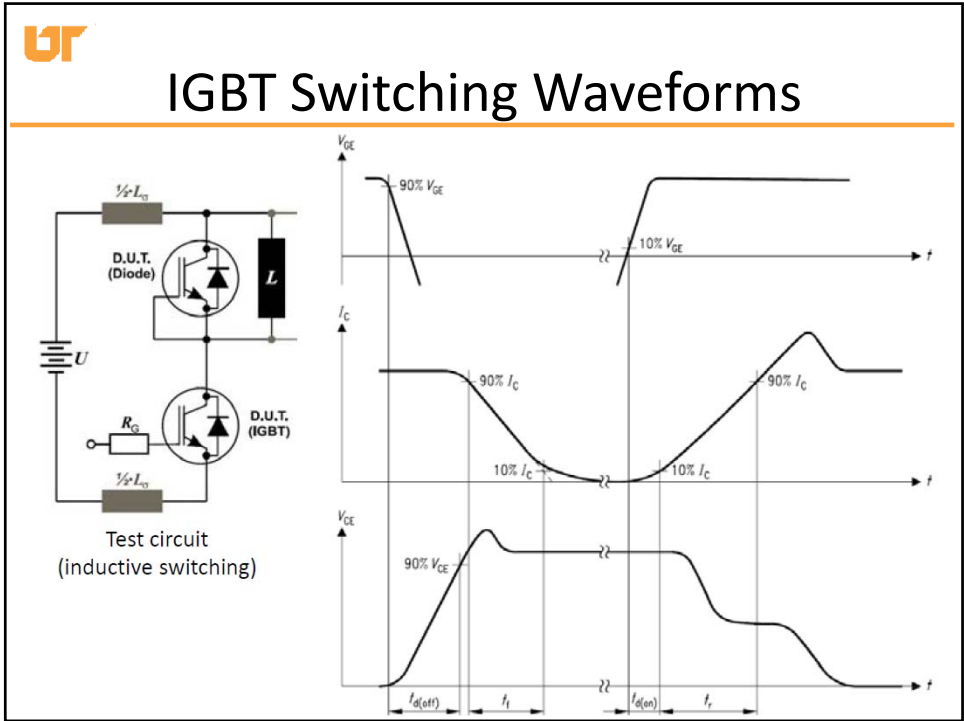




Inductor Core Loss

- Governed by Steinmetz Equation:



$$P_v = K_{fe} f_s^\alpha (\Delta B)^\beta \quad [\text{mW/cm}^3]$$

- Parameters K_{fe} , α , and β extracted from manufacturer data
- $\Delta B \propto \Delta i_L \rightarrow$ small losses with small ripple
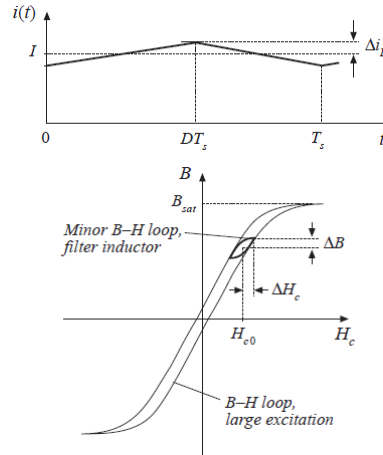
$$P_{fe} = P_v A_c l_m \quad [\text{mW}]$$



Steinmetz Parameter Extraction

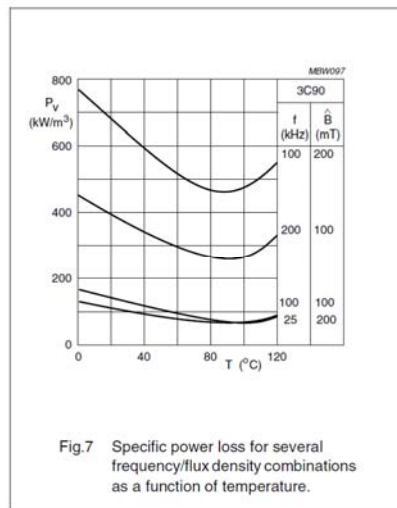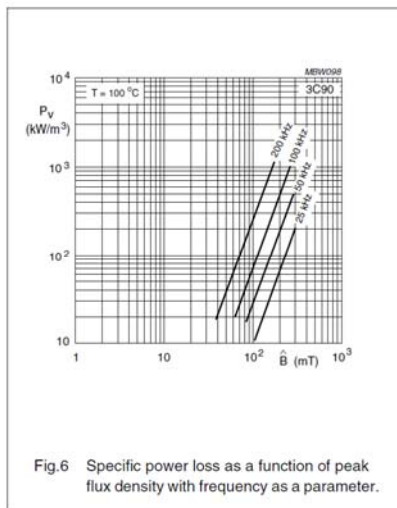



Ferroxcube Curve Fit Parameters

Power losses in our ferrites have been measured as a function of frequency (f in Hz), peak flux density (B in T) and temperature (T in $^{\circ}\text{C}$). Core loss density can be approximated ⁽²⁾ by the following formula :

$$P_{\text{core}} = C_m \cdot f^x \cdot B_{\text{peak}}^y \cdot (ct_0 - ct_1 T + ct_2 T^2) \quad [3]$$

$$= C_m \cdot C_T \cdot f^x \cdot B_{\text{peak}}^y \quad [\text{mW/cm}^3]$$

ferrite	f (kHz)	Cm	x	y	ct ₂	ct ₁	ct ₀
3C30	20-100	7.13.10 ⁻³	1.42	3.02	3.65.10 ⁻⁴	6.65.10 ⁻²	4
	100-200	7.13.10 ⁻³	1.42	3.02	4.10 ⁻⁴	6.8.10 ⁻²	3.8
3C90	20-200	3.2.10 ⁻³	1.46	2.75	1.65.10 ⁻⁴	3.1.10 ⁻²	2.45
3C94	20-200	2.37.10 ⁻³	1.46	2.75	1.65.10 ⁻⁴	3.1.10 ⁻²	2.45
	200-400	2.10 ⁻⁹	2.6	2.75	1.65.10 ⁻⁴	3.1.10 ⁻²	2.45
3F3	100-300	0.25.10 ⁻³	1.63	2.45	0.79.10 ⁻⁴	1.05.10 ⁻²	1.26
	300-500	2.10 ⁻⁵	1.8	2.5	0.77.10 ⁻⁴	1.05.10 ⁻²	1.28
	500-1000	3.6.10 ⁻⁹	2.4	2.25	0.67.10 ⁻⁴	0.81.10 ⁻²	1.14
3F4	500-1000	12.10 ⁻⁴	1.75	2.9	0.95.10 ⁻⁴	1.1.10 ⁻²	1.15
	1000-3000	1.1.10 ⁻¹¹	2.8	2.4	0.34.10 ⁻⁴	0.01.10 ⁻²	0.67


Table 1: Fit parameters to calculate the power loss density



NSE/iGSE

- More complex empirical loss models exist, and remain valid for non-sinusoidal waveforms
- NSE/iGSE:

$$P_{NSE} = \left(\frac{\Delta B}{2} \right)^{\beta - \alpha} \frac{k_N}{T} \int_0^T \left| \frac{dB}{dt} \right|^{\alpha} dt$$

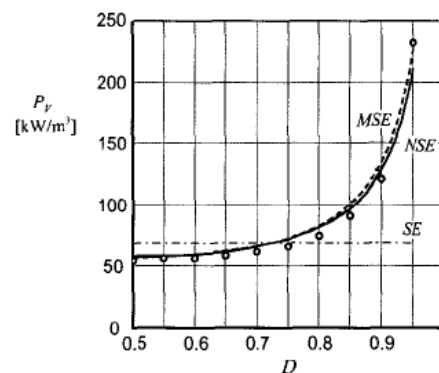



NSE/iGSE Shortcut for Squarewaves

- For square wave excitation, the improved loss model can be reduced to:

$$k_N = \frac{k}{(2\pi)^{\alpha-1} \int_0^{2\pi} |\cos \theta|^\alpha d\theta} \quad (8)$$


$$P_{NSE} = k_N f^\alpha (\Delta B)^\beta \left(\left(\frac{2}{D} \right)^\alpha + \left(\frac{2}{1-D} \right)^\alpha (1-D) \right) \quad (9)$$



- Full Paper included on materials page of website

Van den Bossche, A.; Valchev, V.C.; Georgiev, G.B.; "Measurement and loss model of ferrites with non-sinusoidal waveforms," *Power Electronics Specialists Conference, 2004. PESC 04. 2004 IEEE 35th Annual*, vol.6, no., pp. 4814- 4818 Vol.6, 20-25 June 2004 doi: 10.1109/PESC.2004.1354851



Inductor Design

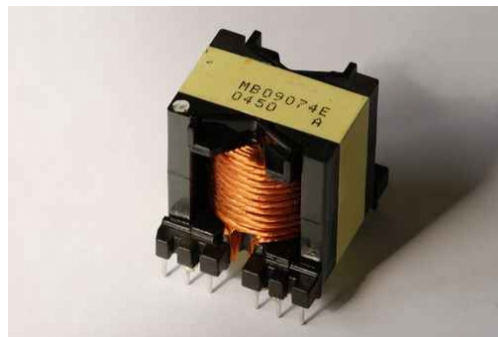

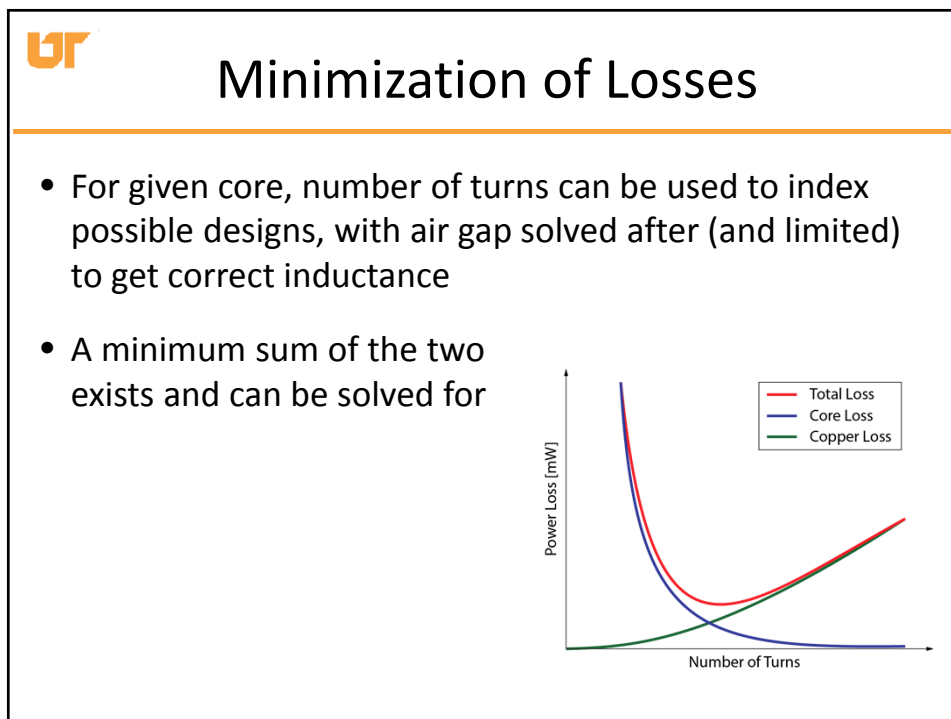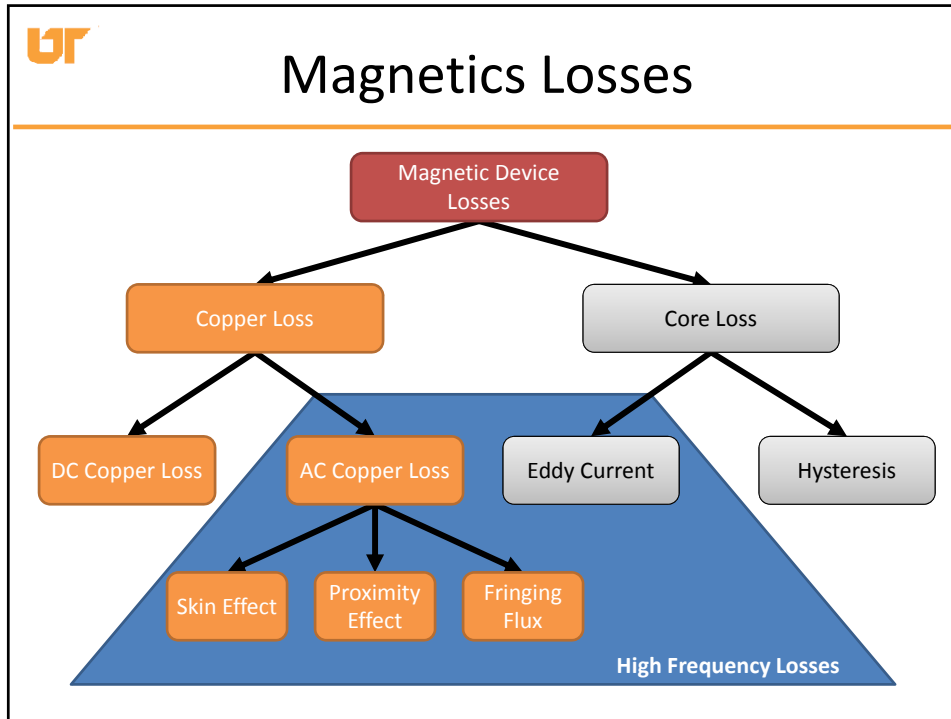



K_g and K_{gfe} Methods



- Two closed-form methods to solve for the optimal inductor design *under certain constraints/assumptions*
- Neither method considers losses other than DC copper and (possibly) steinmetz core loss
- Both methods particularly well suited to spreadsheet/iterative design procedures

	K_g	K_{gfe}
Losses	DC Copper (specified)	DC Copper, SE Core Loss (optimized)
Saturation	Specified	Checked After
B_{max}	Specified	Optimized



K_g Method

- Method useful for filter inductors where ΔB is small
- Core loss is not included, but may be significant particularly if large ripple is present
- Copper loss is specified through a set target resistance
- The desired B_{max} is given as a constraint
- Method does not check feasibility of design; must ensure that air gap is not extremely large or wire size excessively small
- Simple first-cut design technique; useful for determining approximate core size required
- Step-by-step design procedure included on website

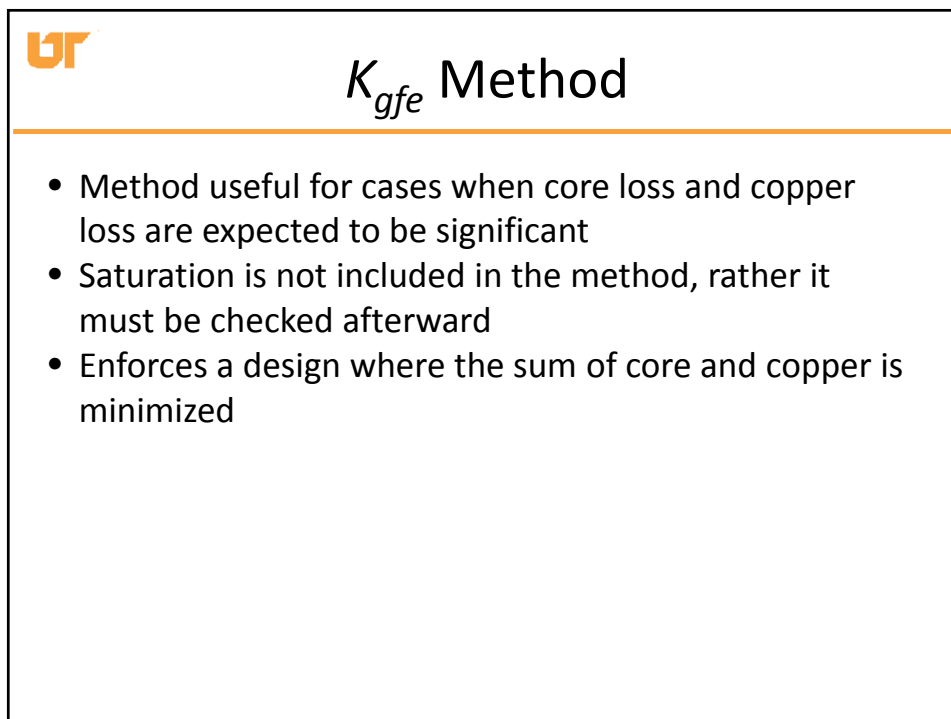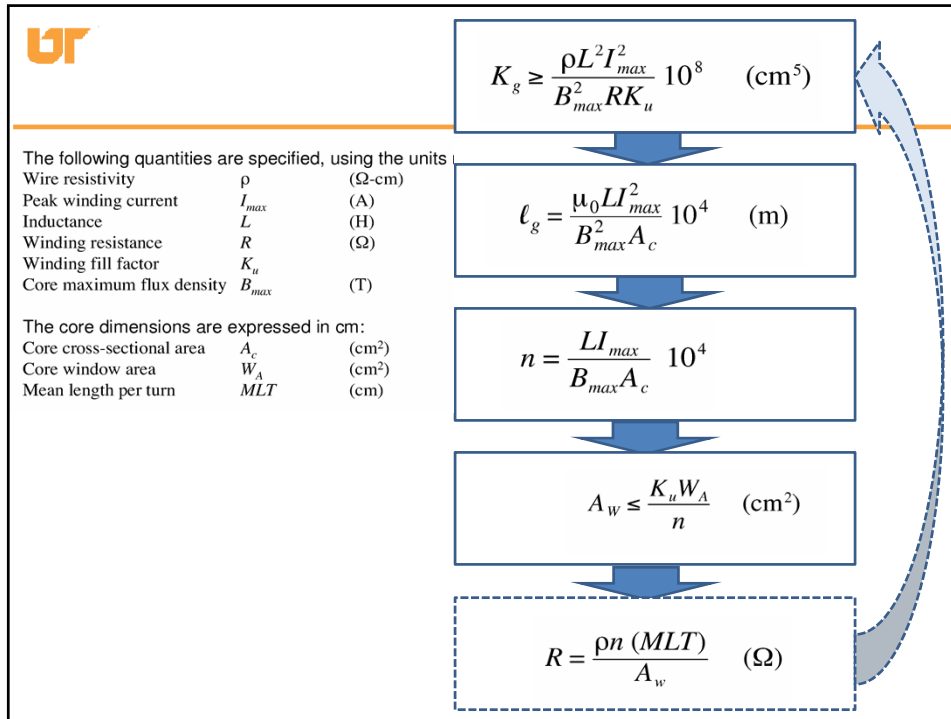



K_{gfe} Procedure

The following quantities are specified, using the units noted:

Wire effective resistivity	ρ	(Ω -cm)
Total rms winding current, ref to pri	I_{tot}	(A)
Desired turns ratios	$n_2/n_1, n_3/n_1, \text{etc.}$	
Applied pri volt-sec	λ_1	(V-sec)
Allowed total power dissipation	P_{tot}	(W)
Winding fill factor	K_u	
Core loss exponent	β	
Core loss coefficient	K_{fe}	(W/cm ³ T ^{β})

Other quantities and their dimensions:

Core cross-sectional area	A_c	(cm ²)
Core window area	W_A	(cm ²)
Mean length per turn	MLT	(cm)
Magnetic path length	ℓ_e	(cm)
Wire areas	A_{w1}, \dots	(cm ²)
Peak ac flux density	ΔB	(T)



$$K_{gfe} \geq \frac{\rho \lambda_1^2 I_{tot}^2 K_{fe}^{(2/\beta)}}{4K_u (P_{tot})^{((\beta+2)/\beta)}} 10^8$$

$$\Delta B = \left[10^8 \frac{\rho \lambda_1^2 I_{tot}^2}{2K_u} \frac{(MLT)}{W_A A_c^3 \ell_m} \frac{1}{\beta K_{fe}} \right]^{(\frac{1}{\beta+2})}$$

$$n_1 = \frac{\lambda_1}{2\Delta B A_c} 10^4 \quad n_k = n_1 \frac{n_k}{n_1}$$

$$\alpha_k = \frac{n_k I_k}{n_1 I_{tot}} \quad A_{wk} \leq \frac{\alpha_2 K_u W_A}{n_2}$$

Verify



K_{gfe} Method: Summary

- Method enforces an operating ΔB in which core and copper losses are minimized
- Only takes into account losses from standard Steinmetz equation; not correct unless waveforms are sinusoidal
- Does not consider high frequency losses
- Step-by-step design procedure included on website