
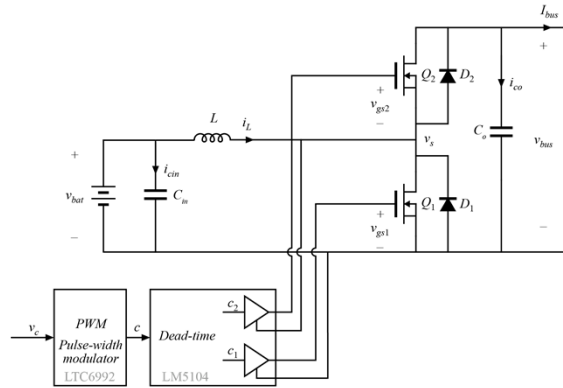


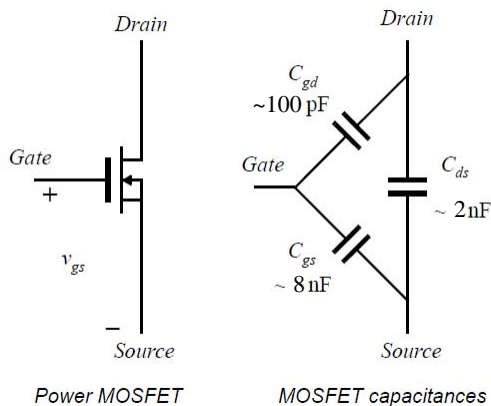

Experiment 2: Open Loop Boost




Driving a Power MOSFET Switch



- MOSFET is off when $v_{gs} < V_{th} \approx 3 \text{ V}$
- MOSFET fully on when v_{gs} is sufficiently large (10-15 V)
- Warning: MOSFET gate oxide breaks down and the device fails when $v_{gs} > 20 \text{ V}$.
- Fast turn on or turn off (10's of ns) requires a large spike (1-2 A) of gate current to charge or discharge the gate capacitance
- MOSFET gate driver is a logic buffer that has high output current capability



Driving a Power MOSFET Switch


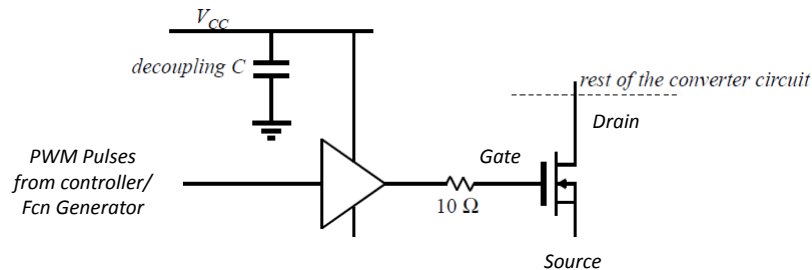


- MOSFET gate driver is used as a logic buffer with high output current ($\sim 1.8\text{ A}$) capability
- The amplitude of the gate voltage equals the supply voltage V_{CC}
- Decoupling capacitors are necessary at all supply pins of LM5104 (and all ICs)
- Gate resistance used to slow dv/dt at switch node



Power Converter Layout: Buck Example

Use loop analysis

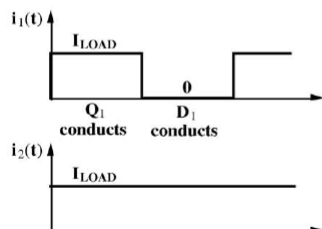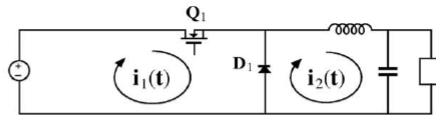


switched input current $i_1(t)$ contains large high frequency harmonics
 —hence inductance of input loop is critical
 inductance causes ringing, voltage spikes, switching loss, generation of B- and E-fields, radiated EMI


the second loop contains a filter inductor, and hence its current $i_2(t)$ is nearly dc
 —hence additional inductance is not a significant problem in the second loop



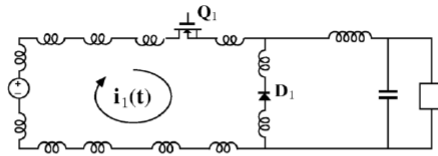Parasitic inductances of input loop explicitly shown:



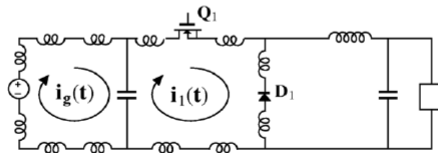
Addition of bypass capacitor confines the pulsating current to a smaller loop:



high frequency currents are shunted through capacitor instead of input source




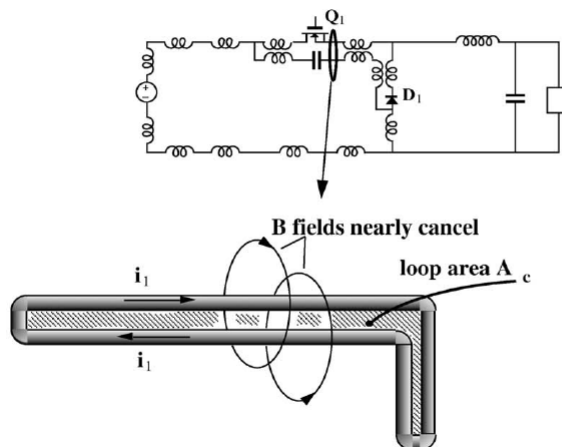Even better: minimize area of the high frequency loop, thereby minimizing its inductance






Gate Driver Example

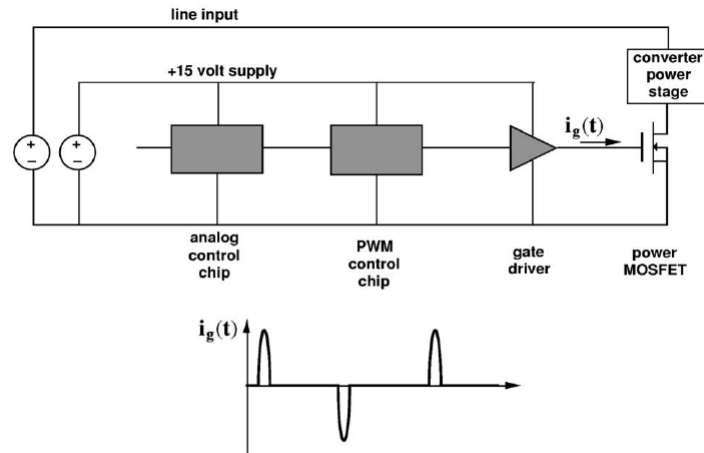

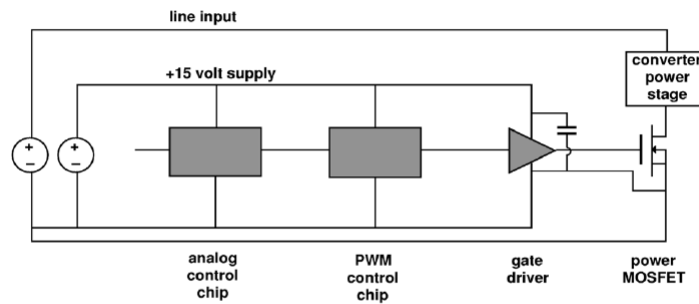Solution: bypass capacitor and close coupling of gate and return leads




High frequency components of gate drive current are confined to a small loop

A dc component of current is still drawn output of 15V supply, and flows past the control chips. Hence, return conductor size must be sufficiently large



Half Bridge Gate Drive Waveforms

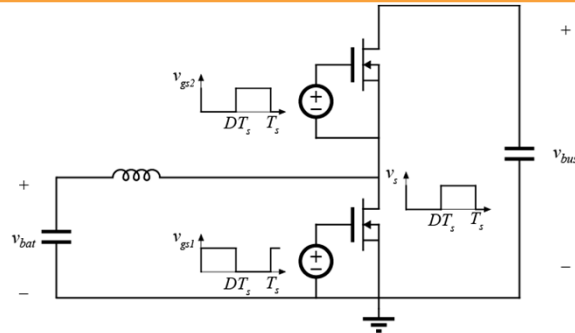


- Gate driver chip must implement v_{gs} waveforms
- Sources will have pulsating currents and need decoupling



MOSFET Gate Charge

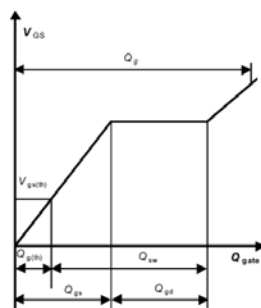
- Charge is supplied to both C_{gs} and C_{gd} in order to move gate voltage and switch MOSFET
- Would like to supply the charge in minimum time to quickly switch FET
- Results in high peak currents




14 Typ. gate charge

$V_{GS} = f(Q_{gate})$; $I_D = 100$ A pulsed

parameter: V_{DD}

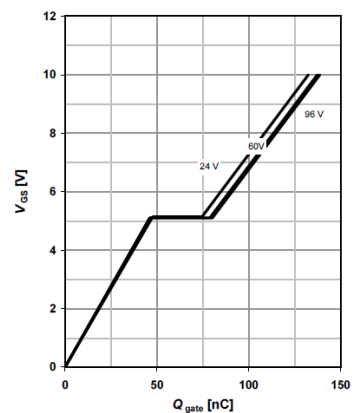

16 Gate charge waveforms

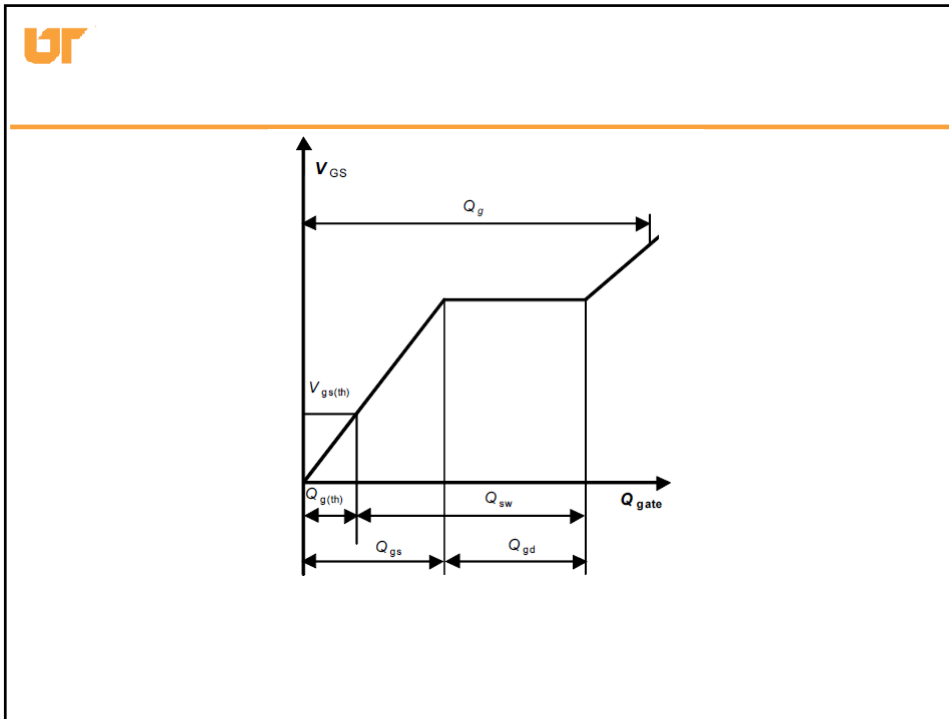


The left diagram shows a cascode driver consisting of a PMOS and an NMOS transistor in series, with a signal input c and a supply voltage V_{DD} . The gate of the NMOS is driven by the PMOS, and the gate of the PMOS is driven by the NMOS. The gate current i_g is shown as a pulse. The right diagram shows a similar driver but with a decoupling capacitor connected between the gates of the PMOS and NMOS transistors.

Gate Drive Implementation

- Gate driver is cascades back half-bridges of decreasing size to obtain quick rise times
- Reminder: keep loops which handle pulsating current small by decoupling and making close connections




Capacitor Sizing Notes

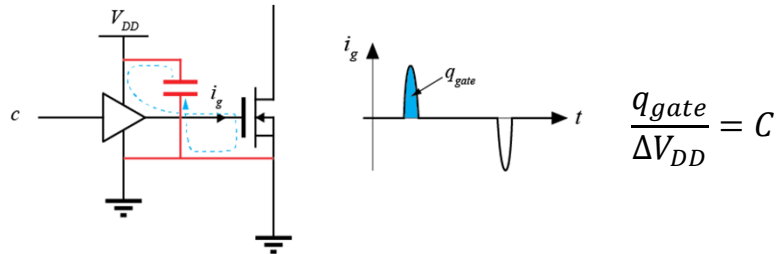

- Area of current pulse is total charge supplied to gate of capacitor
- All charge must be supplied from gate drive decoupling capacitor




Gate Drive Losses

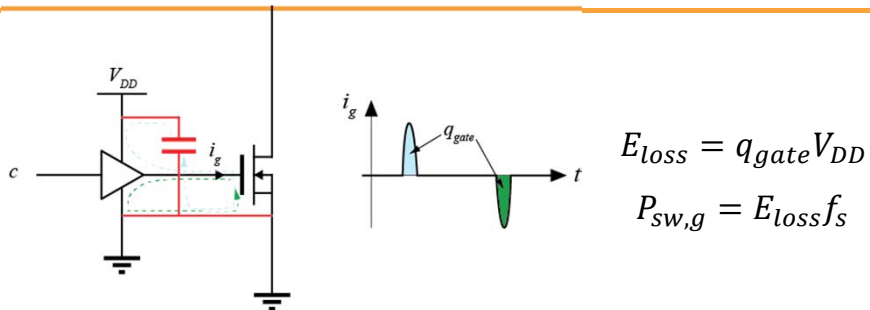

- Gate charge is supplied through driver resistance during switch turn-on
- Gate charge is dissipated in gate driver on switch turn-off




High Side Signal Ground

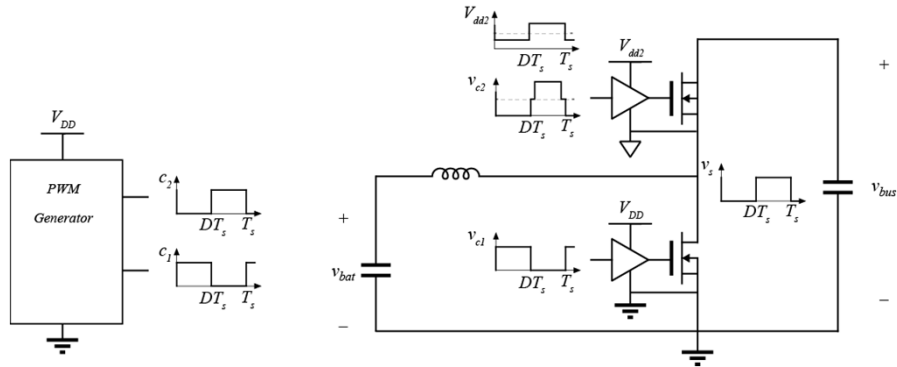

- Gate driver chip must implement v_{gs} waveforms
- Issue: source of Q_2 is not grounded




Generating Floating Supply

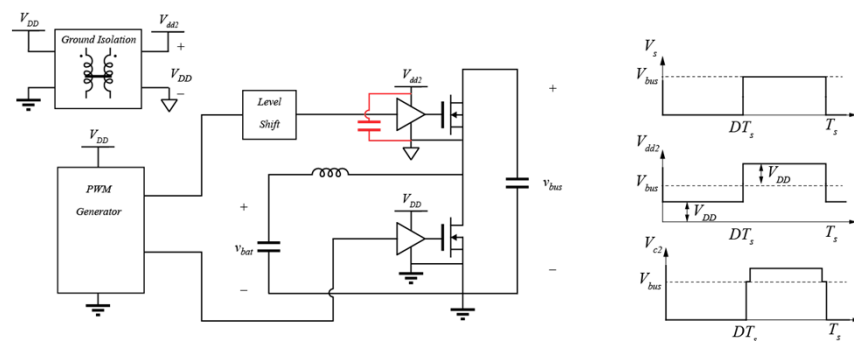


- Isolated supplies sometimes used; Isolated DC-DC, batteries
- Bootstrap concept: capacitor can be charged when V_s is low, then switched



IRS21094 Gate Driver

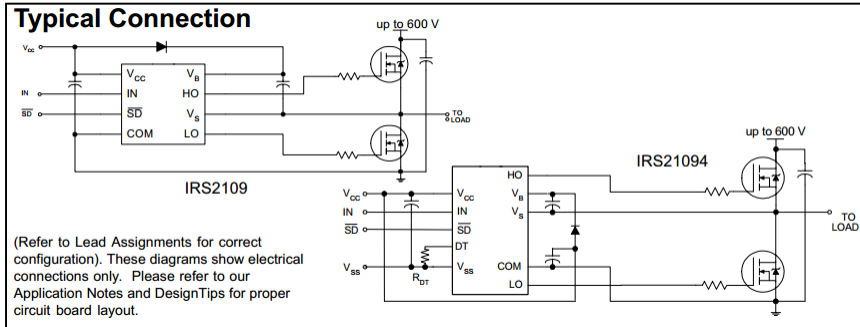

IRS21094 Internal Block Diagram

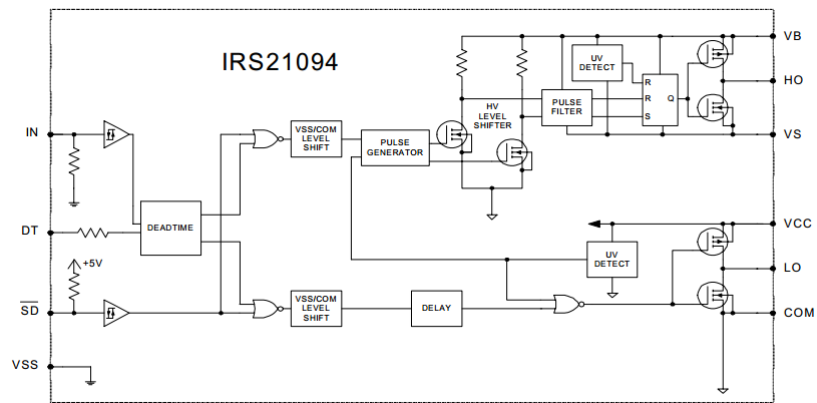



Bootstrap Diode Loss

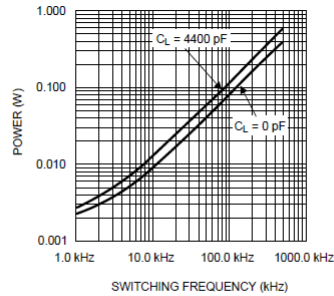


Figure 5. Diode Power Dissipation $V_{IN} = 80V$

- Conduction losses due to pulsating currents are relatively small
- Switching losses are significant
- Diode capacitance and reverse recovery play a role

Direct Drive		<p>Easiest high-side application the MOSFET and can be driven directly by the PWM controller or by a ground referenced driver, but it must meet two conditions, as follows:</p> $V_{CC} < V_{GS_MAX} \text{ and } V_{DC} < V_{CC} - V_{GS_Miller}$
Floating Supply Gate Drive		<p>Cost impact of isolated supply is significant. Optocoupler tends to be relatively expensive, limited in bandwidth, and noise sensitive.</p>
Transformer Coupled Drive		<p>Gives full gate control for an indefinite period of time, but is somewhat limited in switching performance. This can be improved with added complexity.</p>
Charge Pump Drive		<p>The turn-on times tend to be long for switching applications. Inefficiencies in the voltage multiplication circuit may require more than low stages of pumping.</p>
Bootstrap Drive		<p>Simple and inexpensive with limitations; such as, the duty cycle and on-time are both constrained by the need to refresh the bootstrap capacitor. Requires level shift, with the associated difficulties.</p>

Fairchild Semi App Note AN-6076