



# Power Converter Simulation

ECE 482 Lecture 6  
January 27, 2014



# Announcements

- Lab report 1 due today
- This week: Continue Experiment 2
  - Boost open-loop construction and modeling

8. Jan. 27 Simulation of Power Converters <a href="#">Lecture 5 handout slides</a> <a href="#">Experiment 1 Report due</a>	9. Jan. 29 Lab 2 (cont): Steady-State Modeling and Efficiency Analysis of Boost Converter	Jan. 31 Average Current Mode Control
10. Feb. 3 Feedback Loop Design	11. Feb. 5 Lab 3: Closed-Loop Operation of Boost Converter <a href="#">Prelab 3 due</a>	Feb. 7 <a href="#">Experiment 2 Report Due</a>





## Analytical Loss Modeling

- High efficiency approximation is acceptable for hand calculations, as long as it is justified
  - Solve waveforms of lossless converter, then calculate losses
- Alternate approach: average circuit
  - Uses average, rather than RMS currents
  - Difficult to include losses other than conduction
- Argue which losses need to be included, and which may be neglected



## Power Stage Losses

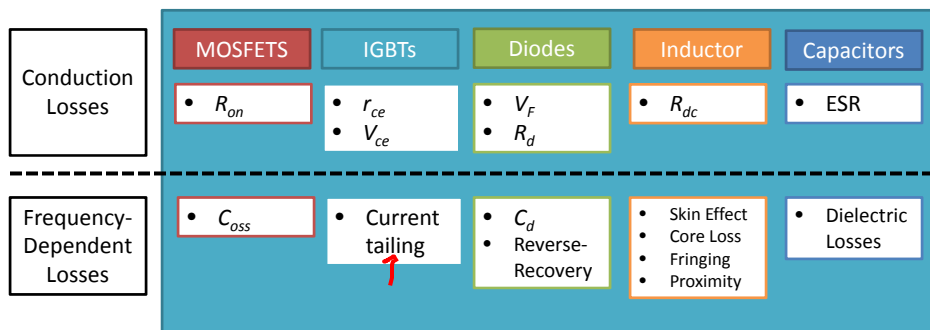

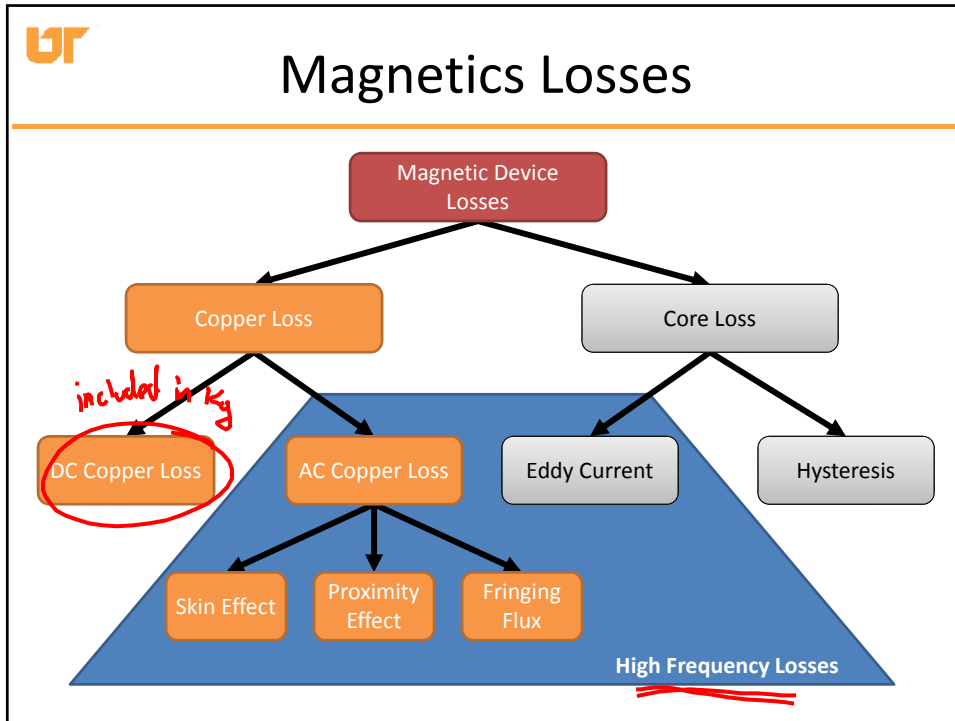

## Inductor Core Loss

- Governed by Steinmetz Equation: *Empirical, curve fit*

$$P_v = K_{fe} f_s^\alpha (\Delta B)^\beta \text{ [mW/cm}^3\text{]}$$



- Parameters  $K_{fe}$ ,  $\alpha$ , and  $\beta$  extracted from manufacturer data
- $\Delta B \propto \Delta i_L \rightarrow$  small losses with small ripple

$\rightarrow P_{fe} = P_v A_c l_m \text{ [mW]}$


$2\Delta B = \frac{1}{nN_c} \int v_c dt$   
*Pos. cycle*



# Steinmetz Parameter Extraction

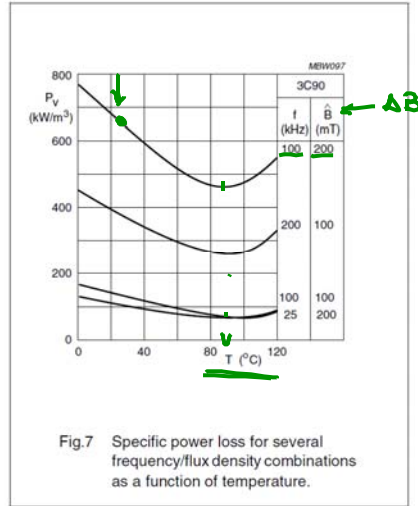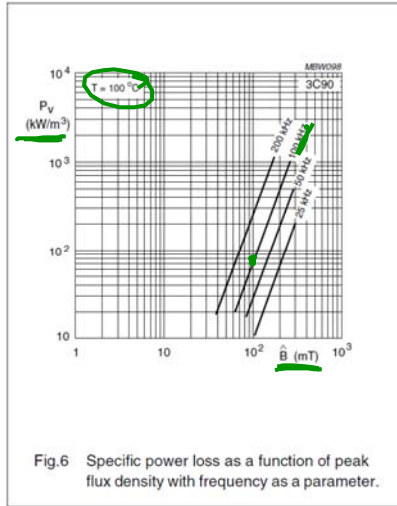

# Ferroxcube Curve Fit Parameters

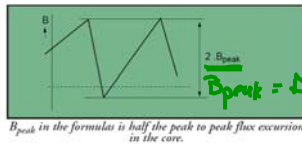

Power losses in our ferrites have been measured as a function of frequency ( $f$  in Hz), peak flux density ( $B$  in T) and temperature ( $T$  in °C). Core loss density can be approximated (2) by the following formula :

$$P_{core} = C_m \cdot f^x \cdot B_{peak}^y \cdot (ct_0 - ct_1 T + ct_2 T^2) \quad [3]$$

$$= C_m \cdot C_T \cdot f^x \cdot B_{peak}^y \quad [mW/cm^3]$$

ferrite	f (kHz)	Cm	x	y	ct <sub>2</sub>	ct <sub>1</sub>	ct <sub>0</sub>
3C30	20-100	7.13.10 <sup>-3</sup>	1.42	3.02	3.65.10 <sup>-4</sup>	6.65.10 <sup>-2</sup>	4
	100-200	7.13.10 <sup>-3</sup>	1.42	3.02	4.10 <sup>-4</sup>	6.8.10 <sup>-2</sup>	3.8
3C90	20-200	3.2.10 <sup>-3</sup>	1.46	2.75	1.65.10 <sup>-4</sup>	3.1.10 <sup>-2</sup>	2.45
3C94	20-200	2.37.10 <sup>-3</sup>	1.46	2.75	1.65.10 <sup>-4</sup>	3.1.10 <sup>-2</sup>	2.45
	200-400	2.10 <sup>-3</sup>	2.6	2.75	1.65.10 <sup>-4</sup>	3.1.10 <sup>-2</sup>	2.45
3F3	100-300	0.25.10 <sup>-3</sup>	1.63	2.45	0.79.10 <sup>-4</sup>	1.05.10 <sup>-2</sup>	1.26
	300-500	2.10 <sup>-5</sup>	1.8	2.5	0.77.10 <sup>-4</sup>	1.05.10 <sup>-2</sup>	1.28
	500-1000	3.6.10 <sup>-9</sup>	2.4	2.25	0.67.10 <sup>-4</sup>	0.81.10 <sup>-2</sup>	1.14
3F4	500-1000	12.10 <sup>-4</sup>	1.75	2.9	0.95.10 <sup>-4</sup>	1.1.10 <sup>-2</sup>	1.15
	1000-3000	1.1.10 <sup>-11</sup>	2.8	2.4	0.34.10 <sup>-4</sup>	0.01.10 <sup>-2</sup>	0.67


Table 1: Fit parameters to calculate the power loss density



## → NSE/iGSE

- More complex empirical loss models exist, and remain valid for non-sinusoidal waveforms
- NSE/iGSE:

$$P_{NSE} = \left(\frac{\Delta B}{2}\right)^{\beta-\alpha} \frac{k_N}{T} \int_0^T \left|\frac{dB}{dt}\right|^\alpha dt$$

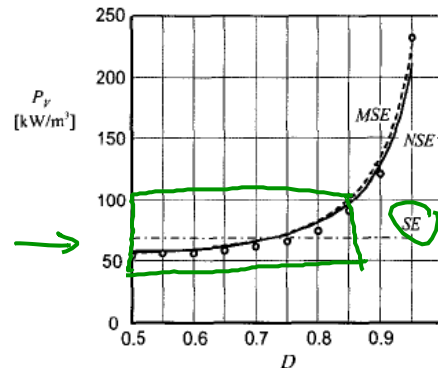

## NSE/iGSE Shortcut for Squarewaves

- For square wave excitation, the improved loss model can be reduced to:


$$k_N = \frac{k_{ge}}{(2\pi)^{\alpha-1} \int_0^{2\pi} |\cos \theta|^\alpha d\theta} \quad (8)$$

$$P_{NSE} = k_N f^\alpha (\Delta B)^\beta \left[ \left(\frac{2}{D}\right)^\alpha + \left(\frac{2}{1-D}\right)^\alpha (1-D) \right] \quad (9)$$


- Full Paper included on materials page of website



# Inductor Design

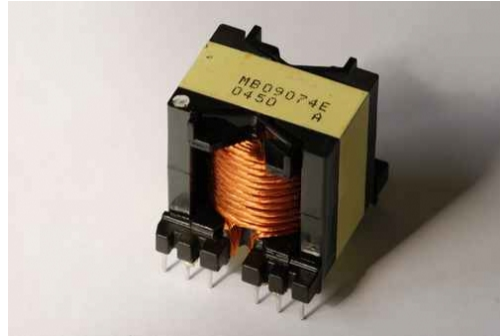

# Magnetics Losses

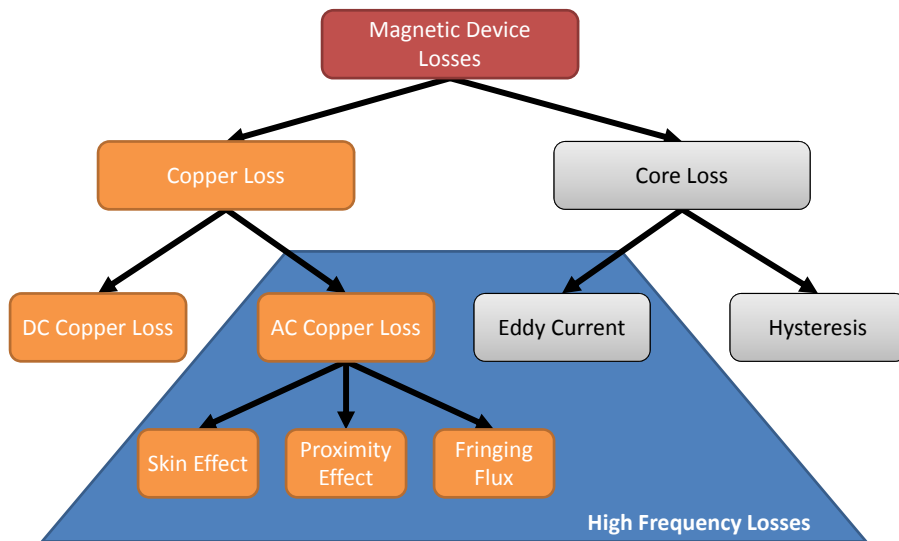



## $K_g$ and $K_{gfe}$ Methods

- Two closed-form methods to solve for the optimal inductor design *under certain constraints/assumptions*
- Neither method considers losses other than DC copper and (possibly) Steinmetz core loss
- Both methods particularly well suited to spreadsheet/iterative design procedures

	$K_g$	$K_{gfe}$
Losses	DC Copper (specified)	DC Copper, SE Core Loss (optimized)
Saturation	Specified	Checked After
$B_{max}$	Specified	Optimized



## $K_g$ Method Derivation

The four constraints:

$$nI_{max} = B_{max} A_c \mathcal{R}_g = B_{max} \frac{\ell_g}{\mu_0} \quad L = \frac{n^2}{\mathcal{R}_g} = \frac{\mu_0 A_c n^2}{\ell_g}$$

$$K_u W_A \geq n A_W \quad R = \rho \frac{n (MLT)}{A_W}$$

These equations involve the quantities

$A_c$ ,  $W_A$ , and  $MLT$ , which are functions of the core geometry,

$I_{max}$ ,  $B_{max}$ ,  $\mu_0$ ,  $L$ ,  $K_u$ ,  $R$ , and  $\rho$ , which are given specifications or other known quantities, and

$n$ ,  $\ell_g$ , and  $A_W$ , which are unknowns.

Elimination of  $n$ ,  $\ell_g$ , and  $A_W$  leads to

$$\frac{A_c^2 W_A}{(MLT)} \geq \frac{\rho L^2 I_{max}^2}{B_{max}^2 R K_u}$$

$\uparrow K_g$



## Simulation Modeling

15




## Circuit Simulation

- Matlab, Simulink, LTSpice
  - Other tools accepted, but not supported
- Choose model type (switching, averaged,  
dynamic)
- Supplement analytical work rather than repeating it
- Show results which clearly demonstrate what matches and what does not with respect to experiments (i.e. ringing, slopes, etc.)






# LTSpice Modeling Examples

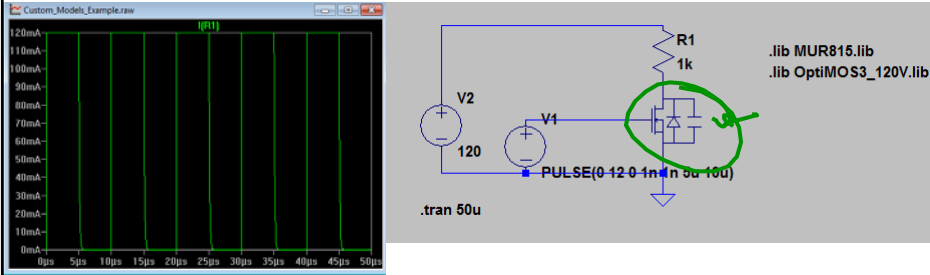

- Example files added to course materials page



# Custom Transistor Model

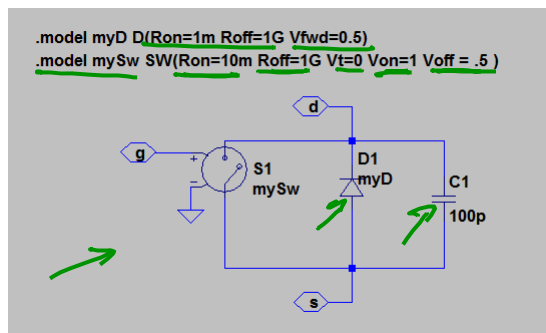




## Manufacturer Device Model

- Text-only netlist model of device including additional parasitics and temperature effects
- May slow or stop simulation if timestep and accuracy are not adjusted appropriately




## Full Switching Simulation

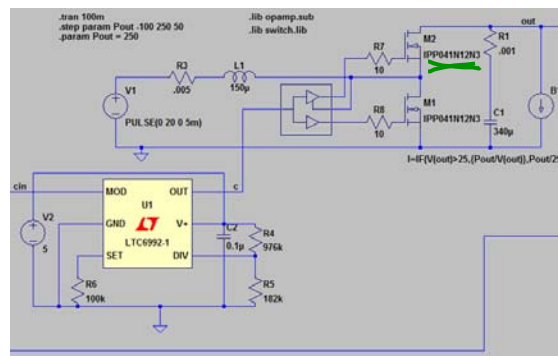



## Switching Model Simulation Results

- Simulation Time  $\approx$  15 minutes

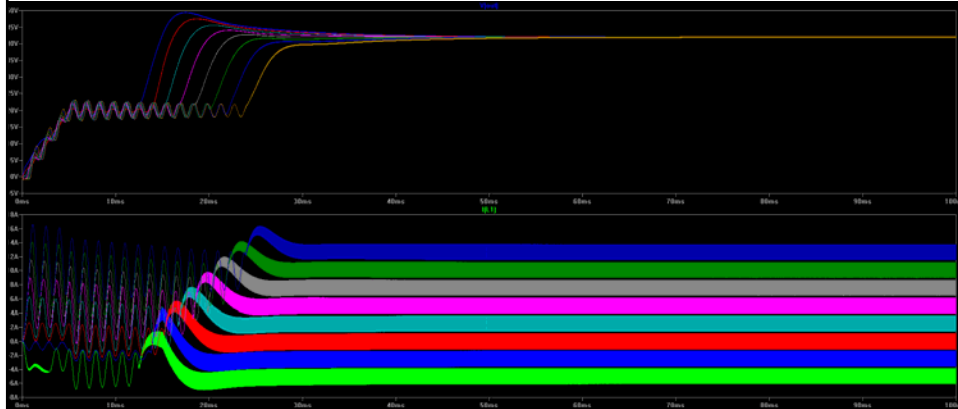

## Full Switching Model

- Gives valuable insight into circuit operation
  - Understand expected waveforms
  - Identify discrepancies between predicted and experimental operation
- Slow to simulate; significant high frequency content
- Cannot perform AC analysis




## Averaged Switch Modeling: Motivation

- A large-signal, nonlinear model of converter is difficult for hand analysis, but well suited to simulation across a wide range of operating points
- Want an *averaged* model to speed up simulation speed
- Also allows linearization (AC analysis) for control design



## Nonlinear, Large-Signal Equations

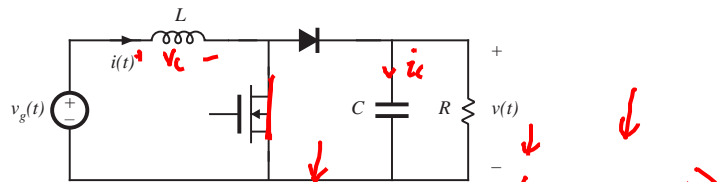

$$\langle v_L \rangle = L \frac{d\langle i_L \rangle}{dt} = d(t) \langle v_g(t) \rangle + d'(t) \langle v_g(t) \rangle - \langle v(t) \rangle$$

$$\langle i_C \rangle = C \frac{d\langle v(t) \rangle}{dt} = -\frac{\langle v \rangle}{R} + d'(t) \langle i_L(t) \rangle - \frac{\langle v(t) \rangle}{R}$$

DC only

$$\hat{\phi} = V_g - D'V$$

$$\hat{\phi} = D'I_L - \frac{V}{R}$$

Averaged AC

$$L \frac{d\hat{i}_L}{dt} = \hat{v}_g - D'\hat{v} + \hat{v}_d$$

$$C \frac{d\hat{v}}{dt} = -\frac{\hat{v}}{R} + D'\hat{i}_L - I_L d$$

**UF**

## Nonlinear, Averaged Circuit

$$L \frac{d\langle i_L \rangle}{dt} = \langle v_{bat} \rangle - (1-d)\langle v_{bus} \rangle$$

$$C \frac{d\langle v_{bus} \rangle}{dt} = (1-d)\langle i_L \rangle - \langle i_{bus} \rangle$$

**UF**

## Implementation in LTSpice

*Averaged switch model*

$V=(1-V(d))*V(2,3)$


$I=(1-V(d))*I(B1)$

$d$

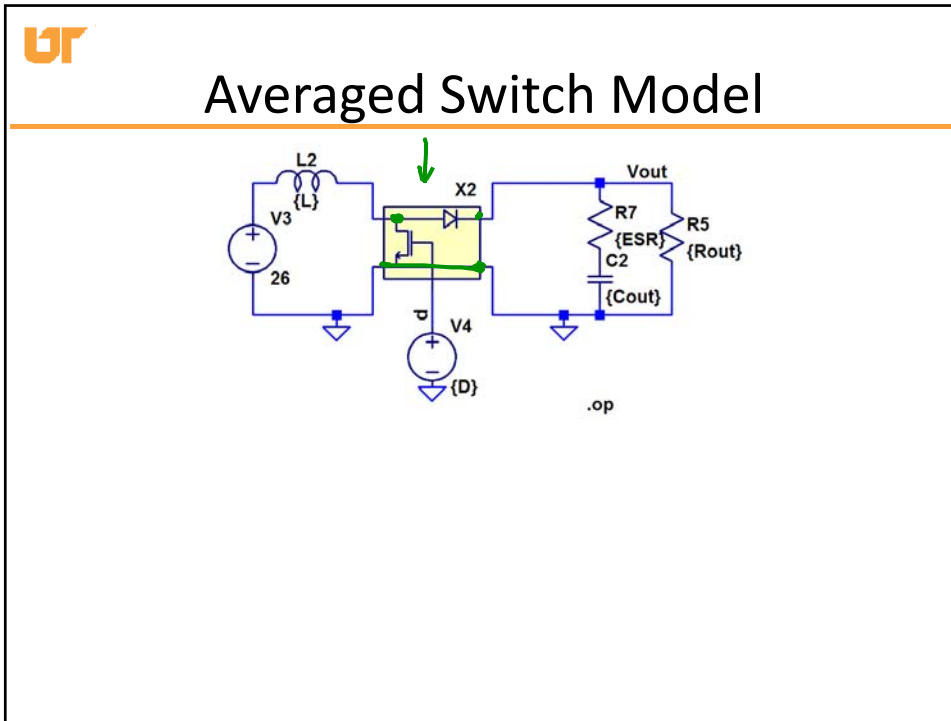**X1**

$$\langle v_1(t) \rangle_{T_s} = d'(t) \langle v_2(t) \rangle_{T_s}$$

$$\langle i_2(t) \rangle_{T_s} = d'(t) \langle i_1(t) \rangle_{T_s}$$



### Averaged Model With Losses

$P_{loss,c} = C_{eg} V_{in}^2 f_s = \frac{V_{in}^2}{2 C_{eg} f_s}$

$P_{rr} = V_{out} f_s [I_c + r_r + Q_r]$

$I_{sw} = f_s Q_r$

```

.op
.param Rout = 10
.step param Rout 10 100 10
    
```

