



Power Converter Simulation

ECE 482 Lecture 6
January 27, 2014



Announcements

- Lab report 1 due today
- This week: Continue Experiment 2
 - Boost open-loop construction and modeling




Analytical Loss Modeling

- High efficiency approximation is acceptable for hand calculations, as long as it is justified
 - Solve waveforms of lossless converter, then calculate losses
- Alternate approach: average circuit
 - Uses average, rather than RMS currents
 - Difficult to include losses other than conduction
- Argue which losses need to be included, and which may be neglected



Power Stage Losses

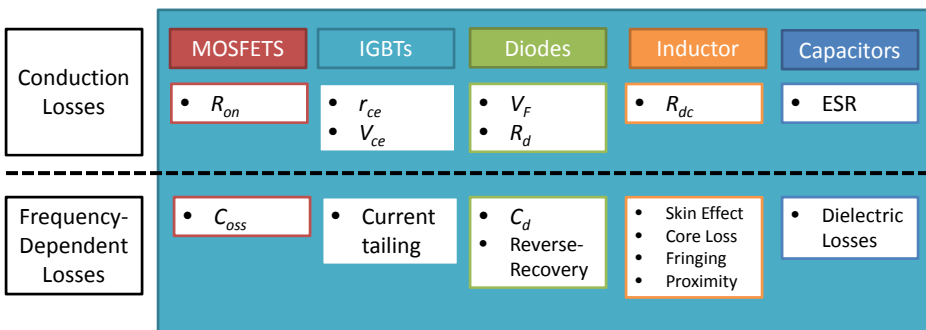




Inductor Core Loss

- Governed by Steinmetz Equation:



$$P_v = K_{fe} f_s^\alpha (\Delta B)^\beta \quad [\text{mW/cm}^3]$$

- Parameters K_{fe} , α , and β extracted from manufacturer data
- $\Delta B \propto \Delta i_L \rightarrow$ small losses with small ripple
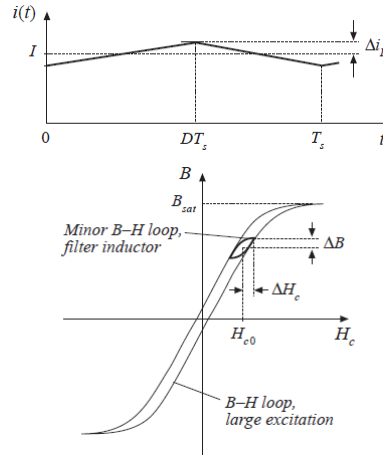
$$P_{fe} = P_v A_c l_m \quad [\text{mW}]$$




Steinmetz Parameter Extraction

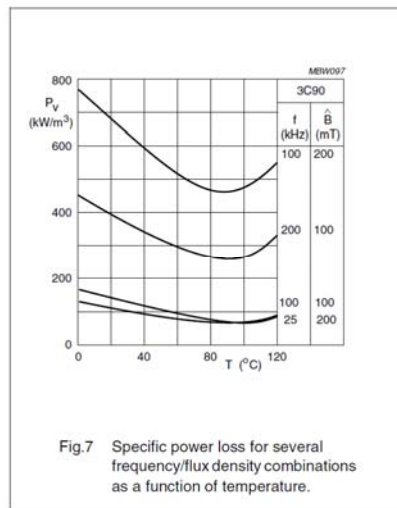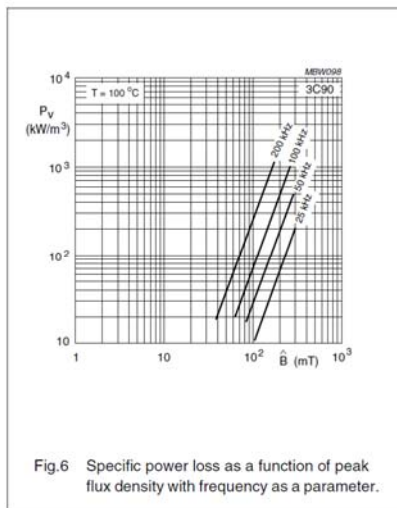



Ferroxcube Curve Fit Parameters

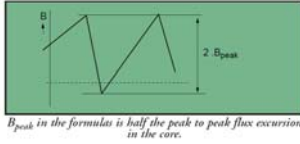

Power losses in our ferrites have been measured as a function of frequency (f in Hz), peak flux density (B in T) and temperature (T in °C). Core loss density can be approximated ⁽²⁾ by the following formula :

$$P_{core} = C_m \cdot f^x \cdot B_{peak}^y \cdot (ct_0 - ct_1 T + ct_2 T^2) \quad [3]$$

$$= C_m \cdot C_T \cdot f^x \cdot B_{peak}^y \quad [mW/cm^3]$$

ferrite	f (kHz)	Cm	x	y	ct ₂	ct ₁	ct ₀
3C30	20-100	7.13.10 ⁻³	1.42	3.02	3.65.10 ⁻⁴	6.65.10 ⁻²	4
	100-200	7.13.10 ⁻³	1.42	3.02	4.10 ⁻⁴	6.8 .10 ⁻²	3.8
3C90	20-200	3.2.10 ⁻³	1.46	2.75	1.65.10 ⁻⁴	3.1.10 ⁻²	2.45
3C94	20-200	2.37.10 ⁻³	1.46	2.75	1.65.10 ⁻⁴	3.1.10 ⁻²	2.45
	200-400	2.10 ⁻⁹	2.6	2.75	1.65.10 ⁻⁴	3.1.10 ⁻²	2.45
3F3	100-300	0.25.10 ⁻³	1.63	2.45	0.79.10 ⁻⁴	1.05.10 ⁻²	1.26
	300-500	2.10 ⁻⁵	1.8	2.5	0.77.10 ⁻⁴	1.05.10 ⁻²	1.28
	500-1000	3.6.10 ⁻⁹	2.4	2.25	0.67.10 ⁻⁴	0.81.10 ⁻²	1.14
3F4	500-1000	12.10 ⁻⁴	1.75	2.9	0.95.10 ⁻⁴	1.1.10 ⁻²	1.15
	1000-3000	1.1.10 ⁻¹¹	2.8	2.4	0.34.10 ⁻⁴	0.01.10 ⁻²	0.67


Table 1: Fit parameters to calculate the power loss density



NSE/iGSE

- More complex empirical loss models exist, and remain valid for non-sinusoidal waveforms
- NSE/iGSE:

$$P_{NSE} = \left(\frac{\Delta B}{2}\right)^{\beta-\alpha} \frac{k_N}{T} \int_0^T \left|\frac{dB}{dt}\right|^\alpha dt$$

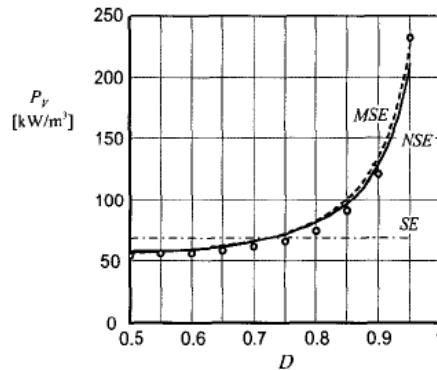



NSE/iGSE Shortcut for Squarewaves

- For square wave excitation, the improved loss model can be reduced to:

$$k_N = \frac{k}{(2\pi)^{\alpha-1} \int_0^{2\pi} |\cos \theta|^\alpha d\theta} \quad (8)$$


$$P_{NSE} = k_N f^\alpha (\Delta B)^\beta \left(\left(\frac{2}{D} \right)^\alpha + \left(\frac{2}{1-D} \right)^\alpha (1-D) \right) \quad (9)$$


- Full Paper included on materials page of website

Van den Bossche, A.; Valchev, V.C.; Georgiev, G.B.; "Measurement and loss model of ferrites with non-sinusoidal waveforms," *Power Electronics Specialists Conference, 2004. PESC 04. 2004 IEEE 35th Annual*, vol.6, no., pp. 4814- 4818 Vol.6, 20-25 June 2004 doi: 10.1109/PESC.2004.1354851



Inductor Design

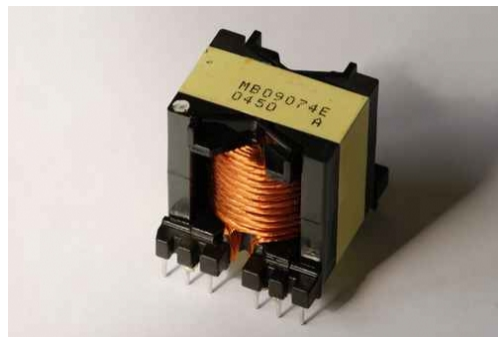

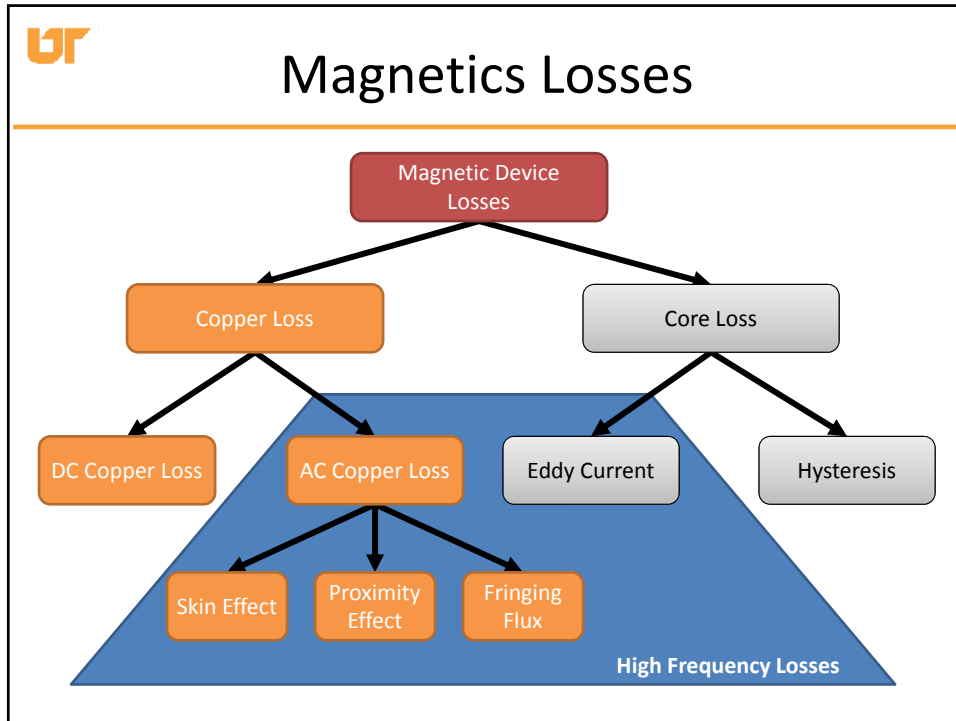

UF

K_g and K_{gfe} Methods

- Two closed-form methods to solve for the optimal inductor design *under certain constraints/assumptions*
- Neither method considers losses other than DC copper and (possibly) steinmetz core loss
- Both methods particularly well suited to spreadsheet/iterative design procedures

	K_g	K_{gfe}
Losses	DC Copper (specified)	DC Copper, SE Core Loss (optimized)
Saturation	Specified	Checked After
B_{max}	Specified	Optimized



Simulation Modeling

13




Circuit Simulation

- Matlab, Simulink, LTSpice
 - Other tools accepted, but not supported
- Choose model type (switching, averaged, dynamic)
- Supplement analytical work rather than repeating it
- Show results which clearly demonstrate what matches and what does not with respect to experiments (i.e. ringing, slopes, etc.)



LTSpice Modeling Examples

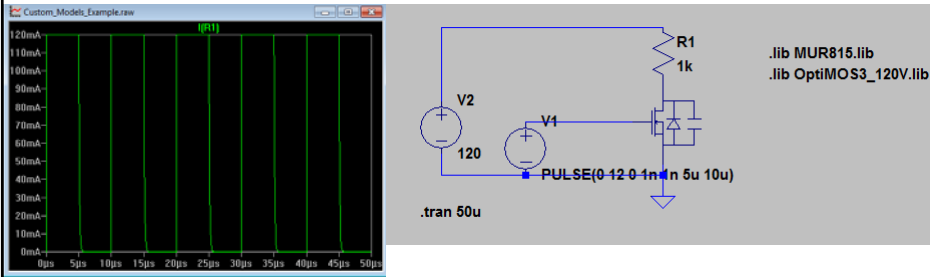


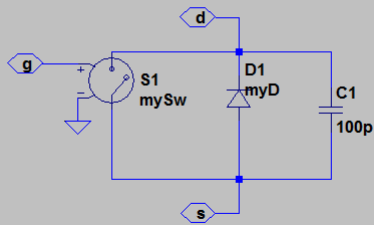- Example files added to course materials page



Custom Transistor Model

```
.model myD D(Ron=1m Roff=1G Vfwd=0.5)
.model mySw SW(Ron=10m Roff=1G Vt=0 Von=1 Voff = .5 )
```






Manufacturer Device Model

- Text-only netlist model of device including additional parasitics and temperature effects
- May slow or stop simulation if timestep and accuracy are not adjusted appropriately




Full Switching Simulation

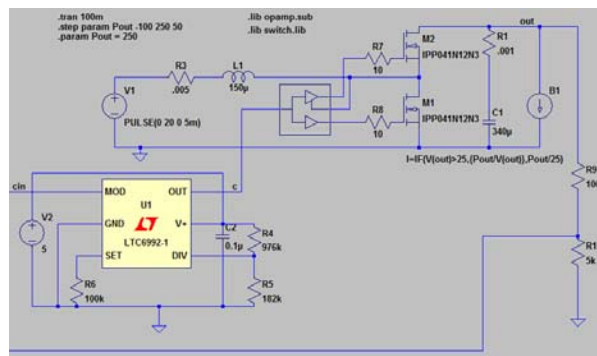



Switching Model Simulation Results

- Simulation Time \approx 15 minutes

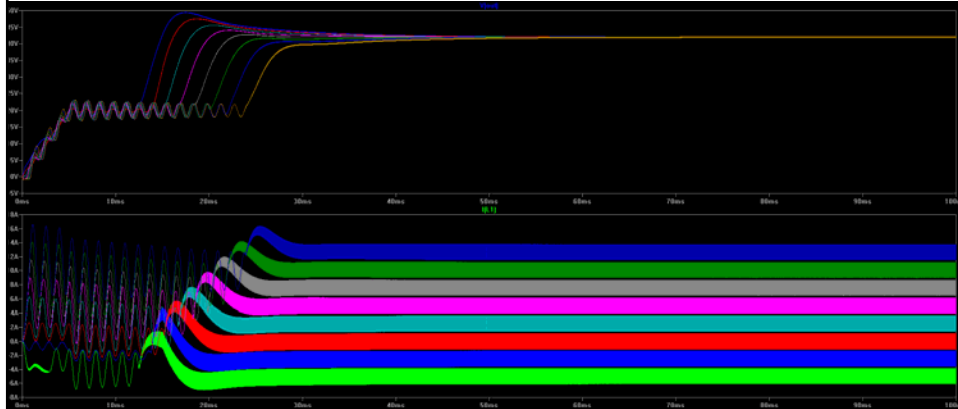

Full Switching Model

- Gives valuable insight into circuit operation
 - Understand expected waveforms
 - Identify discrepancies between predicted and experimental operation
- Slow to simulate; significant high frequency content
- Cannot perform AC analysis




Averaged Switch Modeling: Motivation

- A *large-signal, nonlinear* model of converter is difficult for hand analysis, but well suited to simulation across a wide range of operating points
- Want an *averaged* model to speed up simulation speed
- Also allows linearization (AC analysis) for control design



Nonlinear, Large-Signal Equations

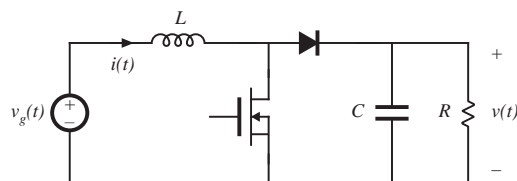

UF

Nonlinear, Averaged Circuit

$$L \frac{d\langle i_L \rangle}{dt} = \langle v_{bat} \rangle - (1-d)\langle v_{bus} \rangle$$

$$C \frac{d\langle v_{bus} \rangle}{dt} = (1-d)\langle i_L \rangle - \langle i_{bus} \rangle$$

UF

Implementation in LTSpice

Averaged switch model

$$\langle v_1(t) \rangle_{T_s} = d'(t) \langle v_2(t) \rangle_{T_s}$$

$$\langle i_2(t) \rangle_{T_s} = d'(t) \langle i_1(t) \rangle_{T_s}$$




Circuit Averaging and Averaged Switch Modeling

- Historically, circuit averaging was the first method known for modeling the small-signal ac behavior of CCM PWM converters
- It was originally thought to be difficult to apply in some cases
- There has been renewed interest in circuit averaging and its corrolary, averaged switch modeling, in the last two decades
- Can be applied to a wide variety of converters
 - We will use it to model DCM, CPM, and resonant converters
 - Also useful for incorporating switching loss into ac model of CCM converters
 - Applicable to 3 ϕ PWM inverters and rectifiers
 - Can be applied to phase-controlled rectifiers
- Rather than averaging and linearizing the converter state equations, the averaging and linearization operations are performed directly on the converter circuit




Boost converter example

Ideal boost converter example

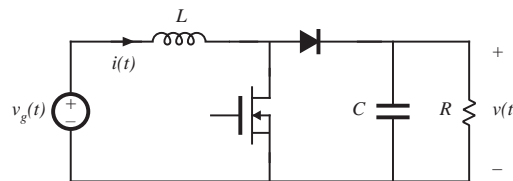


Two ways to define the switch network

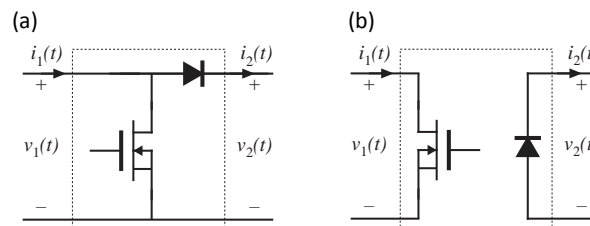




Circuit Averaging

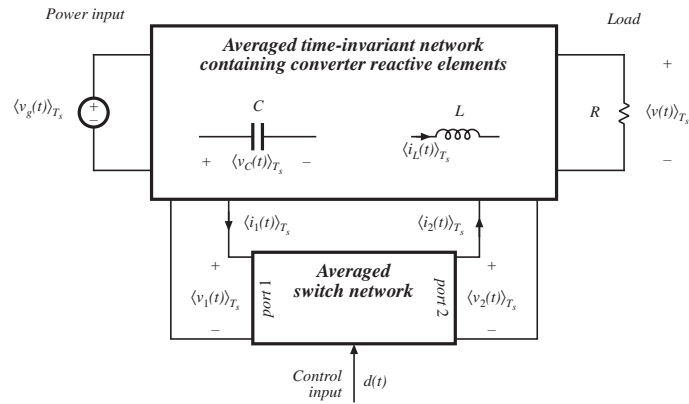


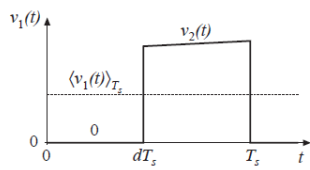Compute average values of dependent sources




Average the waveforms of the dependent sources:
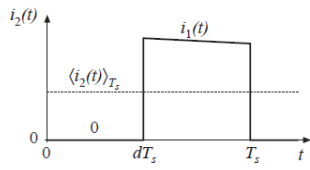
$$\langle v_1(t) \rangle_{T_s} = d'(t) \langle v_2(t) \rangle_{T_s}$$


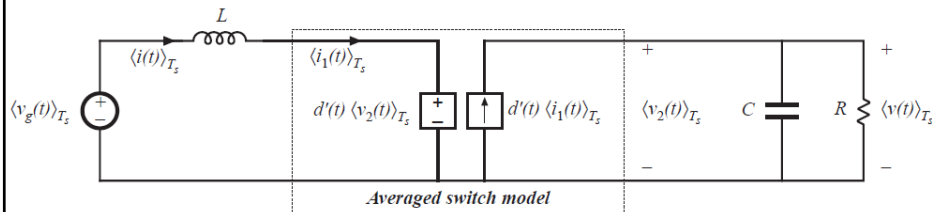
$$\langle i_2(t) \rangle_{T_s} = d'(t) \langle i_1(t) \rangle_{T_s}$$








Summary: Circuit averaging method

Model the switch network with equivalent voltage and current sources, such that an equivalent time-invariant network is obtained

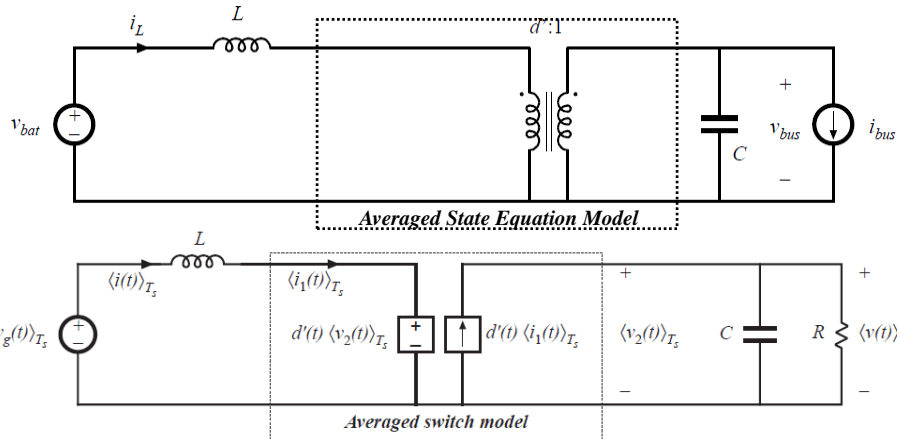Average converter waveforms over one switching period, to remove the switching harmonics





Implementation in LTSpice

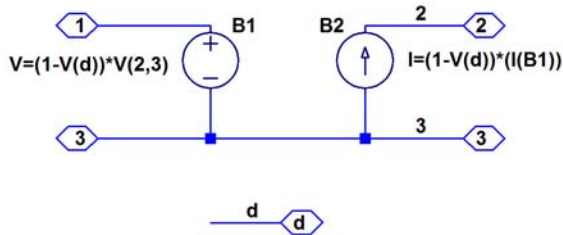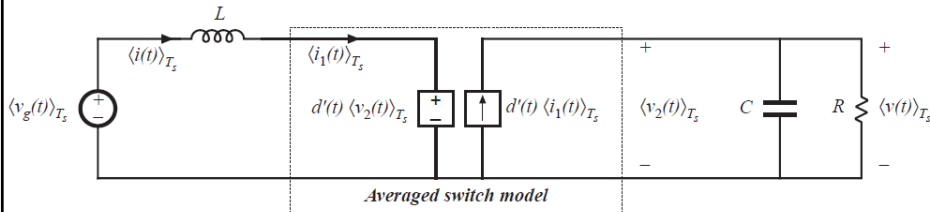

$$\langle v_1(t) \rangle_{T_s} = d'(t) \langle v_2(t) \rangle_{T_s}$$
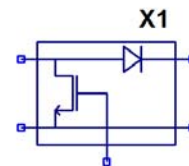
$$\langle i_2(t) \rangle_{T_s} = d'(t) \langle i_1(t) \rangle_{T_s}$$



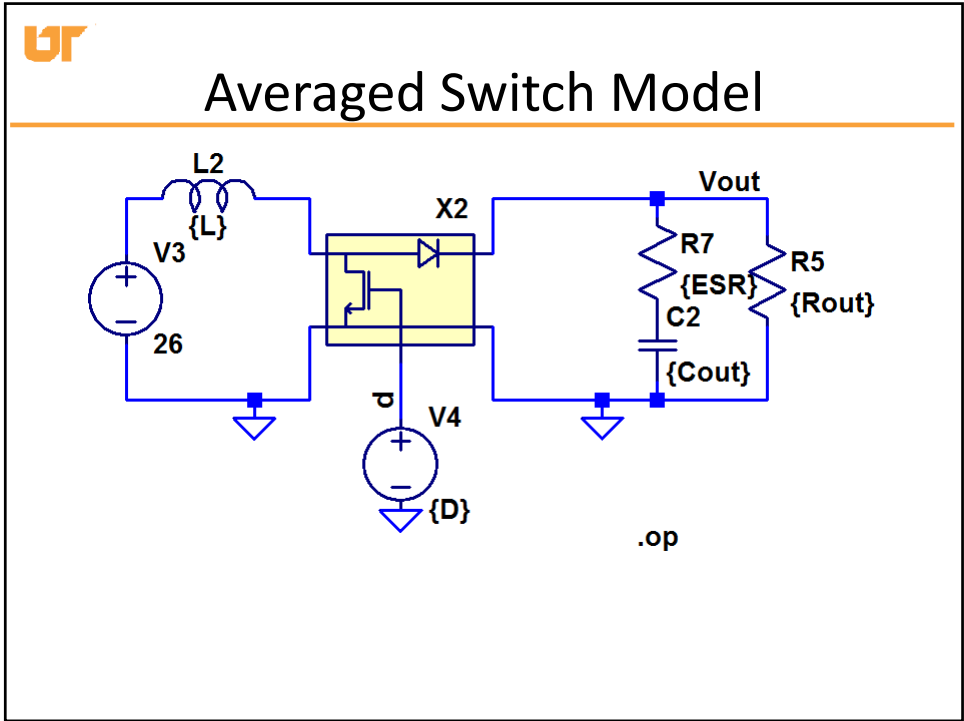


Three Basic Switch Cells

- Can perturb an linearize as normal for linear SSM
- Most general switch cell is included in library file, switch.lib



Switch.lib CCM1 Model

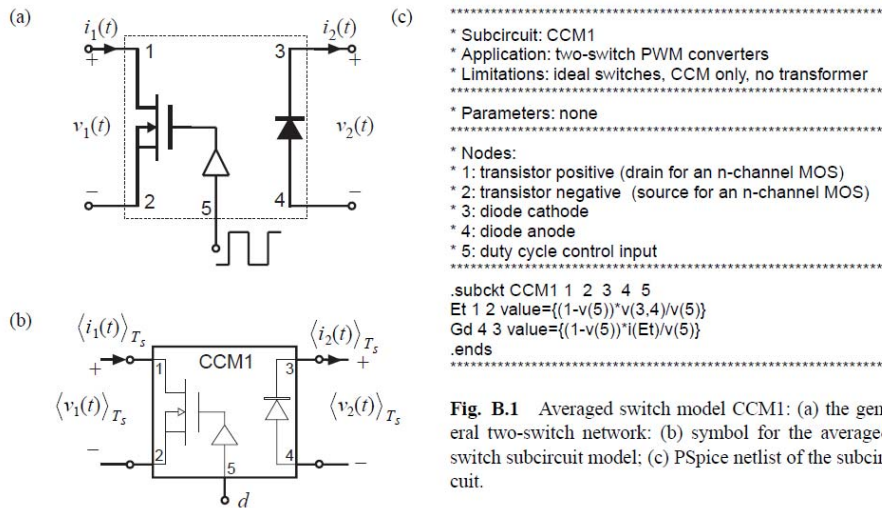Generalized Equations: $\langle v_1(t) \rangle_{T_s} = \frac{d'(t)}{d(t)} \langle v_2(t) \rangle_{T_s}$ $\langle i_2(t) \rangle_{T_s} = \frac{d'(t)}{d(t)} \langle i_1(t) \rangle_{T_s}$





Averaged Switch Modeling: Further Comments

- Model is slightly different but can be produced in same manner for
 - Inclusion of loss models
 - Transformer isolated converters
 - Converters in DCM
- See book appendix B.2 for further notes



Averaged Model With Losses

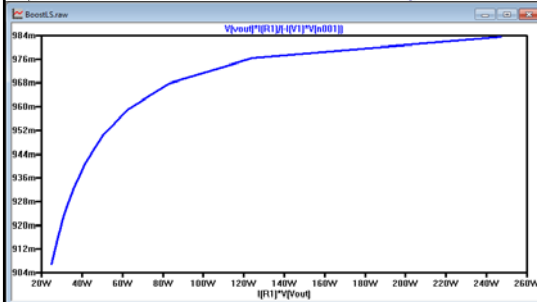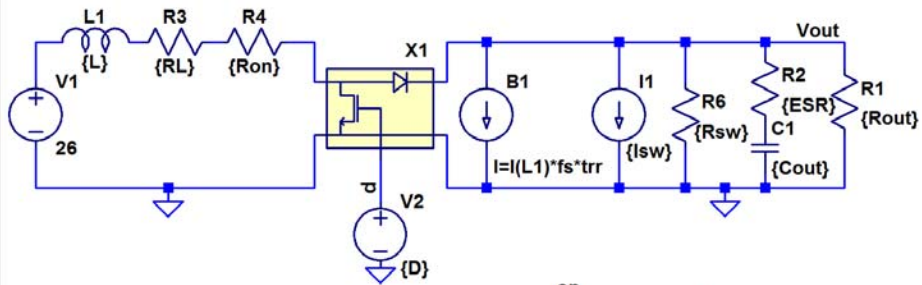

```
.op
.param Rout = 10
.step param Rout 10 100 10
```

What known error will be present in loss predictions with this model?