




Boost Controller Design (cont.)

ECE 482 Lecture 8
February 7, 2014



Controller Implementation

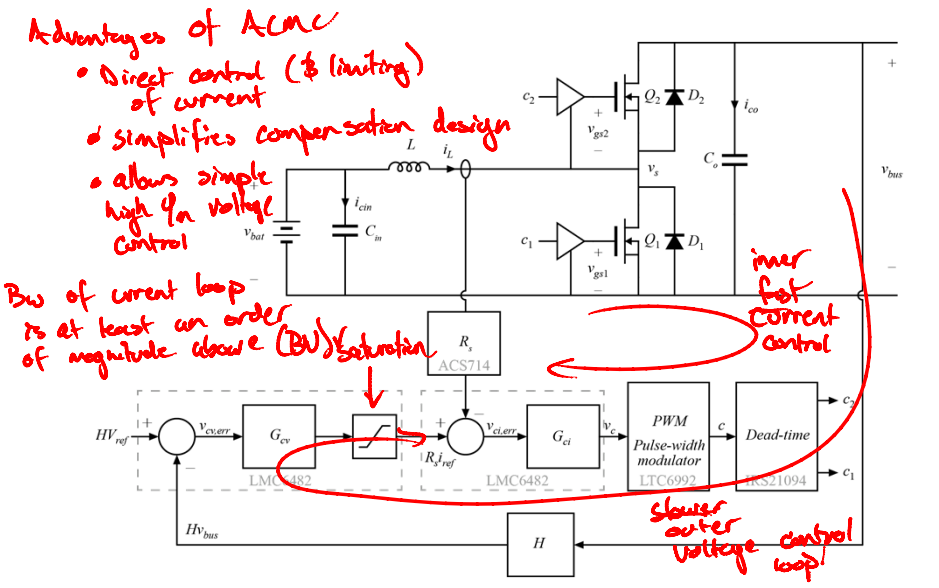



Open-Loop Control-to-Current TF

$$G_{id}(s) = \left. \frac{\hat{i}_L}{\hat{d}} \right|_{\hat{v}_{bat}=0, \hat{i}_{bus}=0} = G_{ido} \frac{1 + \frac{s}{\omega_{zi}}}{1 + \frac{s}{\omega_o}}$$


$$G_{ido} = \frac{I_L}{D'} = \frac{I_{bus}}{(D')^2}$$

$$f_{zi} = \frac{1}{2\pi} \frac{1}{C} \frac{I_{bus}}{V_{bus}}$$

$$f_o = \frac{1}{2\pi} \frac{D'}{\sqrt{LC}}$$



Current Loop Gain

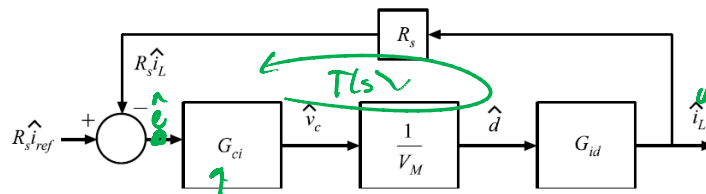


$T(s) = G_{ci} \frac{1}{V_M} G_{id} R_s$
 $\hat{e} = R_s \hat{i}_{ref} - R_s \hat{i} = R_s \hat{i}_{ref} - R_s G_{id} \frac{1}{V_M} G_{ci} \hat{e}$
 $\hat{e} = R_s \hat{i}_{ref} - T(s) \hat{e}$
 $\hat{e} = \frac{R_s \hat{i}_{ref}}{1 + T(s)}$

Design goal #1: Large range of freqs. $T(s) \rightarrow \infty$
 Design goal #2: Extend range of freq w/ $|T(s)| > 1$

$\hat{i} = \hat{e} G_{ci} \frac{1}{V_M} G_{id}$
 $\hat{i} = \hat{i}_{ref} \frac{T}{1+T}$



Loop Gain & Stability

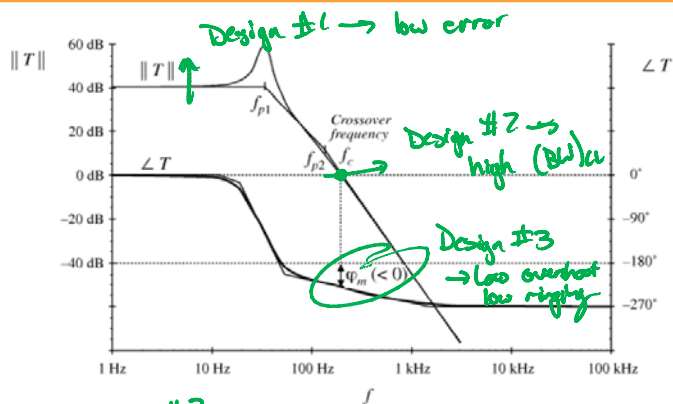

Design Goal #3
 system well stabilized
 → large ϕ_m




ACMC Limits and Saturation




Loop Gain T_i

$$\begin{aligned} I_{bus} &= 5\text{A} \\ V_{bus} &= 50\text{V} \\ V_{bat} &= 26\text{V} \\ L &= 100\mu\text{H} \\ C &= 4 \times 270\mu\text{F} \end{aligned}$$
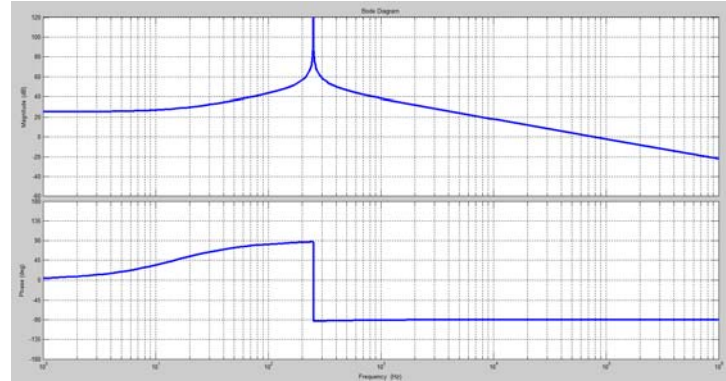
$$\begin{aligned} G_{id0} &= 25.4\text{dB} \\ \omega_{zi} &= 92 \frac{\text{rad}}{\text{sec}} \\ \omega_0 &= 1.6\text{k} \frac{\text{rad}}{\text{sec}} \end{aligned}$$



Compensated Loop Gain

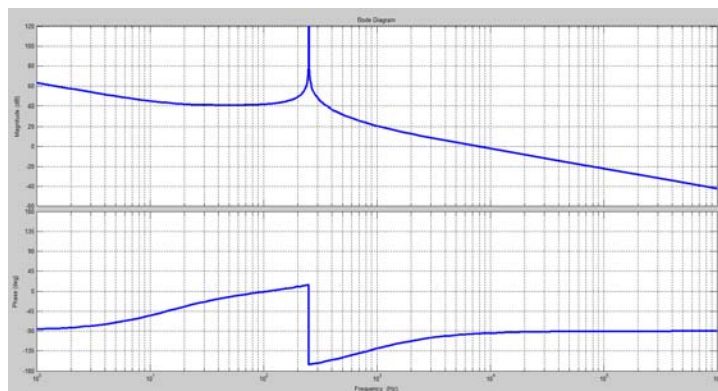


$$G_{ci} = \frac{1}{10} \left(1 + \frac{\omega_{zi}}{s} \right)$$


$$\omega_{zi} = 5 \frac{\text{krad}}{\text{sec}}, \varphi_m = 84^\circ$$





Closed Loop G_i

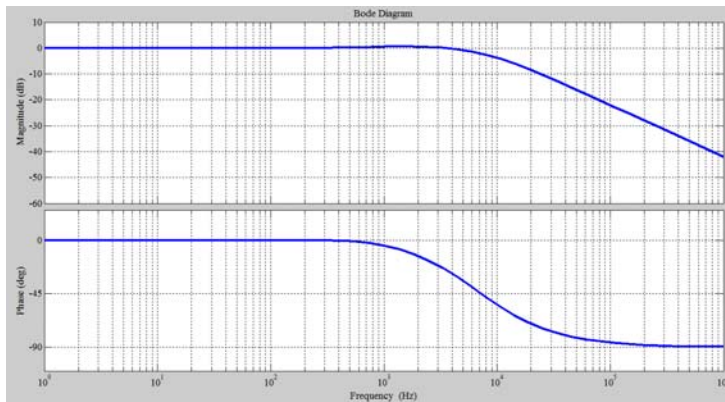


Voltage Loop

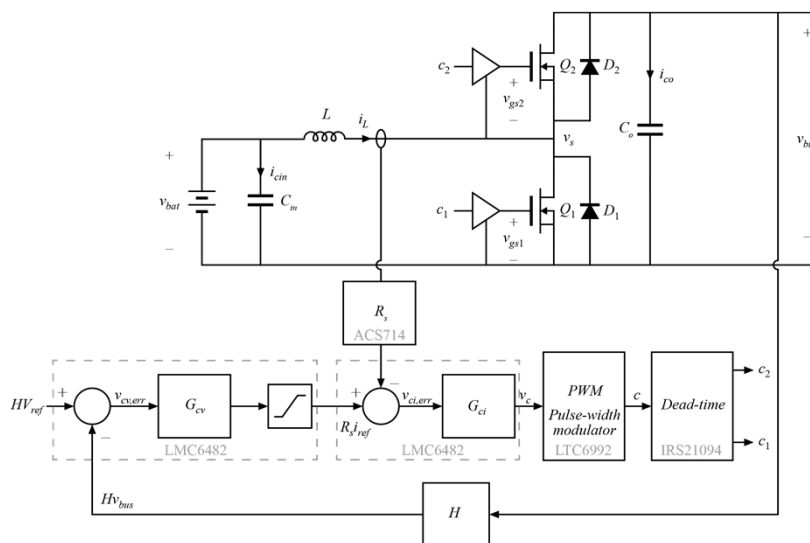

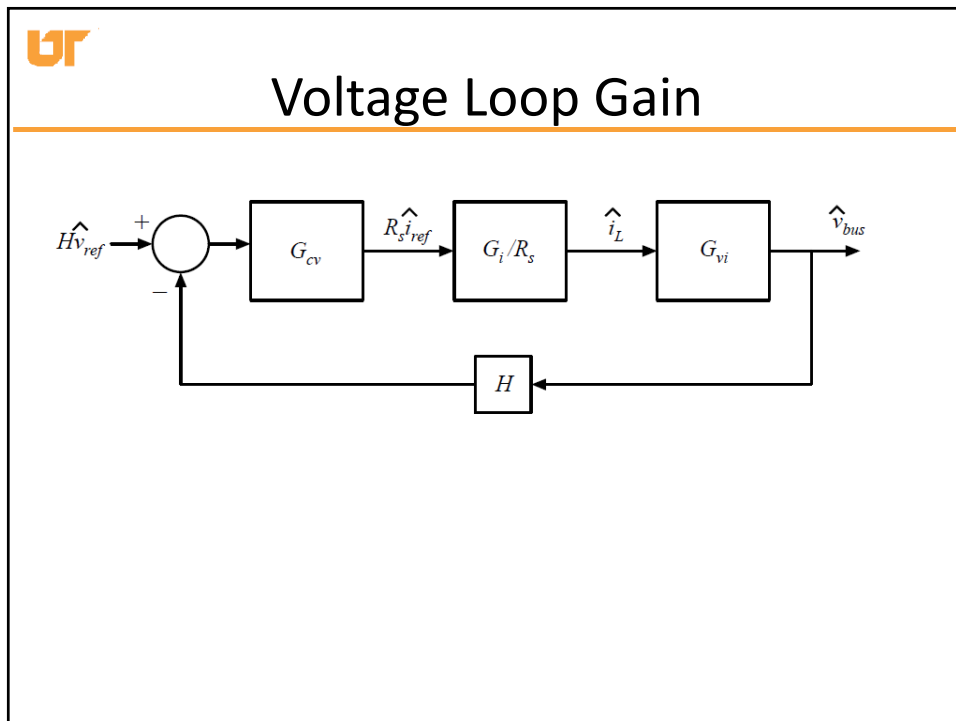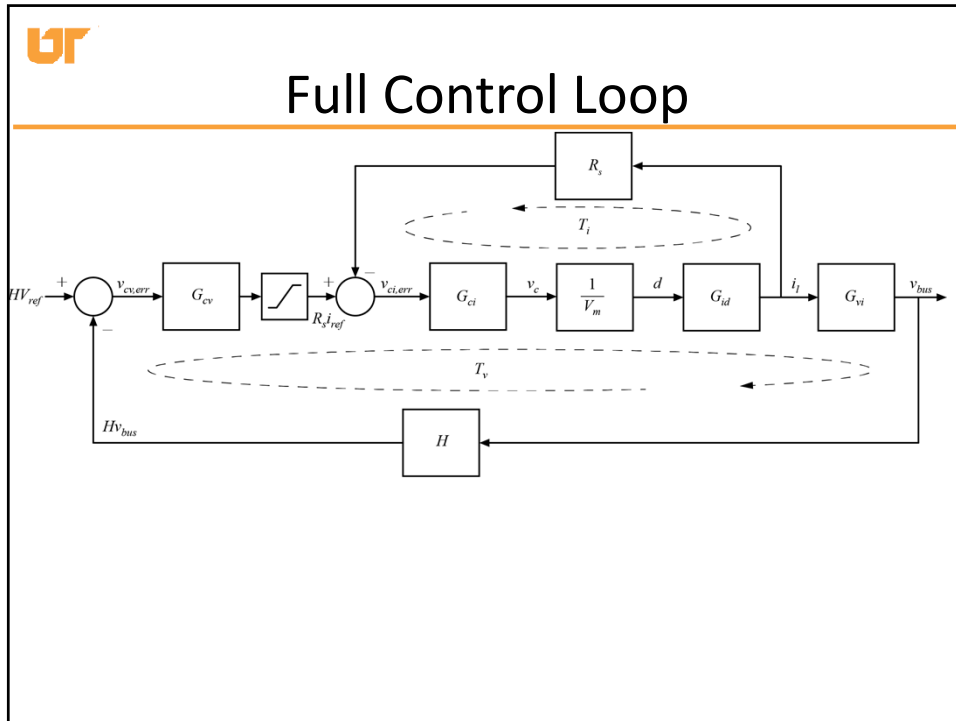



Solving G_{vi}

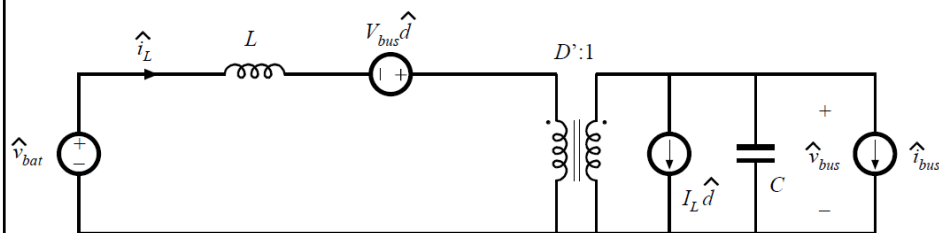

$$G_{vi} = \left. \frac{\hat{v}_{bus}}{\hat{i}_L} \right|_{\hat{v}_{bat}=0, \hat{i}_{bus}=0}$$



Solving G_{vi}



Solving G_{vi}

$$G_{vi} = \left. \frac{\hat{v}_{bus}}{\hat{i}_L} \right|_{\hat{v}_{bat}=0, \hat{i}_{bat}=0} = G_{vio} \frac{1 - \frac{s}{\omega_z}}{1 + \frac{s}{\omega_{zi}}}$$


$$G_{vio} = D' \frac{V_{bus}}{I_{bus}}$$

$$f_z = \frac{1}{2\pi} \frac{D'^2 V_{bus}}{L I_{bus}}$$

$$f_{zi} = \frac{1}{2\pi} \frac{1}{C} \frac{I_{bus}}{V_{bus}}$$




Uncompensated Voltage Loop Gain

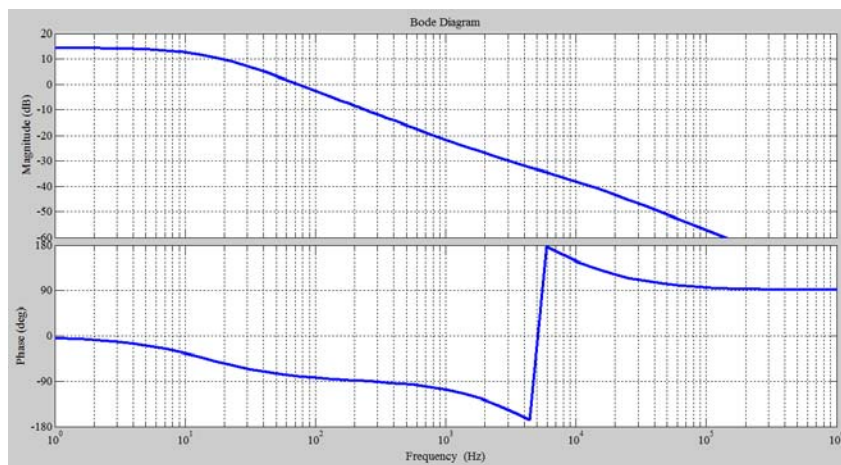



Compensated Loop Gain

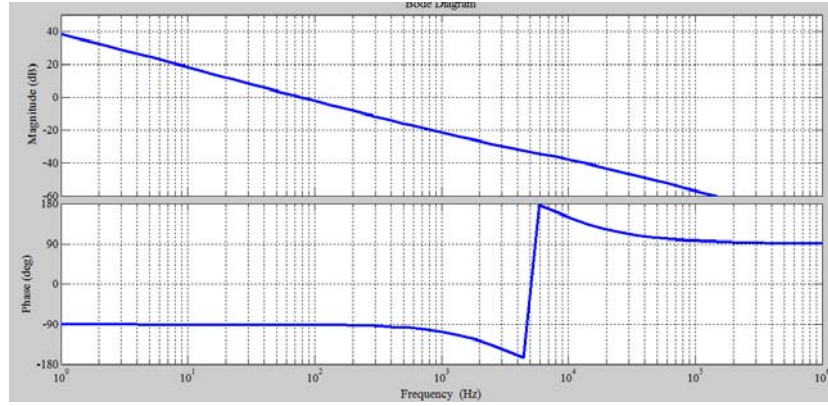

$$G_{ci} = 1 \left(1 + \frac{\omega_{zv}}{s} \right)$$

$$\omega_{zv} = 100 \frac{\text{rad}}{\text{sec}}, \varphi_m = 88^\circ$$



Closed Loop G_v

