



# Voltage Loop and Compensator Design

ECE 482 Lecture 9  
February 10, 2014



## Compensated Loop Gain

### Current Loop Gain

$$T_i = G_{ci} \frac{1}{V_m} G_{id} R_s$$

### Open Loop $d$ -to- $i_L$ TF

$$G_{ido} = \frac{I_L}{D'} = \frac{I_{bus}}{(D')^2}$$


$$f_{ci} = \frac{1}{2\pi} \frac{1}{C} \frac{I_{bus}}{V_{bus}}$$



$$f_o = \frac{1}{2\pi} \frac{D'}{\sqrt{LC}}$$
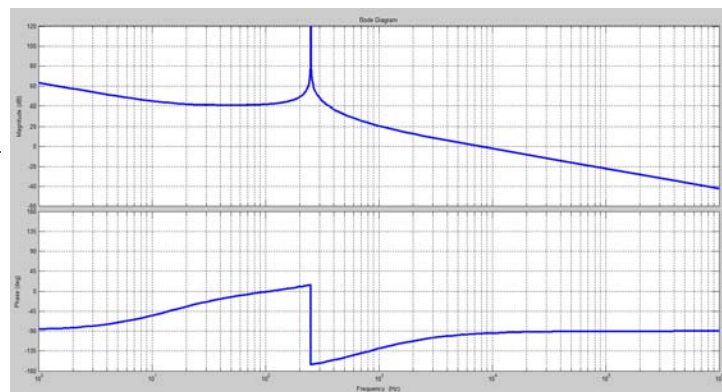
### Compensator

$$G_{ci} = \frac{1}{10} \left( 1 + \frac{\omega_{zi}}{s} \right)$$

$$\omega_{zi} = 5 \frac{\text{krad}}{\text{sec}}, \varphi_m = 84^\circ$$



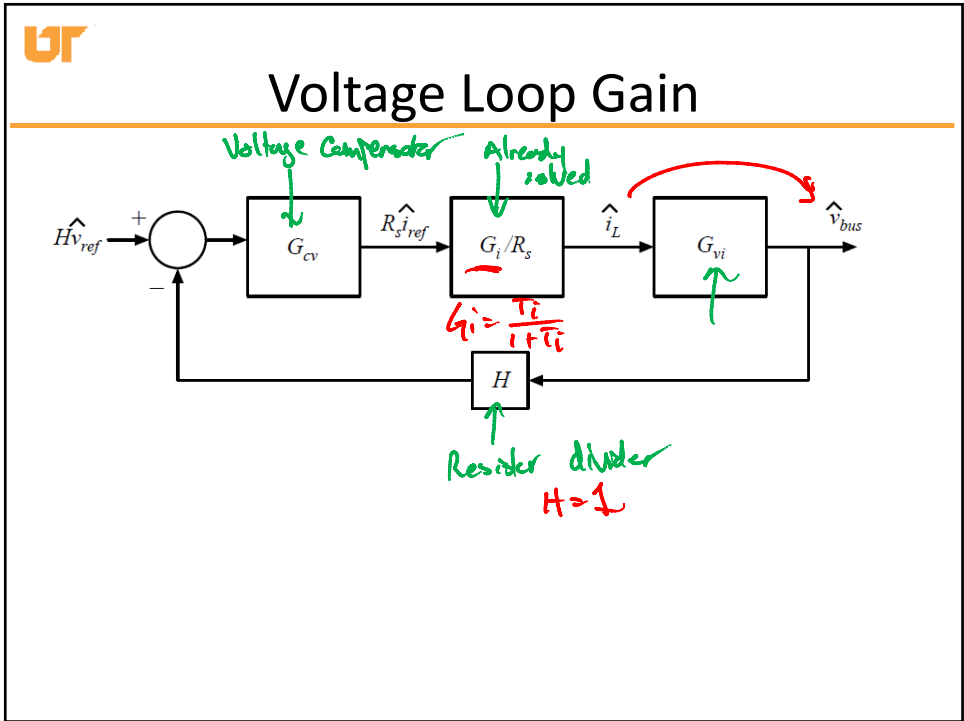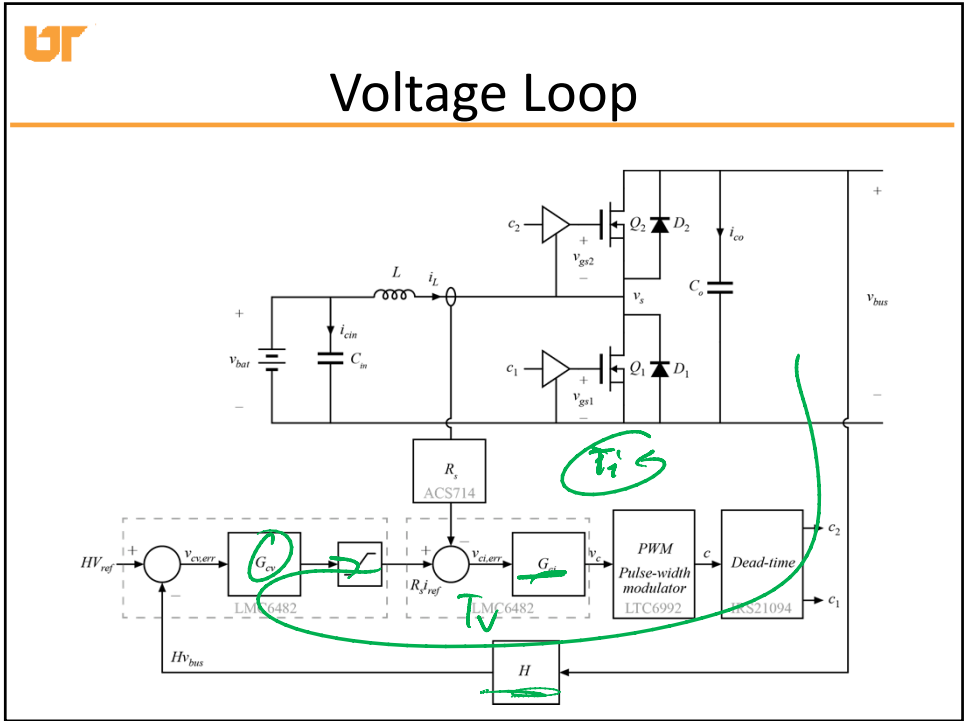

**UT**

## Solving $G_{vi}$

$$G_{vi} = \frac{\hat{v}_{bus}}{\hat{i}_L} \Big|_{\hat{v}_{bat}=0, \hat{i}_{bus}=0}$$

$$\hat{v}_{bus} = \frac{1}{sC} \hat{i}_c = \frac{1}{sC} (\hat{i}_L D' - I_L \hat{d})$$

$$G_{id} = \frac{\hat{i}_c}{\hat{d}} \rightarrow \hat{d} = \frac{\hat{i}_c}{G_{id}}$$

$$\hat{v}_{bus} = \frac{1}{sC} (\hat{i}_L D' - \frac{I_L}{G_{id}} \hat{i}_c)$$

$$G_{vi} = \frac{\hat{v}_{bus}}{\hat{i}_c} = \frac{1}{sC} \left( D' - \frac{I_L}{G_{id}} \right)$$

**UT**

## Solving $G_{vi}$

Open Loop  $d$ -to- $i_L$  TF

$$G_{ido} = \frac{I_L}{D'} = \frac{I_{bus}}{(D')^2}$$

$$f_{zi} = \frac{1}{2\pi} \frac{1}{C} \frac{I_{bus}}{V_{bus}}$$

$$f_o = \frac{1}{2\pi} \frac{D'}{\sqrt{LC}}$$

$$G_{vi} = \frac{1}{sC} \left( D' - \frac{I_L}{G_{id}} \right)$$

$$G_{vi} = \frac{1}{sC} \left( D' - \frac{I_L D'}{I_{bus}} \frac{(1 + \frac{s^2 LC}{D'^2})}{(1 + \frac{sC V_{bus}}{I_{bus}})} \right)$$

$$= \frac{D'}{sC} \left( \frac{1 + \frac{sC V_{bus}}{I_{bus}}}{1 + \frac{sC V_{bus}}{I_{bus}}} - \frac{s^2 LC}{D'^2} \right)$$

$$= D' \left( \frac{\frac{V_{bus}}{I_{bus}} - \frac{sL}{D'^2}}{1 + \frac{sC V_{bus}}{I_{bus}}} \right)$$

$$G_{vi} = D' \frac{V_{bus}}{I_{bus}} \frac{(1 - \frac{sL I_{bus}}{D'^2 V_{bus}})}{1 + \frac{sC V_{bus}}{I_{bus}}} = G_{vio} \frac{1 - \frac{s}{\omega_{zi}}}{1 + \frac{s}{\omega_{pi}}}$$



# Solving $G_{vi}$

$$G_{vi} = \left. \frac{\hat{v}_{bus}}{\hat{i}_L} \right|_{\hat{v}_{bat}=0, \hat{i}_{bat}=0} = G_{vio} \frac{1 - \frac{s}{\omega_z}}{1 + \frac{s}{\omega_{zi}}}$$

$$G_{vio} = D' \frac{V_{bus}}{I_{bus}}$$

$$f_z = \frac{1}{2\pi} \frac{D'^2 V_{bus}}{L I_{bus}}$$

$$f_{zi} = \frac{1}{2\pi} \frac{1}{C} \frac{I_{bus}}{V_{bus}}$$

### Example Values

$$I_{bus} = 5A$$

$$V_{bus} = 50V$$

$$V_{bat} = 26V$$



$$L = 100\mu H$$

$$C = 4 \times 270\mu F$$

$$\left\{ \begin{array}{l} G_{vio} = 5.2 = 14dB \\ f_z = 4.3kHz \rightarrow \text{RHP zero} \\ f_{zi} = 14.7Hz \rightarrow \text{pole} \end{array} \right.$$




# Voltage Loop Gain

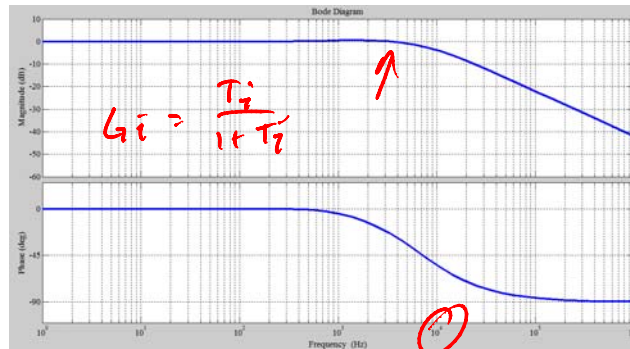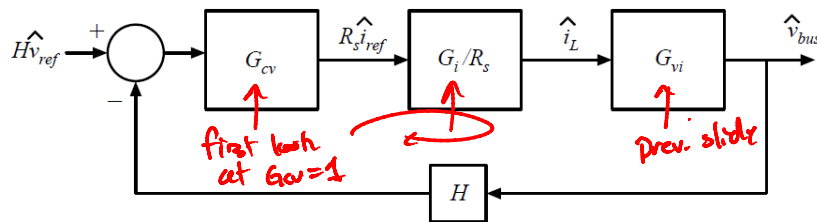




## Uncompensated Voltage Loop Gain

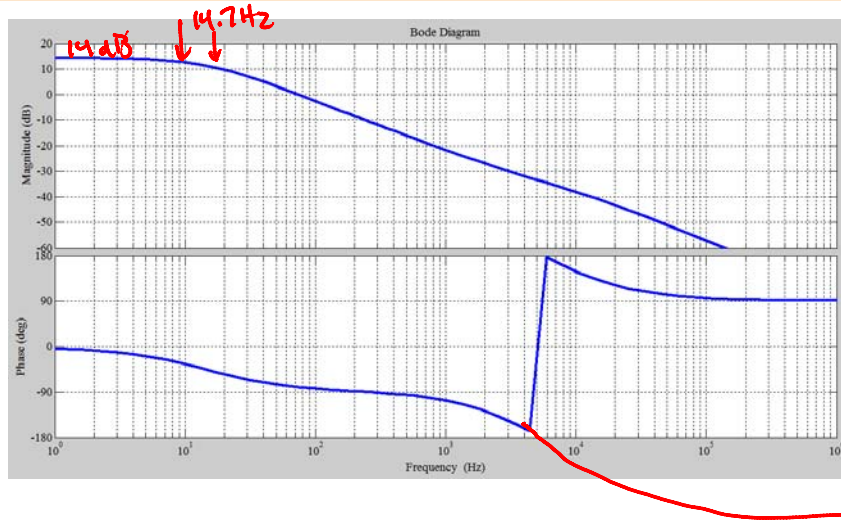

## Compensated Loop Gain

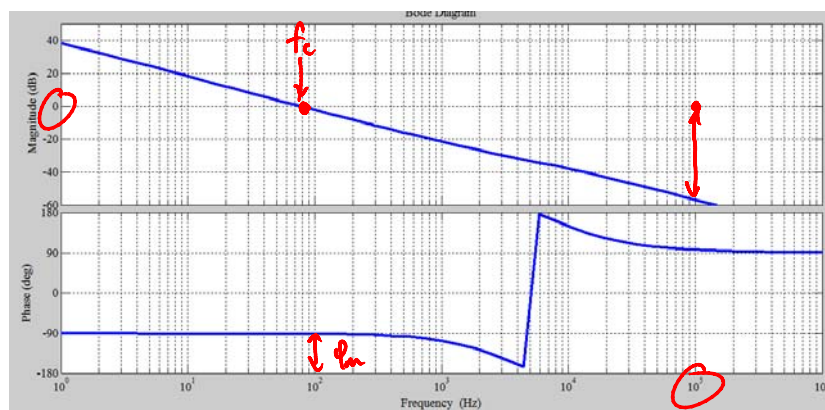


$$G_{ci} = 1 + \frac{\omega_{zv}}{s}$$


Handwritten annotations:  $\omega_{zv} = 100 \frac{\text{rad}}{\text{sec}}$ ,  $\phi_m = 88^\circ$



# Loop Gain with of HF Pole

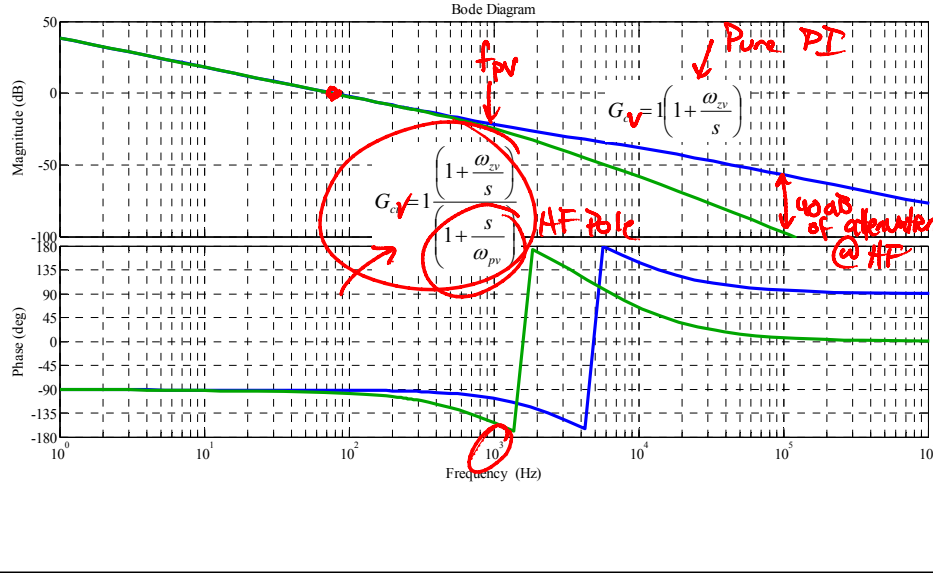


# Closed Loop $G_v$

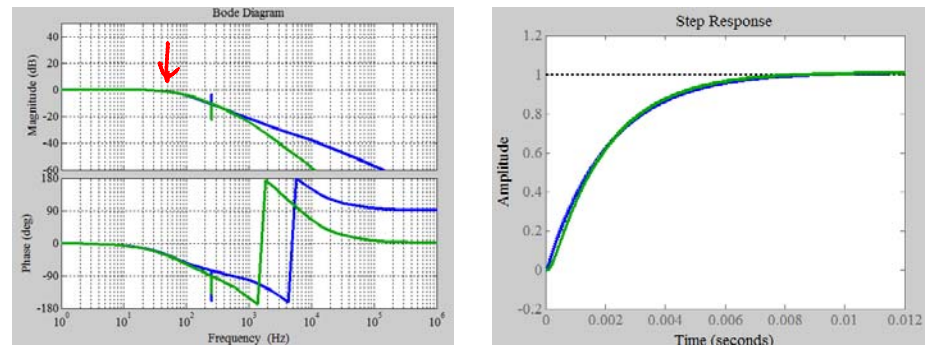




## Variations in DC Operation Point

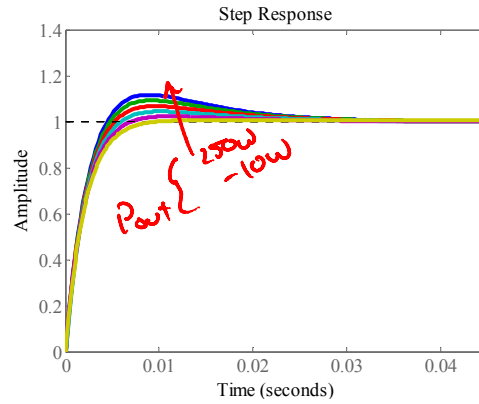

## Compensator Realization

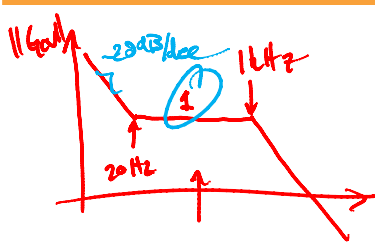

$$||G|| = \frac{V_o}{V_i} = \frac{-Z_z}{Z_i}$$

$$||G|| = \left| \frac{-Z_z}{Z_i} \right| = ||Z_z|| - ||Z_f||$$

Construct  $Z_i$  &  $Z_z$  out of  $R$ 's &  $C$ 's to get  $\frac{-Z_z}{Z_i} = G_{cv}$

