

Prelab Assignment

Experiment 5

ECE 482

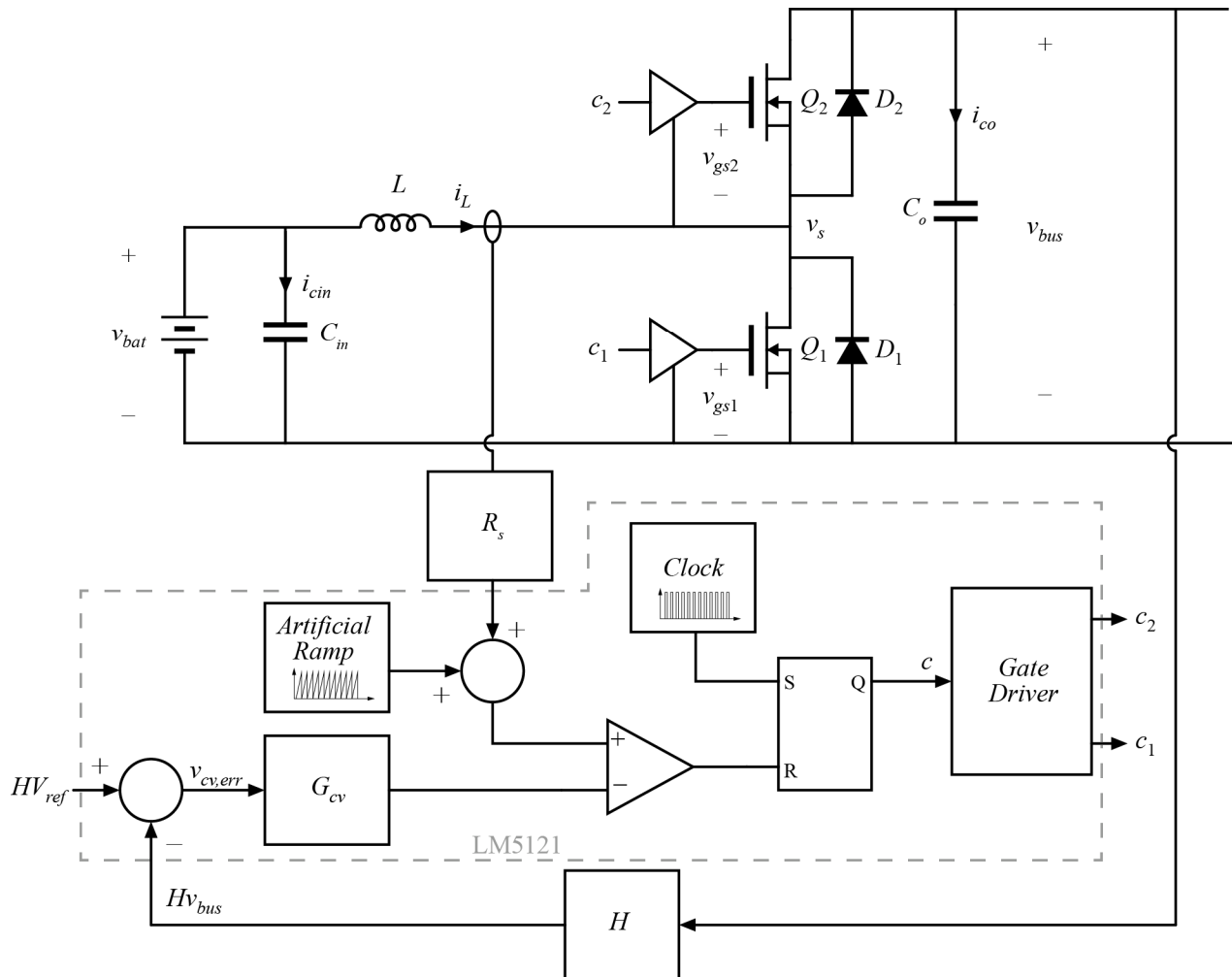


Figure 1: Nominal system diagram for drivetrain boost converter

Fig. 1 shows the nominal system diagram for the closed-loop DC-DC boost converter built in experiments 3 and 4. In this prelab, you are to modify the system beyond the nominal case in order to improve the performance of the system. Improvements should be motivated by one or more of the following metrics

- Improved efficiency / Decreased loss
- Improved dynamic performance
- Expanded operational limits
- Increased operator or circuit safety
- Improved robustness
- Reduced cost
- Reduced size
- Added Functionality
- Other areas (with instructor permission)

These improvements, or combination of improvements, that you propose to make to the system should constitute a significant redesign of one or more aspects of the system. Both several smaller changes and fewer, more significant alterations are acceptable.

This semester, you may choose to use GaNFETs in experiment 5 and beyond. The datasheets for these devices, and some additional recommended devices for experiment 5, have been added to the course webpage, at the top of the parts kit page:

<http://web.eecs.utk.edu/~dcostine/ECE482/Spring2016/components/parts/PartsKit/index.php>

For this prelab assignment, describe all alterations you propose to make to the system, and give any relevant analysis to argue the improvement you expect to see in system performance or characteristics. Turn in a *short* writeup with any relevant calculations attached. Be specific, making clear exactly how and why you plan to change the system; give part numbers and relevant parameters of any new or altered components and include diagrams of any additional circuitry added to the system of Fig. 1.

Though there is no specific quantity which constitutes sufficient alterations to the system, your grade in experiment 4 will rely on your proposed changes being significant enough to warrant additional design work. If you have any questions on whether your proposed changes meet this qualification, speak with the instructor directly.