

Power Electronics Circuits

Prof. Daniel Costinett

ECE 482 Lecture 4
February 15, 2016




THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Simulation Modeling

Circuit Simulation

- LTSpice
 - Other tools accepted, but not supported
- Choose model type (switching, averaged, dynamic)
- Supplement analytical work rather than repeating it
- Show results which clearly demonstrate what matches and what does not with respect to experiments (i.e. ringing, slopes, etc.)


LTSpice Modeling Examples

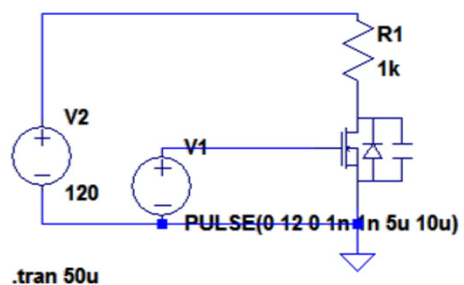

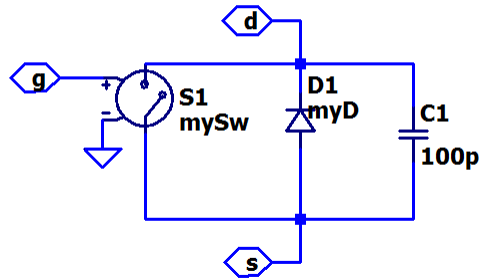- Example files added to course materials page

Custom Transistor Model


```
.model myD D(n=.001)
.model mySw SW(Ron=10m Roff=1G Vt=0 Von=1 Voff = .5 )
```



VDMOS Model

Name	Description	Units	Default	Example
Vto	Threshold voltage	V	0	1.0
Kp	Transconductance parameter	A/V ²	1.	.5
Phi	Surface inversion potential	V	0.6	0.65
Lambda	Channel-length modulation	1/V	0.	0.02
mtriode	Conductance multiplier in triode region(allows independent fit of triode and saturation regions)	-	1.	2.
subthres	Current (per volt Vds) to switch from square law to exponential subthreshold conduction	A/V	0.	1n
BV	Vds breakdown voltage	V	Infin.	40
IBV	Current at Vds=BV	A	100pA	1u
NBV	Vds breakdown emission coefficient	-	1.	10
Rd	Drain ohmic resistance	Ω	0.	1.
Rs	Source ohmic resistance	Ω	0.	1.
Rg	Gate ohmic resistance	Ω	0.	2.
Rds	Drain-source shunt resistance	Ω	Infin.	10Meg
Rb	Body diode ohmic resistance	Ω	0.	.5
Cio	Zero-bias body diode	F	0.	1n
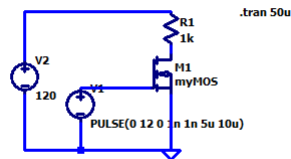
```
.model A06407 VDMOS(nchan Rg=3 Rd=14m Rs=10m Vto=-.8 Kp=32 Cgdmax=.5n Cgdmin=.07n Cgs=.9n Cjo=.26p Is=26p Rb=17m)
```




Manufacturer Device Model

- Text-only netlist model of device including additional parasitics and temperature effects
- May slow or stop simulation if timestep and accuracy are not adjusted appropriately

Full Switching Simulation
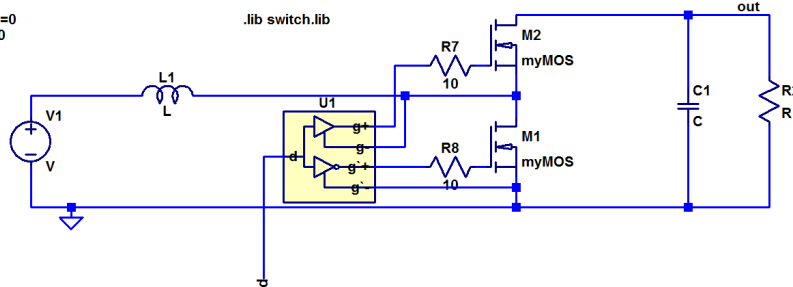
```
.tran 1
.model myMOS VDMOS(Rg=1 Vto=4.5 Rd=14m Rs=10m Rb=17m Kp=30 Cgdmax=.5p Cgdmn=.05n Cgs=.2n Cjo=.03n Is=88p)
.ic V(out)=0
.ic I(L1)=0
```




Full Switching Simulation

```
.tran 1 .model myMOS VDMOS(Rg=1 Vto=4.5 Rd=14m Rs=10m Rb=17m Kp=30 Cgdmax=.5p Cgdmin=.05n Cgs=.2n Cjo=.03n Is=88p)
```

```
.ic V(out)=0
```

```
.ic I(L1)=0
```

.lib switch.lib

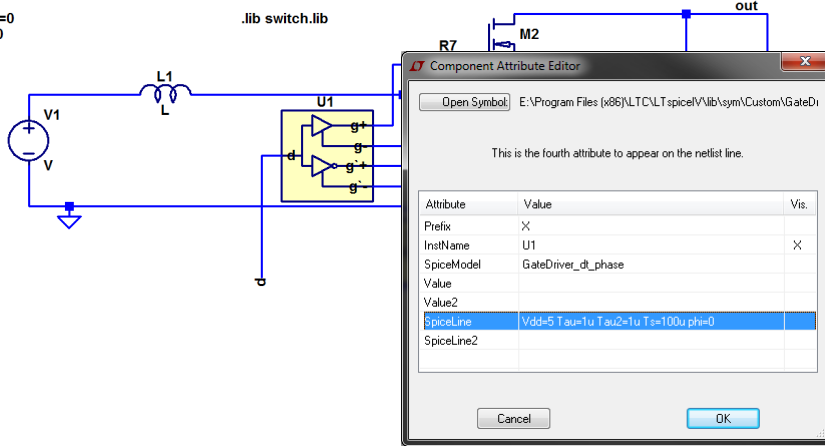

Home
Lecture Schedule
Materials

Experiment Procedure

- [Prelab Assignment](#)
- [Experiment 3 Procedure](#)

Experiment 3 Components

- [Contents of the Experiment 3 Parts Kit](#)
- [Contents of the Magnetics Library](#)
- [Breakout Board Schematics and Layout](#)

Reference Materials

- [Power Converter Layout](#)
- [Reduction of Ringing in Power Converters \(TI App Note\)](#)
- [RMS Values of Commonly Observed Waveforms](#)

LTSpice Example Files


- [Examples of power semiconductor modeling using custom or manufacturer models](#)
- [Example Switching and Averaged Boost LTSpice Models](#)
- [Additional materials on averaged-circuit modeling in SPICE simulators](#)
- [Example averaged_nonlinear boost converter model \(Spring 2014\)](#)

• [Magnetics Design](#)

Available on Exp 3 Webpage

Switching Model Simulation Results

- Simulation Time \approx 15 minutes

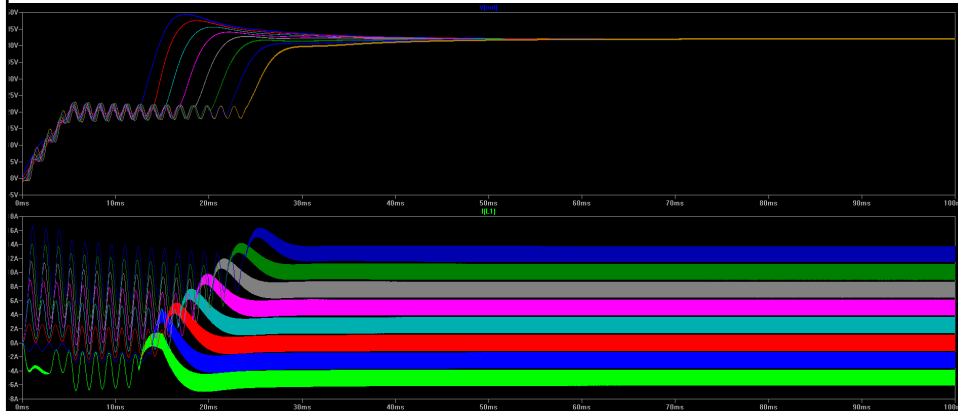

Full Switching Model


- Gives valuable insight into circuit operation
 - Understand expected waveforms
 - Identify discrepancies between predicted and experimental operation
- Slow to simulate; significant high frequency content
- Cannot perform AC analysis

Averaged Switch Modeling: Motivation


- A *large-signal, nonlinear* model of converter is difficult for hand analysis, but well suited to simulation across a wide range of operating points
- Want an *averaged* model to speed up simulation speed
- Also allows linearization (AC analysis) for control design

Averaged, Nonlinear, Large-Signal Equations

ECE 481 Review:

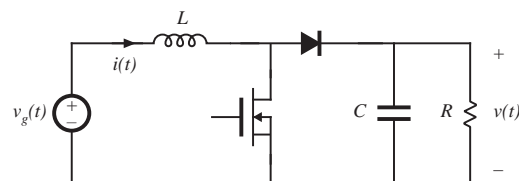



Nonlinear, Averaged Circuit

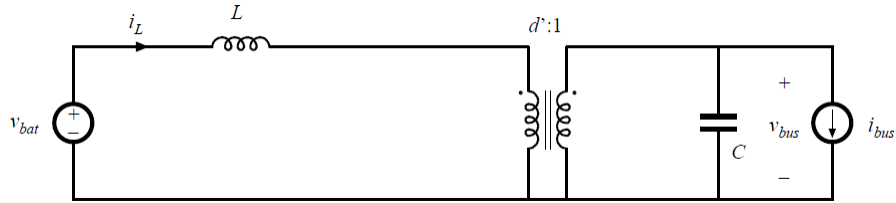

$$L \frac{d\langle i_L \rangle}{dt} = \langle v_{bat} \rangle - (1-d)\langle v_{bus} \rangle$$


$$C \frac{d\langle v_{bus} \rangle}{dt} = (1-d)\langle i_L \rangle - \langle i_{bus} \rangle$$

Implementation in LTSpice

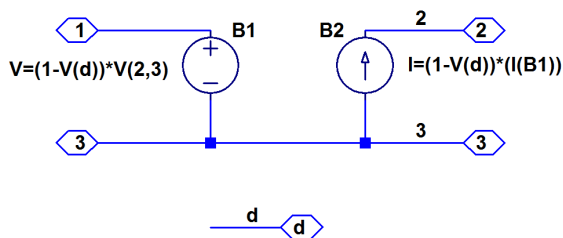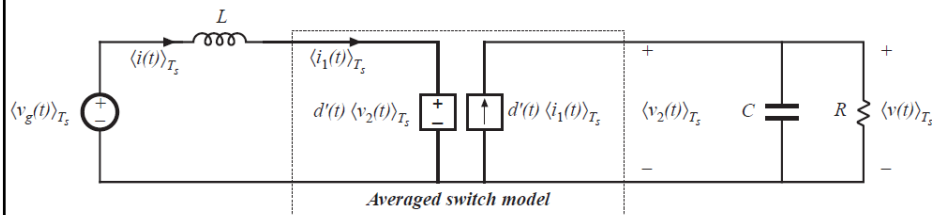


$$\langle v_1(t) \rangle_{T_s} = d'(t) \langle v_2(t) \rangle_{T_s}$$


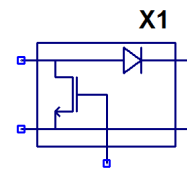
$$\langle i_2(t) \rangle_{T_s} = d'(t) \langle i_1(t) \rangle_{T_s}$$



Averaged Switch Model

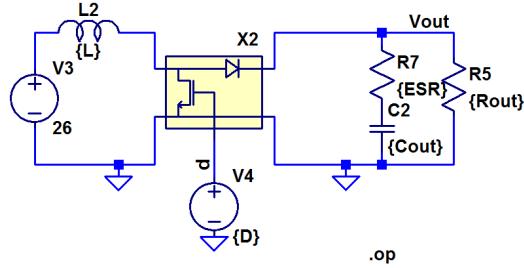

Averaged Model With Losses

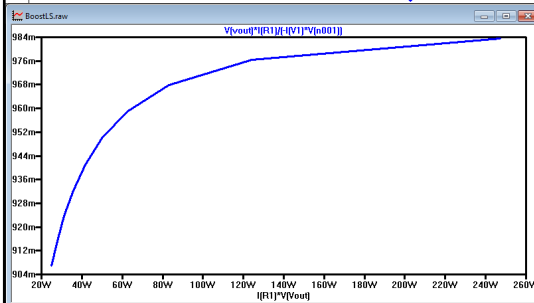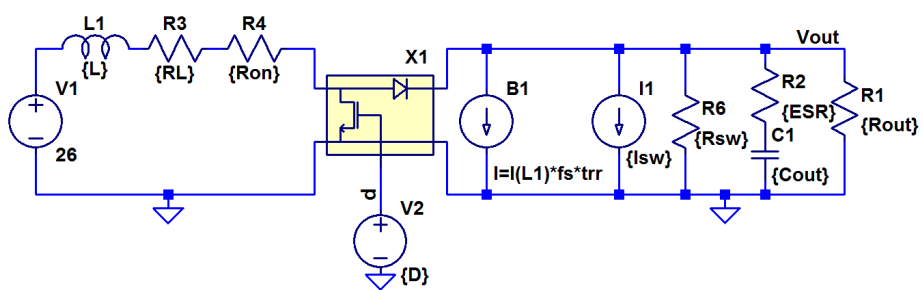


```
.op
.param Rout = 10
.step param Rout 10 100 10
```

What known error(s) will be present in loss predictions with this model?



Experiment 4

Experiment 4: Closed-Loop Boost


Experiment 3: Open Loop

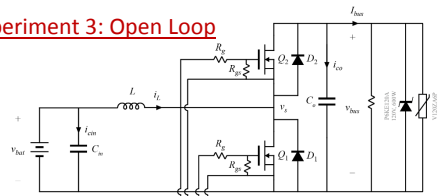


Experiment 4: Closed Loop

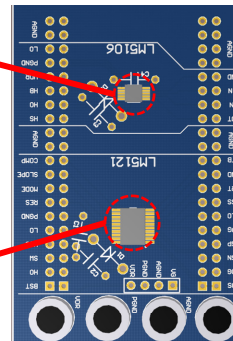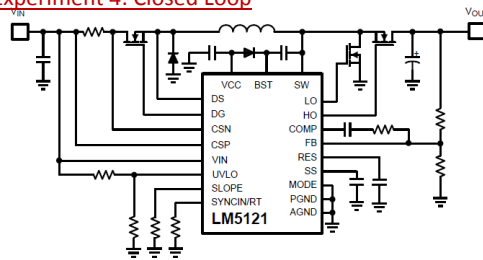


Current Control

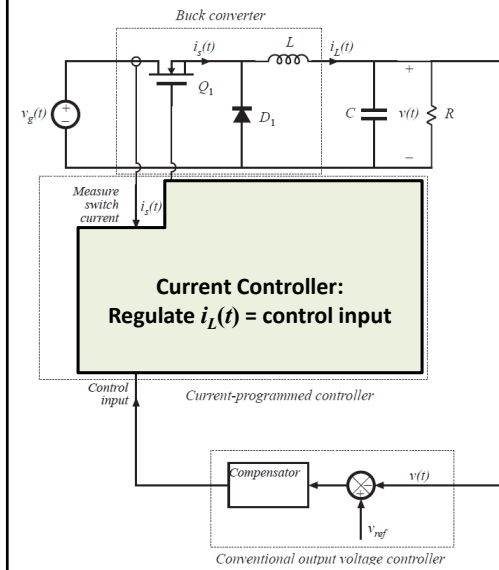

Current Programmed Control (CPM)

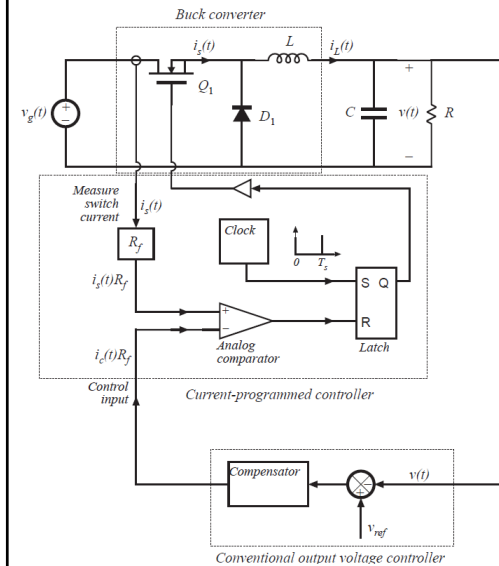

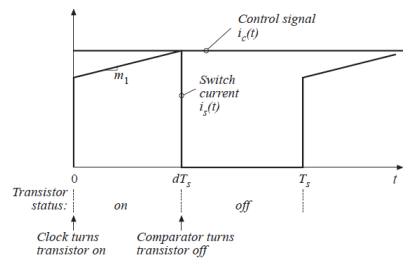
The peak transistor current replaces the duty cycle as the converter control input.



Current Programmed Control

- Covered in Ch. 12 of *Fundamentals of Power Electronics*
- Advantages of current programmed control:
 - Simpler dynamics —inductor pole is moved to high frequency
 - Simple robust output voltage control, with large phase margin, can be obtained without use of compensator lead networks
 - It is always necessary to sense the transistor current, to protect against overcurrent failures. We may as well use the information during normal operation, to obtain better control
 - Transistor failures due to excessive current can be prevented simply by limiting $i_c(t)$
 - Transformer saturation problems in bridge or push-pull converters can be mitigated
- A disadvantage: susceptibility to noise

A Simple First-Order Model

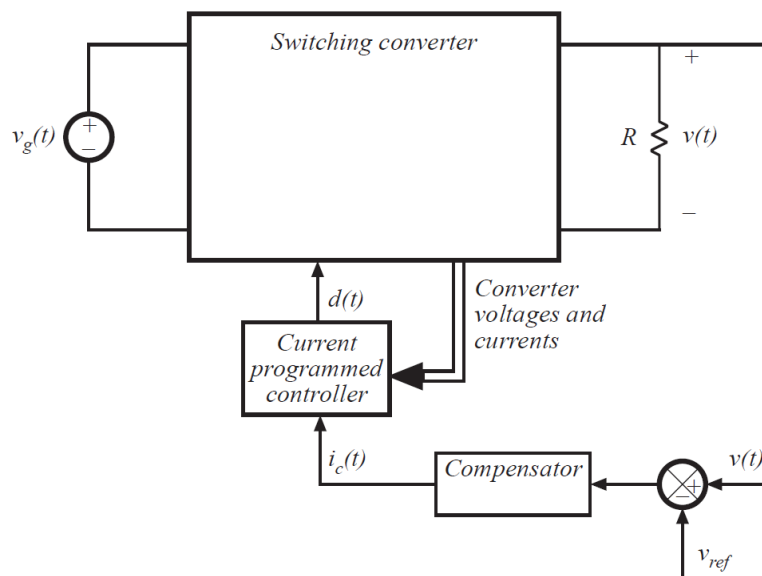


The First-Order Approximation

$$\langle i_L(t) \rangle_{T_s} = i_c(t)$$


- Neglects switching ripple
- Yields physical insight and simple first-order model
- Accurate when converter operates well into CCM (so that switching ripple is small)
- Accurate when artificial ramp (discussed later) small
- Resulting small-signal relation:

$$i_L(s) \approx i_c(s)$$


Averaged Modeling

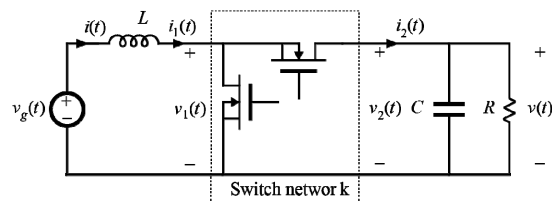

Large-Signal Nonlinear Model

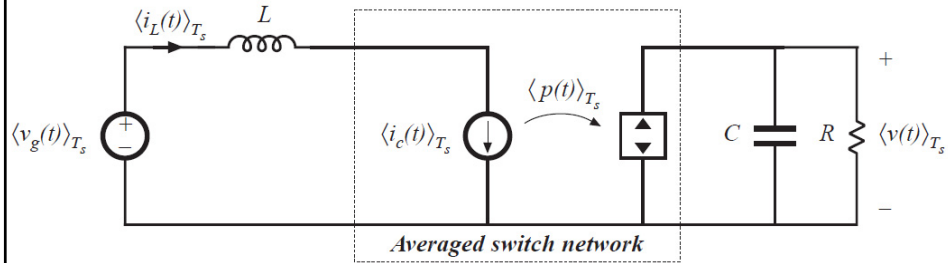


Implementation in LTSpice

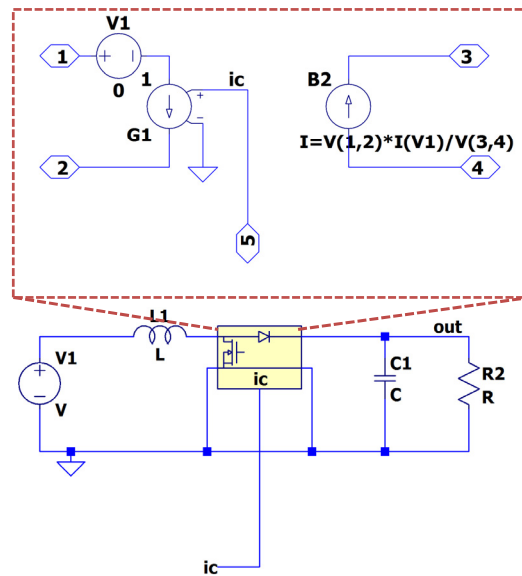

Perturb and Linearize

Boost CCM CPM Small-Signal Model

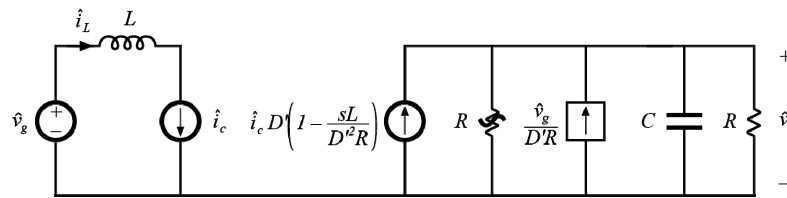

CPM Transfer Functions


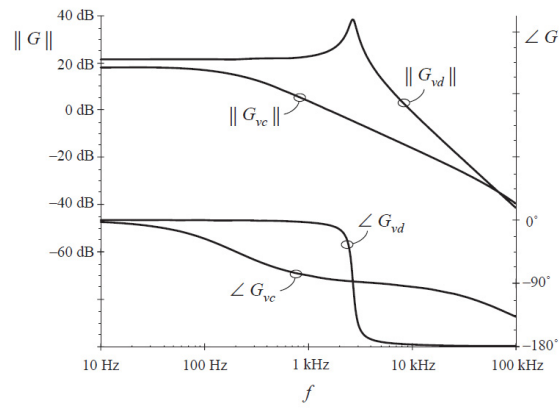


Fig. 12.28 Comparison of CPM control with duty-cycle control, for the control-to-output frequency response of the buck converter example.


Voltage Control

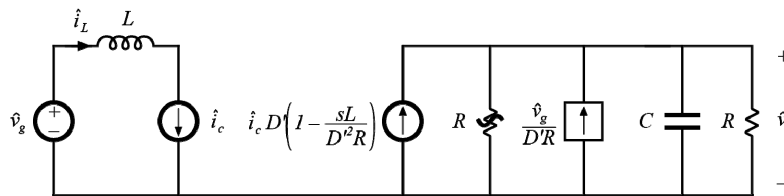

CPM Oscillations for $D > 0.5$

- The current programmed controller is inherently unstable for $D > 0.5$, regardless of the converter topology
- Controller can be stabilized by addition of an artificial ramp

Inductor Current Waveform in CCM

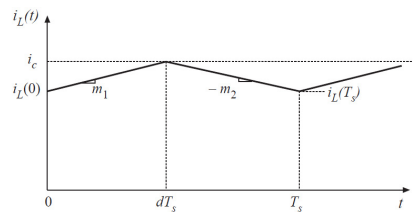

Inductor current slopes m_1
and $-m_2$

buck converter

$$m_1 = \frac{v_g - v}{L} \quad -m_2 = -\frac{v}{L}$$

boost converter

$$m_1 = \frac{v_g}{L} \quad -m_2 = \frac{v_g - v}{L}$$

buck-boost converter

$$m_1 = \frac{v_g}{L} \quad -m_2 = \frac{v}{L}$$

Volt-Second Balancing

First interval:

$$i_L(dT_s) = i_c = i_L(0) + m_1 dT_s$$

Solve for d :

$$d = \frac{i_c - i_L(0)}{m_1 T_s}$$


Second interval:

$$\begin{aligned} i_L(T_s) &= i_L(dT_s) - m_2 dT_s \\ &= i_L(0) + m_1 dT_s - m_2 dT_s \end{aligned}$$


In steady state:

$$0 = M_1 dT_s - M_2 d'T_s$$


$$\frac{M_2}{M_1} = \frac{D}{D'}$$

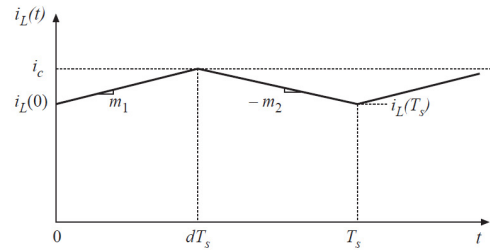

Introducing a Perturbation

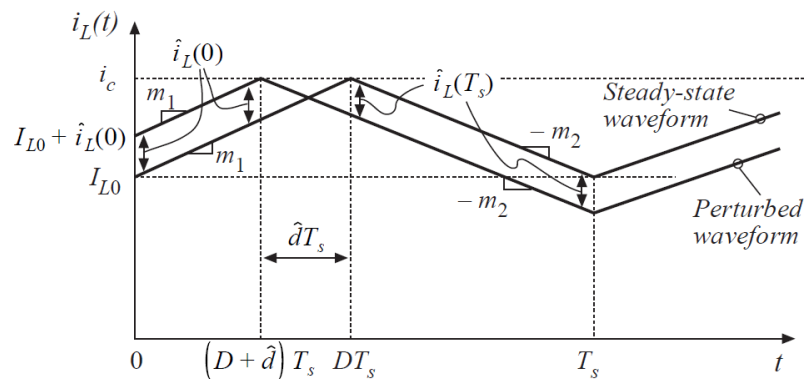

Change in Inductor Current Over T_s

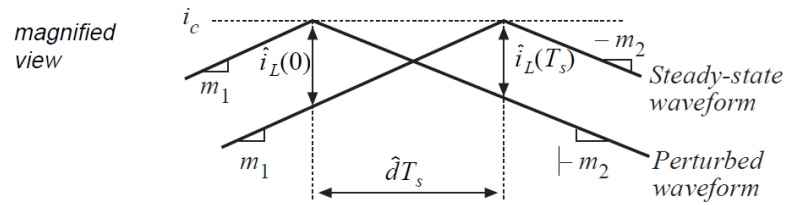

$$\hat{i}_L(0) = -m_1 \hat{\Delta}T_s$$

$$\hat{i}_L(T_s) = m_2 \hat{\Delta}T_s$$

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left(-\frac{D}{D'} \right)$$

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left(-\frac{m_2}{m_1} \right)$$

Final Value of Inductor Current

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left(-\frac{D}{D'} \right)$$

$$\hat{i}_L(2T_s) = \hat{i}_L(T_s) \left(-\frac{D}{D'} \right) = \hat{i}_L(0) \left(-\frac{D}{D'} \right)^2$$


$$\hat{i}_L(nT_s) = \hat{i}_L((n-1)T_s) \left(-\frac{D}{D'} \right) = \hat{i}_L(0) \left(-\frac{D}{D'} \right)^n$$

$$\left| \hat{i}_L(nT_s) \right| \rightarrow \begin{cases} 0 & \text{when } \left| -\frac{D}{D'} \right| < 1 \\ \infty & \text{when } \left| -\frac{D}{D'} \right| > 1 \end{cases}$$

For stability: $D < 0.5$

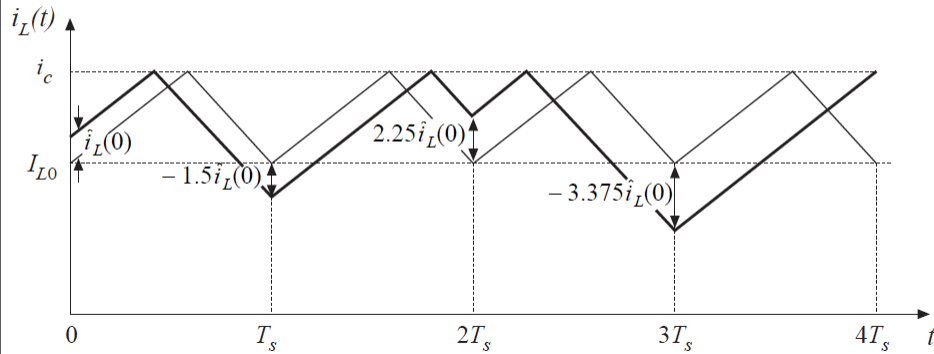
Example: Unstable operation for $D=0.6$

$$\alpha = -\frac{D}{D'} = \left(-\frac{0.6}{0.4}\right) = -1.5$$




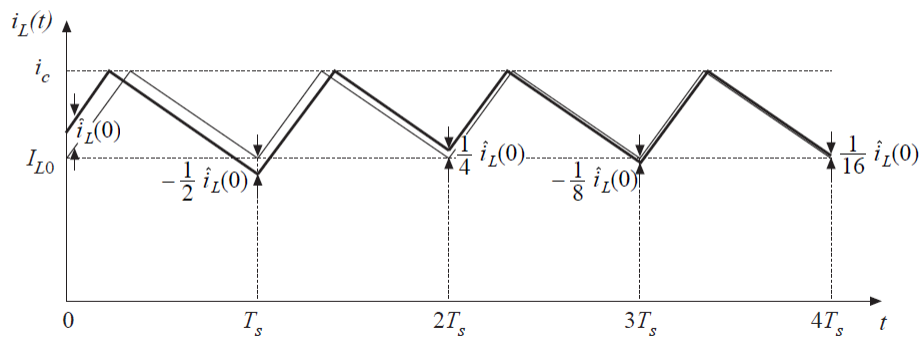Example: Stable operation for $D=1/3$

$$\alpha = -\frac{D}{D'} = \left(-\frac{1/3}{2/3}\right) = -0.5$$



Stabilization Through Artificial Ramp

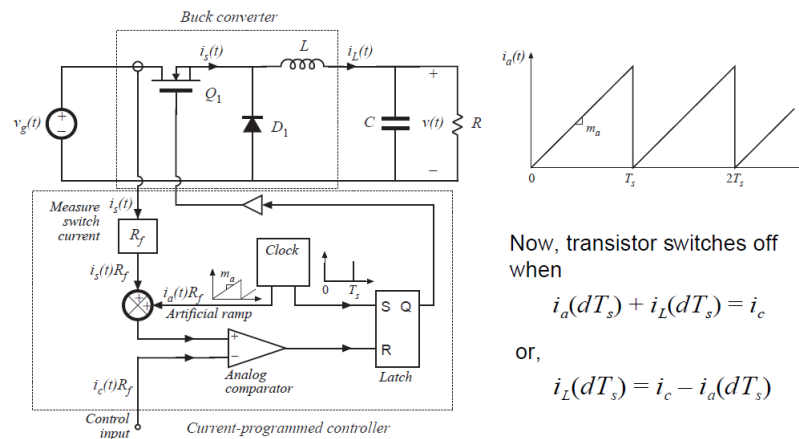

Final Value of Inductor Current

First subinterval:

$$\hat{i}_L(0) = -\hat{d}T_s (m_1 + m_a)$$

Second subinterval:

$$\hat{i}_L(T_s) = -\hat{d}T_s (m_a - m_2)$$

Net change over one switching period:

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left(-\frac{m_2 - m_a}{m_1 + m_a} \right)$$

After n switching periods:

$$\hat{i}_L(nT_s) = \hat{i}_L((n-1)T_s) \left(-\frac{m_2 - m_a}{m_1 + m_a} \right) = \hat{i}_L(0) \left(-\frac{m_2 - m_a}{m_1 + m_a} \right)^n = \hat{i}_L(0) \alpha^n$$


Characteristic value:

$$\alpha = -\frac{m_2 - m_a}{m_1 + m_a} \quad \left| \hat{i}_L(nT_s) \right| \rightarrow \begin{cases} 0 & \text{when } |\alpha| < 1 \\ \infty & \text{when } |\alpha| > 1 \end{cases}$$

Artificial Ramp: Additional Notes

- For stability, require $|\alpha| < 1$
- Common choices:
 - $m_a = 0.5 m_2$
 - $m_a = m_2$
- Artificial ramp decreases sensitivity to noise

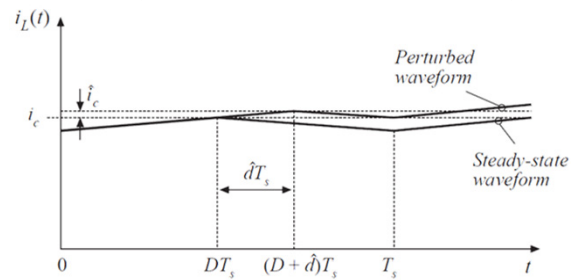
$$\alpha = -\frac{1 - \frac{m_a}{m_2}}{\frac{D'}{D} + \frac{m_a}{m_2}}$$




More Accurate Models

- The simple models of the previous section yield insight into the low-frequency behavior of CPM converters
- Unfortunately, they do not always predict everything that we need to know:
 - Line-to-output transfer function of the buck converter
 - Dynamics at frequencies approaching f_s
- More accurate model accounts for nonideal operation of current mode controller built-in feedback loop
- Converter duty-cycle-controlled model, plus block diagram that accurately models equations of current mode controller
- See Section 12.3 for additional info


Application to Experiment 4

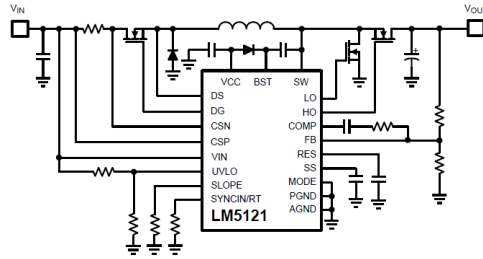

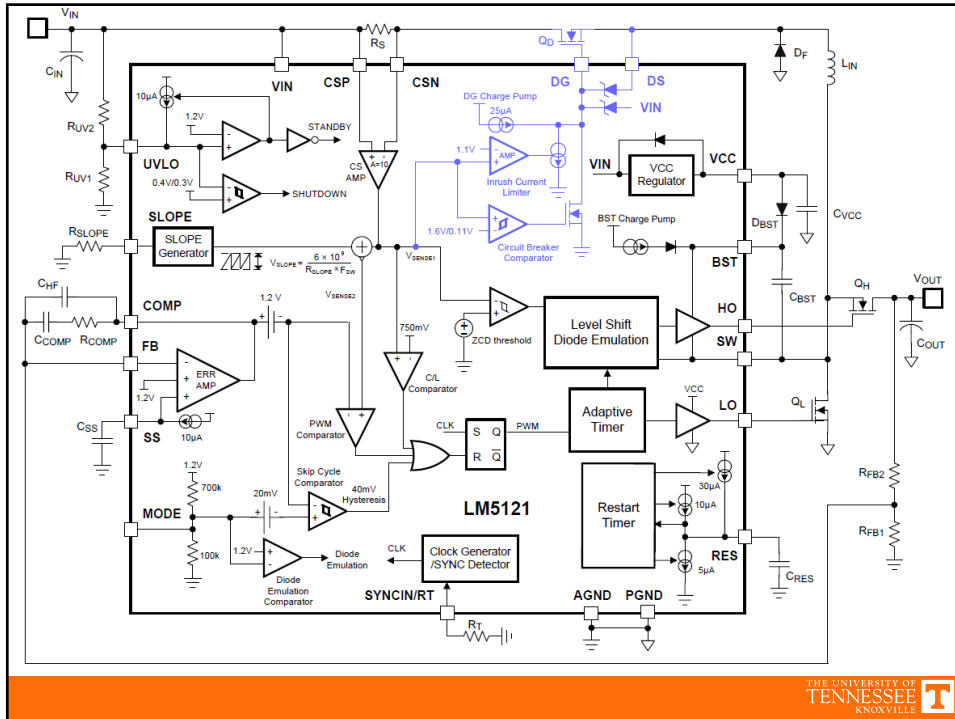- Complex switching controller
- **Read the datasheet first**




Internal Functional Model in LTSpice

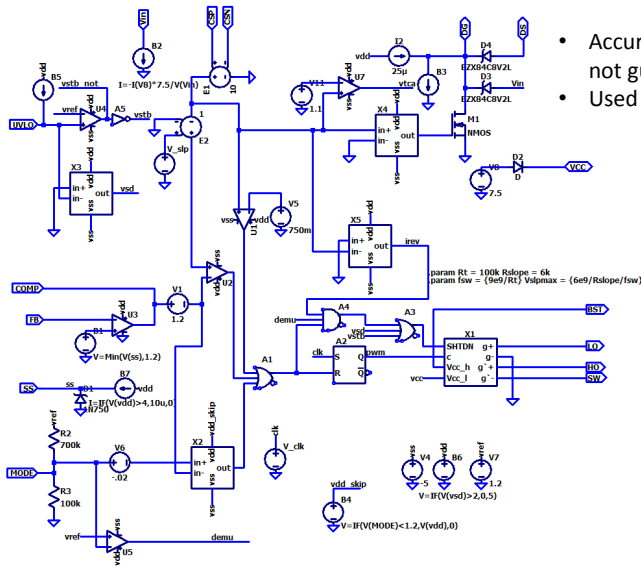


- Accuracy/functionality not guaranteed
- Used for insight only

In-Circuit Simulation

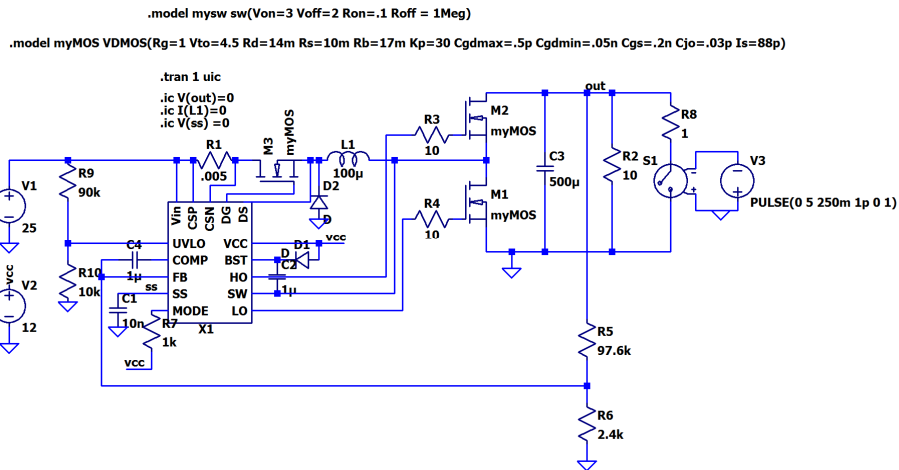

Sim Results

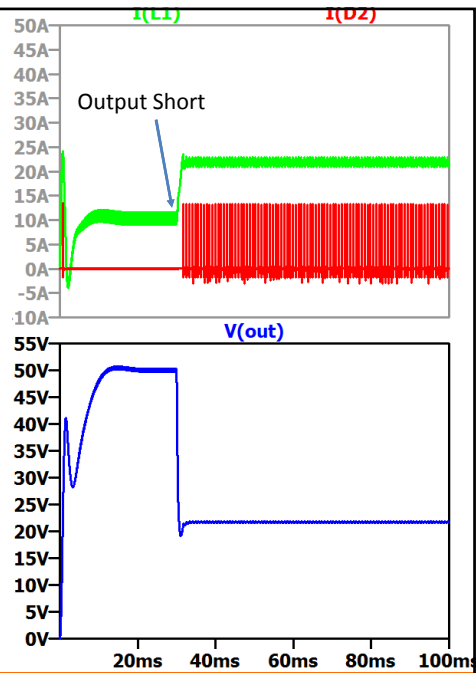

A Tip: Debug Internal of Subcircuit

