

# PCB Layout

ECE 482 Lecture 5  
March 7, 2016




THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE


## Announcements

- Prelab 5 due Tuesday
  - Decide on System Improvements
  - Redesign using GaN Devices
- Experiment 4 report moved to Thurs. 3/24
- Midterm after spring break
  - Open note, book, instructor
- Today: Experiment 5
  - No report; deliverables are layout files

## Prelab 5: HF Attenuation

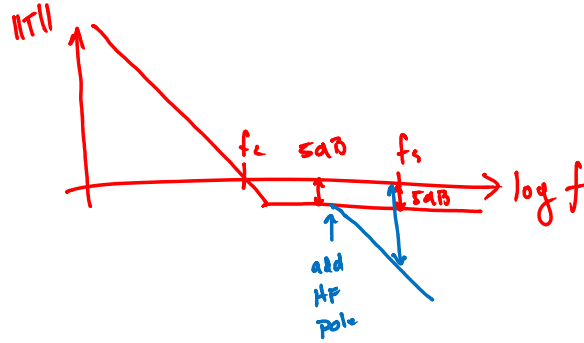

## Lab 5: PCB Layout

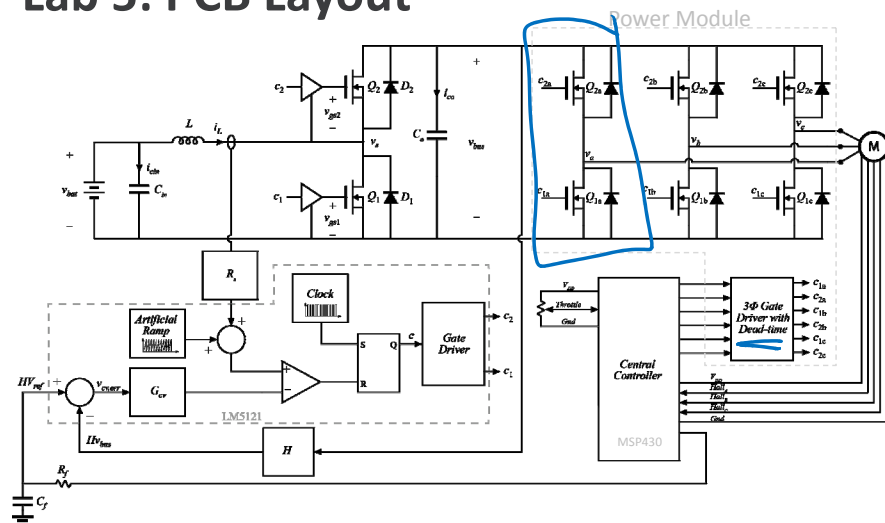


- More information on motor drive in Experiment 5


## Design Modification

- You may order additional parts, at reasonable cost/benefit
  - Will need to provide a listing of parts from digikey with final Exp 5 files
- Reuse components from lab kit where possible
- Use SMD ceramic, low ESR caps for power stage and gate drive decoupling

## Circuit Connections

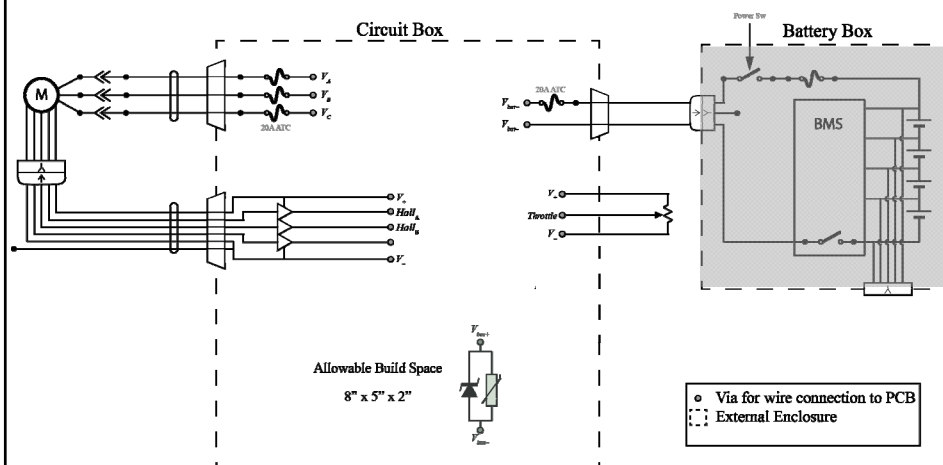

## Circuit Enclosure

 

## Prelab for Experiment 5: Redesign with GaN

### GaN Systems GS61008T

- 7.4 mOhm
- 100V/80A
- $Q_g = 12$  nC
- $C_{oss} = 250$  pF (80V)
- Top-cooled




### EPC EPC2001C


- 7 mOhm
- 100V/36A
- $Q_g = 9$  nC
- $C_{oss} = 375$  pF (80V)
- Bottom-cooled



# GaN Devices

 

Vertical Silicon Power MOSFET

 

Lateral GaN HEMT

- No body diode (reverse conduction due to  $V_{gd} > V_{gd,th} \approx 2V$ )
  - Use antiparallel (schottky) diode or precise dead time
- Significantly faster switching




# Designing with GaN



Fig. 1: Material properties of silicon, silicon carbide, and gallium nitride.

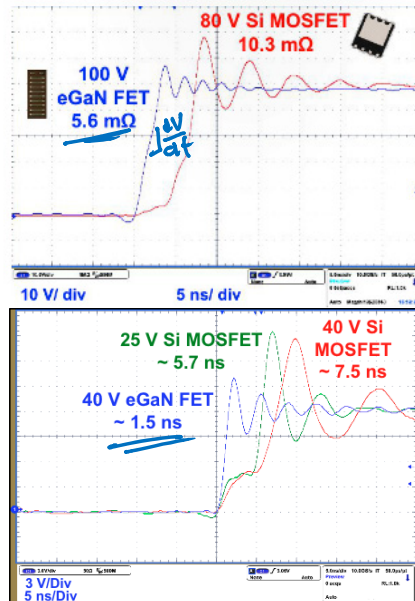- Because of high electric breakdown field and high electron velocity, GaN devices with comparable  $R_{on}$  can be significantly smaller and switch must faster.
- Need **very** good layout to prevent ringing from causing overvoltage and device failure.







How to GaN: Simplifying Design with DrGaN



## GaN Design Issues

    1. Reverse conduction mechanism
2. Sensitivity to parasitics
3. Gate robustness



## WBG Device Characterization

- Seminar Monday, March 7<sup>th</sup>, 12:00-4:00pm
- Registration (w/ lunch)
  - [https://docs.google.com/forms/d/15xaqCM\\_jwjD1CW0e9Iny0jaBLruwjLZXFPu7Za8FWcM/viewform](https://docs.google.com/forms/d/15xaqCM_jwjD1CW0e9Iny0jaBLruwjLZXFPu7Za8FWcM/viewform)
- Also available remotely via WebEx

# Basic PCB Layout Concepts

- Trace Parasitics
- Kelvin Connection
- Parasitic Capacitances and Decoupling
- Loop Inductances
- Ground Plane / Return Currents
- Partitioning



# Trace Parasitics

$R = \frac{\rho Z}{XY}$   
 $\rho = \text{RESISTIVITY}$

**SHEET RESISTANCE CALCULATION FOR 1 OZ. COPPER CONDUCTOR:**

$\rho = 1.724 \times 10^{-6} \Omega\text{cm}, Y = 0.0036\text{cm}$

$R = 0.48 \frac{Z}{X} \text{m}\Omega$

$\frac{Z}{X} = \text{NUMBER OF SQUARES}$

$R = \text{SHEET RESISTANCE OF 1 SQUARE (Z=X)} = 0.48\text{m}\Omega/\text{SQUARE}$

**WIRE INDUCTANCE** =  $0.0002 \left[ \ln \left( \frac{2L}{R} \right) - 0.75 \right] \mu\text{H}$

EXAMPLE: 1cm of 0.5mm o.d. wire has an inductance of 7.26nH (2R = 0.5mm, L = 1cm)

**STRIP INDUCTANCE** =  $0.0002 \left[ \ln \left( \frac{2L}{WH} \right) + 0.2235 \left( \frac{WH}{L} \right) + 0.5 \right] \mu\text{H}$

EXAMPLE: 1cm of 0.25 mm PC track has an inductance of 9.59 nH (H = 0.038mm, W = 0.25mm, L = 1cm)

$C = \frac{0.00885 \epsilon_r A}{d} \text{pF}$

A = plate area in mm<sup>2</sup>  
d = plate separation in mm  
 $\epsilon_r$  = dielectric constant relative to air

• Most common PCB type uses 1.5mm glass-fiber epoxy material with  $\epsilon_r = 4.7$   
• Capacitance of PC track over ground plane is roughly 2.8 pF/cm<sup>2</sup>

**Figure 12.18: Wire and Strip Inductance Calculations**

**Figure 12.24: Capacitance of two parallel plates**

Figure 12.2: Calculation of Sheet Resistance and Linear Resistance for Standard Copper PCB Conductors



# Trace Sizing Rough Guidelines

## 2.2 PCB Etch

Table 1 is helpful to determine the current carrying capacity of PCB etches. The table assumes:

- 1oz/sq foot copper (0.035mm thickness).
- 10°C rise on outer layers, 20°C inner layers
- Groups of high current tracks are de-rated
- Tracks are not near or over heat sink areas

Table 1. Current Capacity PCB Etch

WIDTH	CURRENT CAPACITY
0.010"	0.8 A
0.015"	1.2 A
0.020"	1.5 A
0.050"	3.2 A
0.100"	6.0 A

## 2.3 Vias or Feedthrus

Vias limit the current and add inductance between the power supply and load. Layouts are usually done with 10-mil inner ring feedthrus. At this size, current capability is about 1 A per feedthru.

Kester, W. "Tips about printed circuit board design: Part 1 - Dealing with harmful PCB effects"



# Kelvin Connection

 



Figure 1. Kelvin Connection

Texas Instruments, "LMP8640/-Q1/HV Precision High Voltage Current Sense Amplifiers"






## Common Source Inductance

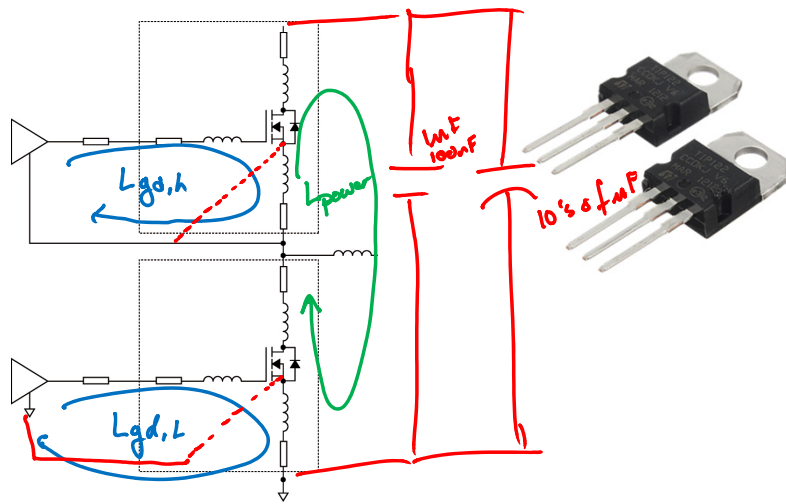

Persson E., "What really limits MOSFET performance: silicon, package, driver or circuit board?"



## Gate-Drain Capacitance

 

Persson E., "What really limits MOSFET performance: silicon, package, driver or circuit board?"



## High Impedance Nodes and Capacitive Coupling

 


Figure 12.29 High Circuit Impedances Increase Susceptibility to Noise Pickup

Analog Devices, "Decoupling Techniques," MT-101



## Capacitive Shielding


 


Figure 12.26: An Operational Model of a Faraday Shield

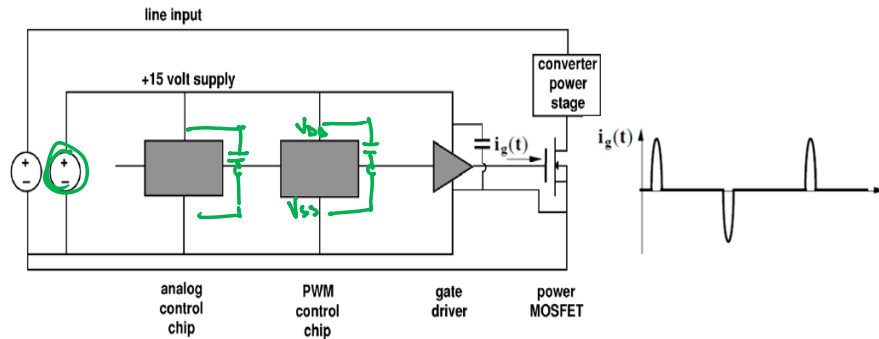Analog Devices, "Decoupling Techniques," MT-101




## Supply Decoupling



High frequency components of gate drive current are confined to a small loop

A dc component of current is still drawn out of 15V supply, and flows past the control chips. Hence, return conductor size must be sufficiently large

## Pulsed Circuit Decoupling

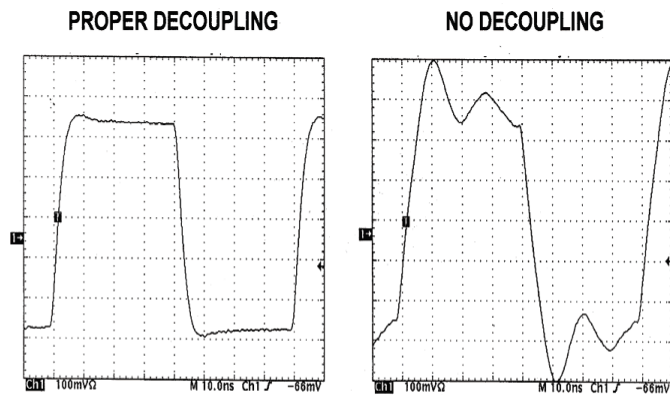

VERTICAL SCALE: 100mV/div  
HORIZONTAL SCALE: 10ns/div

Figure 12.68: Effects of Inadequate Decoupling on the Phase Response of the AD9631 Op Amp

## Decoupling Capacitance


 


Figure 4: Impedance of Various 100µF Capacitors

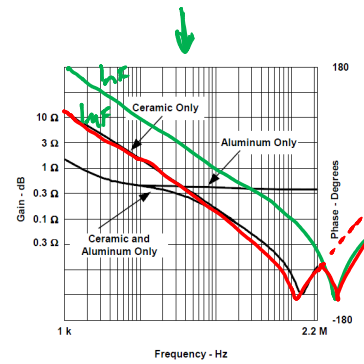

Equivalent Circuit

 


Fig. 8. Paralleled capacitors minimize impedance over frequency.

Analog Devices, "Decoupling Techniques," MT-101

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE



## Decoupling


- Always add bypass capacitor at power supply for any IC/reference
- Use small-valued (~100nf), low ESR and ESL capacitors (ceramic)
- Limit loop for any di/dt

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE



 
## Loop Inductances

*\* Always consider voltage signals as differential!*



 
Bad practice: wide separation of signal and return




Good practice: close coupling of signal and return
 
## Half Bridge Loop Inductance

Parasitic inductances of input loop explicitly shown:





 Addition of bypass capacitor confines the pulsating current to a smaller loop:



high frequency currents are shunted through capacitor instead of input source

  Even better: minimize area of the high frequency loop, thereby minimizing its inductance



## Gate Drive Signal Routing

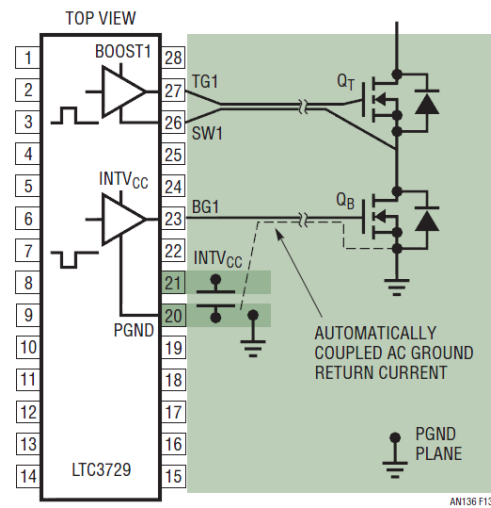


Figure 13. Gate Driver Trace Routing of the MOSFETs

## Complete Routing of Signal

- Always consider return path
- Ground plane can help, but still need to consider the path and optimize

## Buck Example Bridge Layout

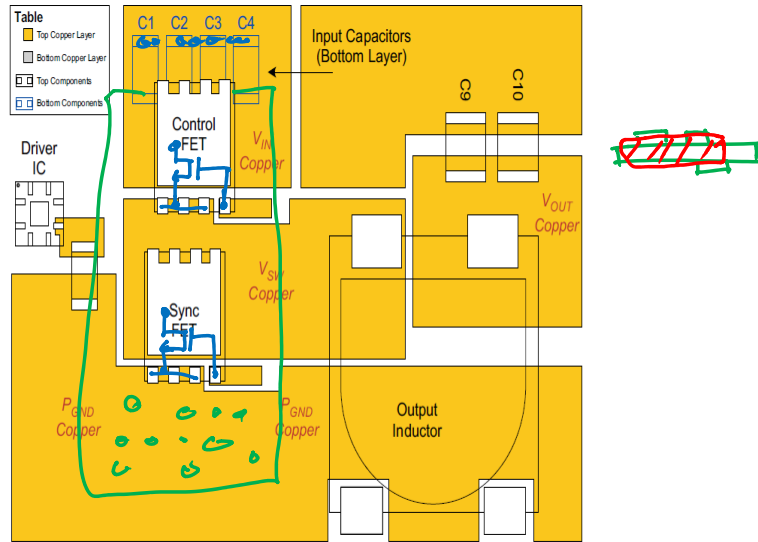


Figure 2. Typical Placement and PCB Layout of the Power Stage Components



## Example Bridge Layout #2


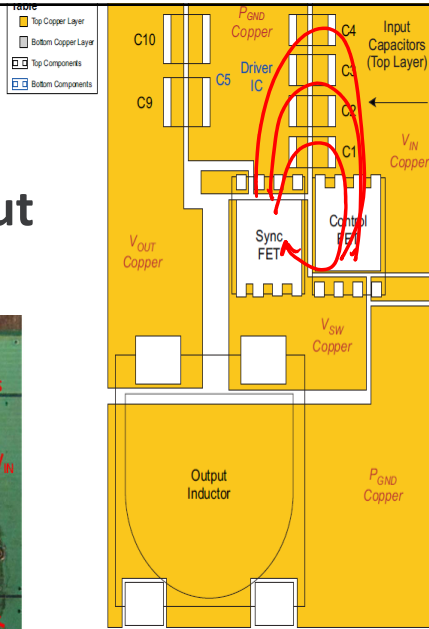


Figure 3. Optimized Placement and PCB Layout of Power Stage Components

 

## Example Layout Experimental Results

Example  
Layout  
#1

 


Figure 4. Switch Node (VSW) Voltage Ringing on Typical Layout

Example  
Layout  
#2


 


Figure 5. Switch Node (VSW) Voltage Ringing on Optimized Layout

## Star-Grounding Vs. Daisy Chain

Undesired

 

Desired


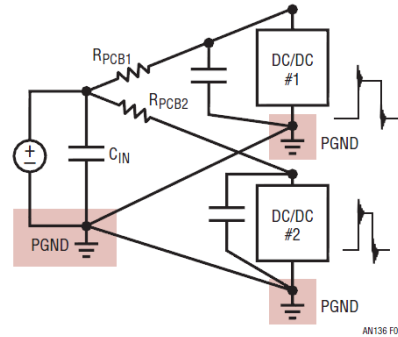


Figure 9. Separate the Input Current Paths Among Supplies

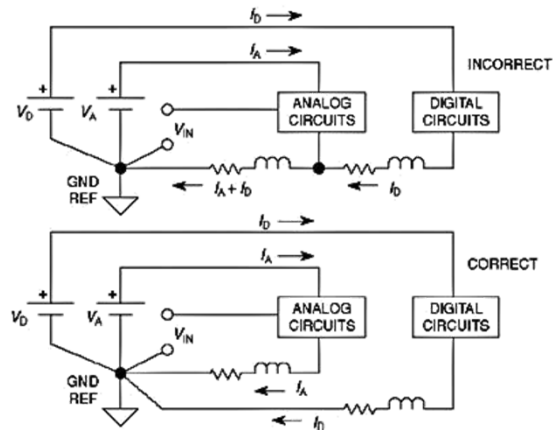

## Another View



Kester, W. "Tips about printed circuit board design: Part 1 - Dealing with harmful PCB effects"




## Ground Plane



- Benefits:
  - Common reference voltage
  - Shielding
  - Heat dissipation
  - Reduced inductance (increased capacitance)
- Resist urge to cut ground plane as much as possible; consider paths of return currents when cuts are unavoidable





## Ground Currents

 

  
No split: high mutual inductance, low ground inductance




Extra return path adds ground inductance

  

## Ground Plane Isolation

 

 Return current of noisy circuit runs underneath sensitive circuits, and can still corrupt their ground references




A solution is to remove the noisy circuit from the ground plane. One could then run a separate ground wire for the noisy circuit. The only drawback is that noise can be coupled into the input signal v.

## Cuts in Ground Plane

- Goals:
  - minimize inductance/loops
  - Minimize ground interference
- Routing cuts should be kept short and out of the path of any significant (high frequency) return paths
- Cuts can be used effectively for ground isolation, and to reduce noise coupled between digital/analog/power circuitry
- Reducing parasitic capacitance in sensitive signal locations (i.e. op-amp circuitry)

## Effective Ground Plane Cuts

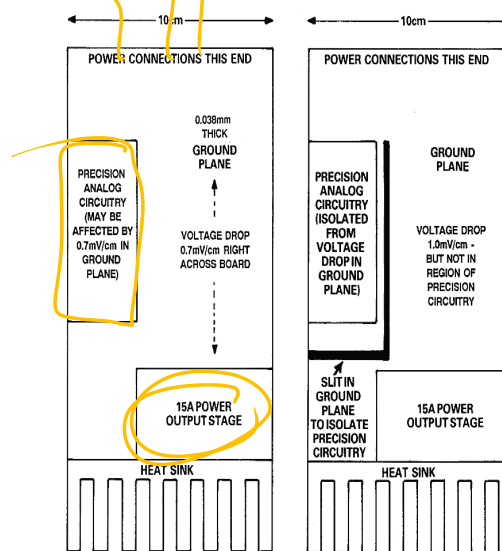

## Experiment 5: Starting Files