
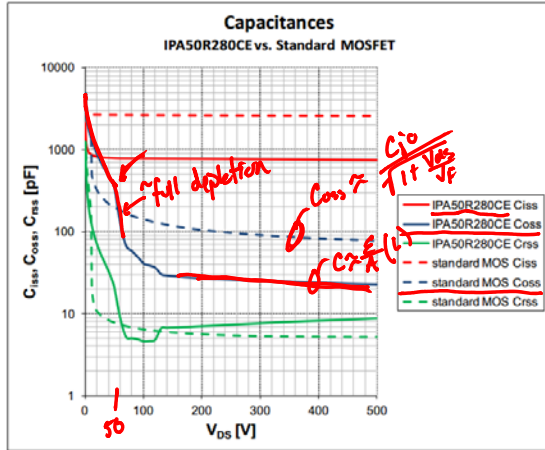


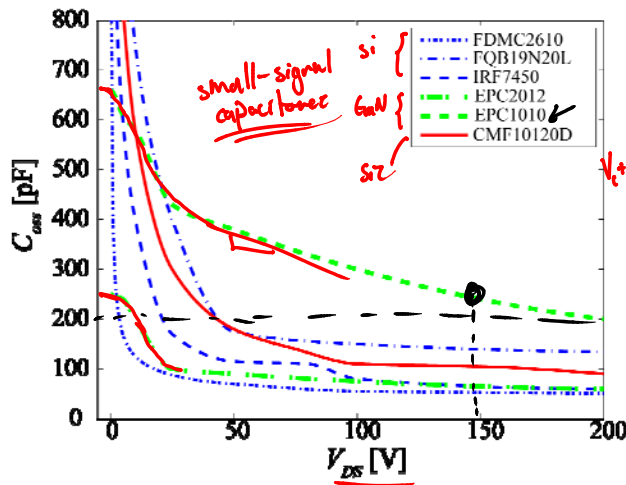

SJ Capacitance



WBG Material Capacitances





Modeling Nonlinear Capacitances

Energy

$$E_c = \int_0^{t_1} i_c v_c dt$$

$$E_c = \int_0^{t_1} C(v_c) \frac{dv_c}{dt} v_c dt$$

Apply chain rule

$$E_c = \int_{v_c(0)}^{v_c(t_1)} C(v_c) v_c dv_c$$

$$E_c = \int_0^{V_{bc}} C(v_c) v_c dv_c$$

Assume linear:

$$E_c = \int_0^{V_{bc}} C v_c dv_c$$

$$\rightarrow E_c = C \frac{V_{bc}^2}{2}$$

Charge

$$Q_c = \int_0^{t_1} i_c dt$$

$$Q_c = \int_0^{t_1} C(v_c) \frac{dv_c}{dt} dt$$

$$Q_c = \int_0^{V_{bc}} C(v_c) dv_c$$

$$Q_c = \int_0^{V_{bc}} C dv_c$$

$$Q_c = C V_{bc}$$



Energy and Charge Equivalents

$$\Rightarrow E_c = \int_0^{V_{bc}} C(v_c) v_c dv_c$$

$$Q_c = \int_0^{V_{bc}} C(v_c) dv_c$$

If we want to know what linear capacitance would give the same energy stored at V_{bc} :

$$E_{c,lin} = \frac{1}{2} C_{eq} V_{bc}^2 = \int_0^{V_{bc}} C(v_c) v_c dv_c$$


$$C_{eq} = \frac{2}{V_{bc}^2} \int_0^{V_{bc}} C(v_c) v_c dv_c$$

$$Q_{c,lin} = C_{eq} V_{bc} = \int_0^{V_{bc}} C(v_c) dv_c$$

$$C_{eq} = \frac{1}{V_{bc}} \int_0^{V_{bc}} C(v_c) dv_c$$



Switching Losses in a Half Bridge

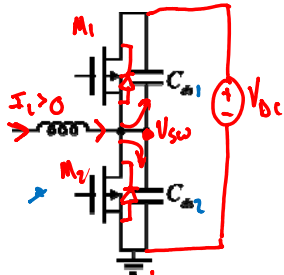


Two switching transitions:

① M_2 turns off, M_1 turns on



Possible to have no switching losses due to C_{ds}

② M_1 turns off, M_2 turns on

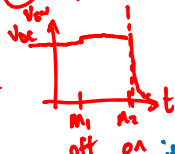


Hard-switched; $E_{sw} \neq 0$

two components of $E_{sw} = E_1 + E_2$

$E_2 = \frac{1}{2} C_{ds2} V_{dc}^2$ (due to discharging C_{ds2})

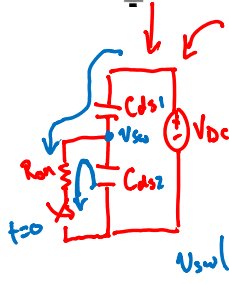$E_1 = \frac{1}{2} C_{ds1} V_{dc}^2$ (due to charging C_{ds1})




$V_{sw}(t=0) = V_{dc}$

in the linear case



M_2 Energy Loss

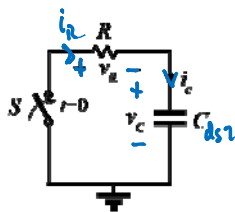

$V_c(t=0) = V_{dc}$

Energy dissipated is all of energy stored in C_{ds2} @ V_{dc}

$$E = E_{C_{ds2}}(t=0) = \frac{1}{2} C_{ds2} V_{dc}^2$$

Verify:


$$E_R = \int_0^{\infty} i_R V_R dt = \int_0^{\infty} i_c (-v_c) dt = \int_0^{\infty} C \frac{dv_c}{dt} dt (-v_c) dt$$

$$E_R = \int_{V_{dc}}^0 C(v_c) (-v_c) dv_c = \int_0^{V_{dc}} C(v_c) v_c dv_c = \frac{1}{2} C_{ds2} V_{dc}^2$$

✓



M₂ Energy Loss

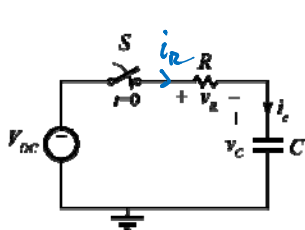

$$\begin{aligned}
 E_R &= \int_0^{\infty} i_R v_R dt \\
 &= \int_0^{\infty} i_c (V_{DC} - v_c) dt \\
 &= \int_0^{\infty} C(v_c) \frac{dv_c}{dt} (V_{DC} - v_c) dt \\
 E_R &= \int_0^{V_{DC}} C(v_c) (V_{DC} - v_c) dv_c = -\int_0^{V_{DC}} (v_c) v_c dv_c + \int_0^{V_{DC}} V_{DC} (v_c) dv_c
 \end{aligned}$$

$$= V_{DC}^2 C_{eff} - \frac{1}{2} C_{eff} V_{DC}^2$$

$$E_{sw} = V_{DC}^2 C_{eff}$$