

Analytical E_{sw} for ideal Silicon DMOS

$$C_{ds} = \frac{C_{j0} A}{\sqrt{1 + \frac{V_{ds}}{V_F}}}, \quad C_{j0} = \sqrt{\frac{\epsilon^2 E_{crit}^2}{4 V_{BV} V_F}}$$

on this week's HW $\rightarrow V_F = 1$

$\rightarrow C_{ds} = \frac{C_{j0} A}{\sqrt{1 + V_{ds}}}$

$$C_{eq,Q} = \frac{1}{V_g} \int_0^{V_g} C_{ds} dv = \frac{1}{V_g} \int_0^{V_g} \frac{C_{j0} A}{\sqrt{1+v}} dv$$

$$= \frac{C_{j0} A}{V_g} 2\sqrt{1+v} \Big|_{v=0}^{v=V_g} = \frac{2 C_{j0} A}{V_g} (\sqrt{1+V_g} - 1)$$

$E_{sw} = 2 V_g C_{j0} A (\sqrt{1+V_g} - 1)$

\hookrightarrow Note: still linearly proportional to A (device area)

UT

Energy Equivalent

Matlab Code:

```
Vdc = 550;
Vds = [0 5 10 40 50 75 100 150 200 300 400 500 600];
Coss = [5500 2500 1900 550 95 50 38 30 29 27 25 24]*1e-12;
vx = 0.01:0.01:Vdc;
Cx = 10.^interp1(Vdc,log10(Coss),vx,'linear');
E = cumtrapz(vx, Cx.*vx);
Cequiv = 2*(E)./vx.^2;
```

$M_1 V_{ds} = N_{sw}$
 $M_2 V_{ds} = V_g - N_{sw}$



Example Buck Efficiency

Drain-source on-state resistance	$R_{DS(on)}$	Min Max Max		
		$V_{GS}=10\text{ V}, I_D=5.2\text{ A}, T_J=25\text{ }^\circ\text{C}$	-	0.35
	$V_{GS}=10\text{ V}, I_D=5.2\text{ A}, T_J=150\text{ }^\circ\text{C}$	-	0.94	-

$V_g = 300\text{V} - 10 - 150\text{V}$
 $\eta \geq 95\%$
 $P_{out} = 100\text{W}$

$$P_{sw} = V_g^2 C_{eq} \alpha f_s$$

$$P_{cond} = i_{L,rms}^2 R_{DS(on)} + i_{L,rms}^2 R_{DS(on)}$$

$$= (\sqrt{D} I_L)^2 R_{DS(on)} + (I_{L,rms})^2 R_{DS(on)}$$

$$= I_L^2 R_{DS(on)}$$

$$I_L = \frac{100\text{W}}{150\text{V}}$$

$$C_{eq} = 247\text{pF}$$

$$\eta = \frac{P_{out}}{P_{out} + P_{cond} + P_{sw}} = \frac{100\text{W}}{100\text{W} + \left(\frac{100\text{W}}{150\text{V}}\right)^2 (385\Omega) + (300\text{V})^2 (247\text{pF}) f_s}$$

$$f_s \leq \frac{\frac{100\text{W}}{0.95} - 100\text{W} - \left(\frac{100\text{W}}{150\text{V}}\right)^2 (385\Omega)}{(300\text{V})^2 (247\text{pF})} = 230\text{kHz}$$

$$P_{cond} = I_L^2 R_{on} = 0.171\text{W}$$

$$P_{sw} = V_g^2 C_{eq} \alpha f_s = 5.1\text{W}$$

what if we could have a device half as big as us IPB60R385, & it scaled proportionally?

$$P_{cond}' = 0.342\text{W}$$

$$P_{sw}' = 2.55\text{W}$$

$$P_{tot} = 2.892$$


$$\eta \approx 97.3\%$$

C_{eq}	E_{sw}
$C_{eq,Q}$	$22\mu\text{S}$
$C_{oss}(V_{ds}=300)$	$2.6\mu\text{S}$
$C_{eq,E}$	$2.5\mu\text{S}$
C_{eq} from table	$3.4\mu\text{S}$



Wrong



Nonlinear Capacitance Waveforms

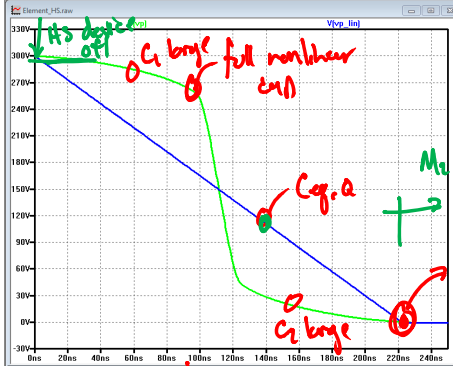

Develop their equivalent based on charge

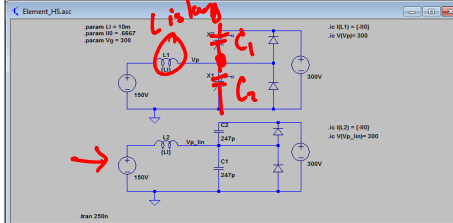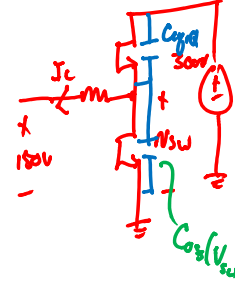


Gate Charge

9 Typ. gate charge


$$V_{GS} = f(Q_{gate}); I_D = 5.2 \text{ A pulsed}$$

parameter: V_{DD}

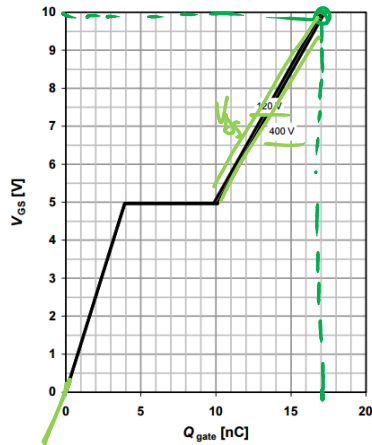

Until now, we have assumed we can switch MOSFET channel instantaneously

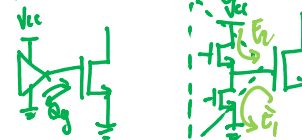Some non-zero charge must be supplied to change V_{GS}



$$P_g = Q_g V_{GS} f_s$$