

UT

$E = \int i_g (V_{GS} + v_r) dt$

Overlap Time

9 Typ. gate charge
 $V_{GS} = f(Q_{gate})$; $I_D = 5.2$ A pulsed
 parameter: V_{DD}

Gate threshold voltage	$V_{GS(th)}$	$V_{DS} = V_{GS}$, $I_D = 0.34$ mA	2.5	3	3.5
Gate resistance	R_G	$f = 1$ MHz, open drain	-	1.8	-

$C_{gd} \ll C_{gs}$



simplifying Assumption
 $I_g \approx \text{const during switching}$

turn-on

$\langle P_{overlap} \rangle = \frac{1}{2} I_D V_{DS} t_{overlap} f_s$
 $= \frac{1}{2} I_D V_{DS} \frac{t_{overlap}}{T_s}$

$t_{overlap} = 7.5 \text{ ns}$ for $I_G = 1 \text{ A}$

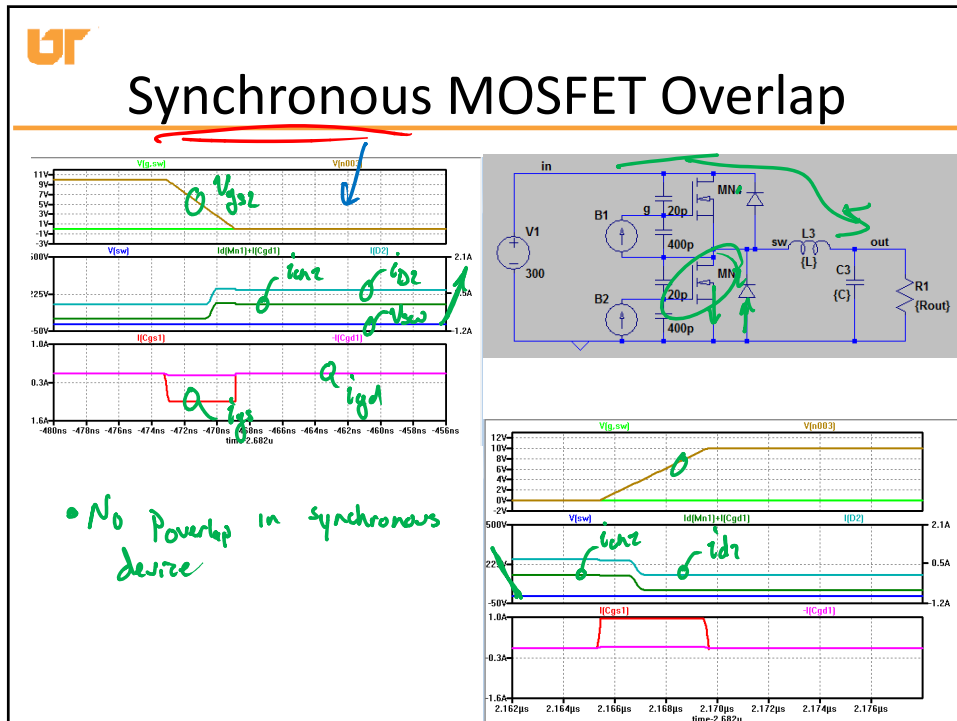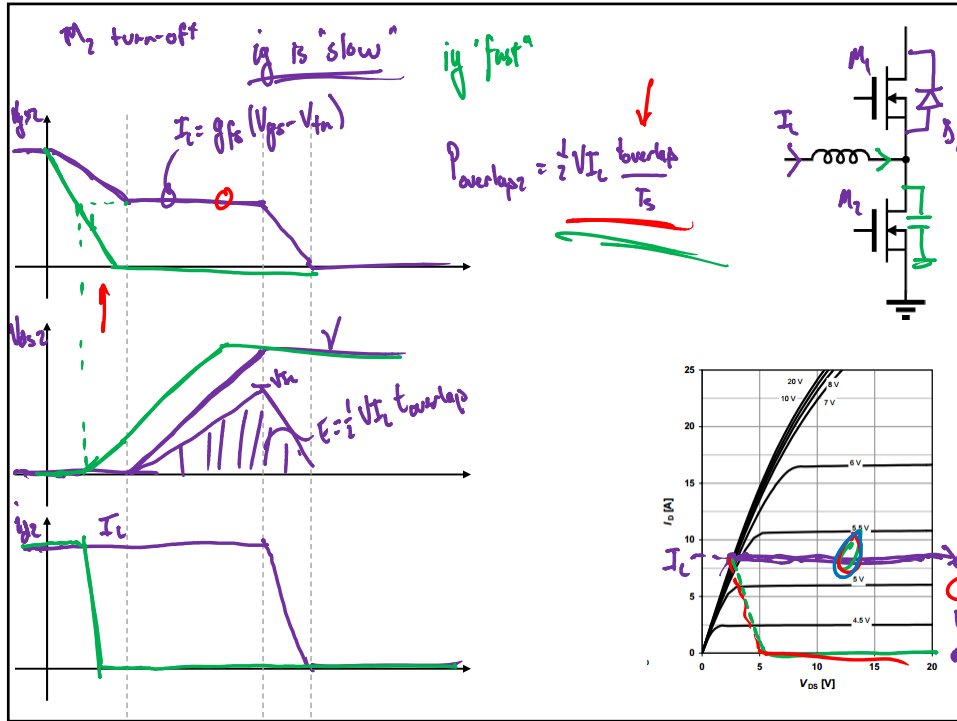$i_{GS} = g_{fs} (V_{GS} - V_{th})$ (in Act/Sat)



Example Calculation

Assume gate driver supplies $\pm I_g$ (or ϕ)

$$t_{on} = t_{off} = \frac{Q_g}{I_g}$$

$$t_{overlap} = \frac{Q_{sw}}{I_g} = \begin{cases} 7.5 \text{ ns} @ I_g = 1 \text{ A} \\ 750 \text{ ps} @ I_g = 10 \text{ A} \end{cases}$$

Worst case:

$$P_{overlap} = \frac{1}{2} V_g I_c \frac{t_{overlap}}{T_s} + \frac{1}{2} V_g I_c \frac{t_{overlap}}{T_s}$$

\rightarrow M_1 turn-on M_1 turn-off (worst-case)

$$= V_g I_c \frac{Q_{sw}}{I_g T_s} = \begin{cases} 345 \text{ mW} @ I_g = 1 \text{ A} \\ 34.5 \text{ mW} @ I_g = 10 \text{ A} \end{cases}$$

Example Buck Efficiency (L14)

Drain-source on-state resistance	$R_{DS(on)}$	$V_{GS}=10 \text{ V}, I_D=5.2 \text{ A}, T_J=25 \text{ }^\circ\text{C}$	-	0.25	0.385
		$V_{GS}=10 \text{ V}, I_D=5.2 \text{ A}, T_J=150 \text{ }^\circ\text{C}$	-	0.94	-

$V_g = 300\text{V} - 150\text{V} = 150\text{V}$
 $\eta \geq 95\%$
 $P_{out} = 100\text{W}$

$I_c = \frac{100\text{W}}{150\text{V}}$

$C_{gd} = 277\text{pF}$

$P_{sw} = V_g^2 C_{gd} f_s$

$P_{cond} = i_{rms}^2 R_{th(on)} + i_{crms}^2 R_{ds(on)}$

$= (\sqrt{D} I_c)^2 R_{th(on)} + (\sqrt{1-D} I_c)^2 R_{ds(on)}$


$= I_c^2 R_{th(on)}$

$\eta = \frac{P_{out}}{P_{out} + P_{cond} + P_{sw}} = \frac{100\text{W}}{100\text{W} + \left(\frac{100\text{W}}{150\text{V}}\right)^2 (385\Omega) + (300\text{V})^2 (277\text{pF}) f_s}$

$f_s \leq \frac{100\text{W} - 100\text{W} - \left(\frac{100\text{W}}{150\text{V}}\right)^2 (385\Omega)}{(300\text{V})^2 (277\text{pF})} = 230\text{kHz}$

$P_{cond} = I_c^2 R_{th(on)} = 0.171\text{W}$

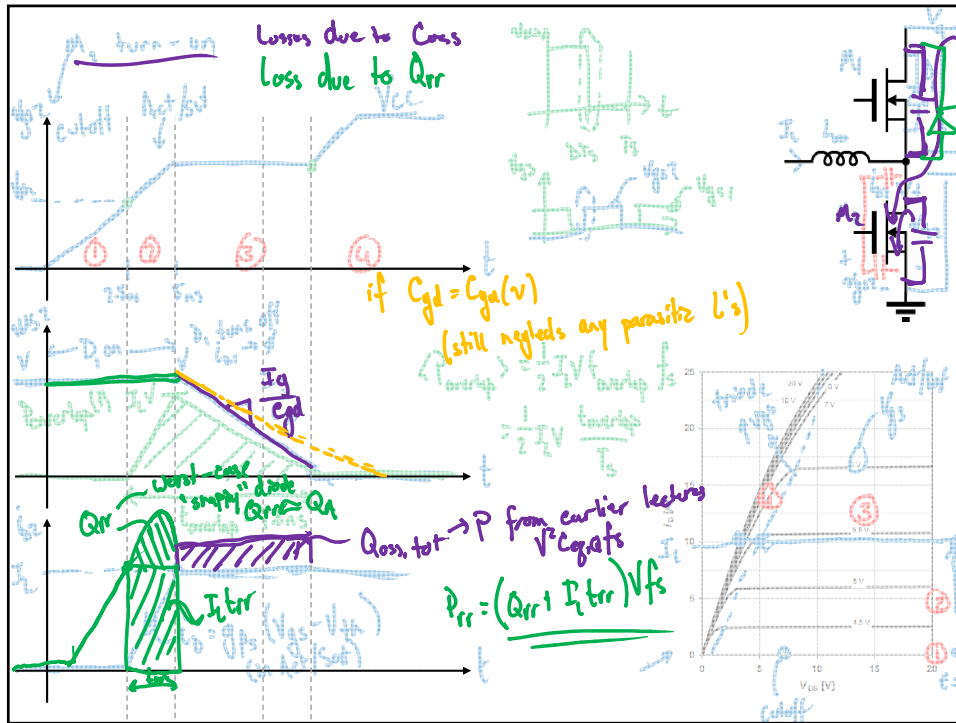$P_{sw} = V_g^2 C_{gd} f_s = 5.1\text{W}$



UF

Switching Loss Summary

For a hard-switched device (MOSFET turns on w/ $V_{ds} \gg \phi$)

Switching losses:

$$P_{Coss} \Rightarrow P = \underbrace{\left(\frac{1}{2} C_{gd,E} V_{dc}^2\right)}_{\text{this device}} + \underbrace{\left(C'_{gd} V_{dc}^2 - \frac{1}{2} C_{gd,E} V_{dc}^2\right)}_{\text{opposite device}} f_s$$



$Q_g \Rightarrow P_g = V_{gs} Q_g f_s \rightarrow$ Losses occur in gate drive circuit (occur 1x for each MOSFET)

V-I overlap $\Rightarrow P_{overlap} = V_{dc} I_L \frac{t_{overlap}}{T_s} \rightarrow t_{overlap} = \frac{Q_{sw}}{f_g}$

reverse recovery (if present) $\Rightarrow P_{rr} = V_{dc} (Q_{rr} + I_{r,rr}) f_s$



Switching Waveforms

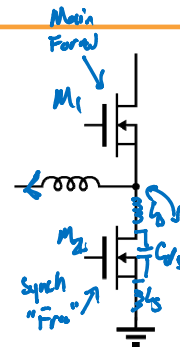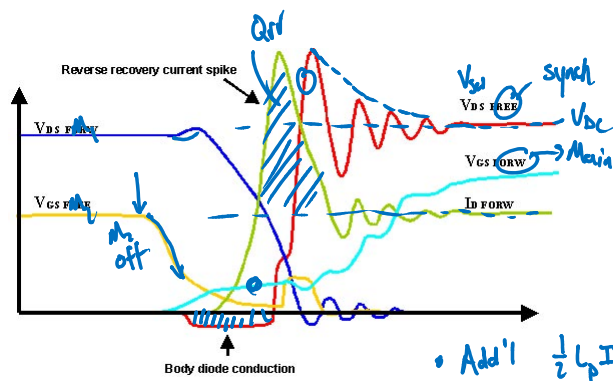

- Add'l $\frac{1}{2} L_p I_{fs}^2$ - type loss
- Voltage / current overshoot
- slowed down